

Lecture 5

Karnaugh Map

Dr. Bassam Atieh

MANARA UNIVERSITY

The idea of Karnaugh Map: (with minterms)

The combining **property 14a** ($x \cdot y + x \cdot \bar{y} = x$) allow us **to replace** any two minterms that **differ** in the value of only one variable **with a** single product term that does not include that variable at all. Also, **theorem 7b** ($x = x + x$) allow us **to use** any minterm **more than once**.

Karnaugh map is an alternative to the truth-table form for representing a function. The map allows easy recognition of minterms that can be combined using **property 14a**.

The more you **practice** using K-maps, the more **intuitive** you become in finding the minimum cost for any circuit.

Example 1: (Two-Variable Map)



Find the minimum-cost SOP form for the following function:

المناصرة
MANARA UNIVERSITY

$f=1$ when $x_1=0$
regardless of x_2

$f=1$ when $x_2=0$
regardless of x_1

$$f(x_1, x_2) = \bar{x}_1 + \bar{x}_2$$

Answer

x_1	x_2	$f(x_1, x_2)$	Minterm#
0	0	1	m_0
0	1	1	m_1
1	0	1	m_2
1	1	0	m_3

K-Map:

$$f(x_1, x_2) =$$

		x_2	
		0	1
x_1	0	m_0	m_1
	1	m_2	m_3

\bar{x}_1

+

\bar{x}_2

		x_2	
		0	1
x_1	0	1	1
	1	1	0

		x_2	
		0	1
x_1	0	1	1
	1	1	

\bar{x}_1 (grouping the top row)
 \bar{x}_2 (grouping the first column)


$$f_{SOP} = \bar{x}_1 + \bar{x}_2$$

Example 2: (Three-Variable Map)

Find the minimum-cost SOP form for the following function:

$$f(x_1, x_2, x_3) = \underbrace{\bar{x}_3}_{**0} + \underbrace{x_1 \bar{x}_2}_{10*}$$

x_1	x_2	x_3	$f(x_1, x_2, x_3)$	Minterm#	Product#
0	0	0	1	m_0	1 st
0	0	1	0	m_1	
0	1	0	1	m_2	1 st
0	1	1	0	m_3	
1	0	0	1	m_4	1 st , 2 nd
1	0	1	1	m_5	2 nd
1	1	0	1	m_6	1 st
1	1	1	0	m_7	

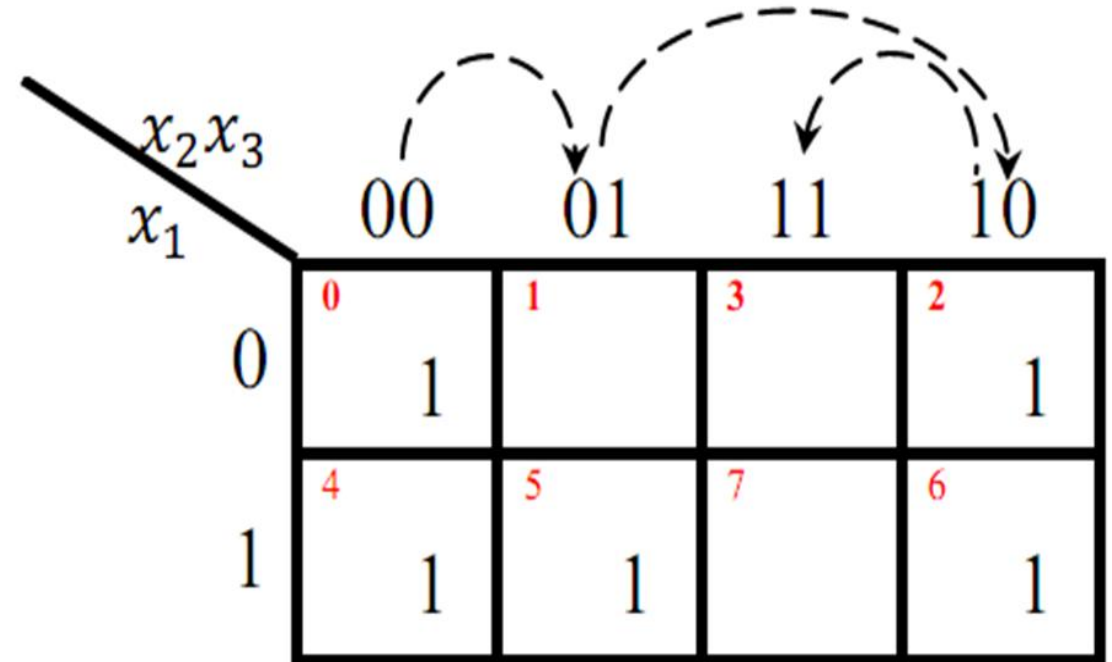



جامعة
المنارة

x_2x_3		00	01	11	10
x_1	0	0 1	1	3	2 1
	1	4 1	5 1	7	6 1




x_2x_3		00	01	11	10
x_1	0	0 1	1	3	2 1
	1	4 1	5 1	7	6 1


$x_1\bar{x}_2$ \bar{x}_3

$$f_{SOP} = \bar{x}_3 + x_1\bar{x}_2$$

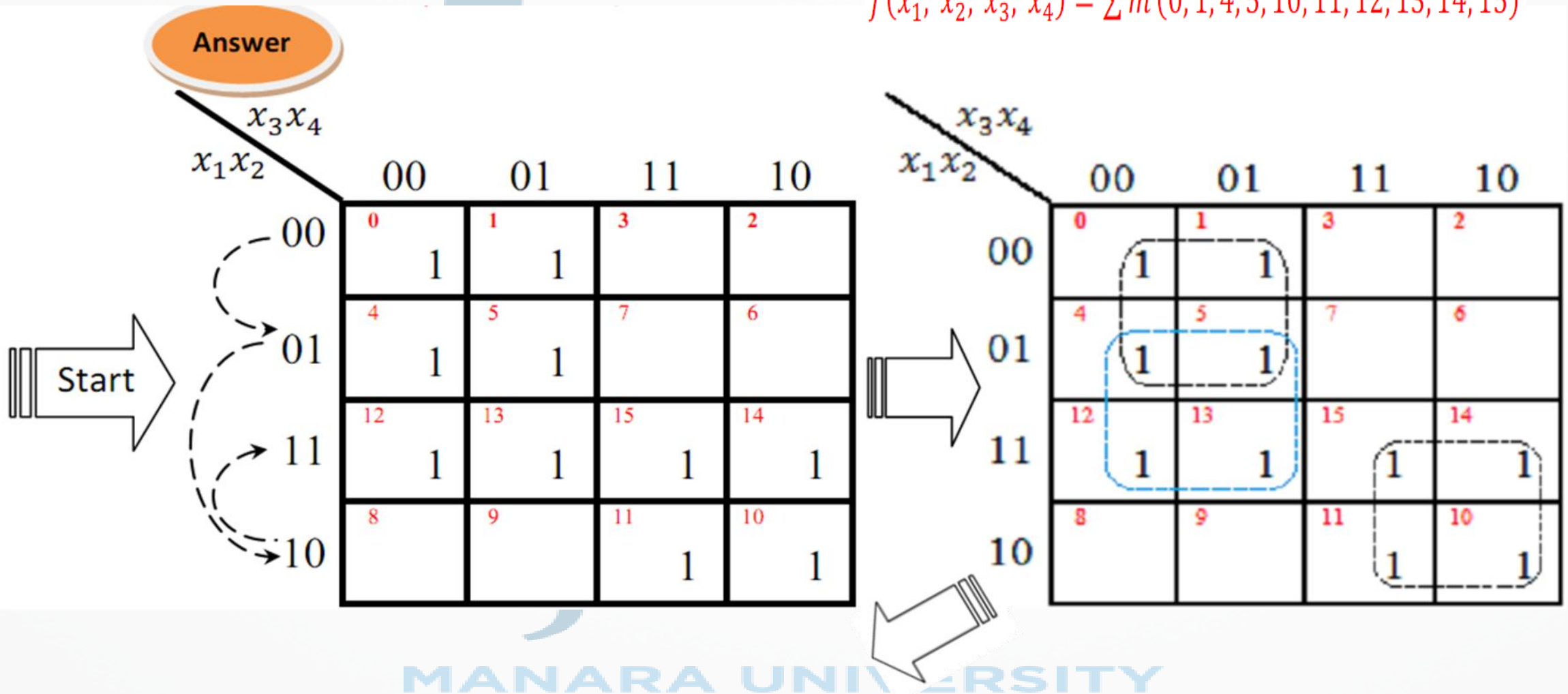
Example 3: (Four-Variable Map)

Find the minimum-cost SOP form for the following function:
 $f(x_1, x_2, x_3, x_4) = \sum m(0, 1, 4, 5, 10, 11, 12, 13, 14, 15)$



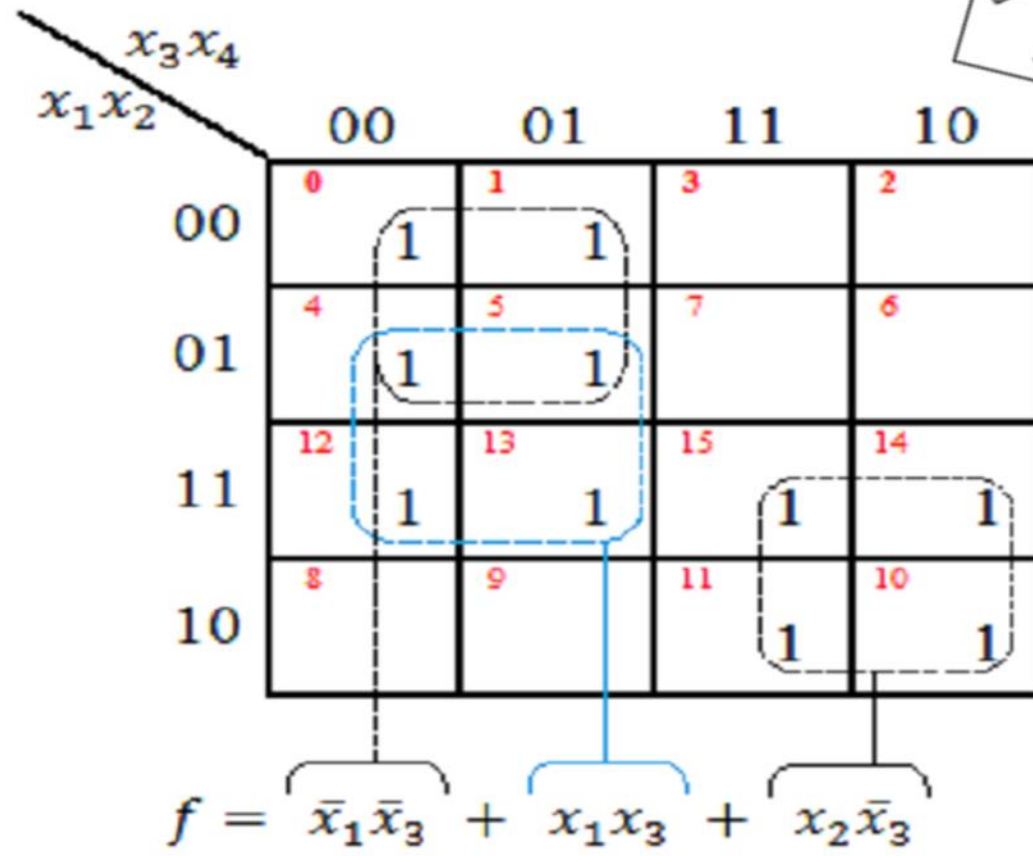

OR

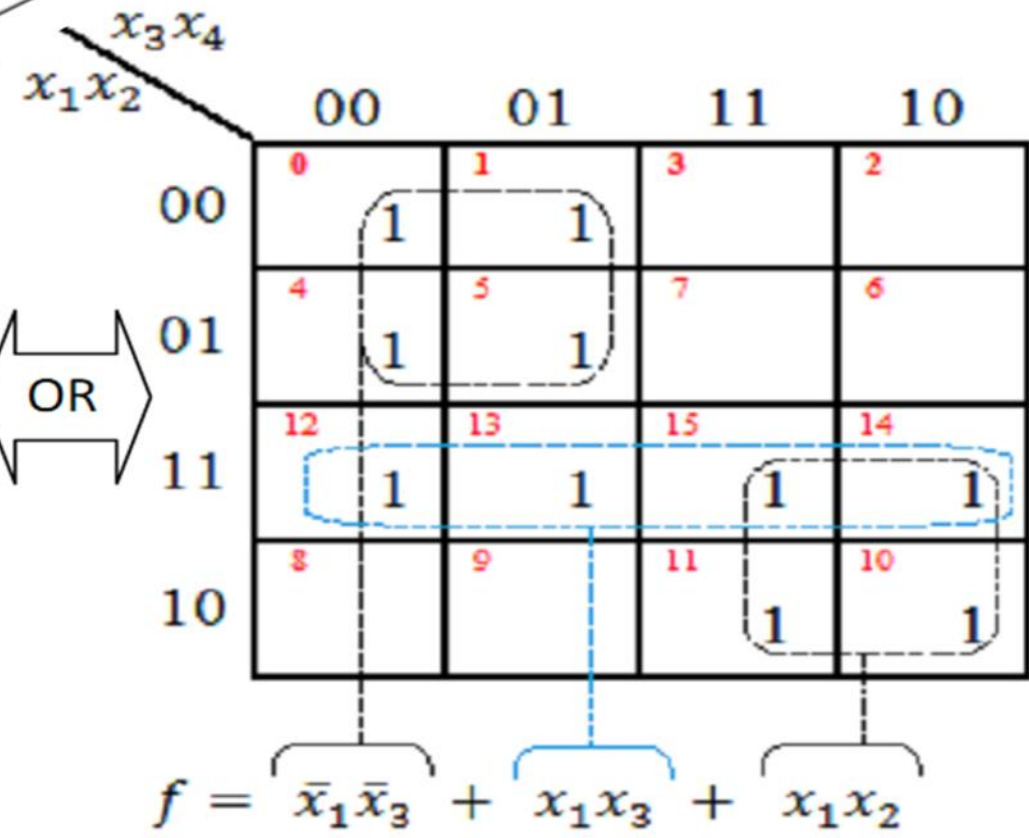



Example 4:

Find the minimum-cost SOP form



$$(a) f(x_1, x_2, x_3, x_4) = \sum m(6, 7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$(b) f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 8, 9, 10, 12, 13, 15)$$

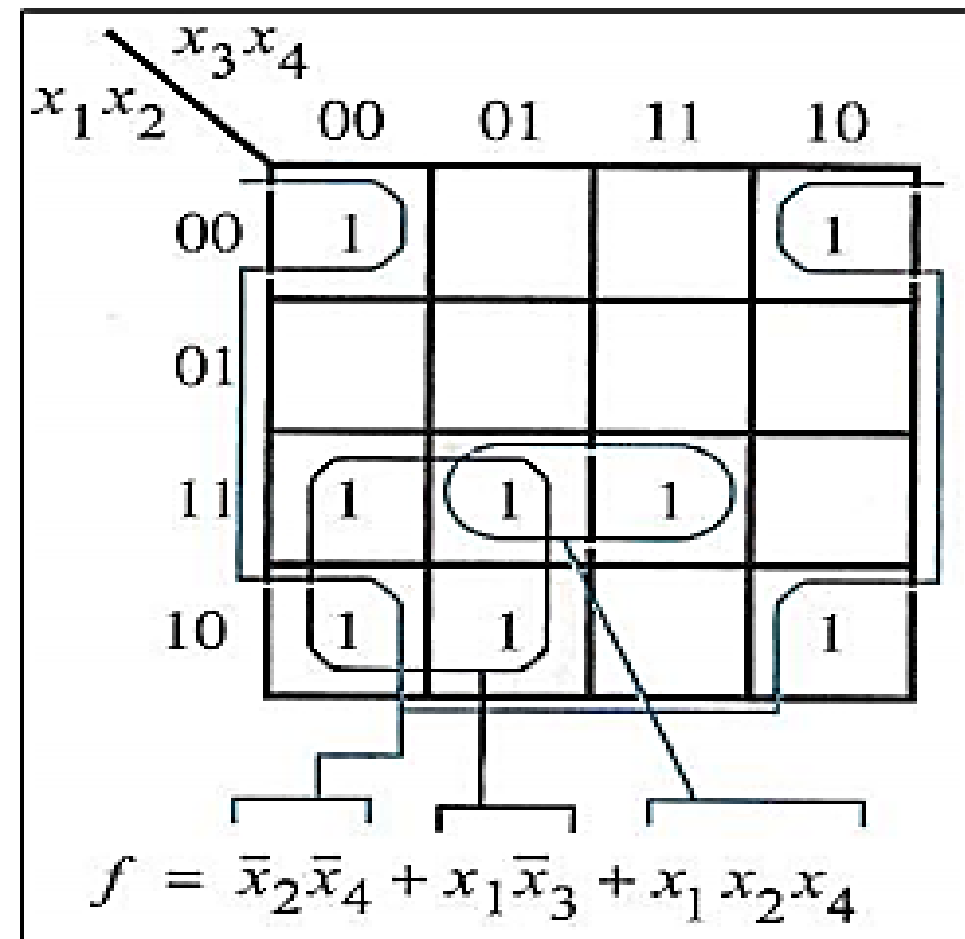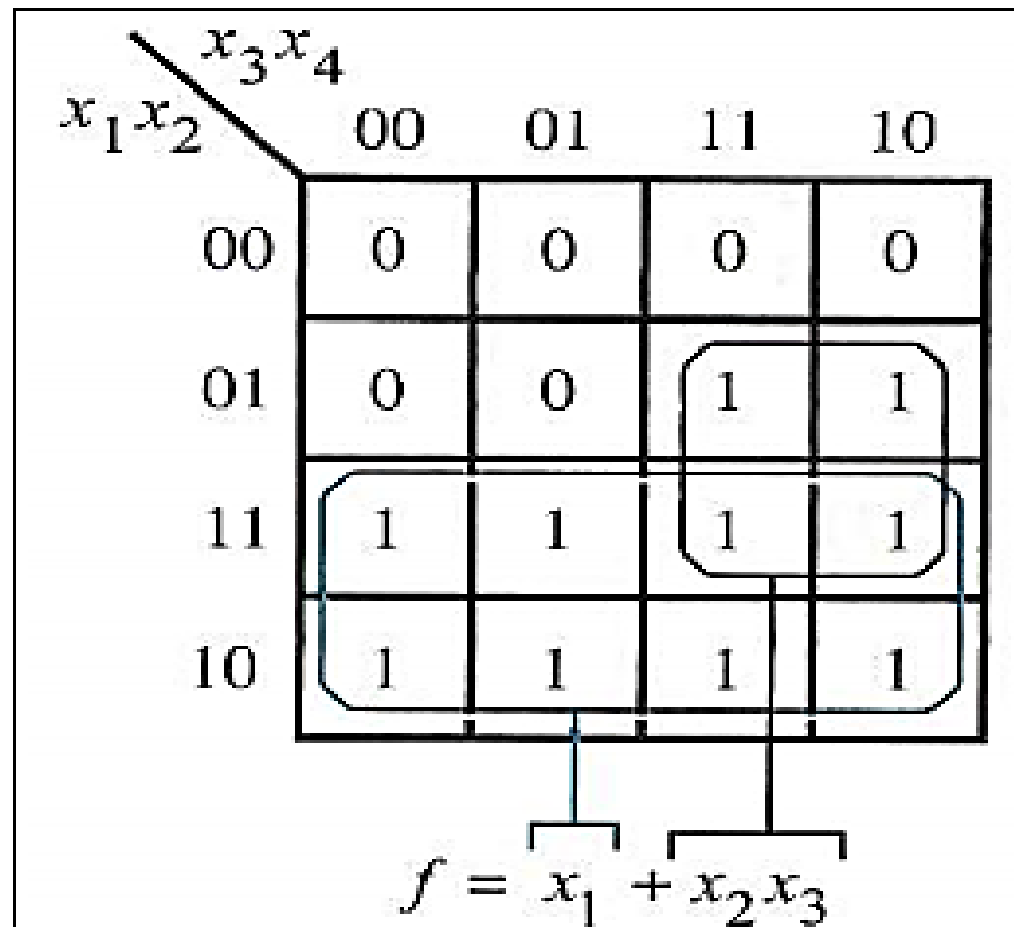


Example 6:

Answer

Find the minimum-cost SOP form for the following function:
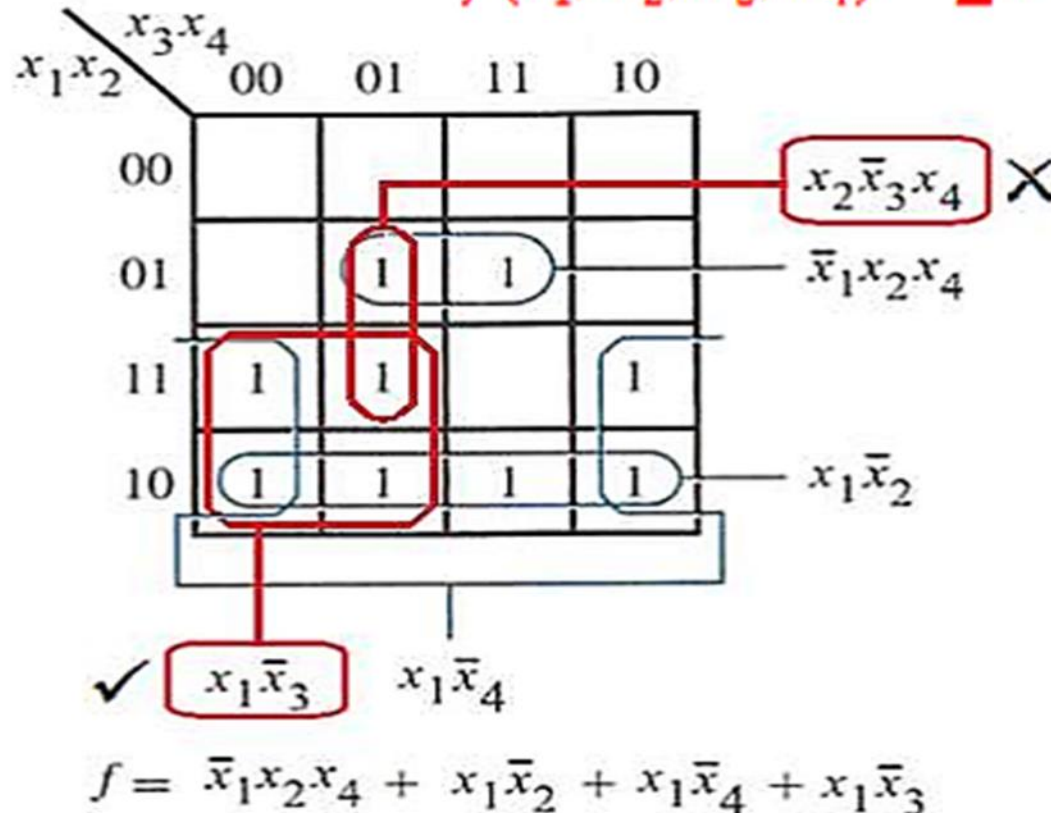
$$f(x_1, x_2, x_3, x_4) = \sum m(5, 6, 8, 9, 10, 11, 12, 13, 14)$$



For m_{13} , we could have formed 2 different clusters (the ones in red boxes). But according to strategy #2, a cluster must be as big as possible. Therefore, we chose the bigger cluster $x_1\bar{x}_3$.

Example 7:

Find the minimum-cost POS form for the following functions:

(a) $f(x_1, x_2, x_3) = \prod M(2, 3, 6)$

(b) $f(x_1, x_2, x_3, x_4) = \prod M(0, 1, 2, 3, 4, 6, 15)$

$x_2 x_3$					
x_1		00	01	11	10
	0	1	1	0	0
1	1	1	1	1	0

$(x_1 + \bar{x}_2)$ $(\bar{x}_2 + x_3)$

$$f = (x_1 + \bar{x}_2)(\bar{x}_2 + x_3)$$

$x_3 x_4$					
$x_1 x_2$		00	01	11	10
	00	0	0	0	0
01	1	0	1	1	0
11	1	1	1	0	1
10	1	1	1	1	1

$(x_1 + x_2)$
 $(x_1 + x_4)$
 $(\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + \bar{x}_4)$

$$f = (x_1 + x_2)(x_1 + x_4)(\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + \bar{x}_4)$$

Find the minimum-cost SOP and POS forms for the following functions:

$$(a) f(x_1, x_2, x_3) = \sum m(1, 2, 3, 5).$$

$$(b) f(x_1, x_2, x_3, x_4) = \prod M(0, 1, 2, 4, 5, 7, 8, 9, 10, 12, 14, 15).$$

Answer

(a)

$x_2 x_3$ x_1					
		00	01	11	10
0	0		1	3	2
1	4		5	7	6

$$f_{SOP} = \bar{x}_2 x_3 + \bar{x}_1 x_2$$

$x_2 x_3$ x_1					
		00	01	11	10
0	0				
1	4				

$$f_{POS} = (x_2 + x_3)(\bar{x}_1 + \bar{x}_2)$$

$x_3 x_4$ $x_1 x_2$					
		00	01	11	10
00	0	1	3	1	2
01	4	5	7		6
11	12	13	15	1	14
10	8	9	11	1	10

$$f_{SOP} = x_1 x_2 \bar{x}_3 x_4 + \bar{x}_2 x_3 x_4 + \bar{x}_1 x_2 x_3 \bar{x}_4$$

$x_3 x_4$ $x_1 x_2$					
		00	01	11	10
00	0	0	1	3	2
01	4	0	5	7	6
11	12	0	13	15	14
10	8	0	9	11	10

$$f_{POS} = (\bar{x}_1 + x_4)(x_2 + x_3)(\bar{x}_2 + \bar{x}_3 + \bar{x}_4)$$