

# Lecture 9




**(BJT BIASING)**

**طرق انحياز BJT**

**DR. BASSAM ATIEH**

المنارة  
MANARA UNIVERSITY

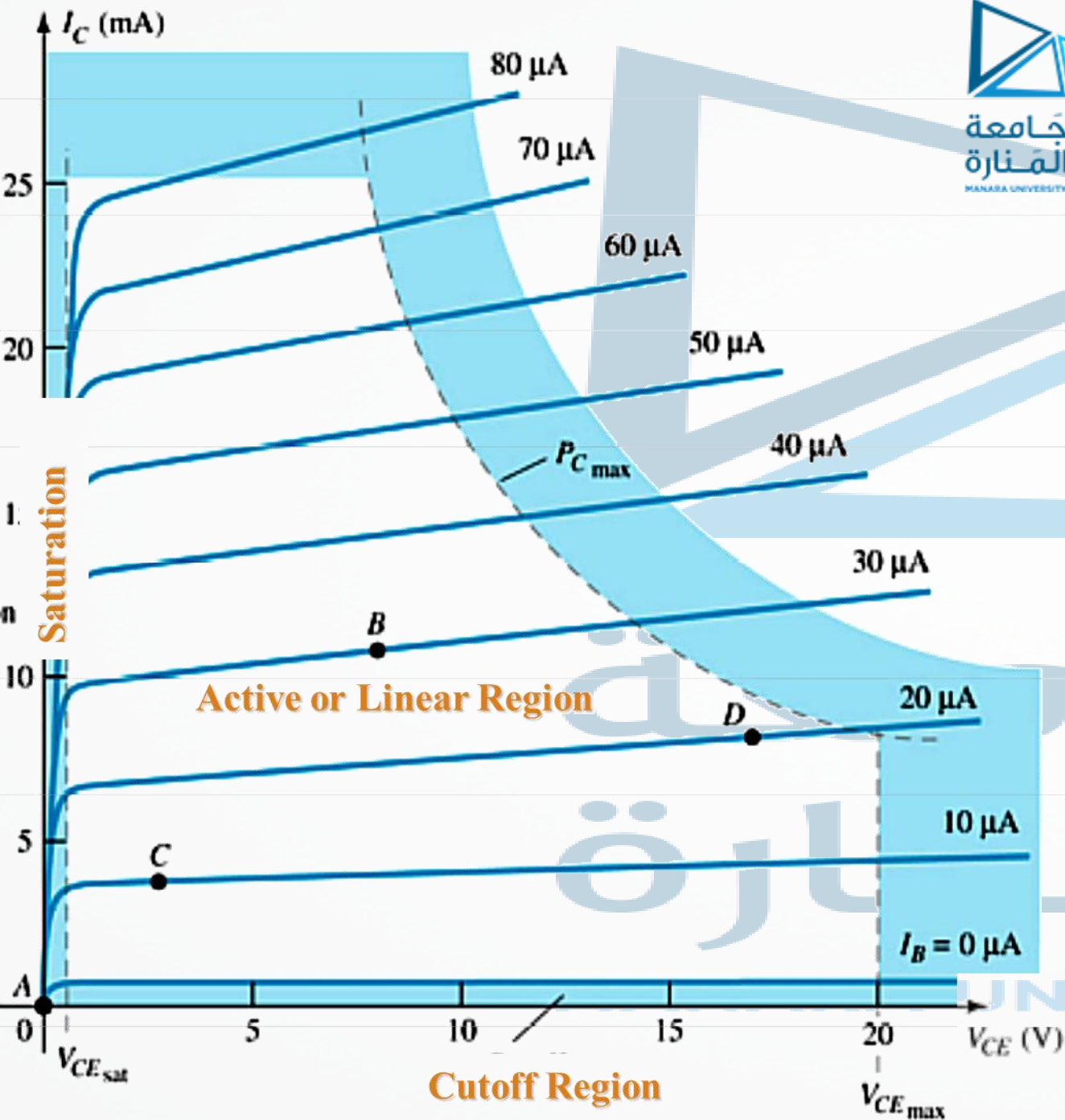

**Biasing:** The DC voltages applied to a transistor in order to turn it on so that it can amplify the AC signal.

- Operating Point**

The DC input establishes an operating or quiescent point called the **Q-point**.

- The Three States of Operation**

- Active or Linear Region Operation**

Base-Emitter junction is forward biased Base-Collector junction is reverse biased.

- Cutoff Region Operation**

Base-Emitter junction is reverse biased.

- Saturation Region Operation**

Base-Emitter junction is forward biased Base-Collector junction is forward biased.

## دارات الانحياز DC Biasing Circuits

- **Fixed-bias circuit** • دارة الانحياز الثابت
- **Emitter-stabilized bias circuit** • دارة انحياز الباعث المستقر
- **Collector-emitter loop** • دارة الانحياز لحلقة الباعث المجمع
- **Voltage divider bias circuit** • دارة انحياز مجزئ الجهد
- **DC bias with voltage feedback** • دارة الانحياز بالتغذية العكسية

# Fixed-bias circuit

## دائرة الانحياز الثابت

### • The Base-Emitter Loop

From Kirchhoff's voltage law:

$$+V_{CC} - I_B R_B - V_{BE} = 0$$

Solving for base current:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B}$$



### • Collector-Emitter Loop

Collector current:

$$I_C = \beta I_B$$

From Kirchhoff's voltage law:

$$V_{CE} = V_{CC} - I_C R_C$$

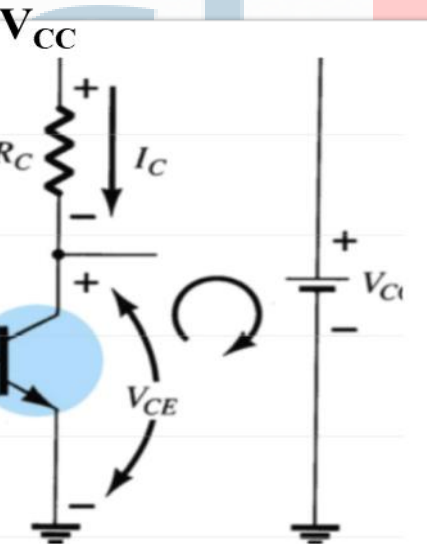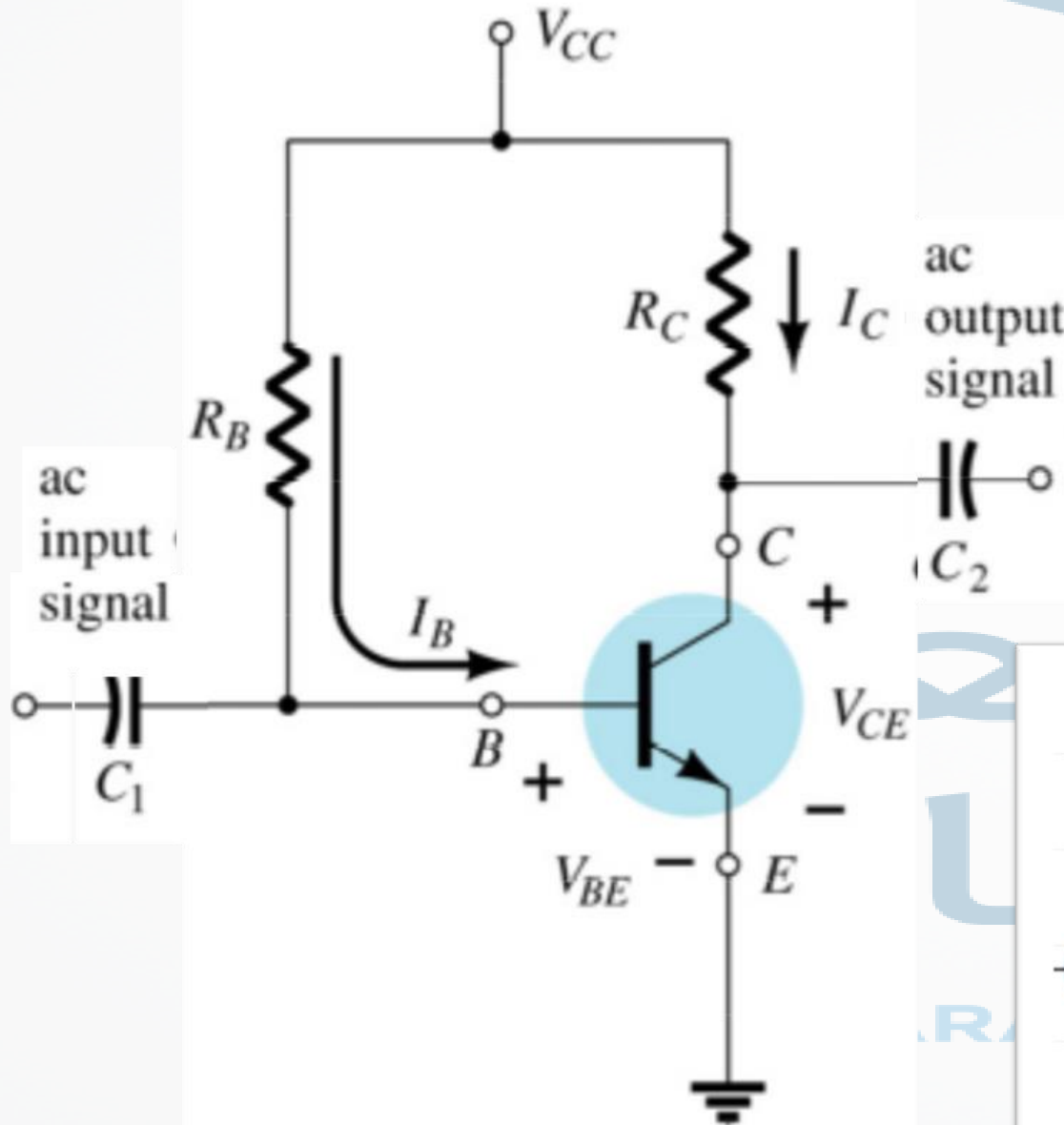

# Load Line Analysis

## • Active or Linear Region

The Q-point is the operating point:


- where the value of  $R_B$  sets the value of  $I_B$
- that sets the values of  $V_{CE}$  and  $I_C$

## • Saturation

When the transistor is operating in saturation, current through the transistor is at its maximum possible value.




$$V_{CE} \approx 0 \text{ V}$$

$$I_{C\text{sat}} = \frac{V_{CC}}{R_C}$$

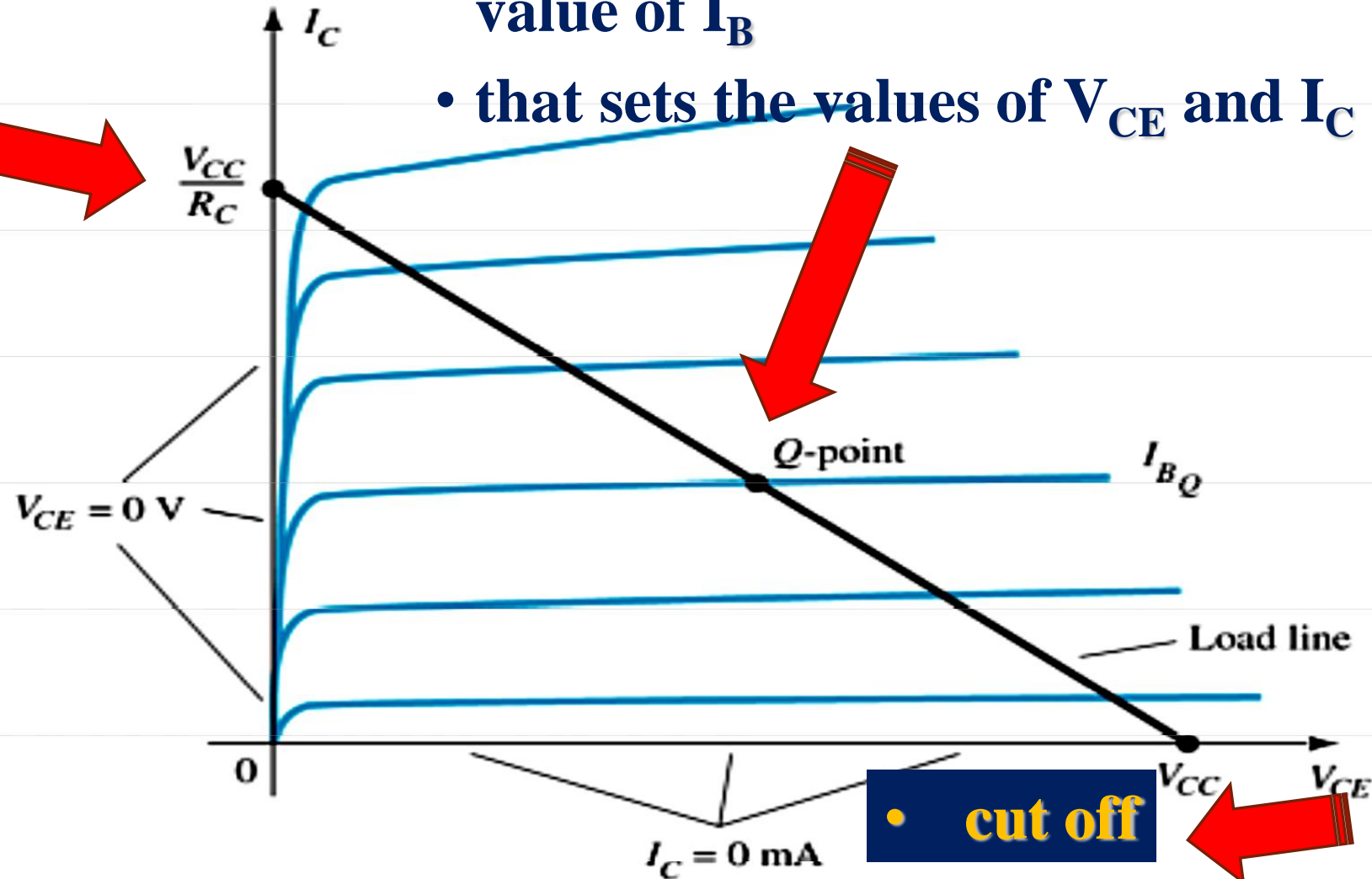




# Circuit Values Affect the Q-Point

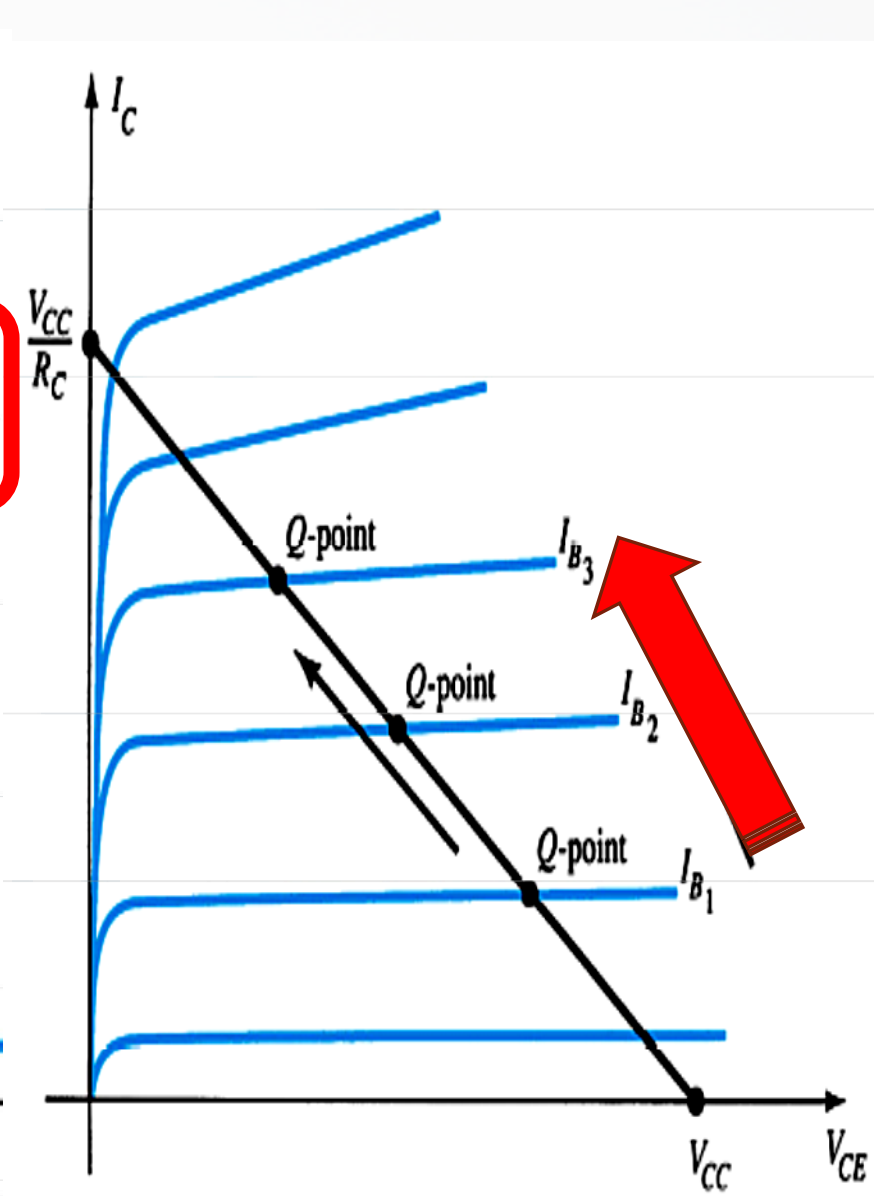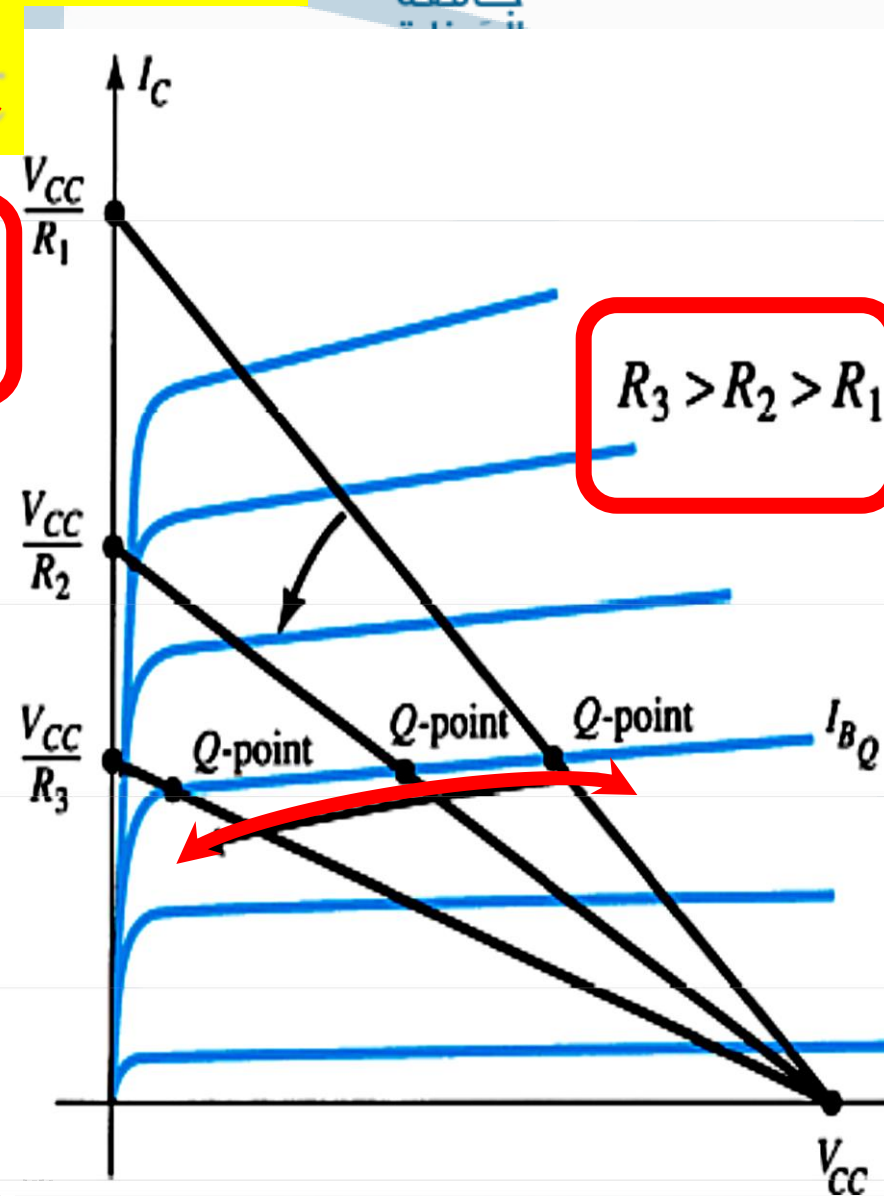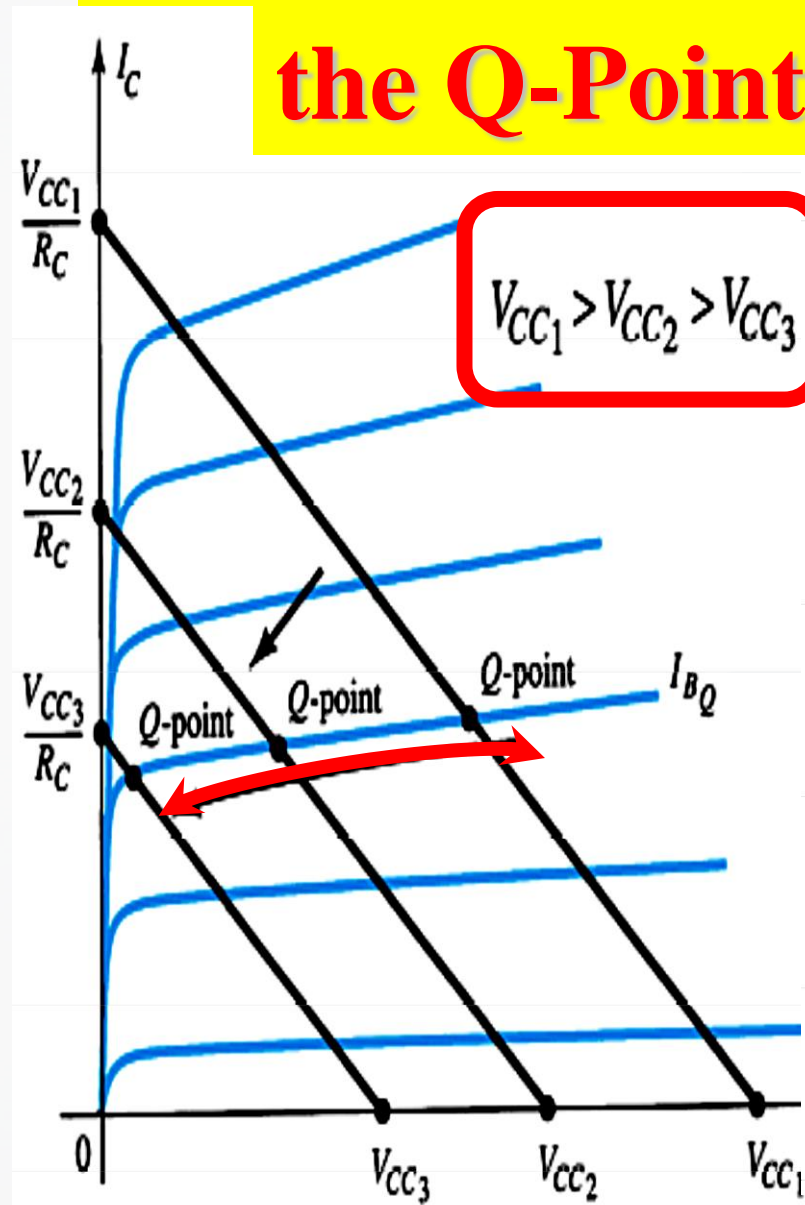

# Emitter-Stabilized Bias Circuit

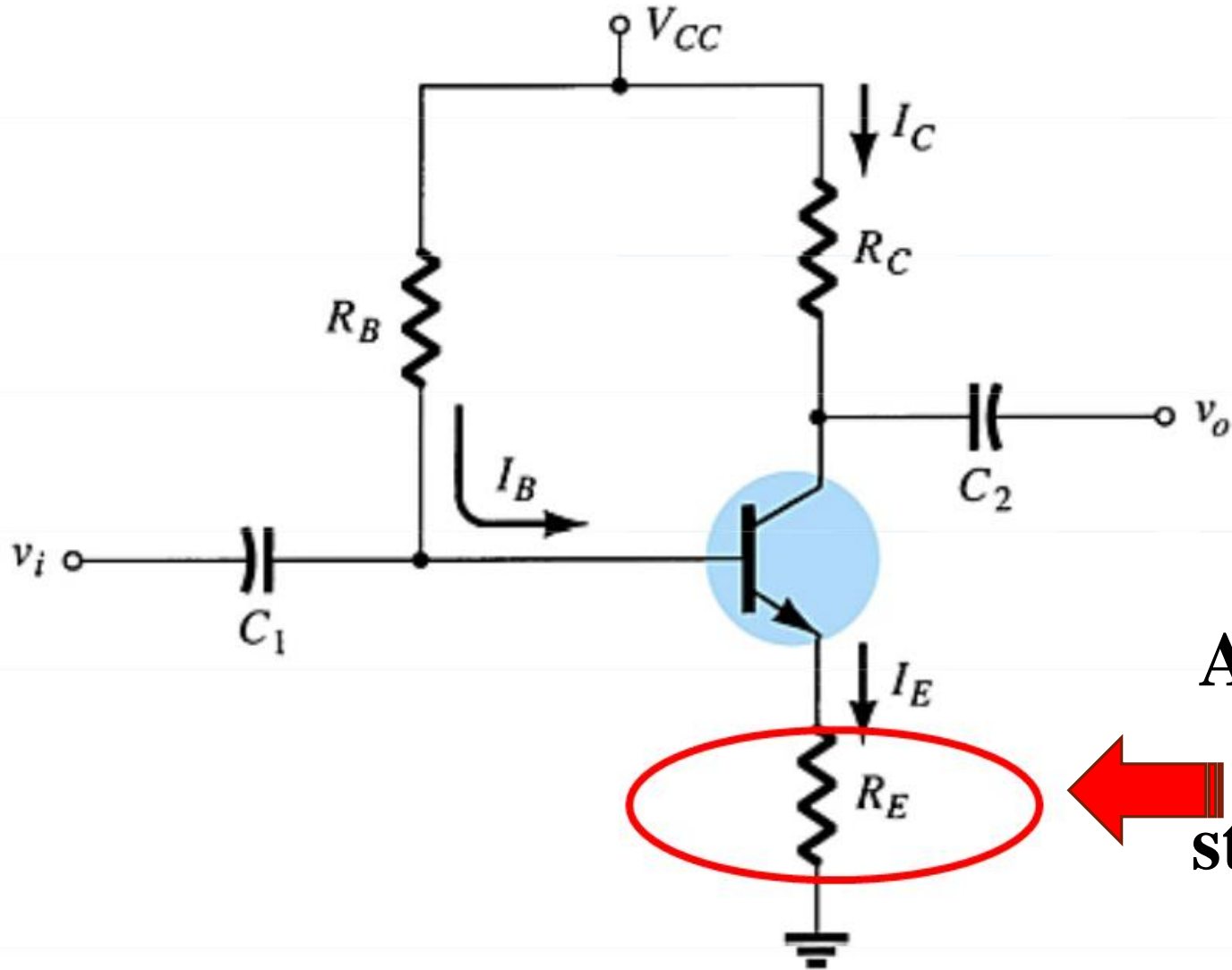

Adding a resistor ( $R_E$ ) to the emitter circuit stabilizes the bias circuit.

## Base-Emitter Loop

From Kirchhoff's voltage law:


$$+ V_{CC} - I_E R_E - V_{BE} - I_E R_E = 0$$

Since  $I_E = (\beta + 1)I_B$ :

$$V_{CC} - I_B R_B - (\beta + 1)I_B R_E = 0$$

Solving for  $I_B$ :
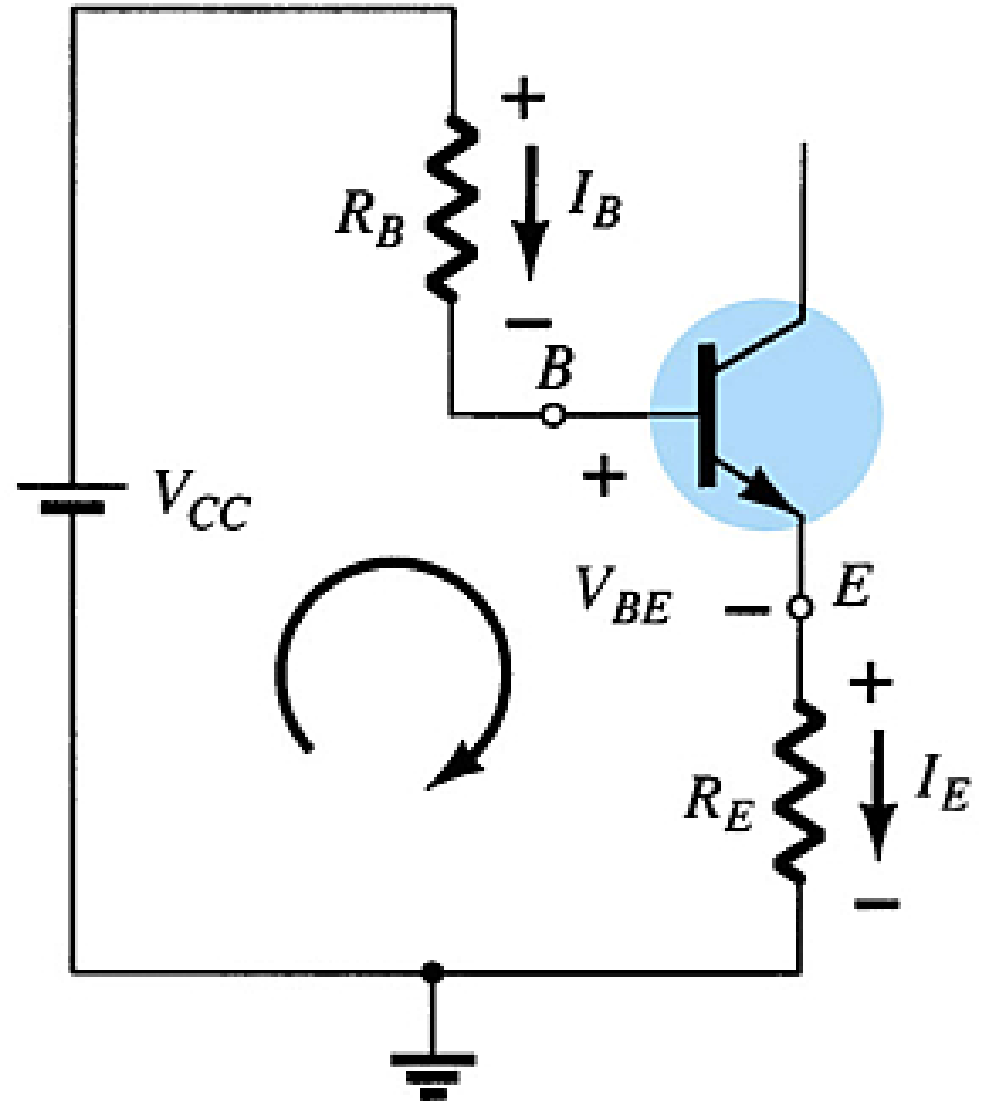
$$I_B = \frac{V_{CC} - V_{BE}}{R_B + (\beta + 1)R_E}$$





## Collector-Emitter Loop

From Kirchhoff's voltage law:

$$I_E R_E + V_{CE} + I_C R_C - V_{CC} = 0$$

Since  $I_E \cong I_C$ :


$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

Also:

$$V_E = I_E R_E$$


$$V_C = V_{CE} + V_E = V_{CC} - I_C R_C$$
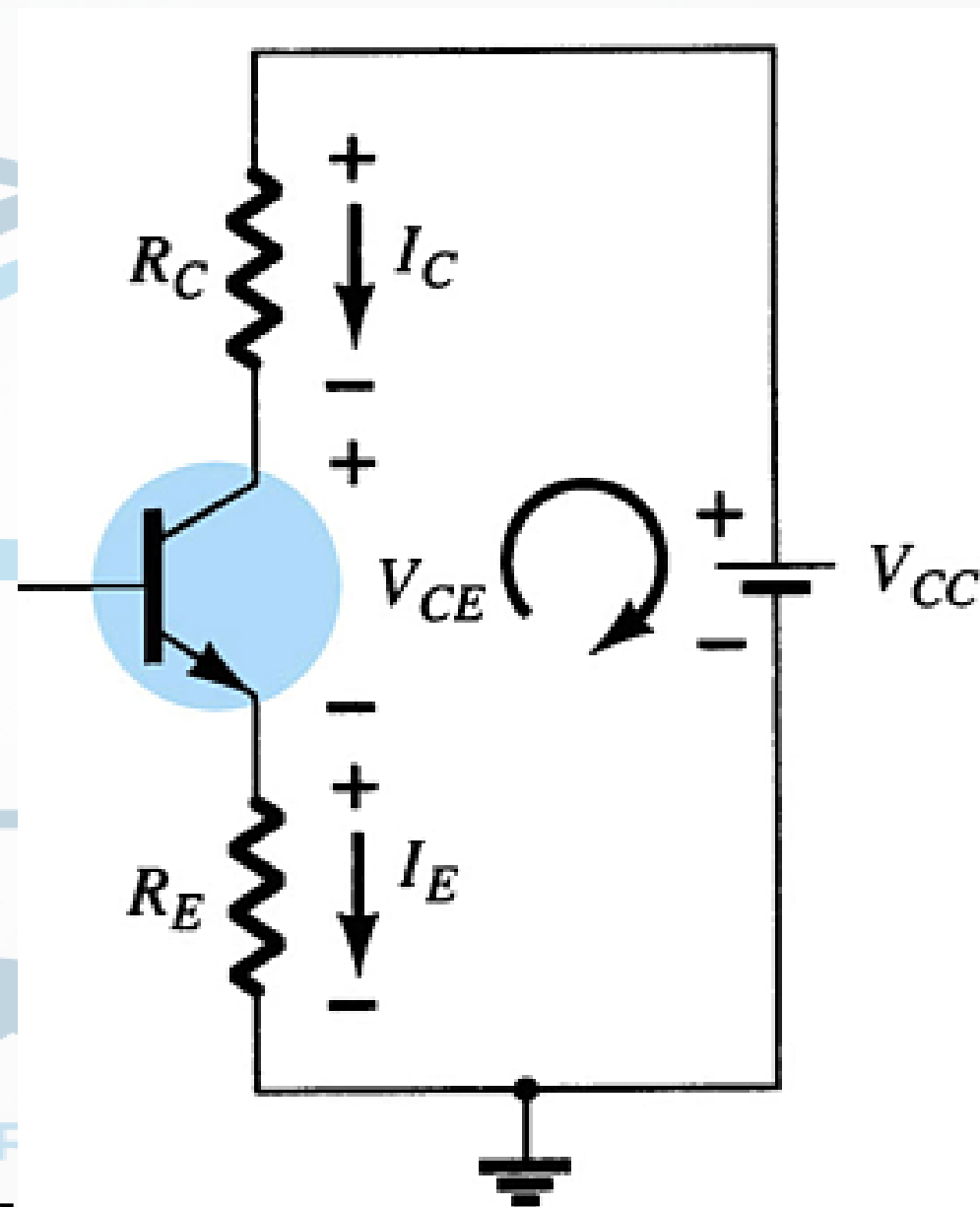
$$V_B = V_{CC} - I_R R_B = V_{BE} + V_E$$



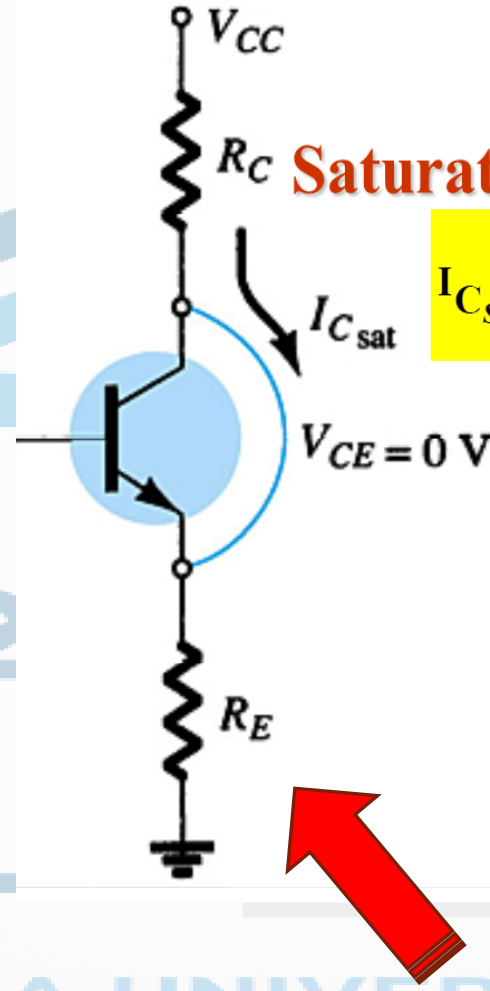
# Improved Biased Stability

*Stability* refers to a circuit condition in which the currents and voltages will remain fairly constant over a **wide range of temperatures and transistor Beta ( $\beta$ ) values.**



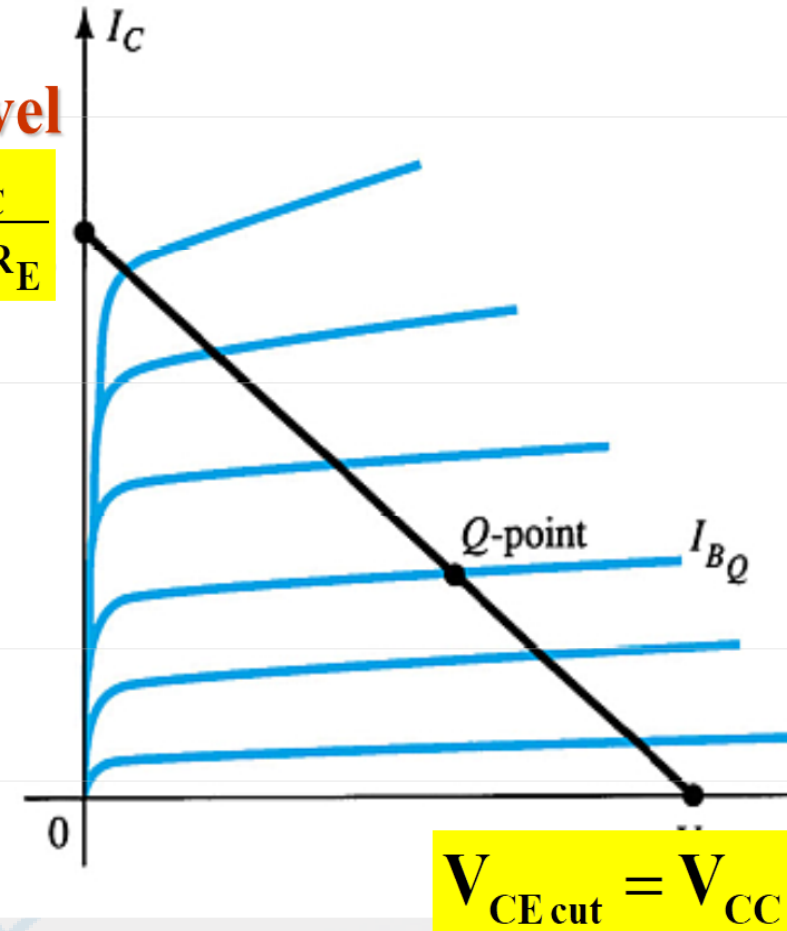**Saturation Level**

$$I_{C_{sat}} = \frac{V_{CC}}{R_C + R_E}$$



**Adding  $R_E$  to the emitter improves the stability of a transistor.**

# Voltage Divider Bias

This is a very stable bias circuit.

The currents and voltages are nearly independent of any variations in  $\beta$ .

## Approximate Analysis

Where  $I_B \ll I_1$  and  $I_1 \cong I_2$ :

$$V_B = \frac{R_2 V_{CC}}{R_1 + R_2}$$

Where  $\beta R_E > 10R_2$ :

$$I_E = \frac{V_E}{R_E}$$

$$V_E = V_B - V_{BE}$$

From Kirchhoff's voltage law:


$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

Transistor Saturation Level

$$I_{Csat} = I_{Cmax} = \frac{V_{CC}}{R_C + R_E}$$

Load Line Analysis  $I_E \cong I_C$

$$V_{CE} = V_{CC} - I_C (R_C + R_E)$$

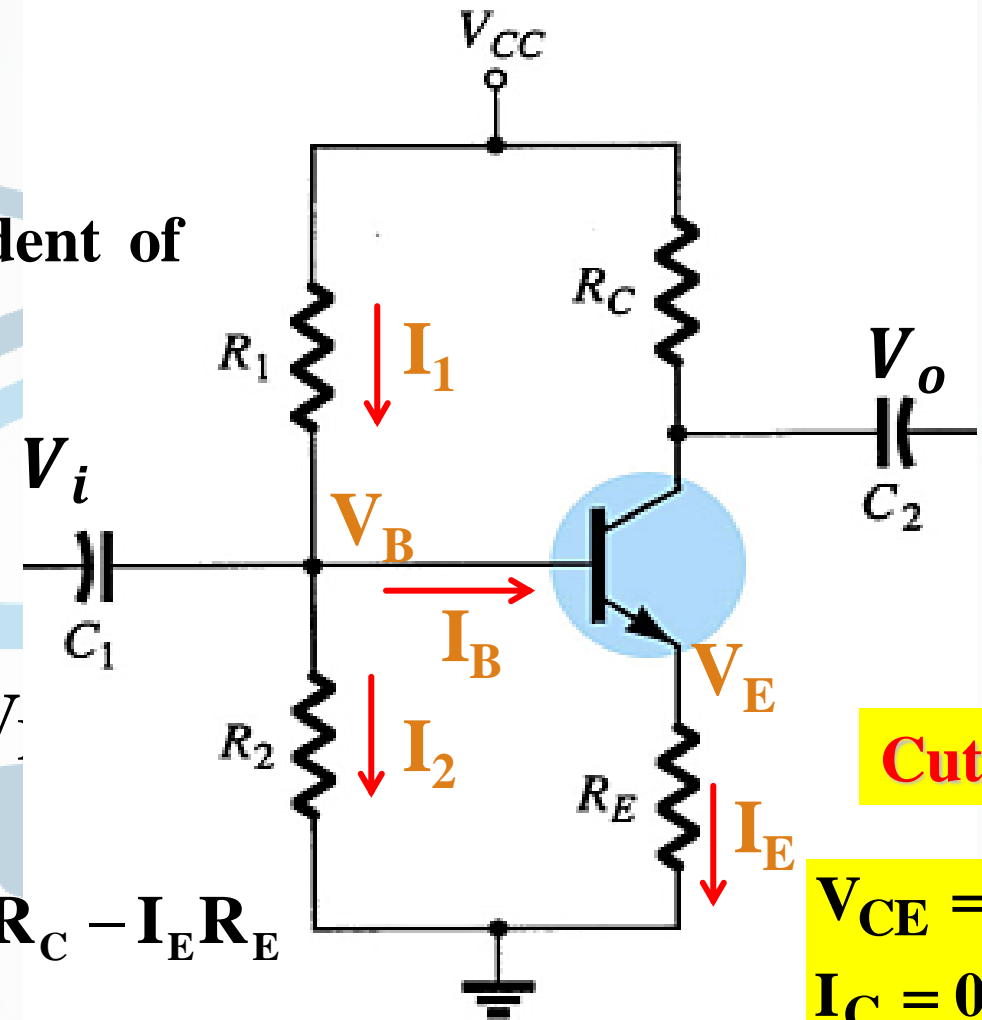


**Cutoff:**


$$V_{CE} = V_{CC}$$
$$I_C = 0\text{mA}$$

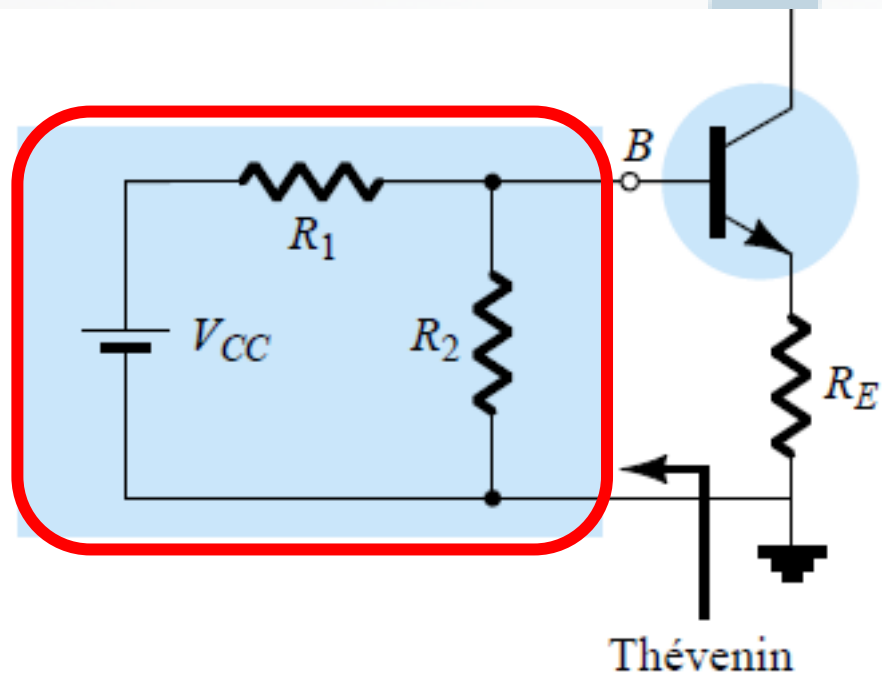**Saturation:**

$$I_C = \frac{V_{CC}}{R_C + R_E}$$
$$V_{CE} = 0\text{V}$$


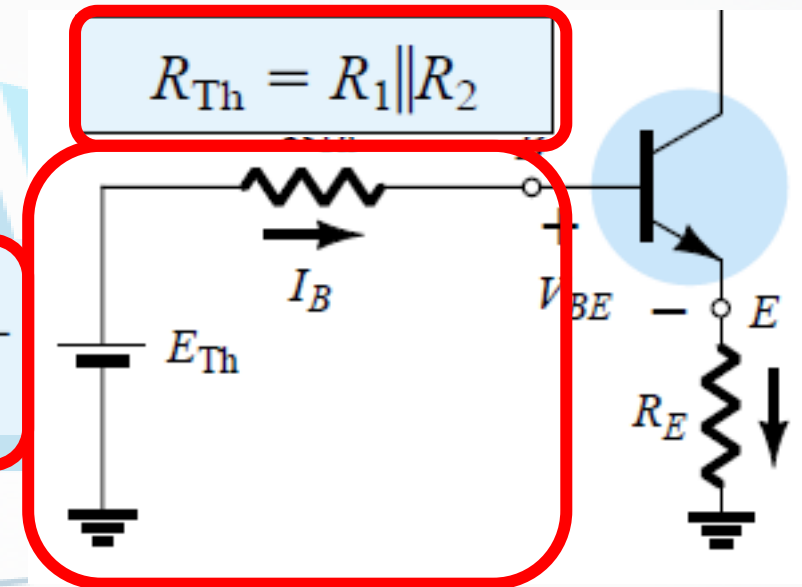
$$E_{Th} = V_{R_2} = \frac{R_2 V_{CC}}{R_1 + R_2}$$



$$I_B = \frac{E_{Th} - V_{BE}}{R_{Th} + (\beta + 1)R_E}$$

$$V_{CE} = V_{CC} - I_C(R_C + R_E)$$

# DC Bias with Voltage Feedback

Another way to improve the stability of a bias circuit is to add a feedback path from collector to base. In this bias circuit the Q-point is only slightly dependent on the transistor beta,  $\beta$ .

From Kirchhoff's voltage law:

$$V_{CC} - I'_C R_C - I_B R_B - V_{BE} - I_E R_E = 0$$


Where  $I_B \ll I_C$ :  $I'_C = I_C + I_B \cong I_C$

Knowing  $I_C = \beta I_B$  and  $I_E \cong I_C$ :

$$V_{CC} - \beta I_B R_C - I_B R_B - V_{BE} - \beta I_B R_E = 0$$

Solving for  $I_B$ :
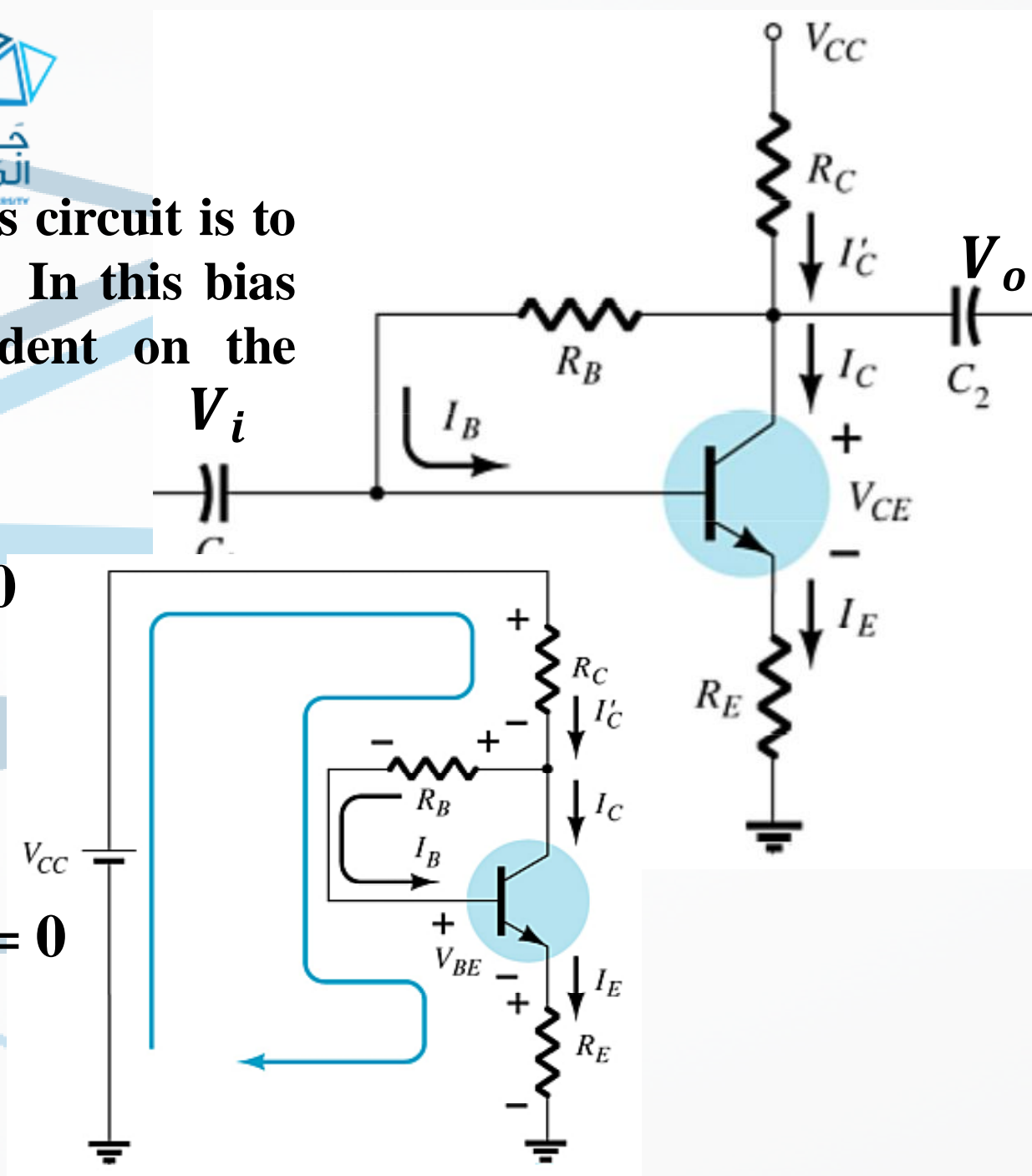
$$I_B = \frac{V_{CC} - V_{BE}}{R_B + \beta(R_C + R_E)}$$



# Collector-Emitter Loop



Applying Kirchoff's voltage law:  $I_E + V_{CE} + I'_C R_C - V_{CC} = 0$

Since  $I'_C \cong I_C$  and  $I_C = \beta I_B$ :  $I_C(R_C + R_E) + V_{CE} - V_{CC} = 0$

Solving for  $V_{CE}$ :  $V_{CE} = V_{CC} - I_C(R_C + R_E)$

Transistor Saturation Level

$$I_{Csat} = I_{Cmax} = \frac{V_{CC}}{R_C + R_E}$$

Load Line Analysis

Cutoff:


$$V_{CE} = V_{CC}$$

$$I_C = 0 \text{ mA}$$

Saturation:

$$I_C = \frac{V_{CC}}{R_C + R_E}$$


$$V_{CE} = 0 \text{ V}$$

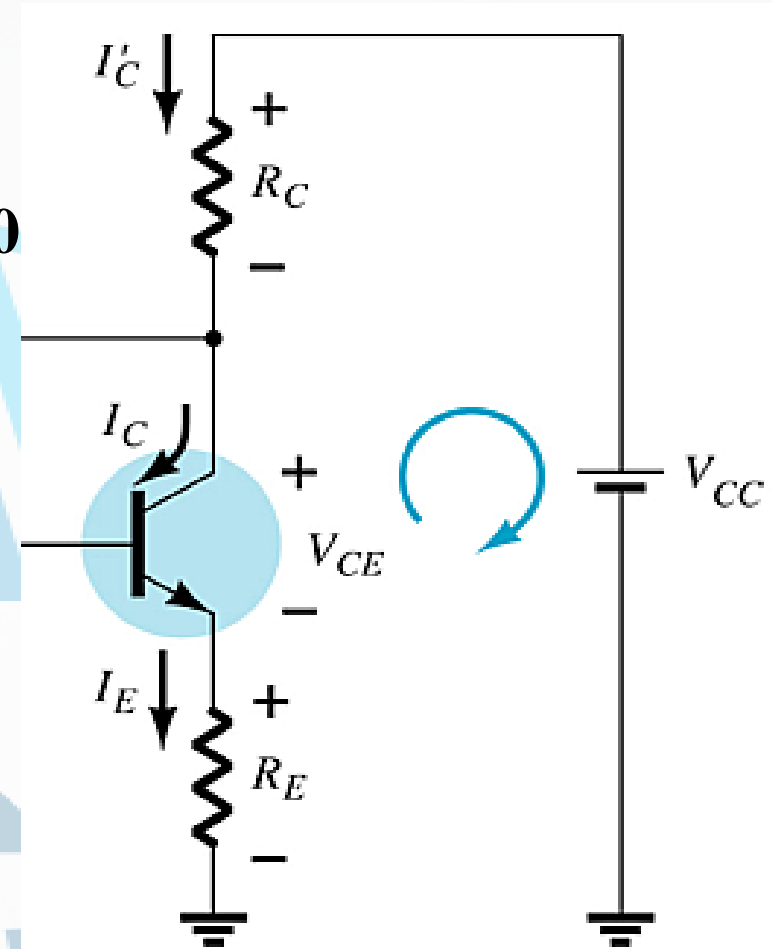


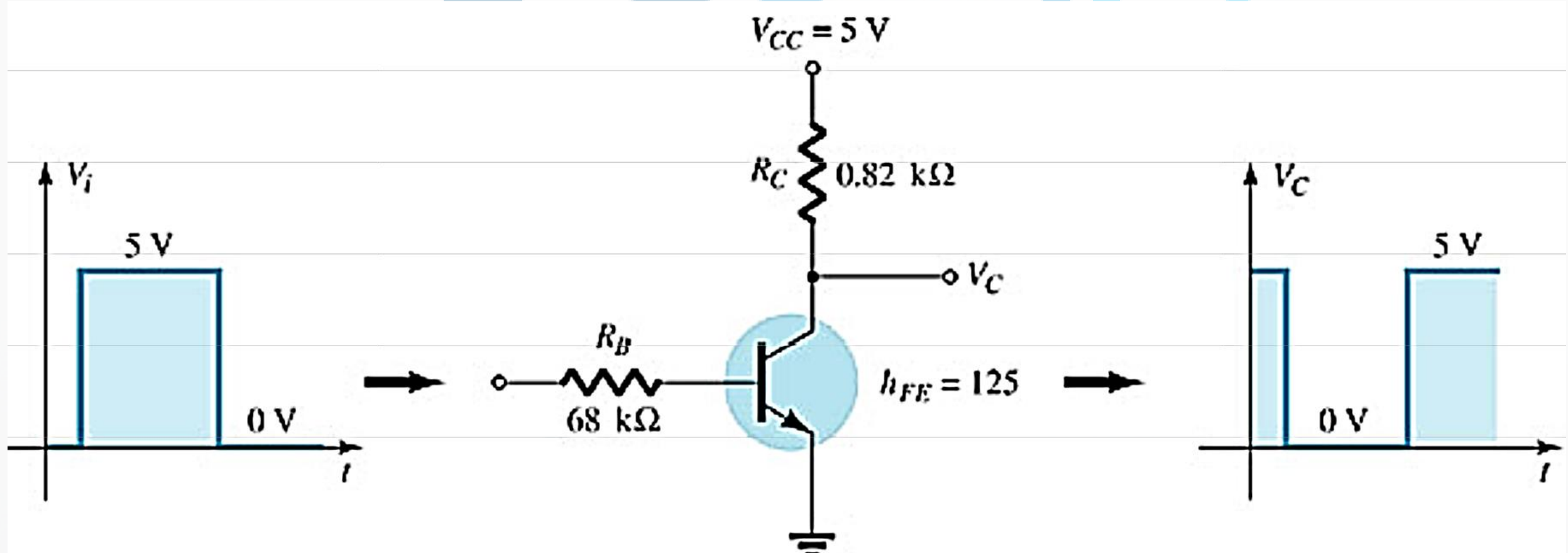
# Transistor Switching Networks

Transistors with only the DC source applied can be used as electronic switches.



# Switching Circuit Calculations



resistance at saturation

$$R_{\text{sat}} = \frac{V_{\text{CEsat}}}{I_{\text{Csat}}}$$

Saturation current:


$$I_{\text{Csat}} = \frac{V_{\text{CC}}}{R_{\text{C}}}$$

To ensure saturation:

$$I_{\text{B}} > \frac{I_{\text{Csat}}}{\beta_{\text{dc}}}$$

resistance at cutoff
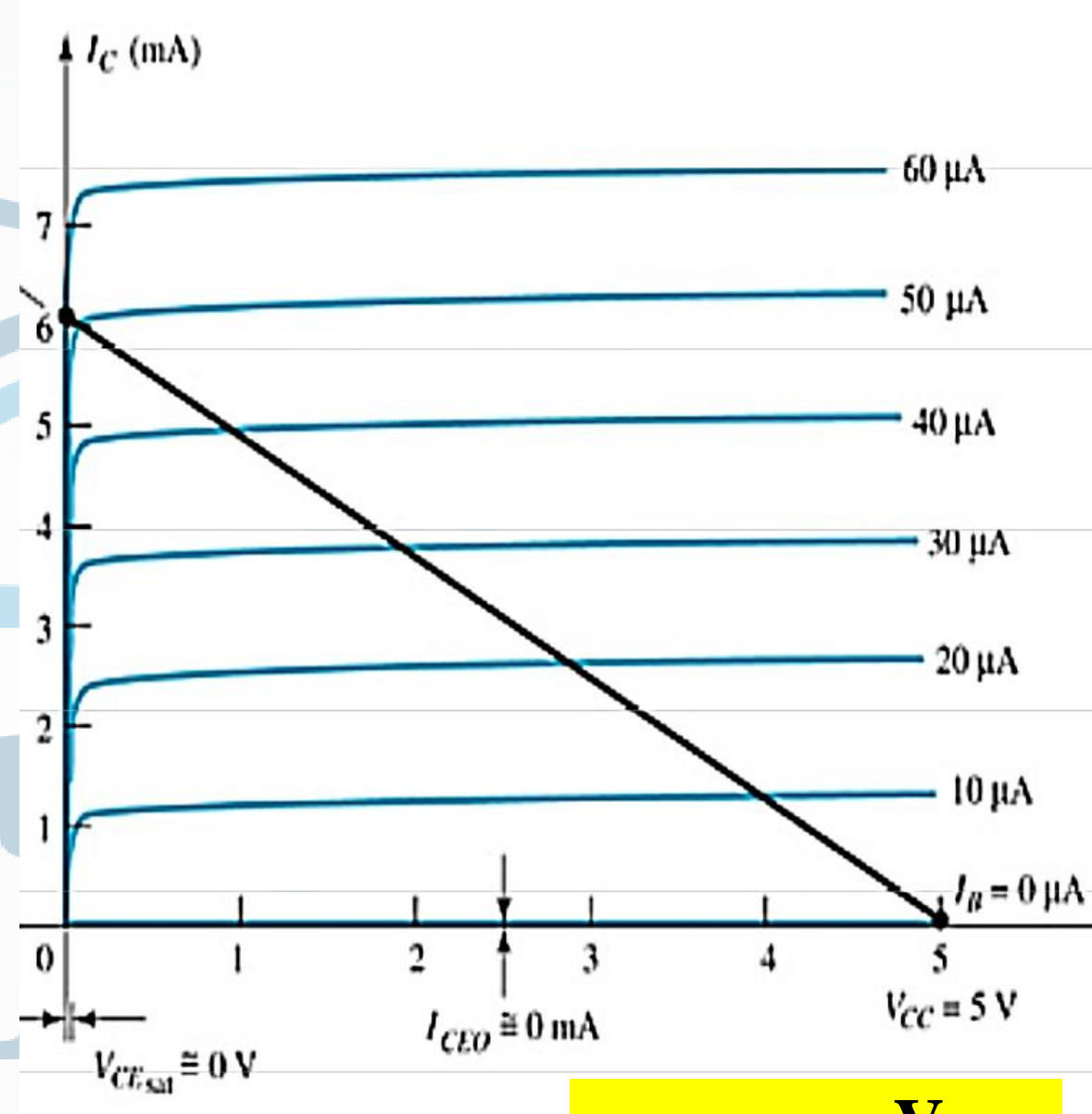
$$R_{\text{cutoff}} = \frac{V_{\text{CC}}}{I_{\text{CEO}}}$$



Transistor "on"

Transistor "off"

$I_c$

$$t_{on} = t_r + t_d$$

Transistor switching times:

100%  
90%

10%

$$t_{off} = t_s + t_f$$

$t_d$

$t_r$


$t_{on}$

$I_{on}$

$t_s$

$t_f$

$t_{off}$

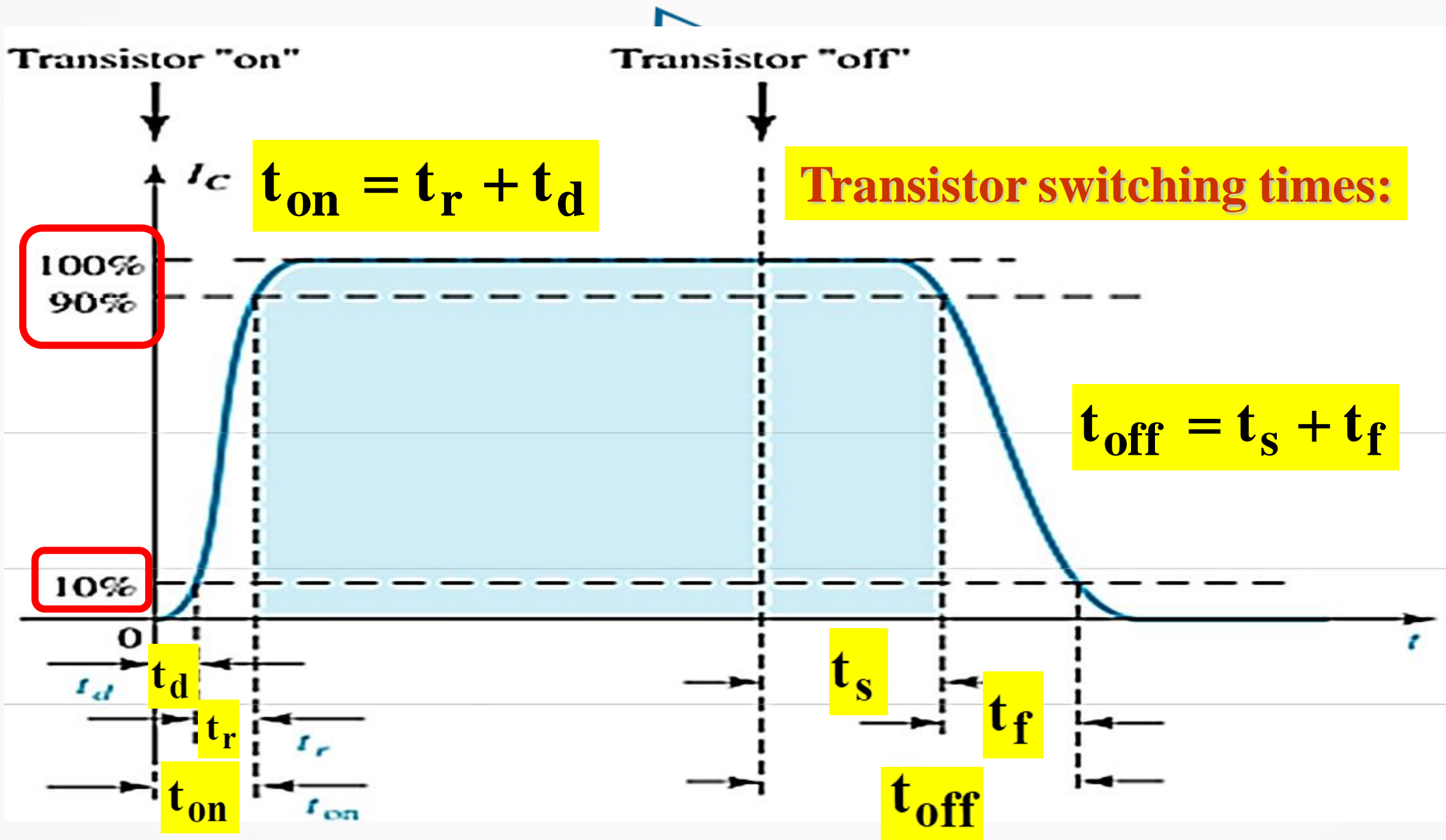

# PNP Transistors

The analysis for *pn*p transistor biasing circuits is the same as that for *np*n transistor circuits. The only difference is that the currents are flowing in the opposite direction.