



جامعة
المنارة


HAMAMA UNIVERSITY

Karnaugh Map

- Adjacent Squares
 - Number of squares = number of combinations
 - Each square represents a minterm
 - 2 Variables \Rightarrow 4 squares
 - 3 Variables \Rightarrow 8 squares
 - 4 Variables \Rightarrow 16 squares
 - Each two adjacent squares differ in one variable
 - Two adjacent minterms can be combined together

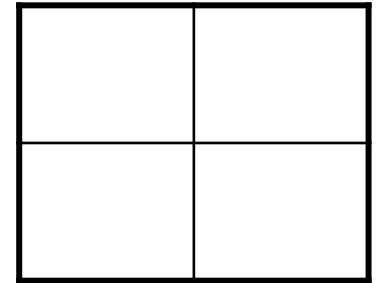Example:

$$\begin{aligned} F &= x y + x y' \\ &= x (y + y') \\ &= x \end{aligned}$$



Two-variable Map

	$x \ y$	Minterm	
0	0 0	m_0	$\bar{x} \bar{y}$
1	0 1	m_1	$\bar{x} y$
2	1 0	m_2	$x \bar{y}$
3	1 1	m_3	$x y$

Note: adjacent squares horizontally and vertically *NOT* diagonally

m_0	m_1
m_2	m_3

	y		
		0	1
x	0	$\bar{x} \bar{y}$	$\bar{x} y$
	1	$x \bar{y}$	$x y$



Two-variable Map

- Example

	x y	F	Minterm	
0	0 0	0	m_0	$\bar{x} \bar{y}$
1	0 1	0	m_1	$\bar{x} y$
2	1 0	0	m_2	$x \bar{y}$
3	1 1	1	m_3	$x y$

m_0	m_1
m_2	m_3

	y	
x	0	0
	0	1

		y	
		0	1
x	0	$\bar{x} \bar{y}$	$\bar{x} y$
	1	$x \bar{y}$	$x y$

Two-variable Map

- Example

	$x \ y$	F	Minterm	
0	0 0	0	m_0	$\bar{x} \bar{y}$
1	0 1	1	m_1	$\bar{x} y$
2	1 0	1	m_2	$x \bar{y}$
3	1 1	1	m_3	$x y$

m_0	m_1
m_2	m_3

	y
$x=0$	0
$x=1$	1

$$F = \bar{x} y + x y + x \bar{y}$$

$$(\bar{x} + x) y \quad x(y + \bar{y})$$

$$F = y + x$$

$x \backslash y$	0	1
0	$\bar{x} \bar{y}$	$\bar{x} y$
1	$x \bar{y}$	$x y$

Three-variable Map

	x y z	Minterm	
0	0 0 0	m_0	$\bar{x} \bar{y} \bar{z}$
1	0 0 1	m_1	$\bar{x} \bar{y} z$
2	0 1 0	m_2	$\bar{x} y \bar{z}$
3	0 1 1	m_3	$\bar{x} y z$
4	1 0 0	m_4	$x \bar{y} \bar{z}$
5	1 0 1	m_5	$x \bar{y} z$
6	1 1 0	m_6	$x y \bar{z}$
7	1 1 1	m_7	$x y z$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

		yz			
		00	01	11	10
x	0	$\bar{x} \bar{y} \bar{z}$	$\bar{x} \bar{y} z$	$\bar{x} y z$	$\bar{x} y \bar{z}$
	1	$x \bar{y} \bar{z}$	$x \bar{y} z$	$x y z$	$x y \bar{z}$

Three-variable Map

- Example

	x	y	z	F	Minterm
0	0	0	0	0	m_0 $\bar{x} \bar{y} \bar{z}$
1	0	0	1	0	m_1 $\bar{x} \bar{y} z$
2	0	1	0	1	m_2 $\bar{x} y \bar{z}$
3	0	1	1	1	m_3 $\bar{x} y z$
4	1	0	0	1	m_4 $x \bar{y} \bar{z}$
5	1	0	1	1	m_5 $x \bar{y} z$
6	1	1	0	0	m_6 $x y \bar{z}$
7	1	1	1	0	m_7 $x y z$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

	yz	00	01	11	10
x	0	$\bar{x} \bar{y} \bar{z}$	$\bar{x} \bar{y} z$	$\bar{x} y z$	$\bar{x} y \bar{z}$
	1	$x \bar{y} \bar{z}$	$x \bar{y} z$	$x y z$	$x y \bar{z}$

		y			
		0	0	1	1
x		1	1	0	0
				z	

$$F = x \bar{y} + \bar{x} y$$

Three-variable Map

- Example

	$x y z$	F	Minterm	
0	0 0 0	0	m_0	$\bar{x} \bar{y} \bar{z}$
1	0 0 1	0	m_1	$\bar{x} \bar{y} z$
2	0 1 0	0	m_2	$\bar{x} y \bar{z}$
3	0 1 1	1	m_3	$\bar{x} y z$
4	1 0 0	1	m_4	$x \bar{y} \bar{z}$
5	1 0 1	0	m_5	$x \bar{y} z$
6	1 1 0	1	m_6	$x y \bar{z}$
7	1 1 1	1	m_7	$x y z$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

	yz	00	01	11	10
x	0	$\bar{x} \bar{y} \bar{z}$	$\bar{x} \bar{y} z$	$\bar{x} y z$	$\bar{x} y \bar{z}$
	1	$x \bar{y} \bar{z}$	$x \bar{y} z$	$x y z$	$x y \bar{z}$

		y			
		0	0	1	0
x	1	0	0	1	1
				z	


Diagram showing Karnaugh map with groupings: a green circle around the 1 in the top-right cell (yz=11, x=0), an orange circle around the 1s in the bottom-right two cells (yz=10, x=1), and a blue circle around the 1s in the bottom-left two cells (yz=00, x=1). An orange arrow labeled "Extra" points from the orange circle to the final equation.

$$F = \bar{x} \bar{z} + yz + \cancel{x y}$$

Three-variable Map

- Example

	x	y	z	F	Minterm
0	0	0	0	0	m_0 $\bar{x} \bar{y} \bar{z}$
1	0	0	1	1	m_1 $\bar{x} \bar{y} z$
2	0	1	0	0	m_2 $\bar{x} y \bar{z}$
3	0	1	1	1	m_3 $\bar{x} y z$
4	1	0	0	0	m_4 $x \bar{y} \bar{z}$
5	1	0	1	1	m_5 $x \bar{y} z$
6	1	1	0	0	m_6 $x y \bar{z}$
7	1	1	1	1	m_7 $x y z$

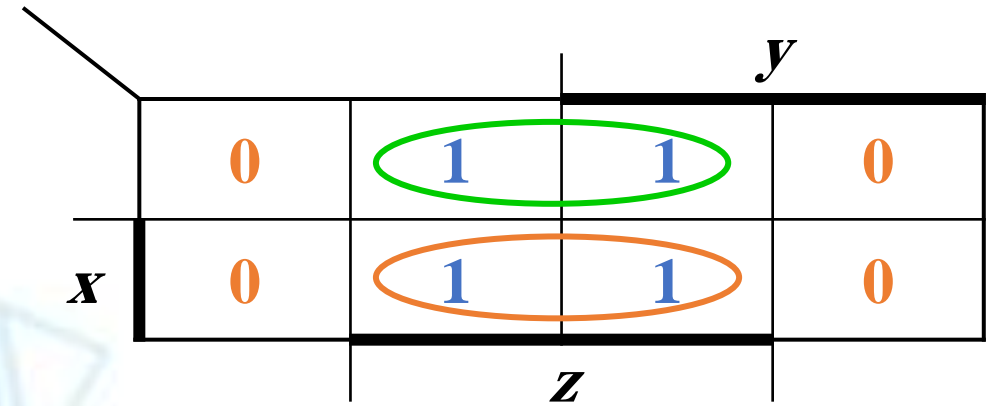


$$F = \bar{x} \bar{y} z + \bar{x} y z + x \bar{y} z + x y z$$

$$\bar{x} z (\bar{y} + y) \quad x z (\bar{y} + y)$$

$$\bar{x} z \quad x z$$

$$z$$

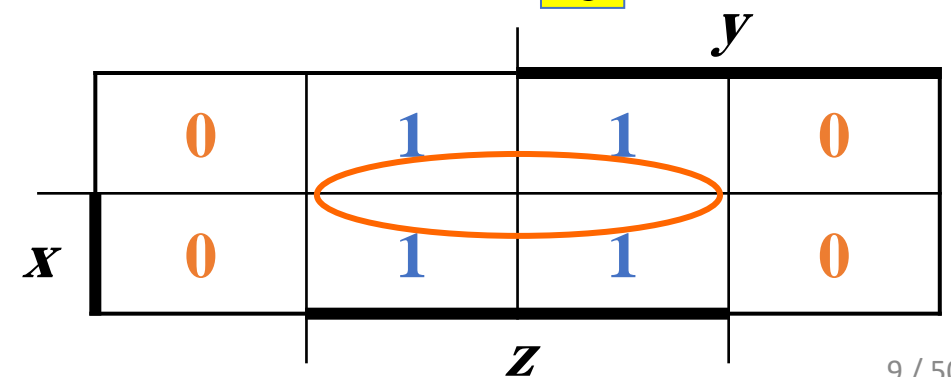

Three-variable Map

- Example

	$x y z$	F	Minterm	
0	0 0 0	1	m_0	$\bar{x} \bar{y} \bar{z}$
1	0 0 1	0	m_1	$\bar{x} \bar{y} z$
2	0 1 0	1	m_2	$\bar{x} y \bar{z}$
3	0 1 1	0	m_3	$\bar{x} y z$
4	1 0 0	1	m_4	$x \bar{y} \bar{z}$
5	1 0 1	1	m_5	$x \bar{y} z$
6	1 1 0	1	m_6	$x y \bar{z}$
7	1 1 1	0	m_7	$x y z$

m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6

		yz			
		00	01	11	10
x	0	$\bar{x} \bar{y} \bar{z}$	$\bar{x} \bar{y} z$	$\bar{x} y z$	$\bar{x} y \bar{z}$
	1	$x \bar{y} \bar{z}$	$x \bar{y} z$	$x y z$	$x y \bar{z}$

		y			
		0	1	0	1
x	0	1	0	0	1
	1	1	1	0	1
		z			

$$F = \bar{z} + x \bar{y}$$

Four-variable Map

	<i>w x y z</i>	Minterm	
0	0 0 0 0	m_0	$\bar{w} \bar{x} \bar{y} \bar{z}$
1	0 0 0 1	m_1	$\bar{w} \bar{x} \bar{y} z$
2	0 0 1 0	m_2	$\bar{w} \bar{x} y \bar{z}$
3	0 0 1 1	m_3	$\bar{w} \bar{x} y z$
4	0 1 0 0	m_4	$\bar{w} x \bar{y} \bar{z}$
5	0 1 0 1	m_5	$\bar{w} x \bar{y} z$
6	0 1 1 0	m_6	$\bar{w} x y \bar{z}$
7	0 1 1 1	m_7	$\bar{w} x y z$
8	1 0 0 0	m_8	$w \bar{x} \bar{y} \bar{z}$
9	1 0 0 1	m_9	$w \bar{x} \bar{y} z$
10	1 0 1 0	m_{10}	$w \bar{x} y \bar{z}$
11	1 0 1 1	m_{11}	$w \bar{x} y z$
12	1 1 0 0	m_{12}	$w x \bar{y} \bar{z}$
13	1 1 0 1	m_{13}	$w x \bar{y} z$
14	1 1 1 0	m_{14}	$w x y \bar{z}$
15	1 1 1 1	m_{15}	$w x y z$


m_0	m_1	m_3	m_2
m_4	m_5	m_7	m_6
m_{12}	m_{13}	m_{15}	m_{14}
m_8	m_9	m_{11}	m_{10}

		<i>yz</i>			
		00	01	11	10
<i>wx</i>	00	$\bar{w} \bar{x} \bar{y} \bar{z}$	$\bar{w} \bar{x} \bar{y} z$	$\bar{w} \bar{x} y z$	$\bar{w} \bar{x} y \bar{z}$
	01	$\bar{w} x \bar{y} \bar{z}$	$\bar{w} x \bar{y} z$	$\bar{w} x y z$	$\bar{w} x y \bar{z}$
	11	$w x \bar{y} \bar{z}$	$w x \bar{y} z$	$w x y z$	$w x y \bar{z}$
	10	$w \bar{x} \bar{y} \bar{z}$	$w \bar{x} \bar{y} z$	$w \bar{x} y z$	$w \bar{x} y \bar{z}$

Four-variable Map

- Example

	w	x	y	z	F	Minterm
0	0	0	0	0	1	m_0 $\bar{w}\bar{x}\bar{y}\bar{z}$
1	0	0	0	1	1	m_1 $\bar{w}\bar{x}\bar{y}z$
2	0	0	1	0	1	m_2 $\bar{w}\bar{x}y\bar{z}$
3	0	0	1	1	0	m_3 $\bar{w}\bar{x}yz$
4	0	1	0	0	1	m_4 $\bar{w}x\bar{y}\bar{z}$
5	0	1	0	1	1	m_5 $\bar{w}x\bar{y}z$
6	0	1	1	0	1	m_6 $\bar{w}xy\bar{z}$
7	0	1	1	1	0	m_7 $\bar{w}xyz$
8	1	0	0	0	1	m_8 $w\bar{x}\bar{y}\bar{z}$
9	1	0	0	1	1	m_9 $w\bar{x}\bar{y}z$
10	1	0	1	0	0	m_{10} $w\bar{x}y\bar{z}$
11	1	0	1	1	0	m_{11} $w\bar{x}yz$
12	1	1	0	0	1	m_{12} $wx\bar{y}\bar{z}$
13	1	1	0	1	1	m_{13} $wx\bar{y}z$
14	1	1	1	0	1	m_{14} $wxy\bar{z}$
15	1	1	1	1	0	m_{15} $wxyz$

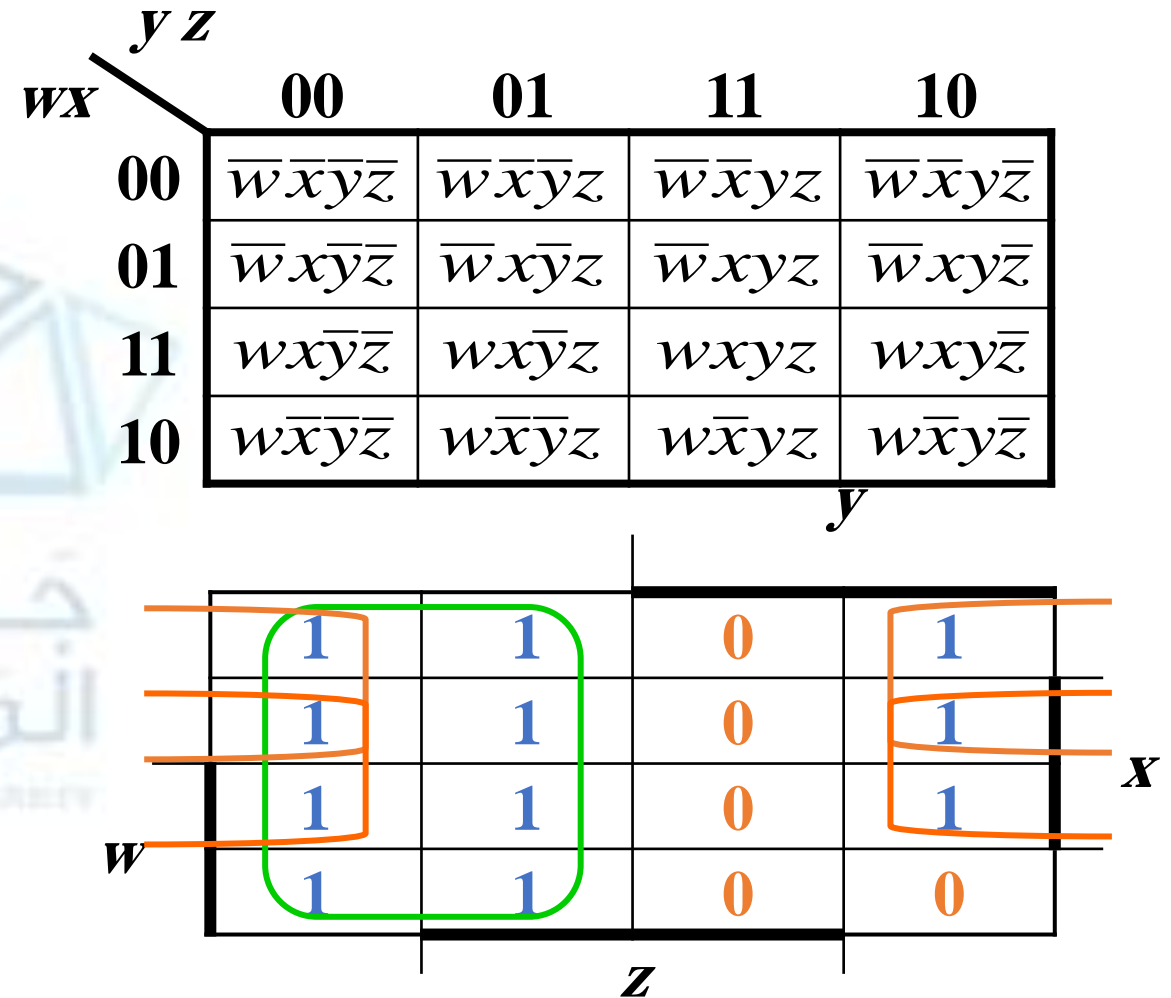


$$F = \bar{y} + \bar{w}\bar{z} + x\bar{z}$$

Four-variable Map

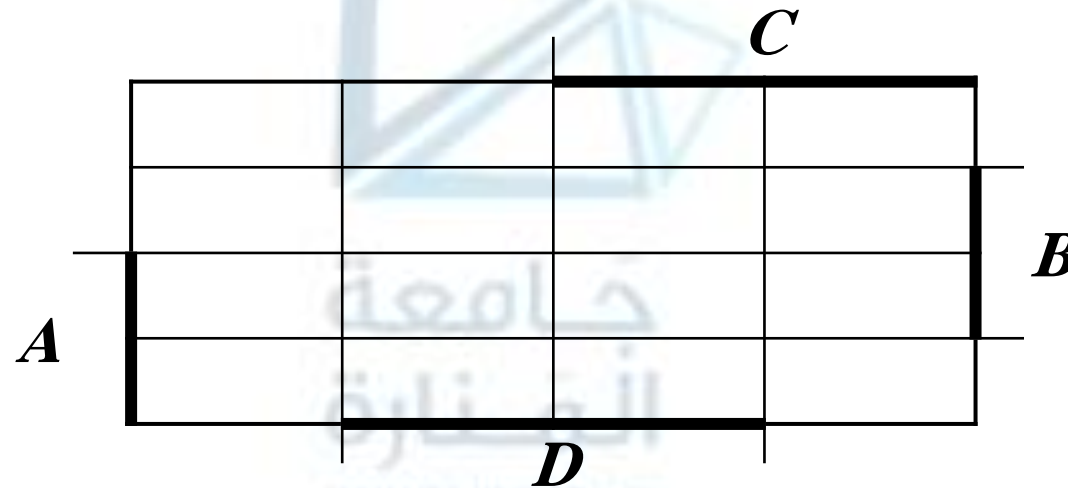- Example


Simplify: $F = A' B' C' + B' C D' + A' B C D' + A B' C'$



Four-variable Map

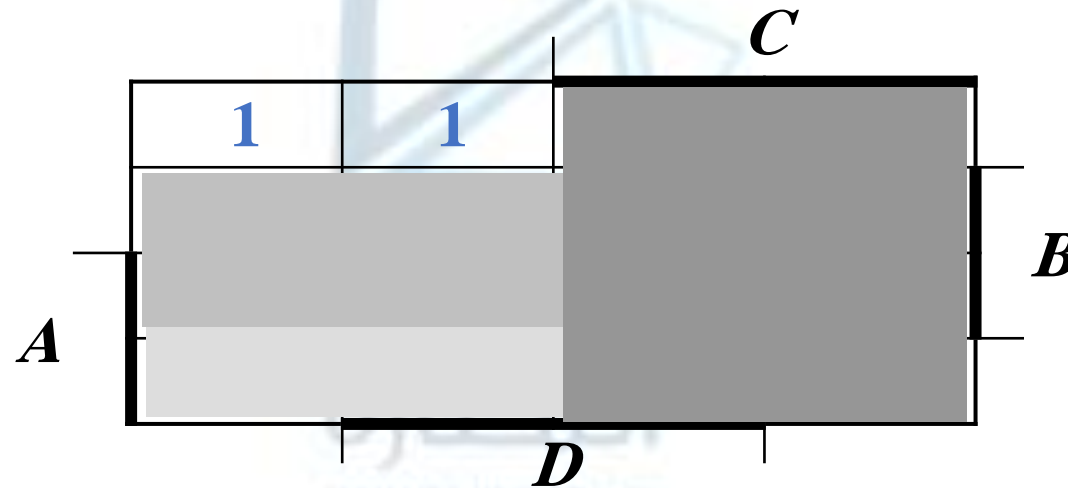- Example


Simplify: $F = A'B'C' + B'CD' + A'BCD' + AB'C'$



Four-variable Map

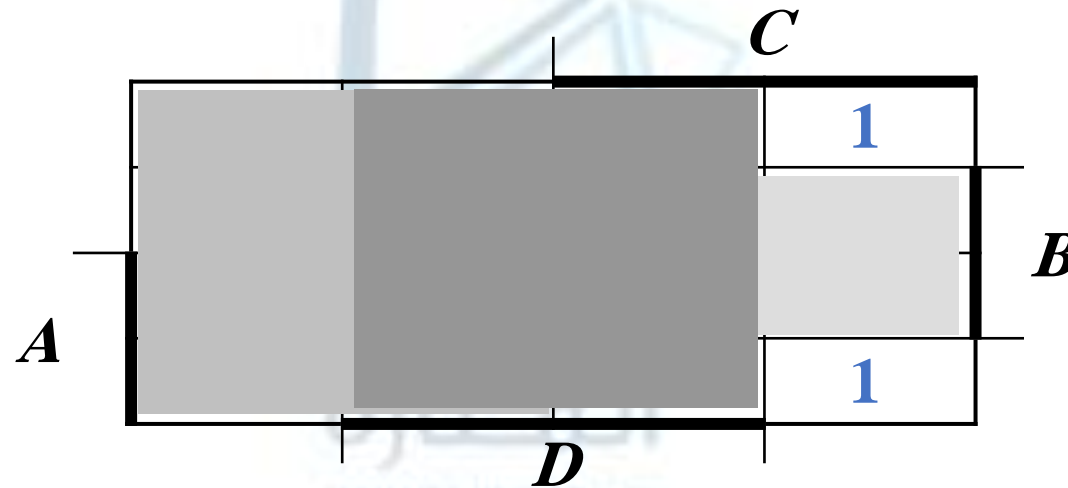- Example


Simplify: $F = A' B' C' + B' C D' + A' B C D' + A B' C'$



Four-variable Map

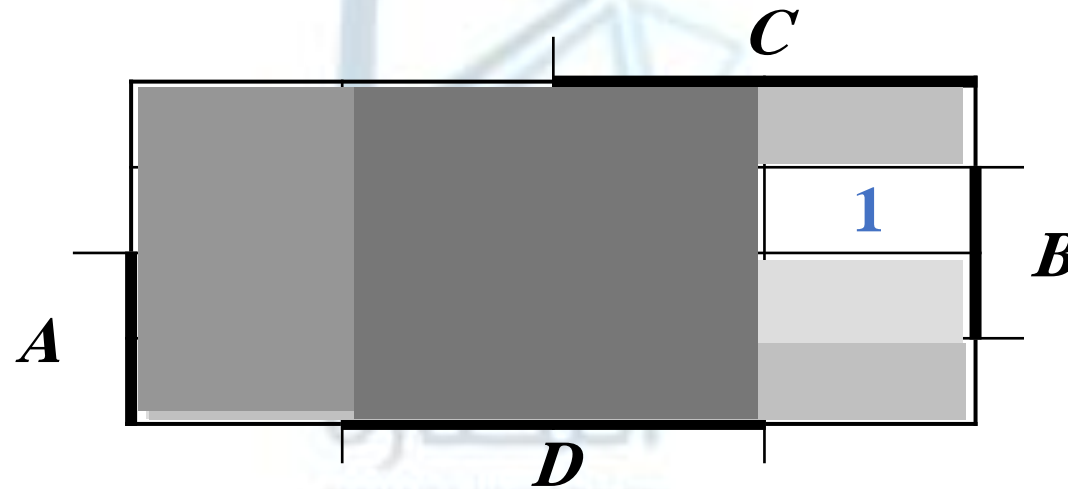- Example


Simplify: $F = A' B' C' + B' C D' + A' B C D' + A B' C'$



Four-variable Map

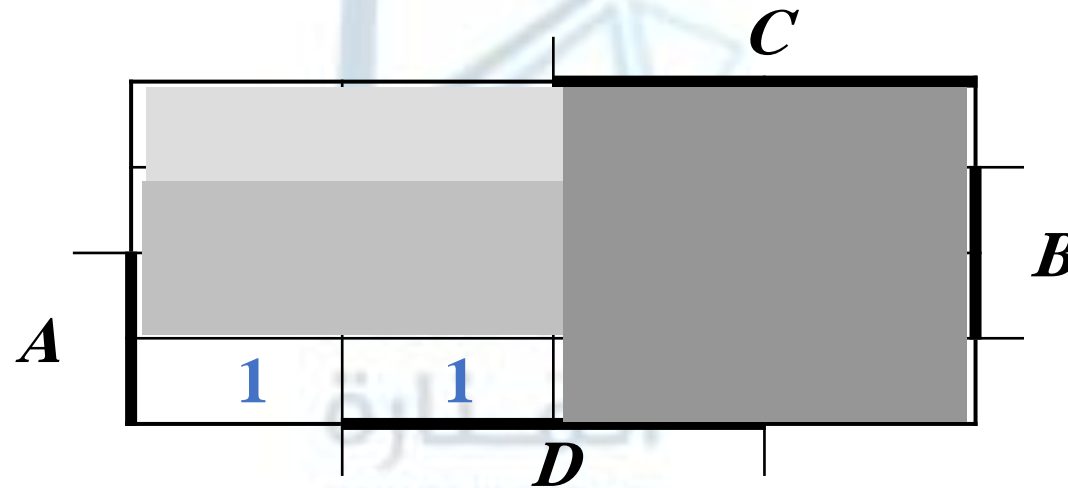- Example

Simplify: $F = A'B'C' + B'CD' + A'BCD' + AB'C'$



Five-variable Map

		<i>DE</i>		D	
		00	01	11	10
B	<i>BC</i>	00	01	11	10
	00	m_0	m_1	m_3	m_2
	01	m_4	m_5	m_7	m_6
	11	m_{12}	m_{13}	m_{15}	m_{14}
	10	m_8	m_9	m_{11}	m_{10}
		E			


A = 0

		<i>DE</i>		D	
		00	01	11	10
B	<i>BC</i>	00	01	11	10
	00	m_{16}	m_{17}	m_{19}	m_{18}
	01	m_{20}	m_{21}	m_{23}	m_{22}
	11	m_{28}	m_{29}	m_{31}	m_{30}
	10	m_{24}	m_{25}	m_{27}	m_{26}
		E			



A = 1

Five-variable Map

$A = 0$

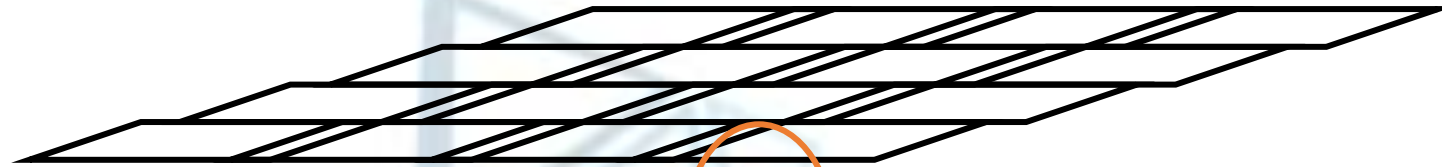

$A = 1$

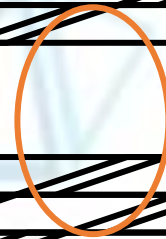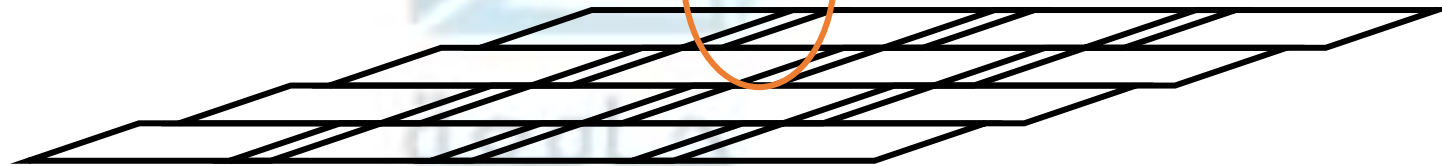

المنارة
HAMARA UNIVERSITY



Implicants

Implicant:

Gives $F=1$

			1	
1	1	1		
	1	1	1	
	1			

Prime Implicants

Prime Implicant:
Can't grow beyond this
size


		1		
	1	1	1	
				1
	1	1		
	1			



Essential Prime Implicants

Essential Prime Implicant:
No other choice

Not essential

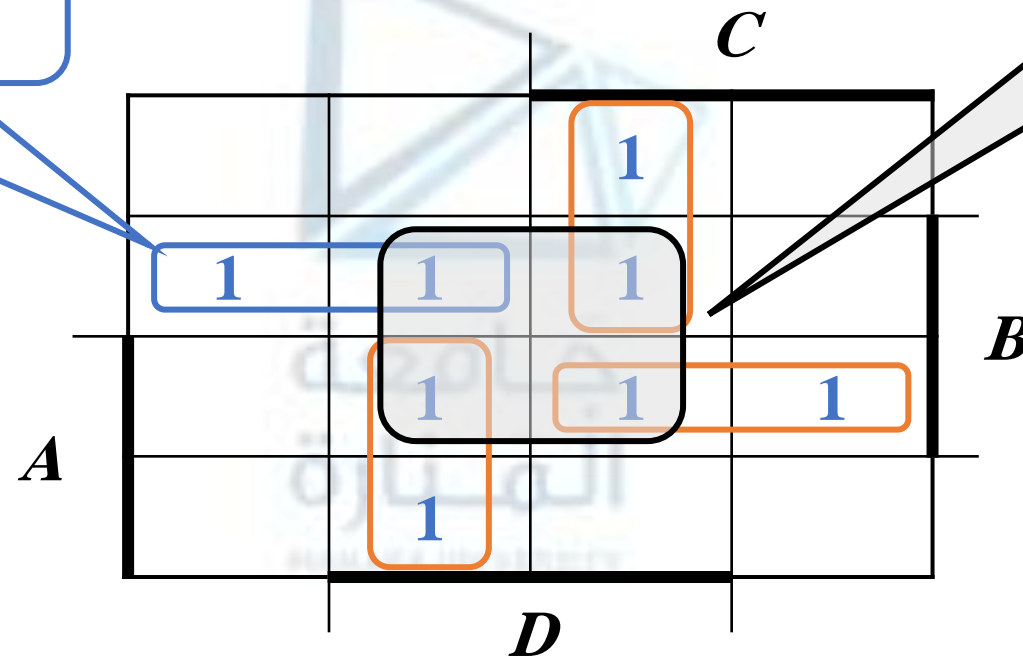

8 Implicants



5 Prime implicants

4 Essential prime implicants




Product of Sums Simplification

	<i>w x y z</i>	<i>F</i>	\overline{F}
0	0 0 0 0	1	0
1	0 0 0 1	1	0
2	0 0 1 0	1	0
3	0 0 1 1	0	1
4	0 1 0 0	1	0
5	0 1 0 1	1	0
6	0 1 1 0	1	0
7	0 1 1 1	0	1
8	1 0 0 0	1	0
9	1 0 0 1	1	0
10	1 0 1 0	0	1
11	1 0 1 1	0	1
12	1 1 0 0	1	0
13	1 1 0 1	1	0
14	1 1 1 0	1	0
15	1 1 1 1	0	1

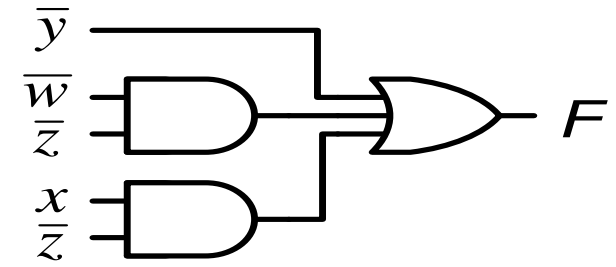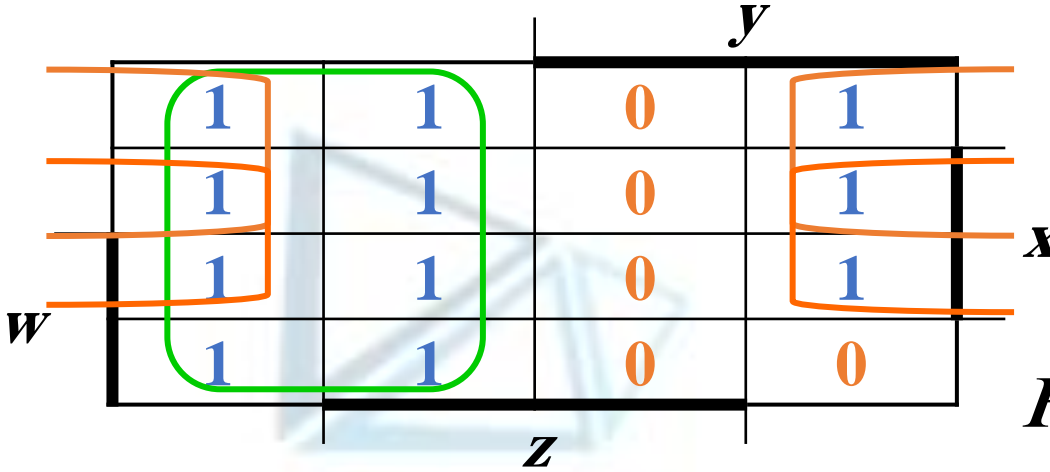

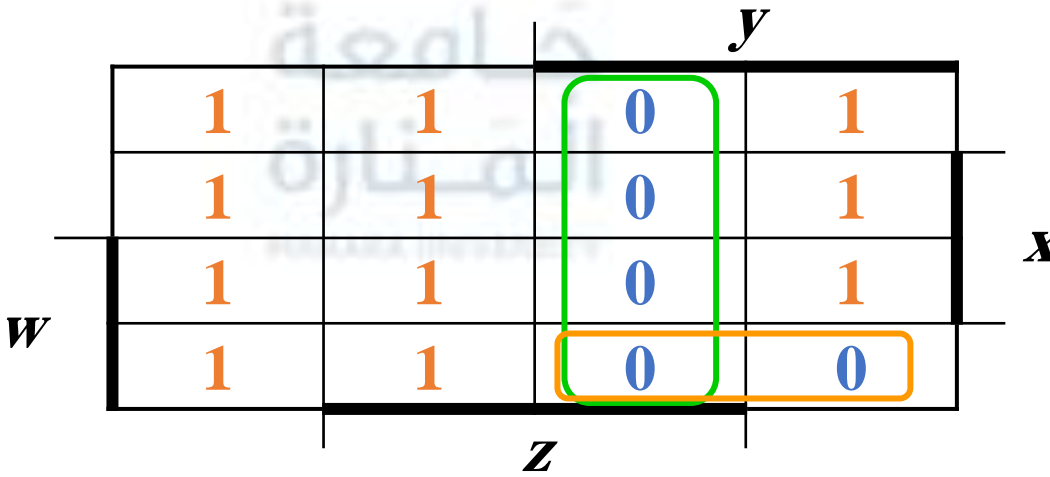
$$F = \overline{y} + \overline{w} \overline{z} + x \overline{z}$$



$$\overline{F} = y z + w \overline{x} y$$
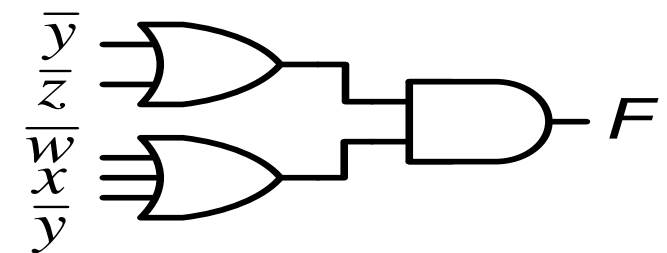
$$\overline{\overline{F}} = \overline{y z + w \overline{x} y}$$



$$F = (\overline{y} + \overline{z}) \cdot (\overline{w} + x + \overline{y})$$

Don't-Care Condition

- Example



$$A = \begin{cases} 1 & \text{if a quarter is deposited} \\ 0 & \text{otherwise} \end{cases}$$

$$B = \begin{cases} 1 & \text{if a dime is deposited} \\ 0 & \text{otherwise} \end{cases}$$

$$C = \begin{cases} 1 & \text{if a nickel is deposited} \\ 0 & \text{otherwise} \end{cases}$$


A	B	C	\$ Value
0	0	0	\$ 0.00
0	0	1	\$ 0.05
0	1	0	\$ 0.10
0	1	1	Not possible
1	0	0	\$ 0.25
1	0	1	Not possible
1	1	0	Not possible
1	1	1	Not possible

You can only drop one coin at a time.

Used as "don't care"

Don't-Care Condition

- Example

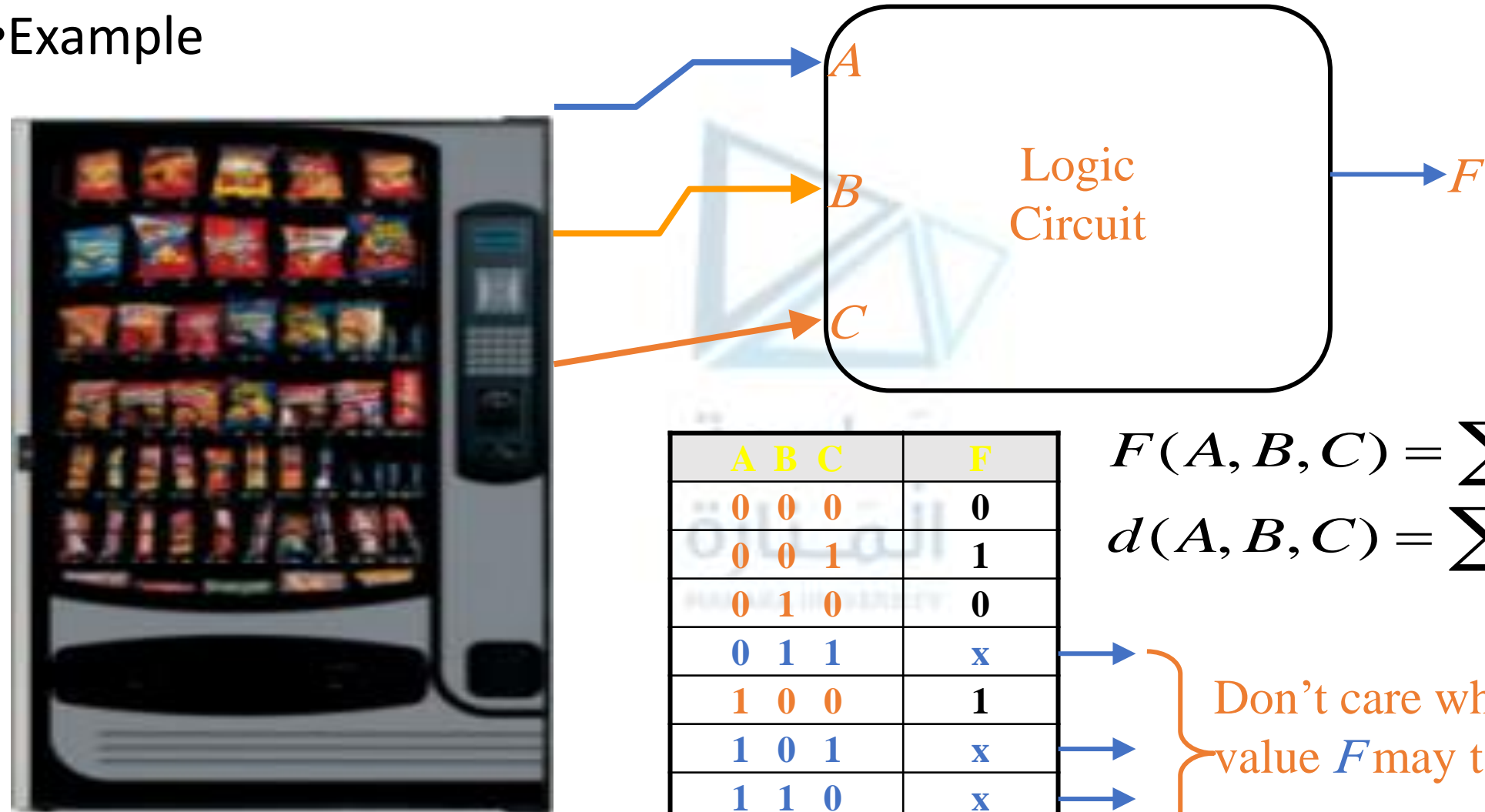

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	x
1	0	0	1
1	0	1	x
1	1	0	x
1	1	1	x


$$F(A, B, C) = \sum (1, 4)$$

$$d(A, B, C) = \sum (3, 5, 6, 7)$$

Don't care what
value F may take

Don't-Care Condition

- Example

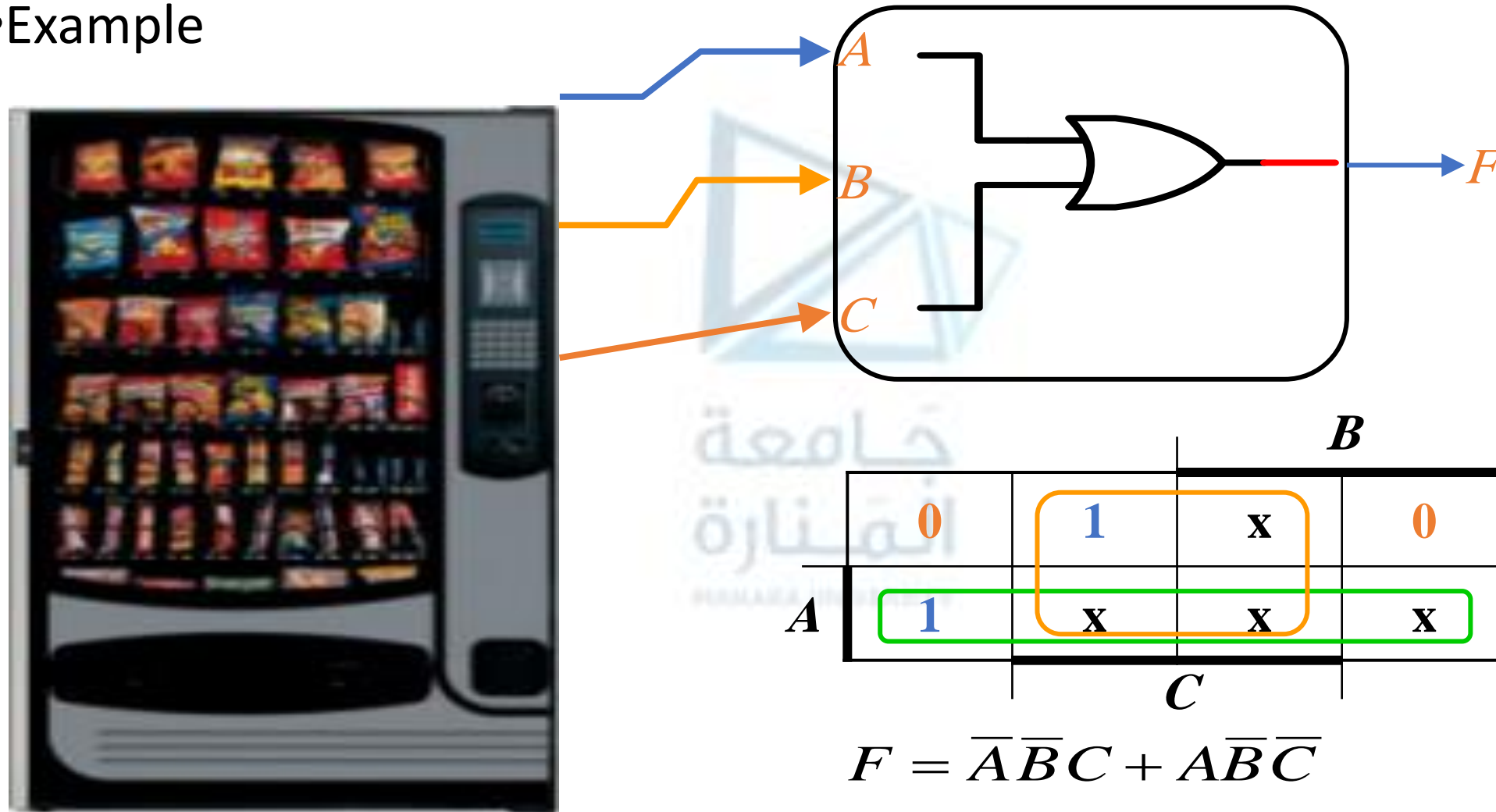

	<i>B</i>			
	0	1	x	0
<i>A</i>	1	x	x	x

$$F = \bar{A}\bar{B}C + A\bar{B}\bar{C}$$

$$F = A + C$$




Don't-Care Condition


- Example

$$F(w, x, y, z) = \sum(1, 3, 7, 11, 15)$$

$$d(w, x, y, z) = \sum(0, 2, 5)$$

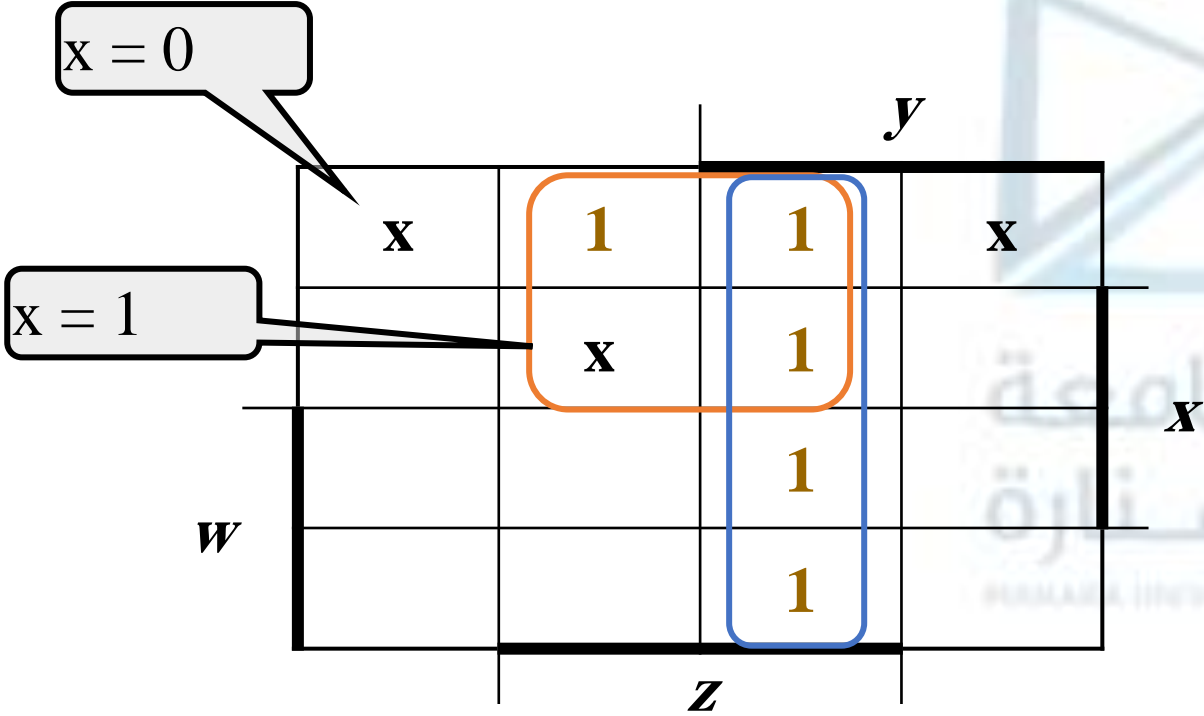

$$F = yz + \bar{w}z$$

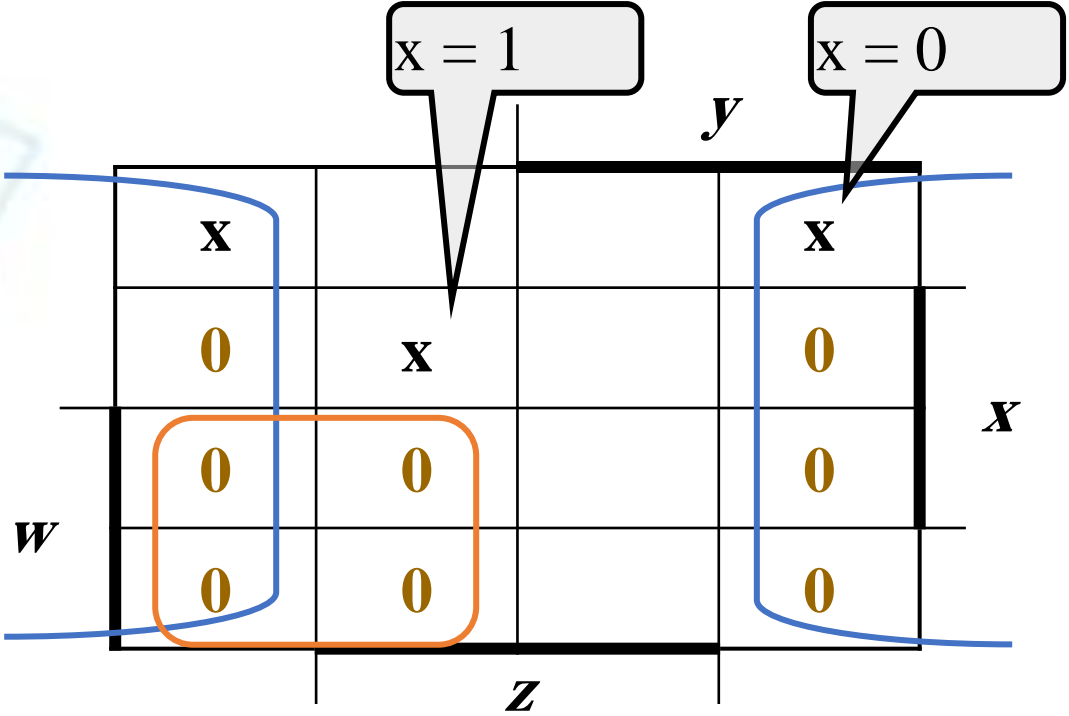

$$\bar{F} = \bar{z} + w\bar{y}$$

Universal Gates

- One Type
 - Use as many as you need (quantity), but one type only.
- Perform Basic Operations
 - AND, OR, and NOT
- NAND Gate
 - NOT-AND functions
 - OR function can be obtained from AND by Demorgan's
- NOR Gate
 - NOT-OR functions (AND by Demorgan's)




قائمة
المنازة




Universal Gates

- NAND Gate


- NOT:

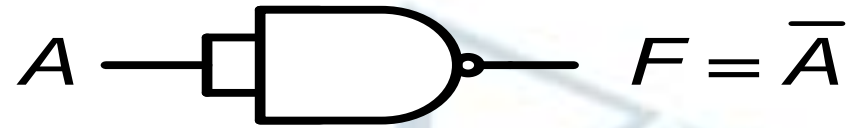

- AND:

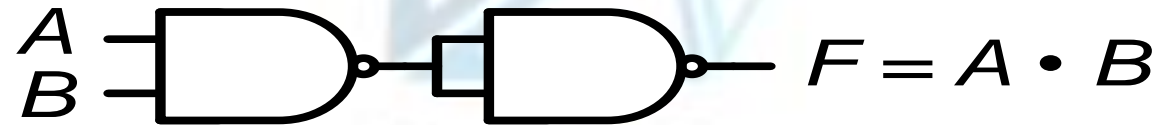

- OR:

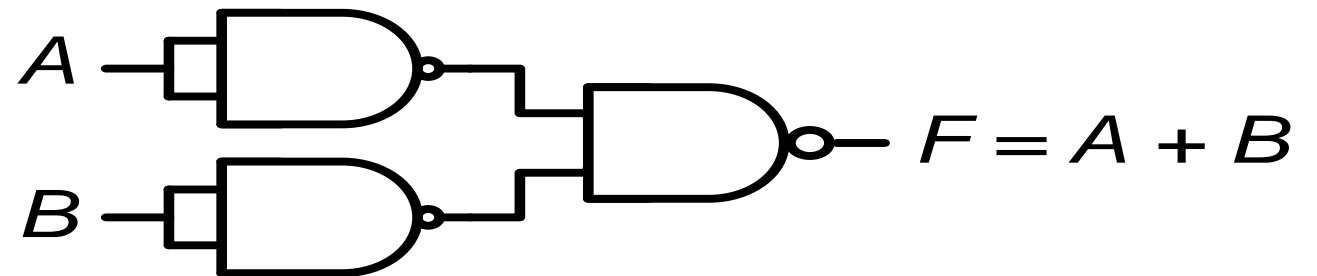

Universal Gates

- NOR Gate


- NOT:



- OR:









- AND:

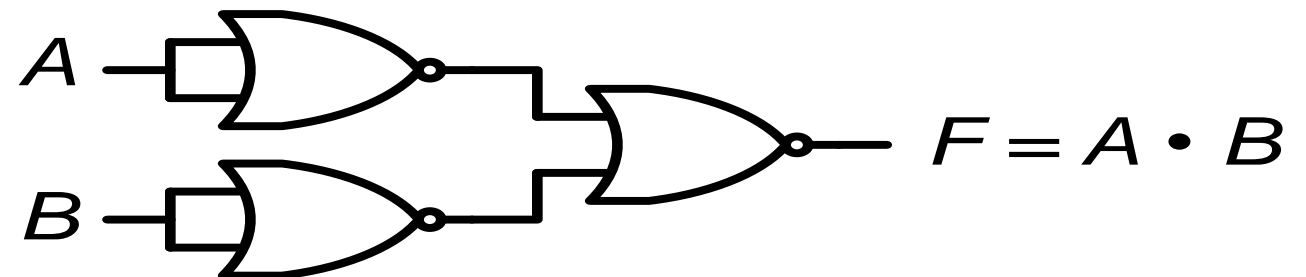







NAND & NOR Implementation

- Two-Level Implementation

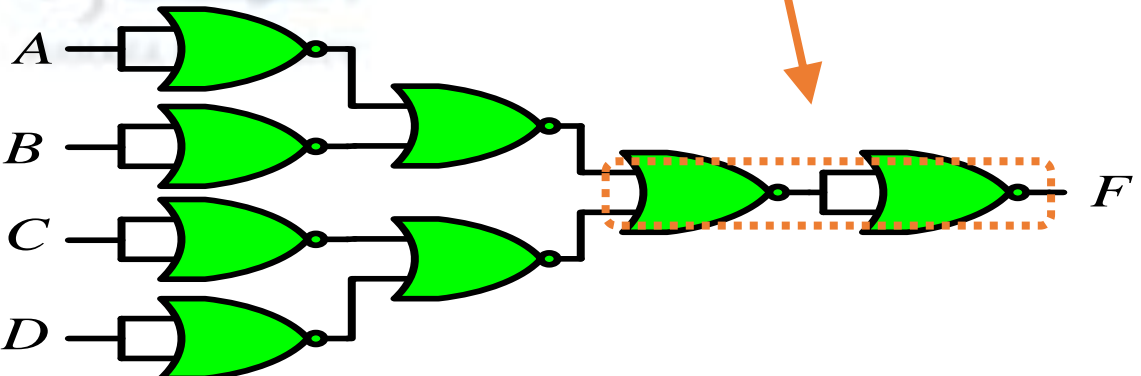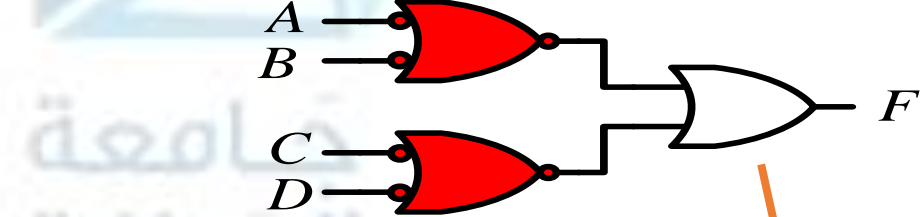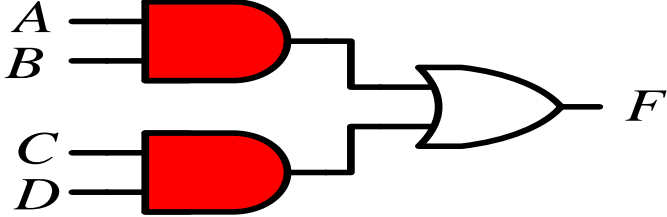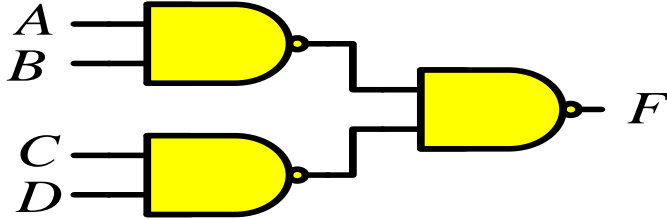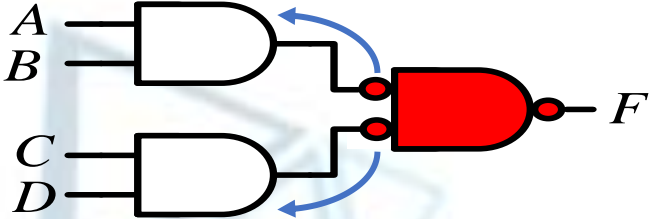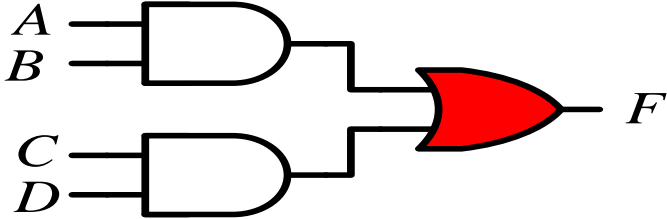


NAND & NOR Implementation

- Two-Level Implementation

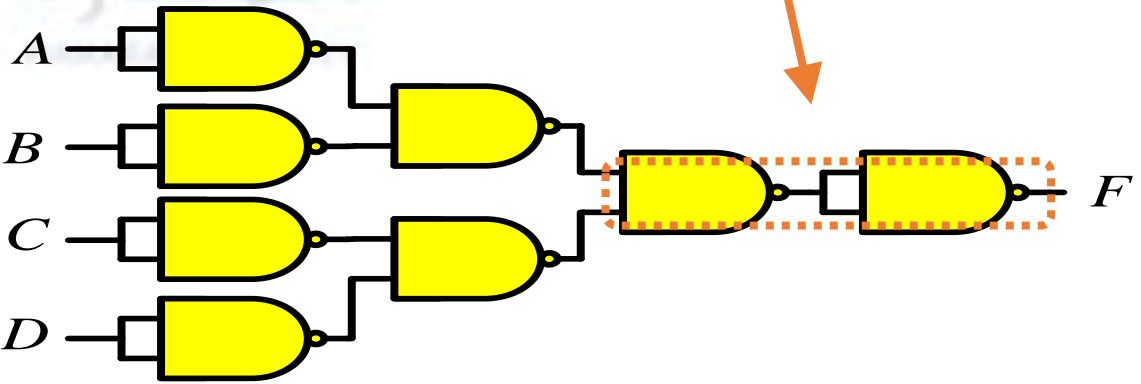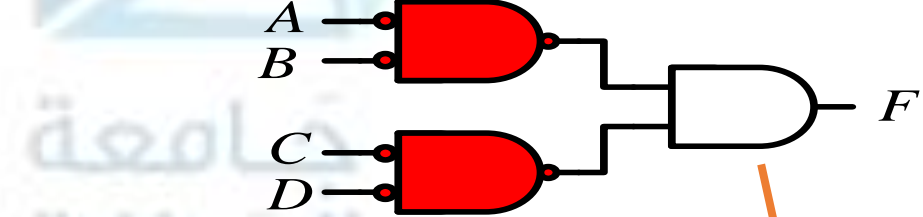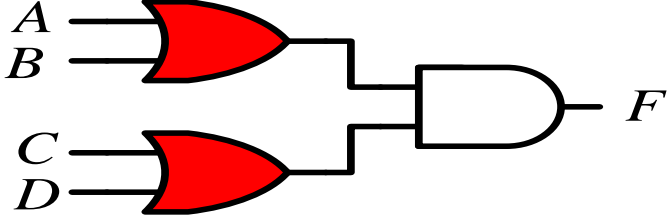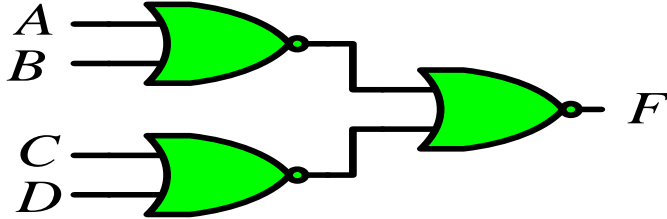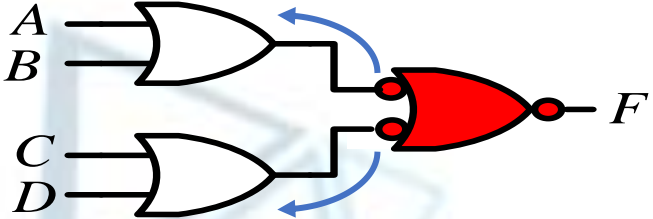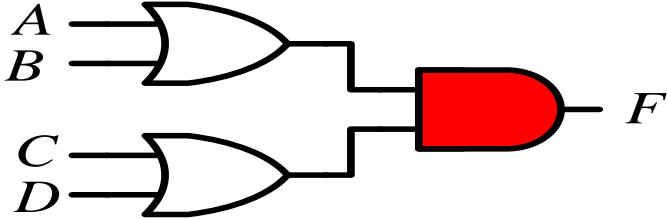


NAND & NOR Implementation

- Multilevel NAND Implementation

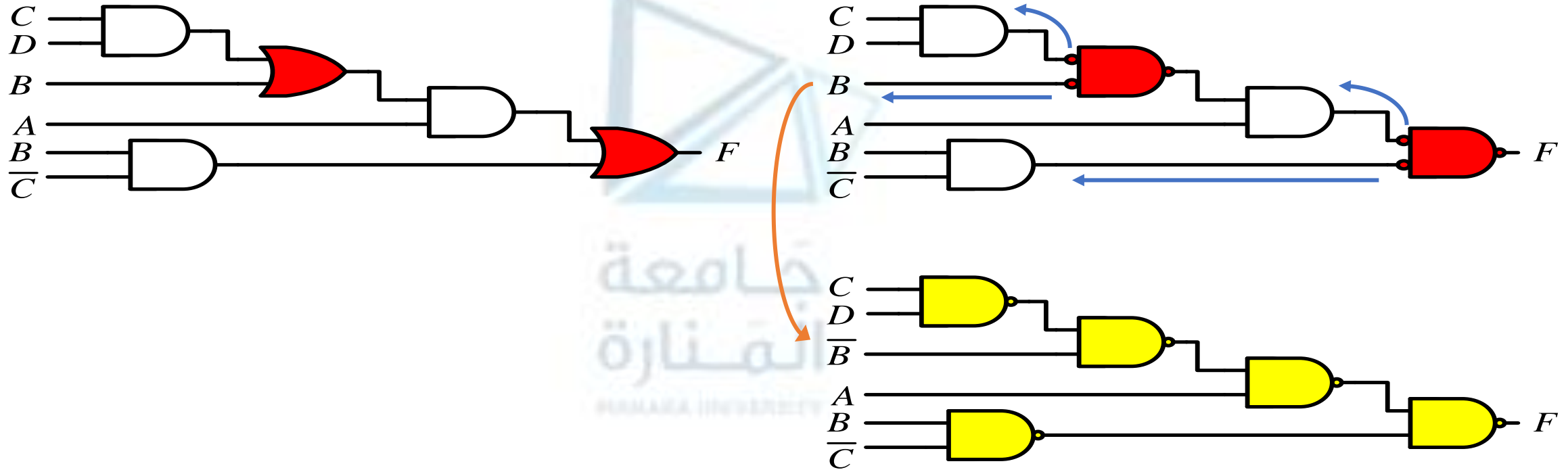


NAND & NOR Implementation

- Multilevel NOR Implementation

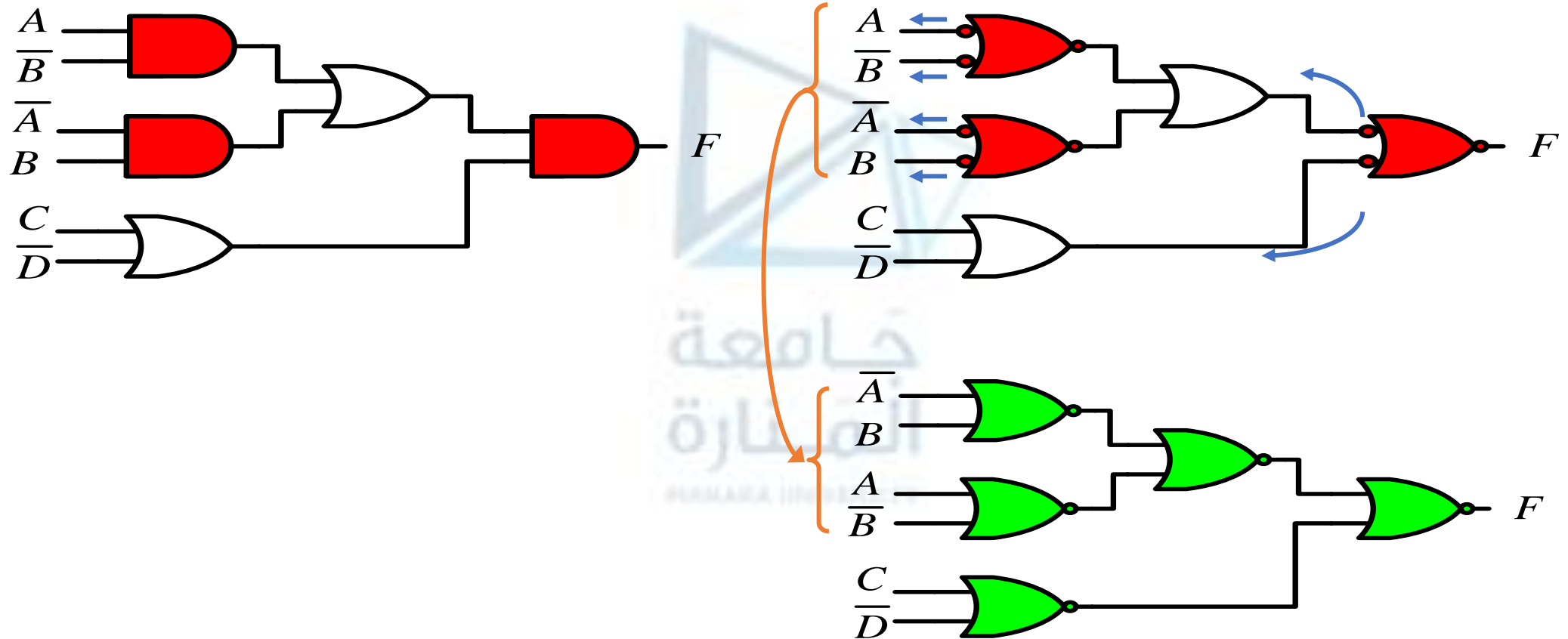


Gate Shapes



- AND

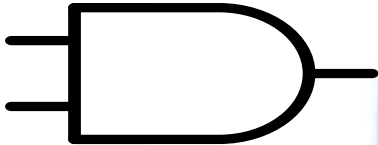

- OR

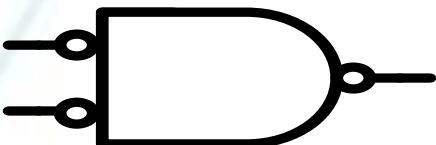

- NAND


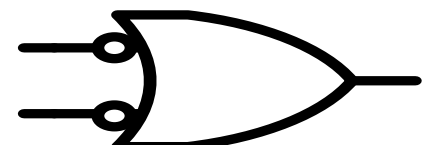
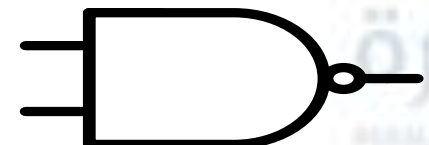


- NOR






Other Implementations

- AND-OR-Invert

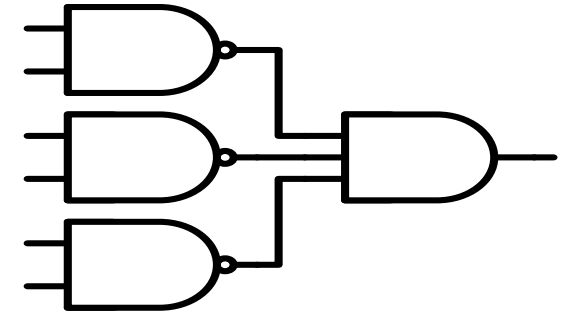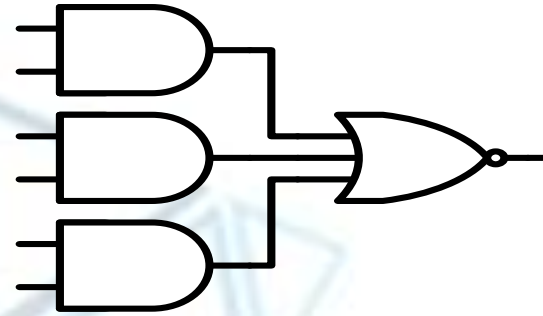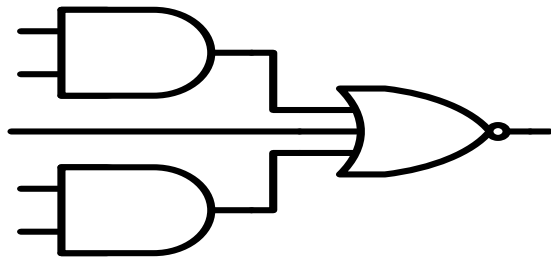


- OR-AND-Invert

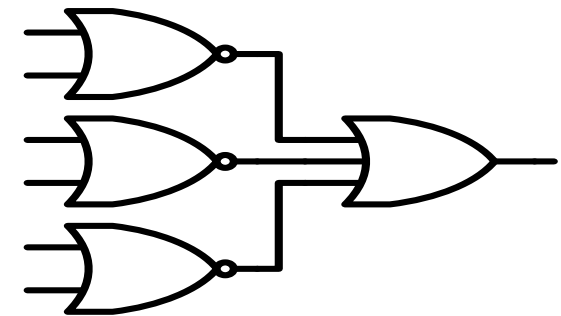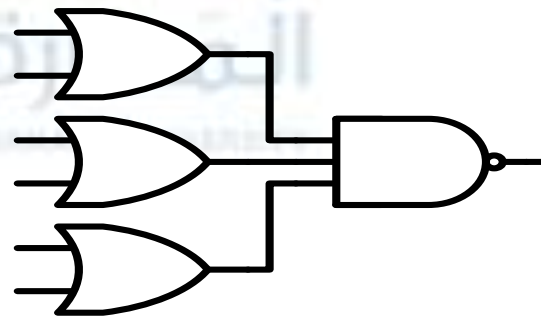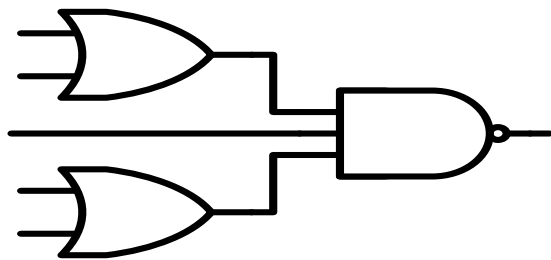

Implementations Summary


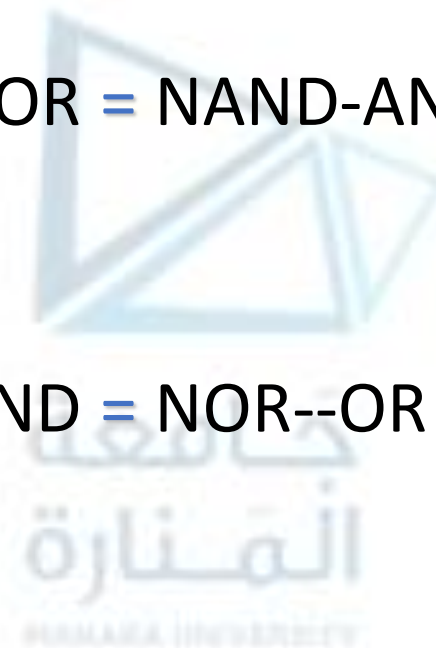
- Sum Of Products:
 - AND-OR
 - AND-OR-Invert = AND-NOR = NAND-AND
- Products Of Sums
 - OR-AND
 - OR-AND-Invert = OR-NAND = NOR--OR



Exclusive-OR



- XOR

$$F = x \oplus y = x\bar{y} + \bar{x}y$$

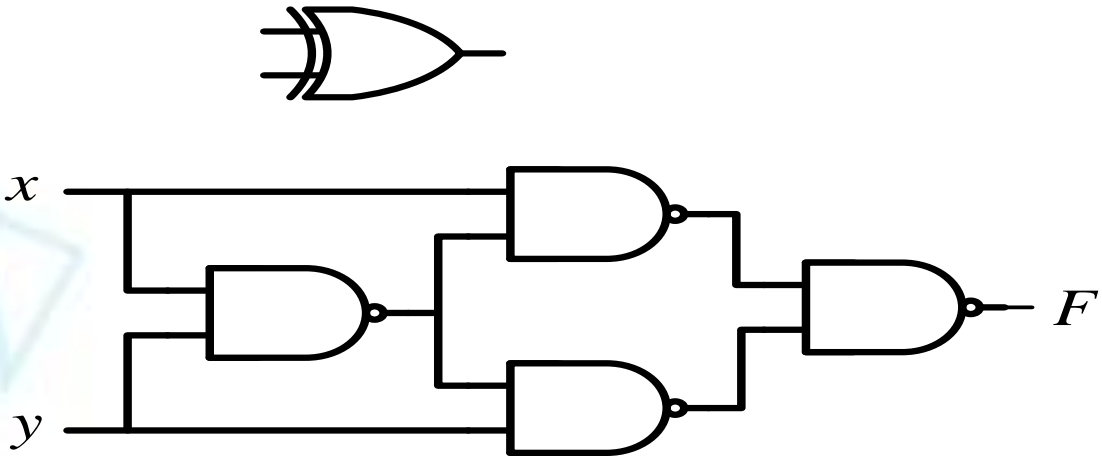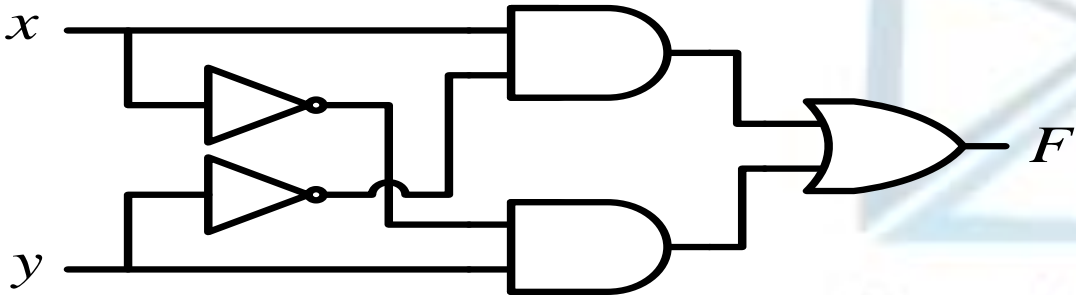

- XNOR
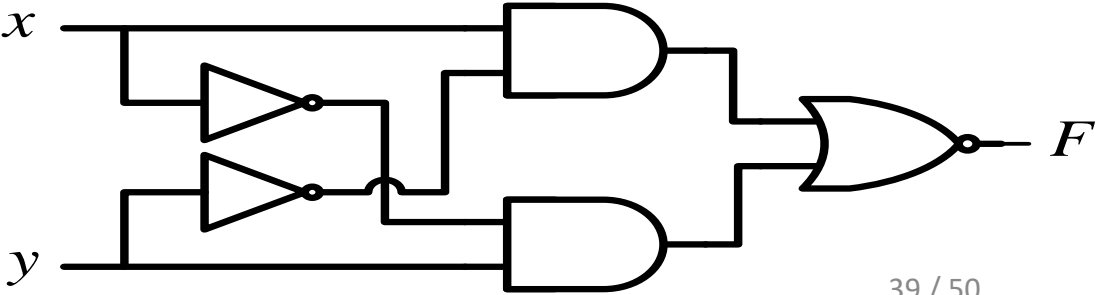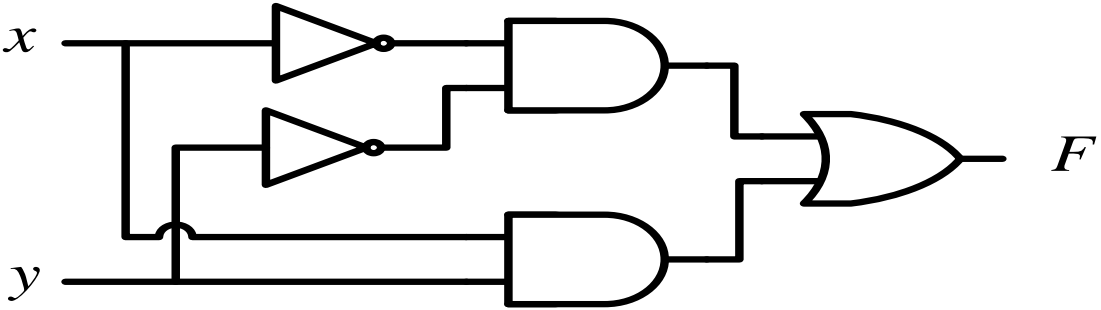
$$F = \overline{x \oplus y} = x \odot y = \bar{x}\bar{y} + xy$$



Exclusive-OR

- Identities

- $x \oplus 0 = x$

- $x \oplus 1 = \overline{x}$

- $x \oplus x = 0$


- $x \oplus \overline{x} = 1$

- $x \oplus \overline{y} = \overline{x} \oplus y = \overline{x \oplus y}$

- Commutative & Associative

- $x \oplus y = y \oplus x$

- $(x \oplus y) \oplus z = x \oplus (y \oplus z) = x \oplus y \oplus z$



<i>x</i>	<i>y</i>	<i>XOR</i>
0	0	0
0	1	1
1	0	1
1	1	0



Exclusive-OR Functions

- Odd Function

$$F = x \oplus y \oplus z$$

$$F = \sum(1, 2, 4, 7)$$



- Even Function


$$F = \overline{x \oplus y \oplus z}$$

$$F = \sum(0, 3, 5, 6)$$





<i>x</i>	<i>y</i>	<i>z</i>	<i>XOR</i>	<i>XNOR</i>
0	0	0	0	1
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	0

<i>x</i>	<i>y z</i> 00	01	11	10
0	0	1	0	1
1	1	0	1	0

 

Parity

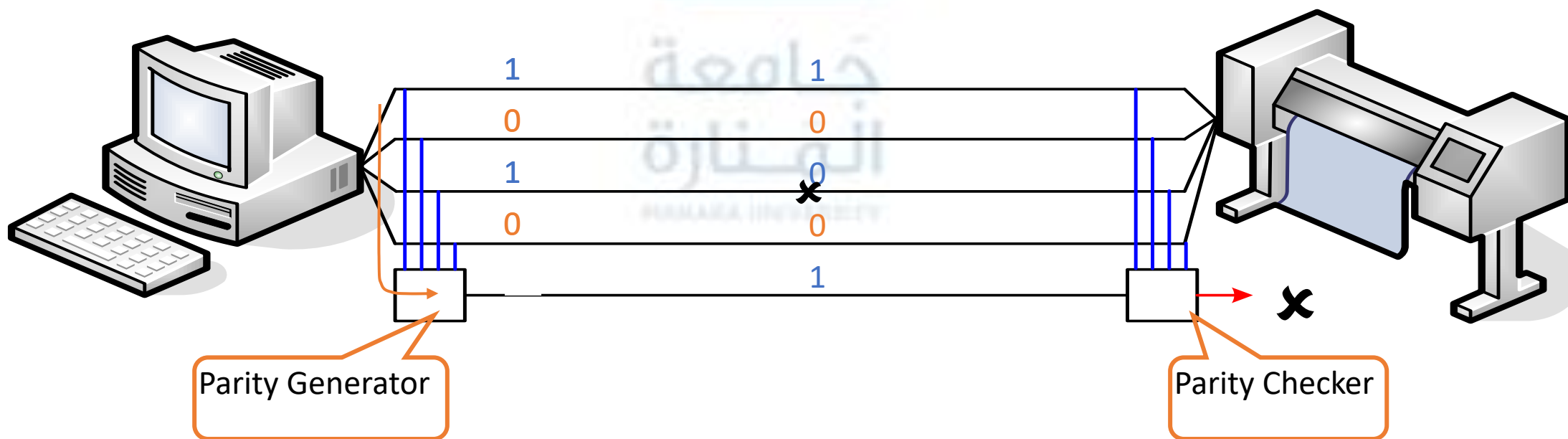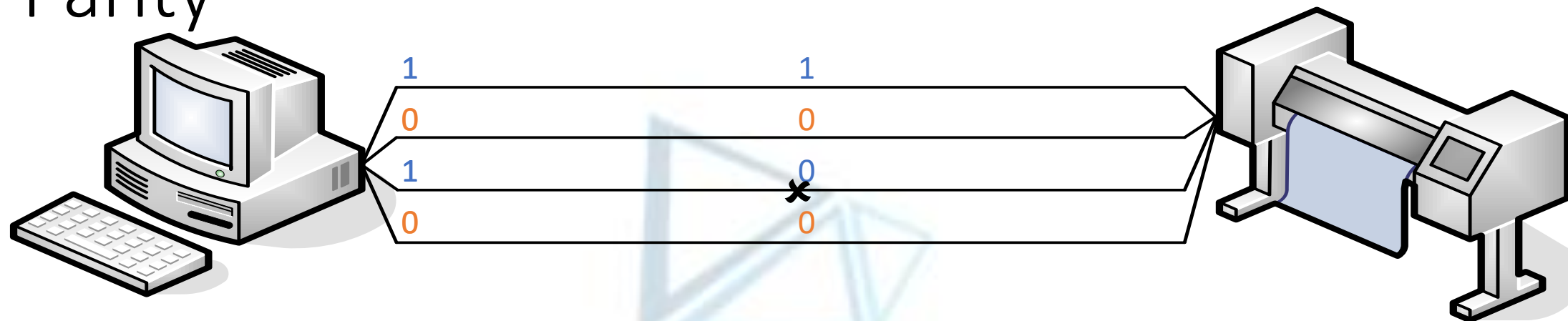


Parity Generator

- Odd Parity




- Even Parity

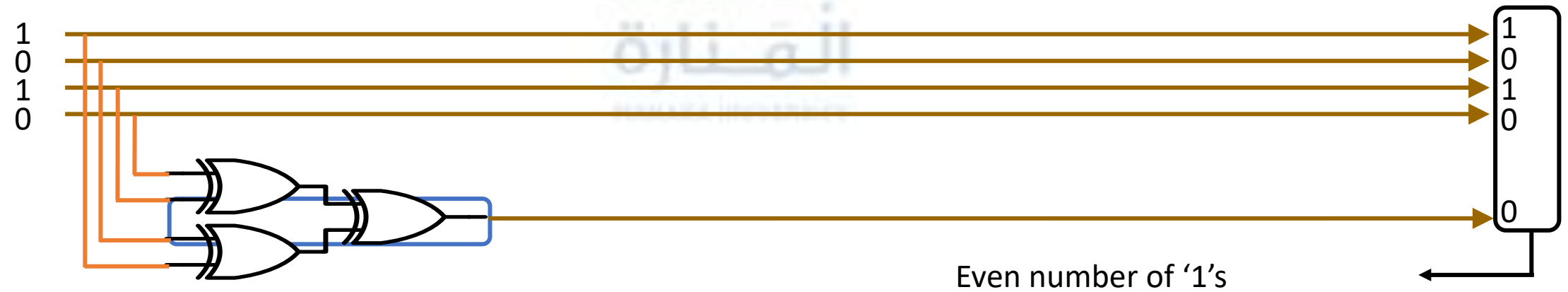


Parity Checker

- Odd Parity

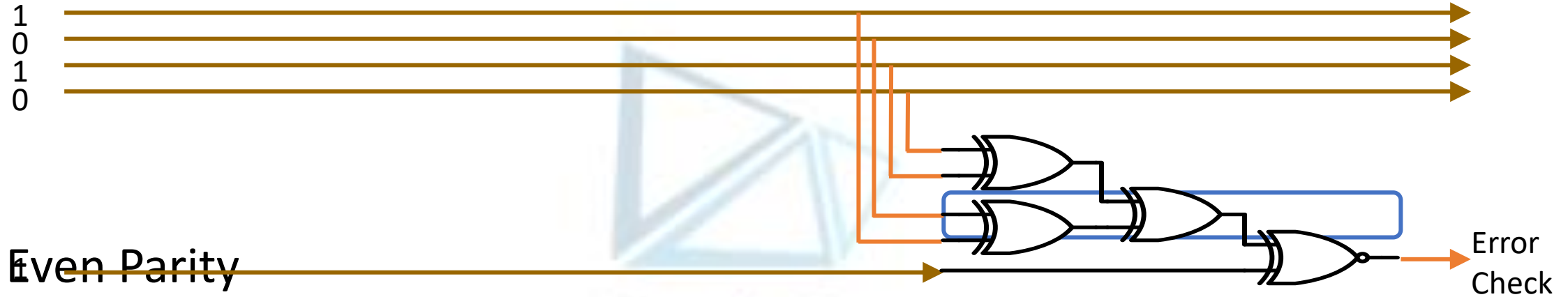

- Even Parity

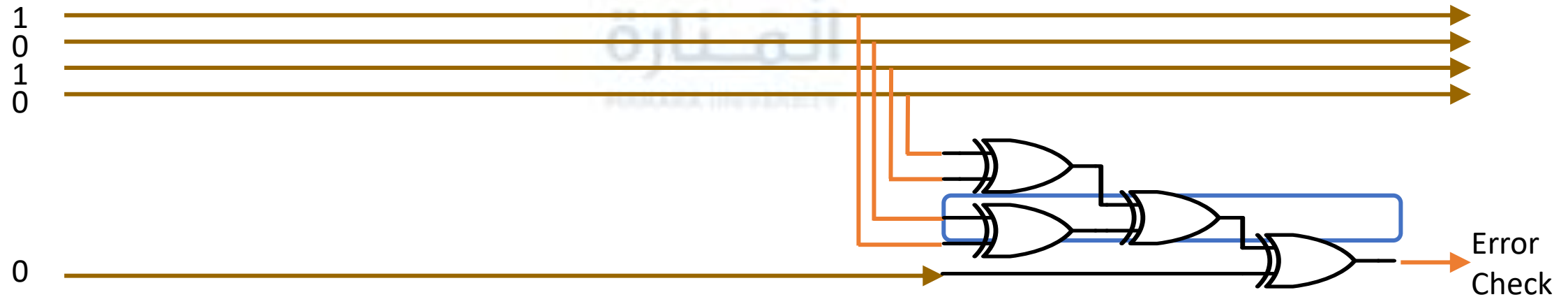

Homework

- Mano
 - Chapter 3
 - 3-1
 - 3-3
 - 3-5
 - 3-7
 - 3-9
 - 3-15
 - 3-16
 - 3-18
 - 3-22



Homework

- Mano

3-1 Simplify the following Boolean functions, using three-variable maps:

(a) $F(x, y, z) = \sum(0, 2, 6, 7)$

(b) $F(A, B, C) = \sum(0, 2, 3, 4, 6)$

(c) $F(a, b, c) = \sum(0, 1, 2, 3, 7)$

(d) $F(x, y, z) = \sum(3, 5, 6, 7)$



Homework

3-3 Simplify the following Boolean functions, using three-variable maps:

(a) $xy + x'y'z' + x'yz'$

(b) $x'y' + xz + x'yz'$

(c) $A'B + BC' + B'C'$

3-5 Simplify the following Boolean functions, using four-variable maps :

(a) $F(w, x, y, z) = \sum(1, 4, 5, 6, 12, 14, 15)$

(b) $F(A, B, C, D) = \sum(0, 1, 2, 4, 5, 7, 11, 15)$

(c) $F(w, x, y, z) = \sum(2, 3, 10, 11, 12, 13, 14, 15)$

(d) $F(A, B, C, D) = \sum(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$

Homework

3-7 Simplify the following Boolean functions, using four-variable maps:

(a) $w'z + xz + x'y + wx'z$ (b) $B'D + A'BC' + AB'C + ABC'$

(c) $AB'C + B'C'D' + BCD + ACD' + A'B'C + A'BC'D$

(d) $wxy + yz + xy'z + x'y$

3-9 Find the prime implicants for the following Boolean functions, and determine which are essential:

(a) $F(w, x, y, z) = \sum(0, 2, 4, 5, 6, 7, 8, 10, 13, 15)$

(b) $F(A, B, C, D) = \sum(0, 2, 3, 5, 7, 8, 10, 11, 14, 15)$

(c) $F(A, B, C, D) = \sum(1, 3, 4, 5, 10, 11, 12, 13, 14, 15)$

Homework

3-15 Simplify the following Boolean function F , together with the don't-care conditions d , and then express the simplified function in sum of products:

(a) $F(x, y, z) = \sum(0, 1, 2, 4, 5)$

$$d(x, y, z) = \sum(3, 6, 7)$$

(b) $F(A, B, C, D) = \sum(0, 6, 8, 13, 14)$

$$d(A, B, C, D) = \sum(2, 4, 10)$$

(c) $F(A, B, C, D) = \sum(1, 3, 5, 7, 9, 15)$

$$d(A, B, C, D) = \sum(4, 6, 12, 13)$$

Homework

3-16 Simplify the following expressions, and implement them with two-level NAND gate circuits:

(a) $AB' + ABD + ABD' + A'C'D' + A'BC'$

(b) $BD + BCD' + AB'C'D'$

3-18 Draw a logic diagram using only two-input NAND gates to implement the following expression:

$$(AB + A'B')(CD' + C'D)$$

Homework

3-22 Convert the logic diagram of the circuit shown in Fig. 4-4 into a multiple-level NAND circuit.

