



Logic Gates

Epp, sections 1.4 and 1.5



Review of Boolean algebra

- Just like Boolean logic
- Variables can only be 1 or 0
 - Instead of true / false



Review of Boolean algebra

- Not is a horizontal bar above the number
 - $\bar{0} = 1$
 - $\bar{1} = 0$
- Or is a plus
 - $0+0 = 0$
 - $0+1 = 1$
 - $1+0 = 1$
 - $1+1 = 1$
- And is multiplication
 - $0*0 = 0$
 - $0*1 = 0$
 - $1*0 = 0$
 - $1*1 = 1$



Review of Boolean algebra


- Example: translate $(x+y+z)(x\bar{y}\bar{z})$ to a Boolean logic expression
 - $(x \vee y \vee z) \wedge (\neg x \wedge \neg y \wedge \neg z)$
- We can define a Boolean function:
 - $F(x,y) = (x \vee y) \wedge (\neg x \wedge \neg y)$
- And then write a “truth table” for it:

x	y	$F(x,y)$
1	1	0
1	0	0
0	1	0
0	0	0





Basic logic gates



- Not

 


- And

  


- Or

  


- Nand

 

- Nor

 


- Xor

 



Converting between circuits and equations

 - Find the output of the following circuit




- Answer: $(x+y)\bar{y}$
– Or $(x\vee y)\wedge\neg y$



Converting between circuits and equations

 - Find the output of the following circuit




- Answer: $\overline{\bar{X}\bar{Y}}$
 - Or $\neg(\neg X \wedge \neg Y) \equiv X \vee Y$ Dr. Iyad Hatem



Converting between circuits and equations

- Write the circuits for the following Boolean algebraic expressions

a) $\bar{x}+y$

 




Converting between circuits and equations

- Write the circuits for the following Boolean algebraic expressions

b) $\overline{(x+y)}x$

 




Writing xor using and/or/not

- $p \oplus q \equiv (p \vee q) \wedge \neg(p \wedge q)$
- $x \oplus y \equiv (x + y)(\overline{xy})$

x	y	$x \oplus y$
1	1	0
1	0	1
0	1	1
0	0	0

 



Converting decimal numbers to binary

- $53 = 32 + 16 + 4 + 1$
 $= 2^5 + 2^4 + 2^2 + 2^0$
 $= 1*2^5 + 1*2^4 + 0*2^3 + 1*2^2 + 0*2^1 + 1*2^0$
 $= 110101$ in binary
 $= 00110101$ as a full byte in binary

- $211 = 128 + 64 + 16 + 2 + 1$
 $= 2^7 + 2^6 + 2^4 + 2^1 + 2^0$
 $= 1*2^7 + 1*2^6 + 0*2^5 + 1*2^4 + 0*2^3 + 0*2^2 + 1*2^1 + 1*2^0$
 $= 11010011$ in binary



Converting binary numbers to decimal

- What is 10011010 in decimal?

$$\begin{aligned}10011010 &= 1*2^7 + 0*2^6 + 0*2^5 + 1*2^4 + 1*2^3 + \\ &\quad 0*2^2 + 1*2^1 + 0*2^0 \\ &= 2^7 + 2^4 + 2^3 + 2^1 \\ &= 128 + 16 + 8 + 2 \\ &= 154\end{aligned}$$

- What is 00101001 in decimal?

$$\begin{aligned}00101001 &= 0*2^7 + 0*2^6 + 1*2^5 + 0*2^4 + 1*2^3 + \\ &\quad 0*2^2 + 0*2^1 + 1*2^0 \\ &= 2^5 + 2^3 + 2^0 \\ &= 32 + 8 + 1 \\ &= 41\end{aligned}$$



A note on binary numbers

- In this slide set we are only dealing with non-negative numbers
- The book (section 1.5) talks about two's-complement binary numbers
 - Positive (and zero) two's-complement binary numbers is what was presented here
 - We won't be getting into negative two's-complmeent numbers



How to add binary numbers

- Consider adding two 1-bit binary numbers x and y

- $0+0 = 0$
- $0+1 = 1$
- $1+0 = 1$
- $1+1 = 10$

x	y	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


- Carry is x AND y
- Sum is x XOR y
- The circuit to compute this is called a half-adder



The half-adder

- $\text{Sum} = x \text{ XOR } y$
- $\text{Carry} = x \text{ AND } y$


x	y	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

 



Using half adders

 - We can then use a half-adder to compute the sum of two Boolean numbers





How to fix this

- We need to create an adder that can take a carry bit as an additional input
 - Inputs: x , y , carry in
 - Outputs: sum, carry out
- This is called a full adder
 - Will add x and y with a half-adder
 - Will add the sum of that to the carry in
- What about the carry out?
 - It's 1 if either (or both):
 - $x+y = 10$
 - $x+y = 01$ and carry in = 1


x	y	c	carry	sum
1	1	1	1	1
1	1	0	1	0
1	0	1	1	0
1	0	0	0	1
0	1	1	1	0
0	1	0	0	1
0	0	1	0	1
0	0	0	0	0



The full adder


- The “HA” boxes are half-adders

x	y	c	s_1	c_1	carry	sum
1	1	1	0	1	1	1
1	1	0	0	1	1	0
1	0	1	1	0	1	0
1	0	0	1	0	0	1
0	1	1	1	0	1	0
0	1	0	1	0	0	1
0	0	1	0	0	0	1
0	0	0	0	0	0	0

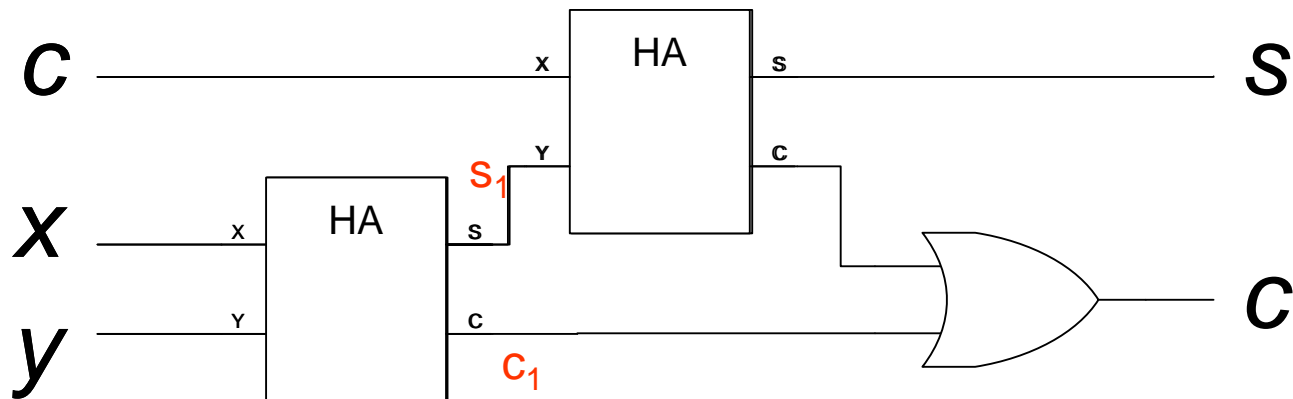

The full adder


- The full circuitry of the full adder

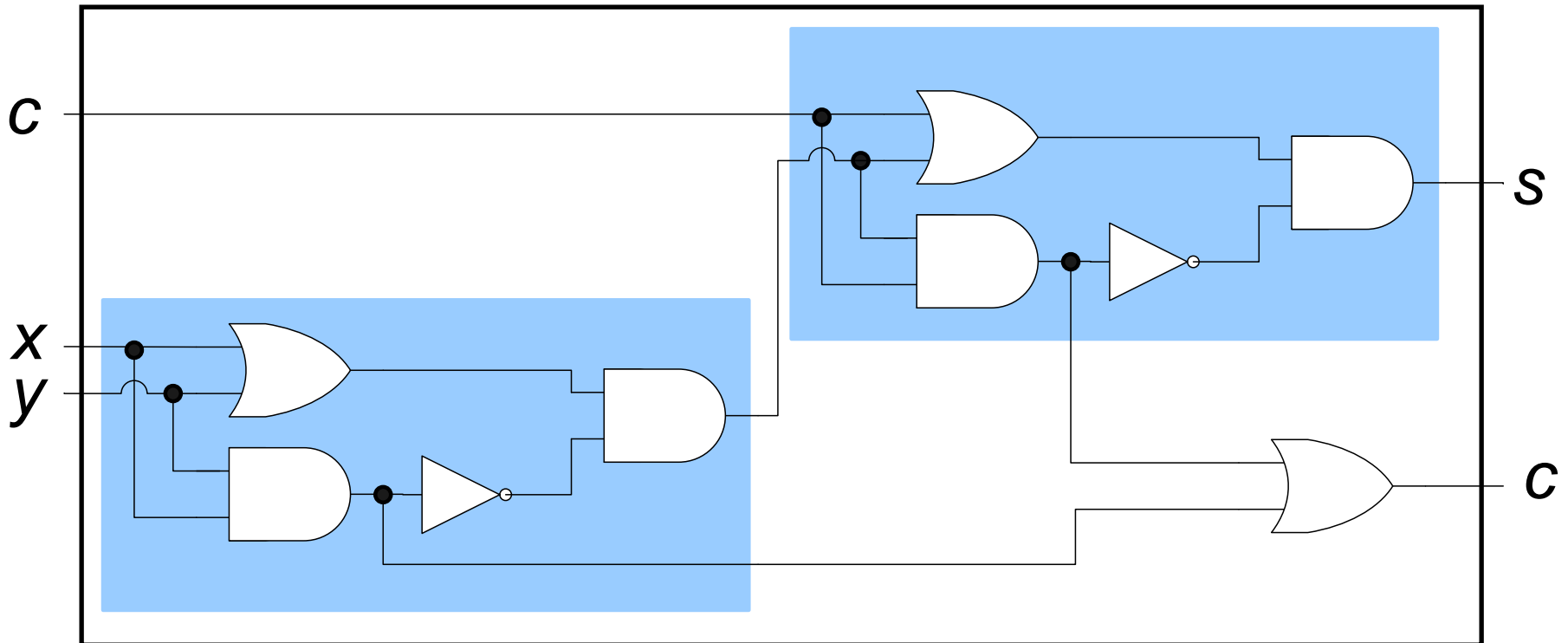



Adding bigger binary numbers

- Just chain full adders together

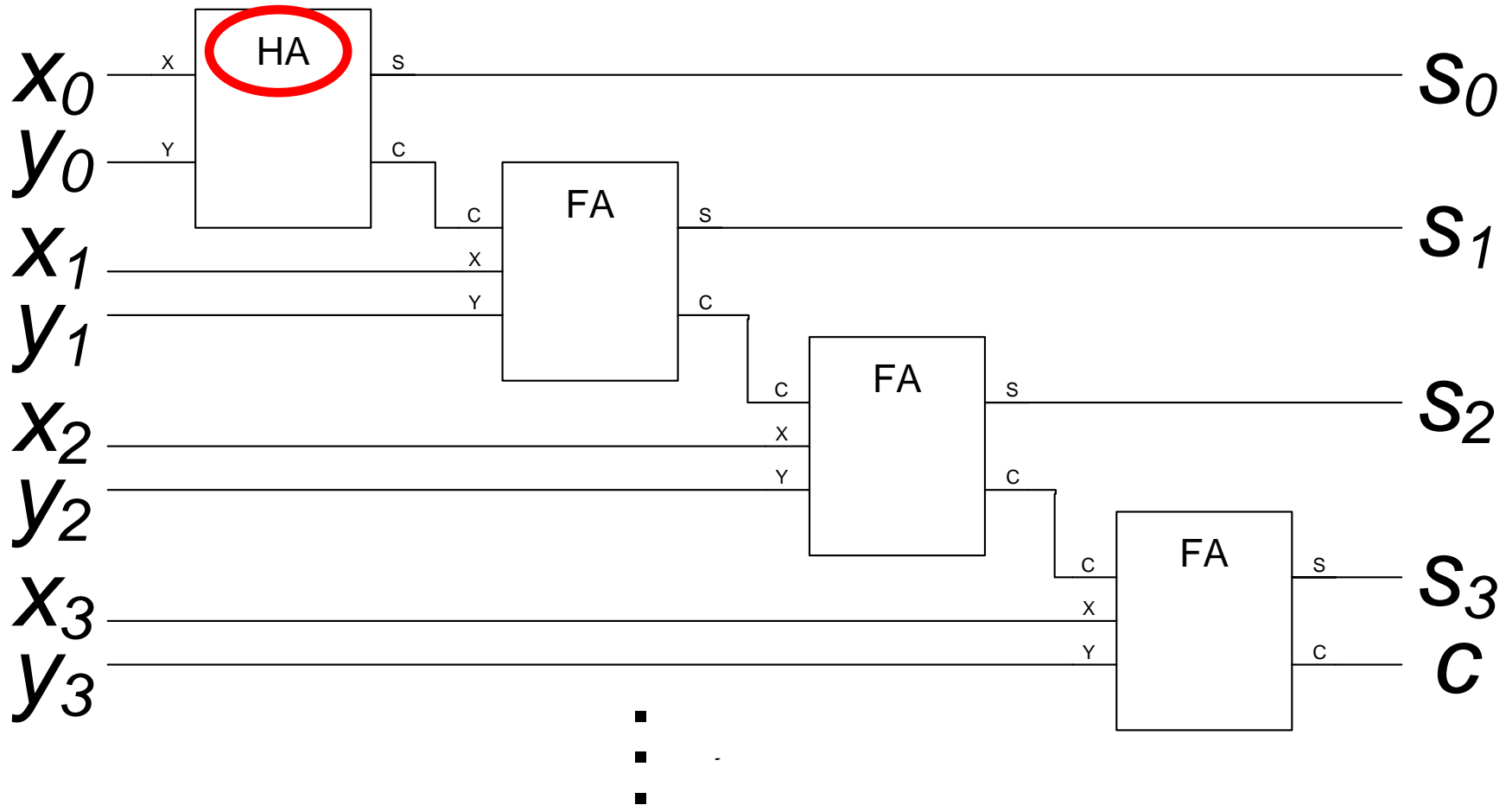



Adding bigger binary numbers

- A half adder has 4 logic gates
- A full adder has two half adders plus a OR gate
 - Total of 9 logic gates
- To add n bit binary numbers, you need 1 HA and $n-1$ FAs
- To add 32 bit binary numbers, you need 1 HA and 31 FAs
 - Total of $4+9*31 = 283$ logic gates
- To add 64 bit binary numbers, you need 1 HA and 63 FAs
 - Total of $4+9*63 = 571$ logic gates




More about logic gates

- To implement a logic gate in hardware, you use a transistor
- Transistors are all enclosed in an “IC”, or integrated circuit
- The current Intel Pentium IV processors have 55 million transistors!



Flip-flops

- Consider the following circuit:

 

- What does it do?

Memory

- A flip-flop holds a single bit of memory
 - The bit “flip-flops” between the two NAND gates
- In reality, flip-flops are a bit more complicated
 - Have 5 (or so) logic gates (transistors) per flip-flop
- Consider a 1 Gb memory chip
 - 1 Gb = 8,589,934,592 bits of memory
 - That’s about 43 million transistors!
- In reality, those transistors are split into 9 ICs of about 5 million transistors each



Table 1.5.3



Hexadecim

- A numerical range from 0-15
 - Where A is 10, B is 11, ... and F is 15
- Often written with a '0x' prefix
- So 0x10 is 10 hex, or 16
 - 0x100 is 100 hex, or 256
- Binary numbers easily translate:

Decimal	Hexadecimal	4-Bit Binary Equivalent
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
10	A	1010
11	B	1011
12	C	1100
13	D	1101
14	E	1110
15	F	1111


Dr. Iyad Hat



From

ThinkGeek

(<http://www.thinkgeek.com>)

 



Also from ThinkGeek

(<http://www.thinkgeek.com>)



Dr. Iy:



DEADBEEF

- Many IBM machines would fill allocated (but uninitialized) memory with the hexadecimal pattern 0xDEADBEEF
 - Decimal -21524111
 - See <http://www.jargon.net/jargonfile/d/DEADBEEF.html>
- Makes it easier to spot in a debugger



Also also from ThinkGeek

(<http://www.thinkgeek.com>)

- $0xDEAD = 57005$
- Now add one to that...

