



جامعة  
المنارة  
MANARA UNIVERSITY


# Lecture 4

## Boolean Algebra

Dr. Bassam Atieh

MANARA UNIVERSITY

# Timing diagram

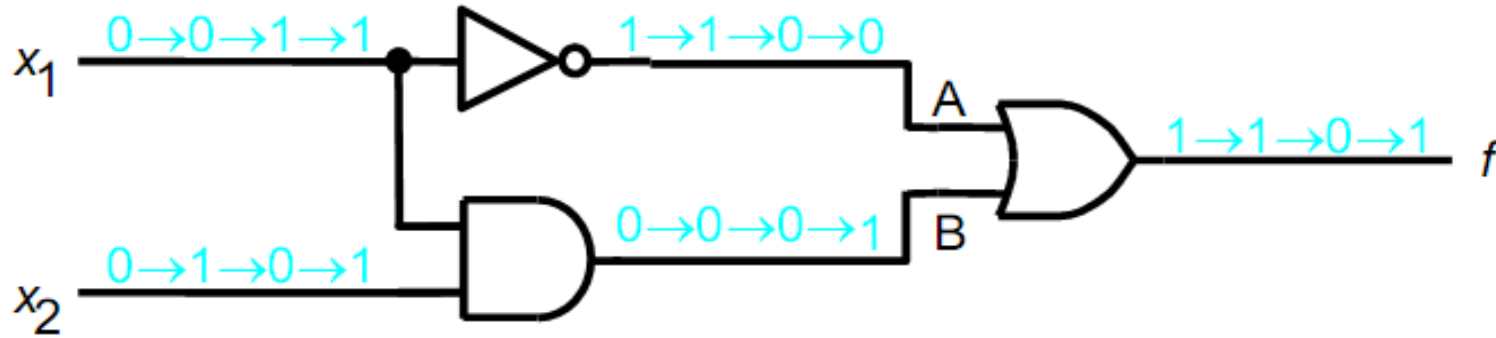


(a) Network that implements  $f = x_1' + x_1 \cdot x_2$

$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

A	B
1	0
1	0
0	0
0	1

(b) Truth table

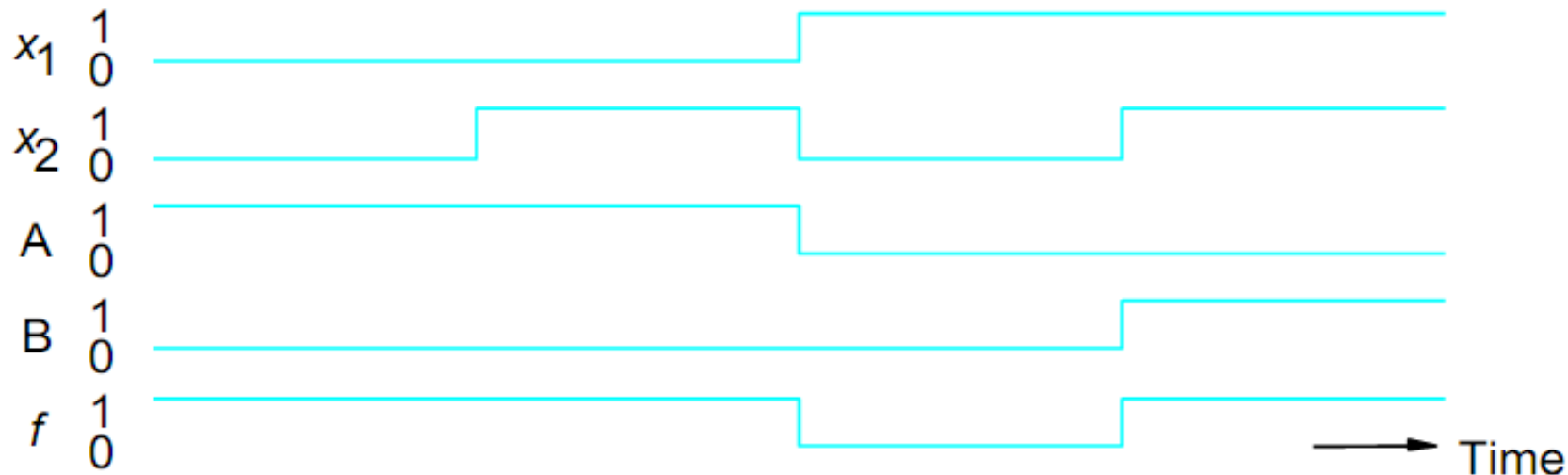

(c) Timing diagram

## Axioms of Boolean Algebra

**A1)**

$$0 \cdot 0 = 0$$

**A1')**

$$1 + 1 = 1$$

**A2)**

$$1 \cdot 1 = 1$$

**A2')**

$$0 + 0 = 0$$

**A3)**

$$0 \cdot 1 = 1 \cdot 0 = 0$$

**A3')**

$$1 + 0 = 0 + 1 = 1$$

**A4)** if  $x = 0$ , then  $x' = 1$

**A4')** if  $x = 1$ , then  $x' = 0$

# • Single variable theorems

$$T1) x \cdot 0 = 0$$

$$T2) x \cdot 1 = x$$

$$T3) x \cdot x = x$$

$$T4) x \cdot x' = 0$$

$$T5) x'' = x$$

$$T1') x + 1 = 1$$

$$T2') x + 0 = x$$

$$T3') x + x = x$$

$$T4') x + x' = 1$$



## • Two and three variable theorems

$$T6) x \cdot y = y \cdot x$$

$$T6') x + y = y + x$$

$$T7) x \cdot (y \cdot z) = (x \cdot y) \cdot z$$

$$T7') x + (y + z) = (x + y) + z$$

$$T8) x \cdot (y + z) = x \cdot y + x \cdot z$$

$$T8') x + y \cdot z = (x + y) \cdot (x + z)$$

$$T9) x + x \cdot y = x$$

$$T9') x \cdot (x + y) = x$$

$$T10) x \cdot y + x \cdot y' = x$$

$$T10') (x + y) \cdot (x + y') = x$$

$$T11) (x \cdot y)' = x' + y'$$

$$T11') (x + y)' = x' \cdot y'$$

$$T12) x + x' \cdot y = x + y$$

$$T12') x \cdot (x' + y) = x \cdot y$$

$$T13) x \cdot y + y \cdot z + x' \cdot z = x \cdot y + x' \cdot z$$


$$T13') (x + y) \cdot (y + z) \cdot (x' + z) = (x + y) \cdot (x' + z)$$

Example: Apply theorems of Boolean Algebra to prove that the left and right hand sides of the following logic equation are identical.

$$X_1 \cdot X_3' + X_2' \cdot X_3' + X_1 \cdot X_3 + X_2' \cdot X_3 = X_1' \cdot X_2' + X_1 \cdot X_2 + X_1 \cdot X_2'$$

- **The Venn Diagram**


- Graphical illustration of various operations and relations in the algebra of sets
- A set  $s$  is a collection of elements that are said to be members of  $s$
- In Venn diagram the elements of a set are represented by the area enclosed by a square, circle or ellipse
- In Boolean algebra there are only two elements in the universe, i.e.  $\{0,1\}$ . Then the area within a contour corresponding to a set  $s$  denotes that  $s = 1$ , while the area outside the contour denotes  $s = 0$
- In a Venn diagram we shade the area where  $s = 1$

 


(a) Constant 1




(b) Constant 0

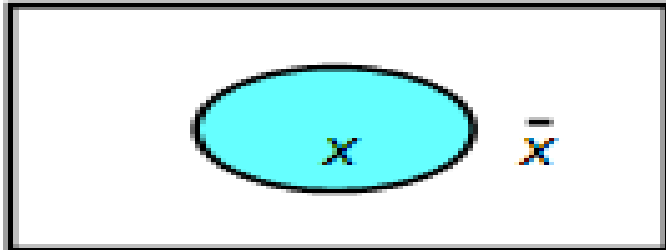


(c) Variable  $x$

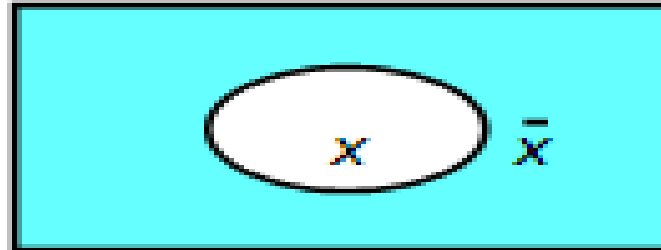


(d)  $\bar{x}$

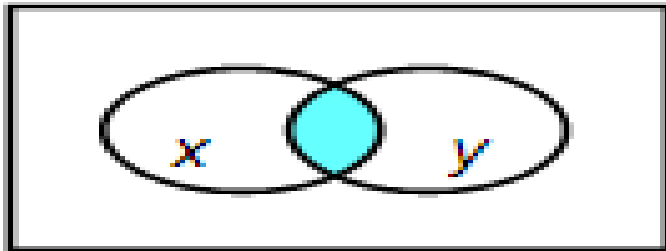


(e)  $x \cdot y$

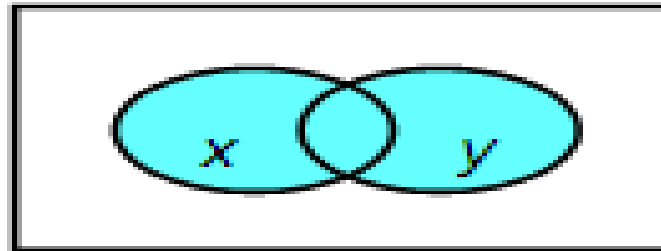

(f)  $x + y$

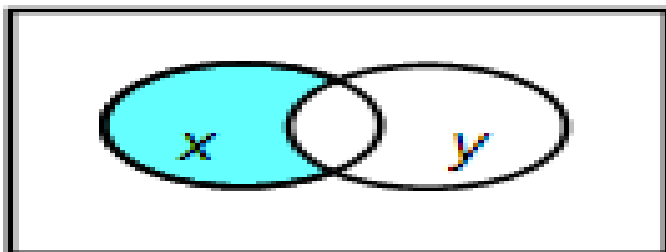


(g)  $x \cdot \bar{y}$

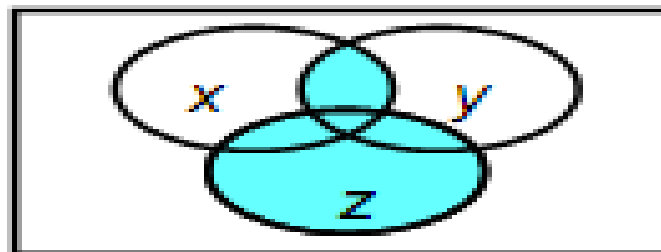


(h)  $x \cdot y + z$

The Venn diagram representation.




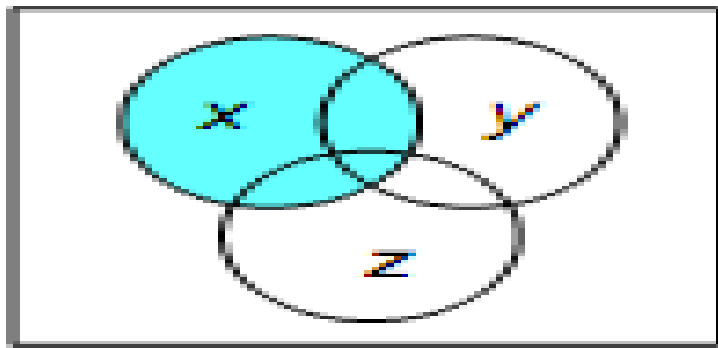

(a)  $x$

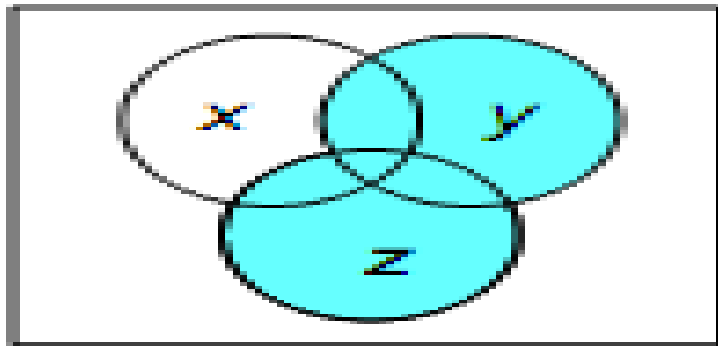

(b)  $y+z$

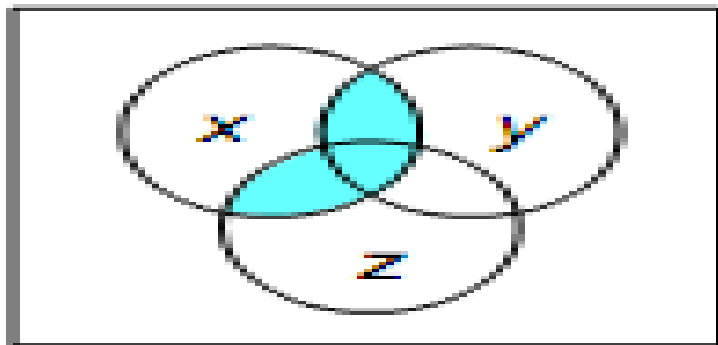


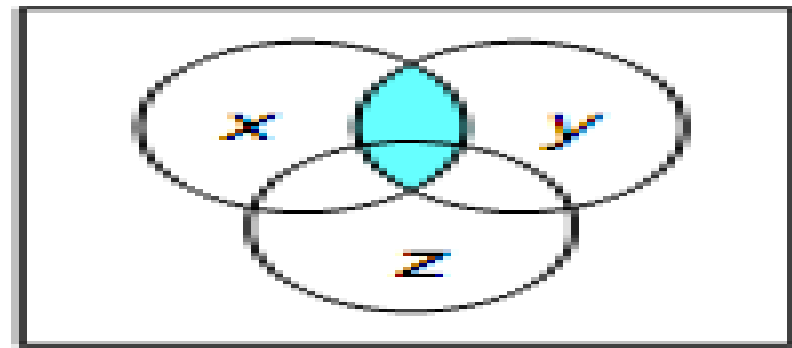(c)  $x \cdot (y+z)$




جامعة  
المنارة  
MANARA UNIVERSITY


$$x \cdot (y + z) = x \cdot y + x \cdot z$$



(d)  $x \cdot y$

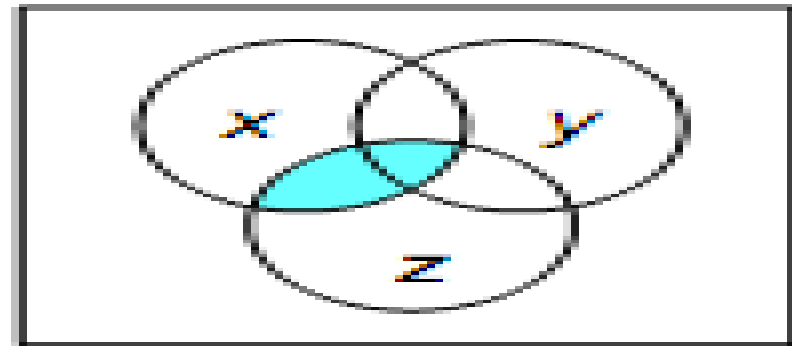


(e)  $x \cdot z$

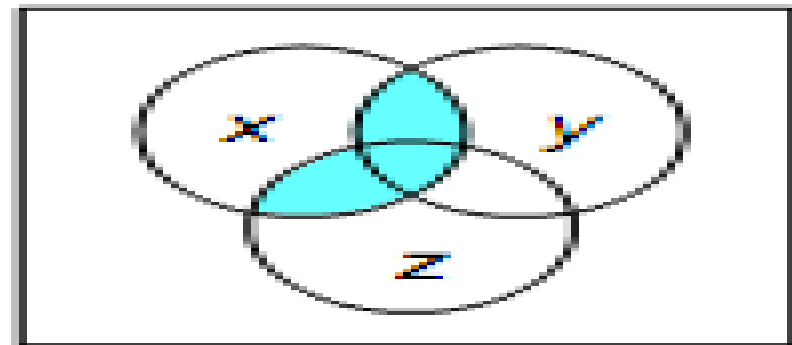



(f)  $x \cdot y + x \cdot z$

جامعة  
المنارة  
MANARA UNIVERSITY


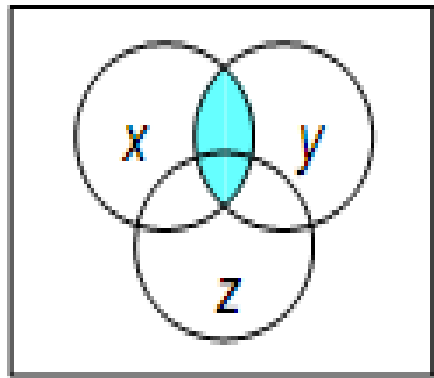
# Verification of $x \cdot y + \bar{x} \cdot z + y \cdot z = x \cdot y + \bar{x} \cdot z$





$x \cdot y$

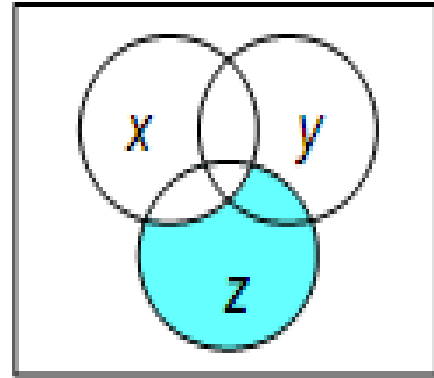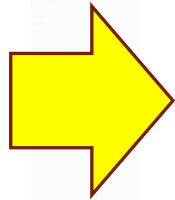


$\bar{x} \cdot z$

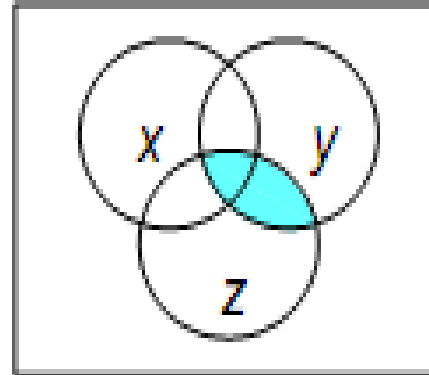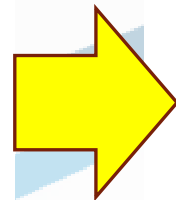



$y \cdot z$

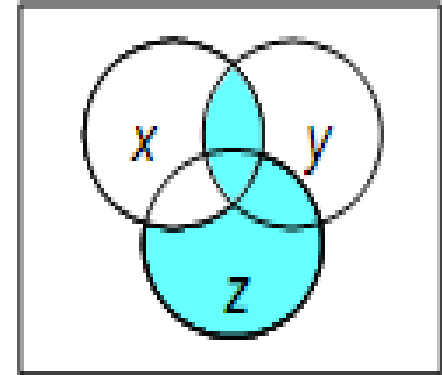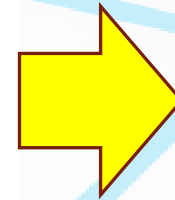


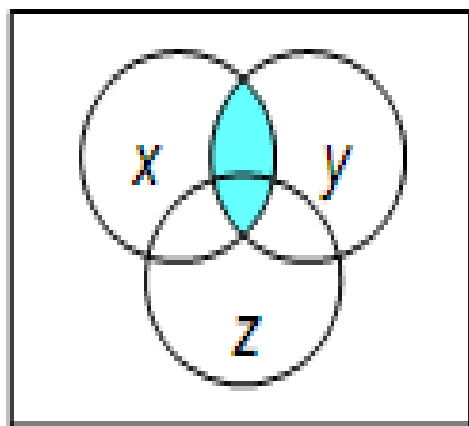
$x \cdot y + \bar{x} \cdot z + y \cdot z$



$x \cdot y$

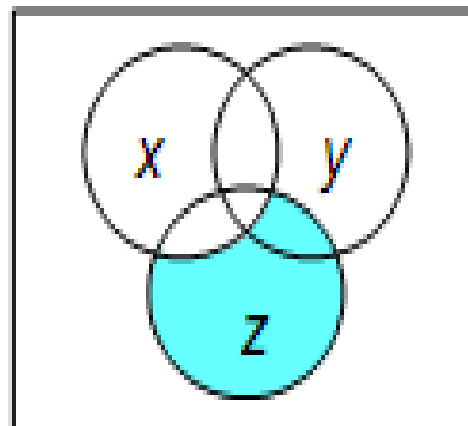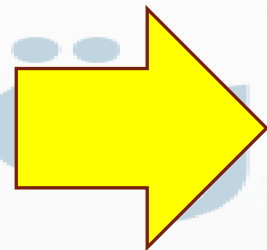

$\bar{x} \cdot z$

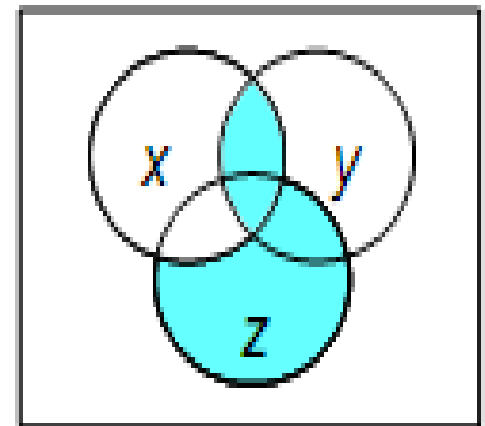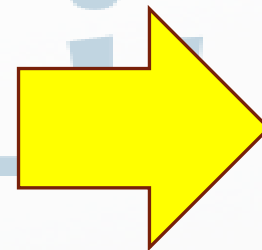

$x \cdot y + \bar{x} \cdot z$

# Synthesis of digital circuits


## Three-variable minterms and maxterms.

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$


# Example:

For the three variable function given by the truth table, determine the minterms, maxterms, canonical SOP, canonical POS, minterm list.

$x_1$	$x_2$	$x_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

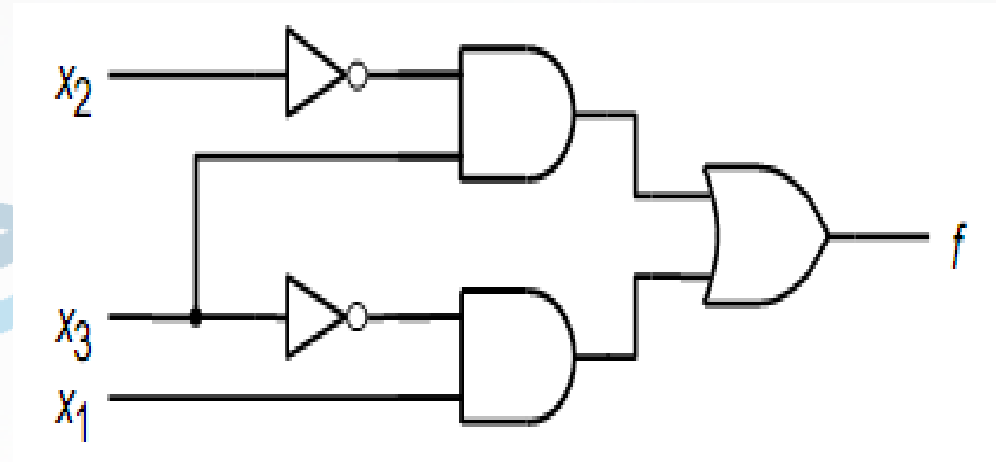

Sum-of-products realization

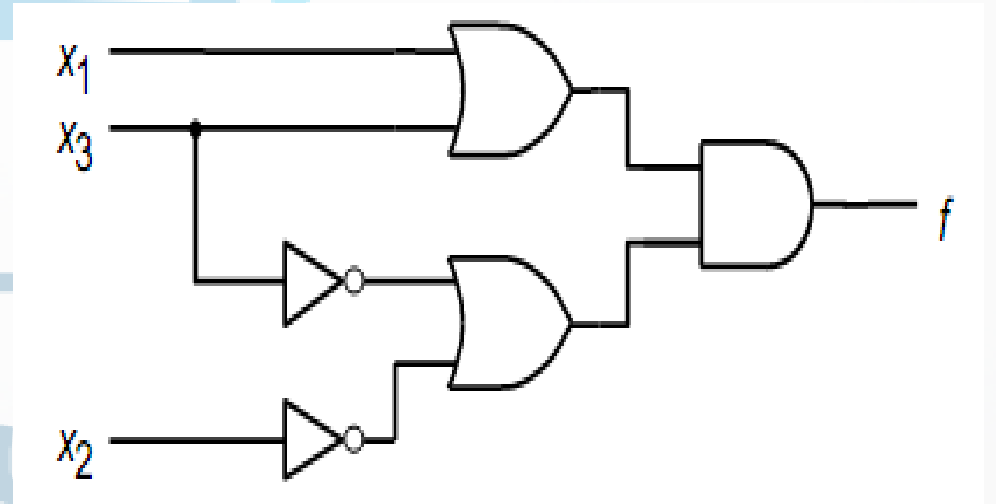


Product-of-sums realizations


# DeMorgan's equivalents



# of NAND and NOR gates.

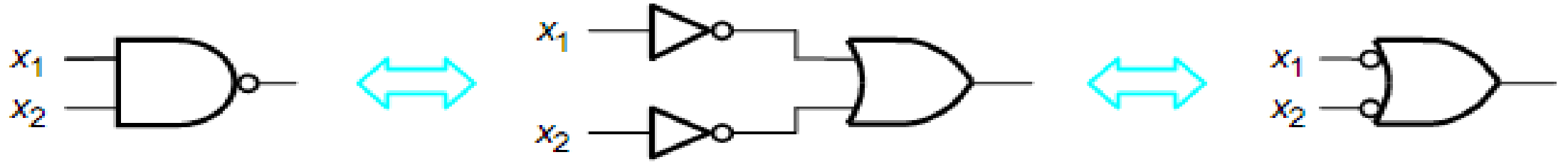

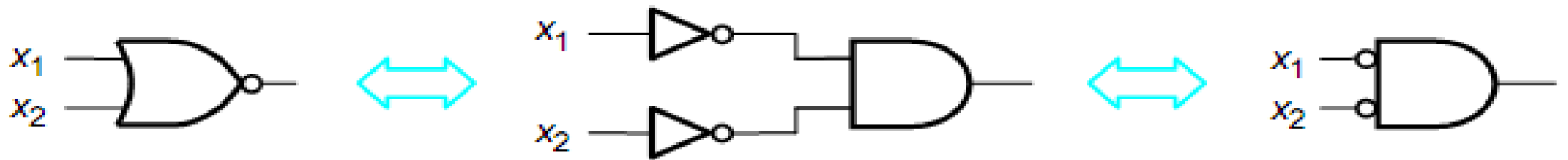
$$(a) \overline{x_1 x_2} = \bar{x}_1 + \bar{x}_2$$




$$(b) \overline{x_1 + x_2} = \bar{x}_1 \bar{x}_2$$

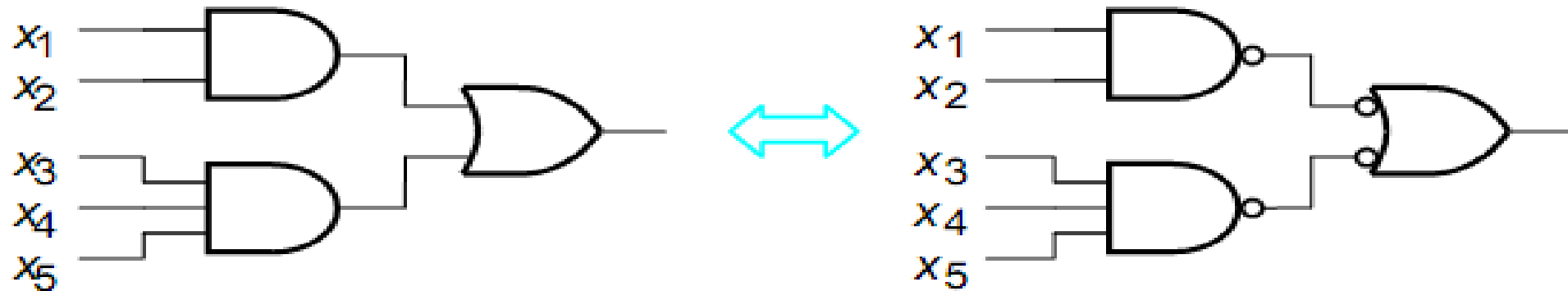- Converting a AND-OR realization of an SOP to a NAND-NAND realization



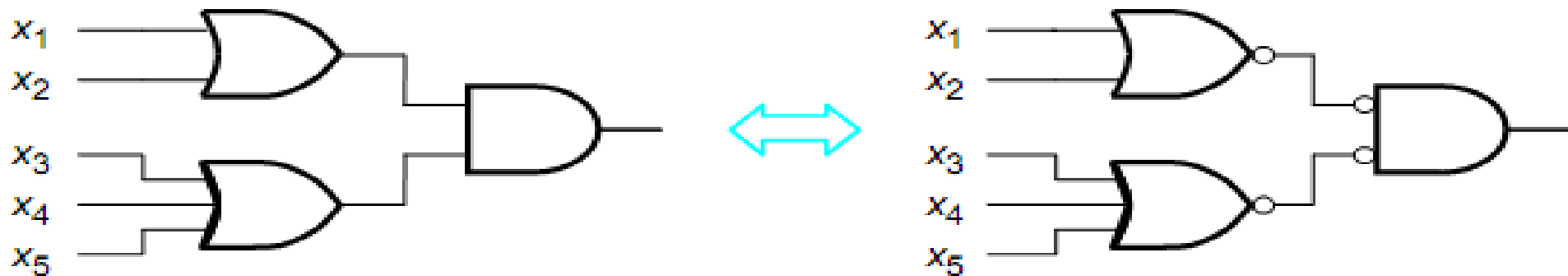- Converting a OR-AND realization of a POS to a NOR-NOR realization




# realization of an SOP



$$f(x_1, x_2, x_3) = \sum m(1, 2, 4, 7)$$
$$= (\bar{x}_1 \cdot \bar{x}_2 \cdot x_3) + (\bar{x}_1 \cdot x_2 \cdot \bar{x}_3) + (x_1 \cdot \bar{x}_2 \cdot \bar{x}_3) + (x_1 \cdot x_2 \cdot x_3)$$

$x_1$	$x_2$	$x_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

## Sum-of-products realizations

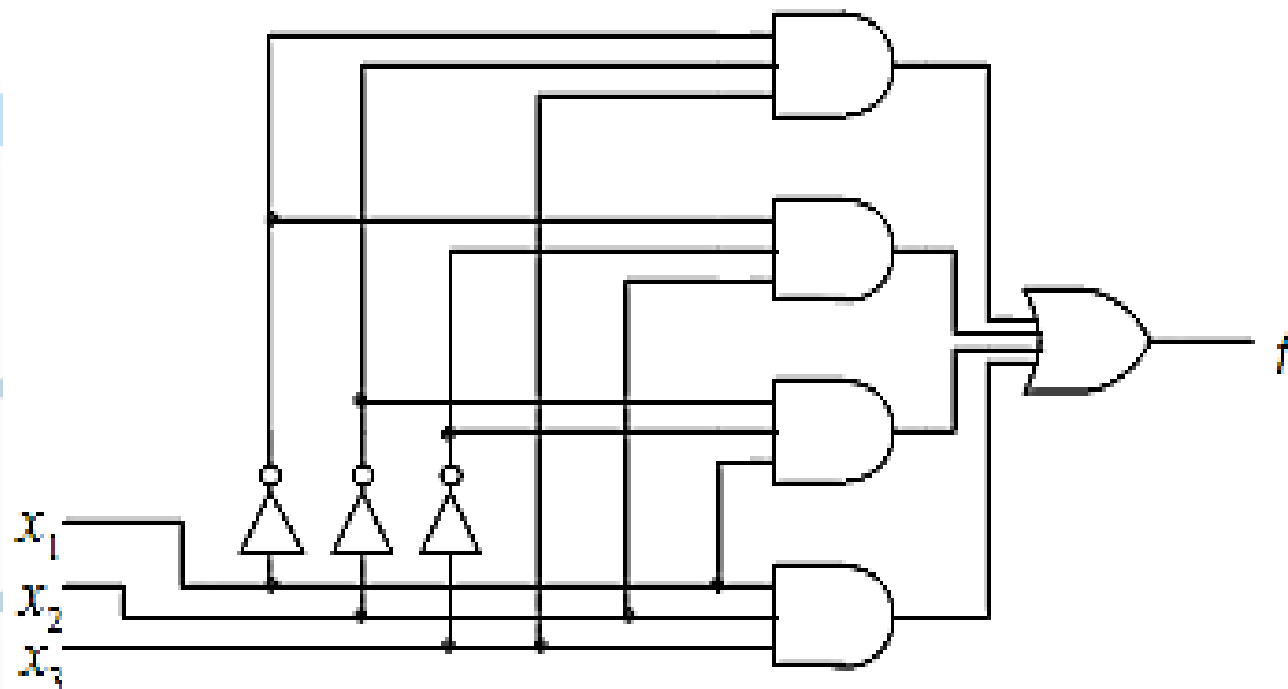

# realization of an POS




$$f(x_1, x_2, x_3) = \prod M(0, 3, 5, 6)$$

$$f(x_1, x_2, x_3) =$$

$$(x_1 + x_2 + x_3)(x_1 + \bar{x}_2 + \bar{x}_3)$$
$$(\bar{x}_1 + x_2 + \bar{x}_3)(x_1 + x_2 + \bar{x}_3)$$


**Product-of-sums realizations**

$x_1$	$x_2$	$x_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

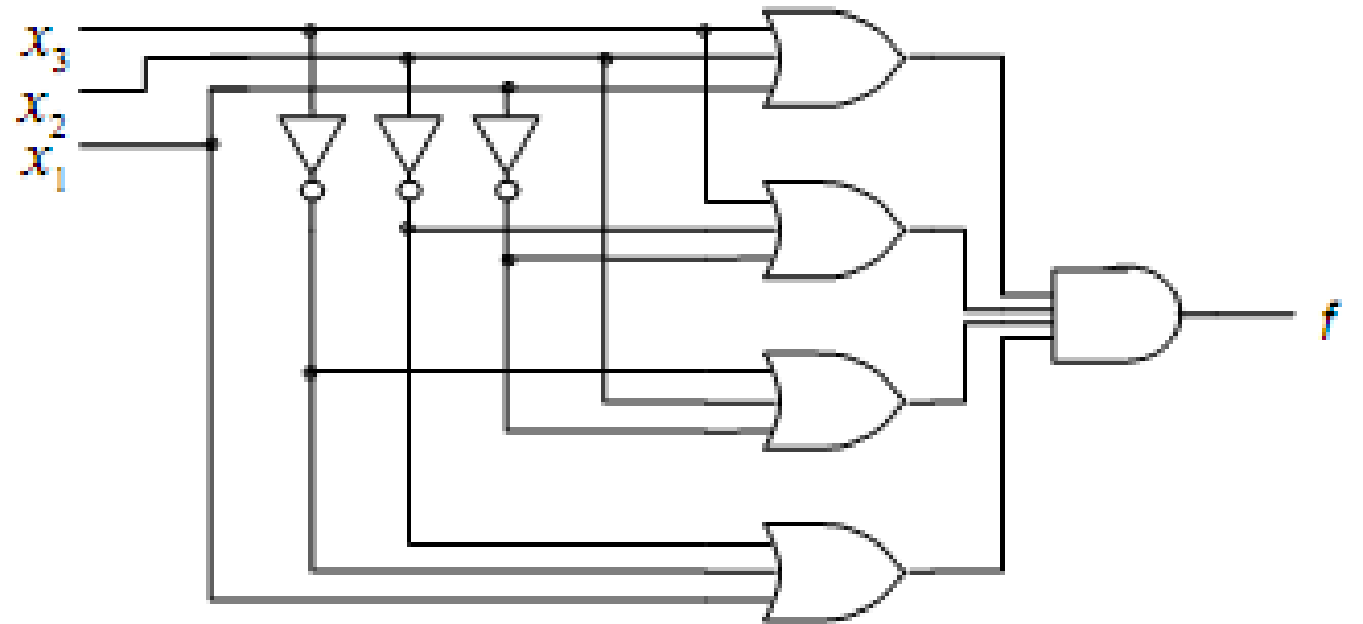




## XOR Gate – Exclusive OR

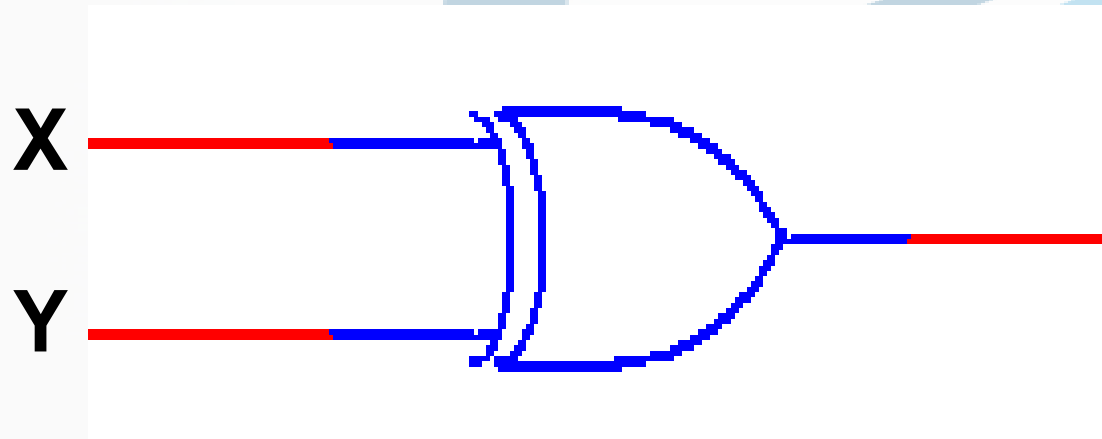

$$Z = \overline{X}Y + X\overline{Y} = X \oplus Y$$

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

## XNOR Gate – Exclusive NOR

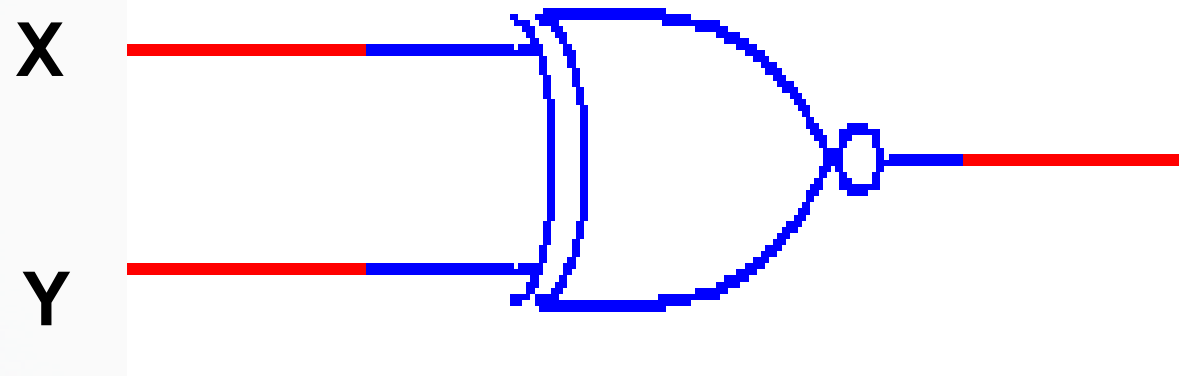

$$Z = \overline{X}Y + X\overline{Y} = X \oplus Y$$

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

## Logic Design with XOR & XNOR

### *Example*

Algebraically manipulate the logic expression for  $F_1$  so that XOR and XNOR gates can be used to implement the function. Other AOI gates can be used as needed.

$$F_1 = X \bar{Y} \bar{Z} + X \bar{Y} Z + X \bar{Y} \bar{Z} + X \bar{Y} Z$$

# Solution

$$F_1 = X \bar{Y} Z + \bar{X} Y Z + \bar{X} \bar{Y} \bar{Z} + X Y Z = Z(X \bar{Y} + \bar{X} Y) + \bar{Y}(\bar{X} \bar{Z} + X Z)$$

$$F_1 = Z(X \oplus Y) + \bar{Y}(X \oplus Z)$$

