

Lecture 9




OTHER COMBINATIONAL LOGIC CIRCUITS

- memory element
- Basic Latch

Dr. Bassam Atieh

MANARA UNIVERSITY

A simple memory element with NOT Gates

   



Basic Latch





Latch with NOR Gates

 Two Different Ways to Draw the Same Circuit







 


**R=0 , S=0
LATCH**

  

**R=1 , S=0
RESET**

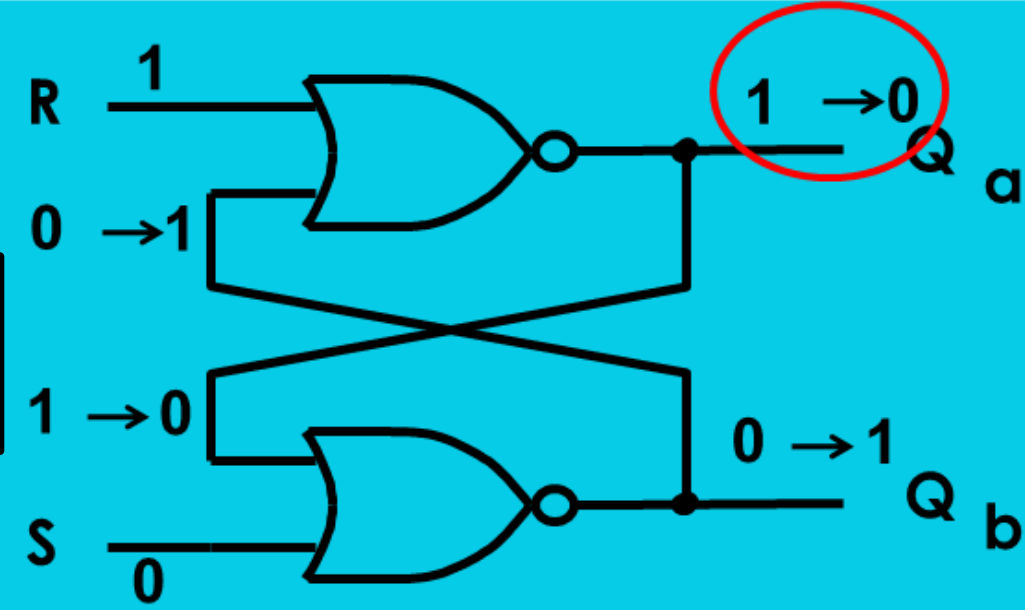

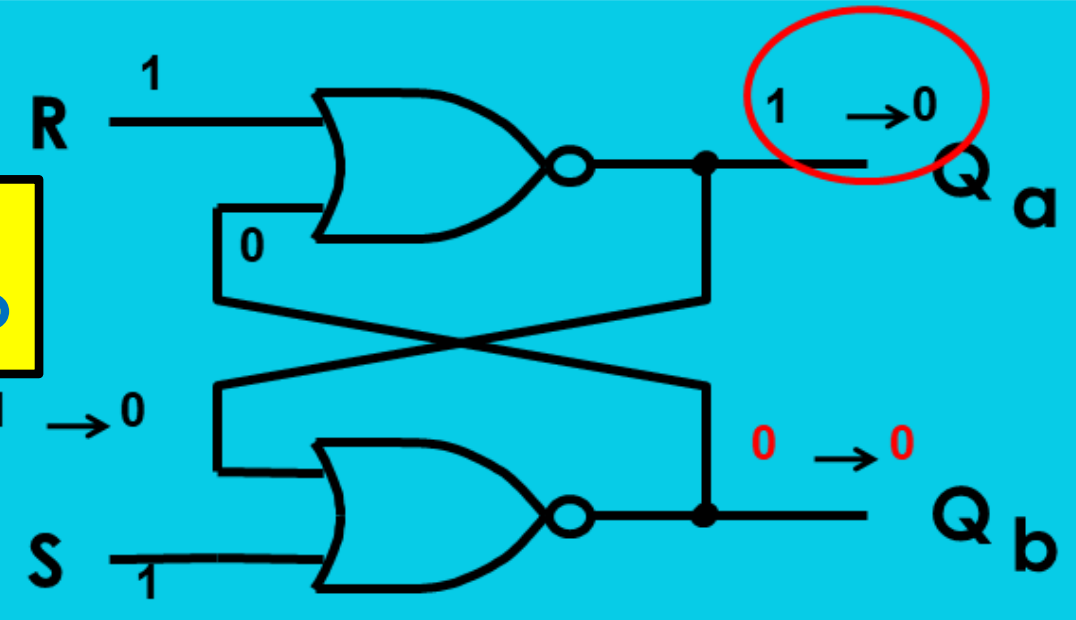 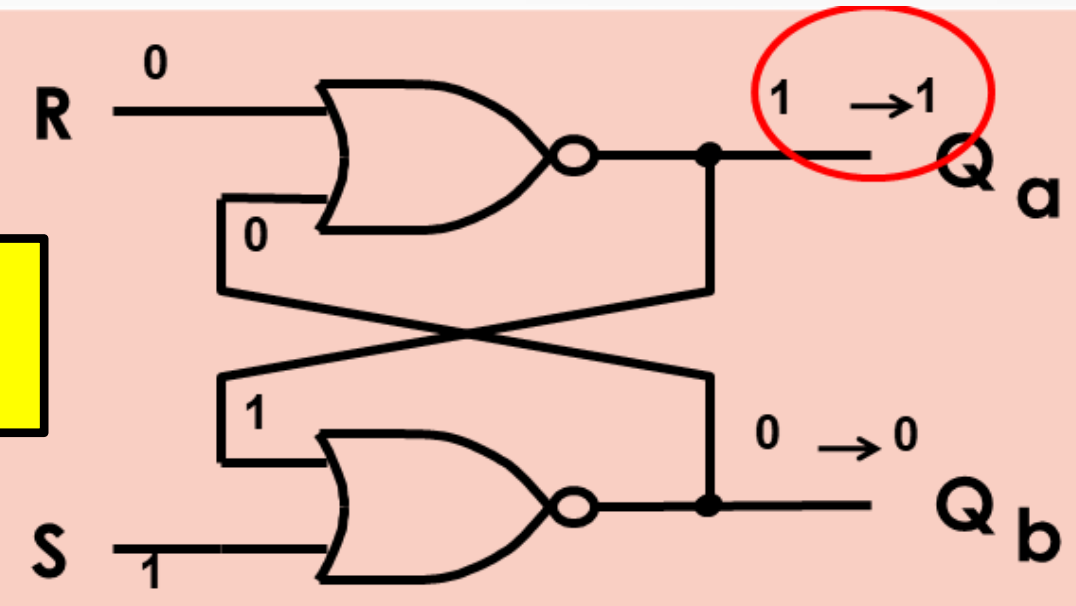 


Characteristic Table Basic Latch with NOR Gates


S	R	Qa-	Qa+	Qb+	state
0	0	0	0	1	R=0 S=0 LAT
0	0	1	1	0	
0	1	0	0	1	R=1 S=0 RESET
0	1	1	0	1	
1	0	0	1	0	R=0 S=1 SET
1	0	1	1	0	
1	1	0	0	0	R=1 S=1 ?
1	1	1	0	0	


تنشيط Windows
انتقل إلى الإعدادات لتنشيط Windows.

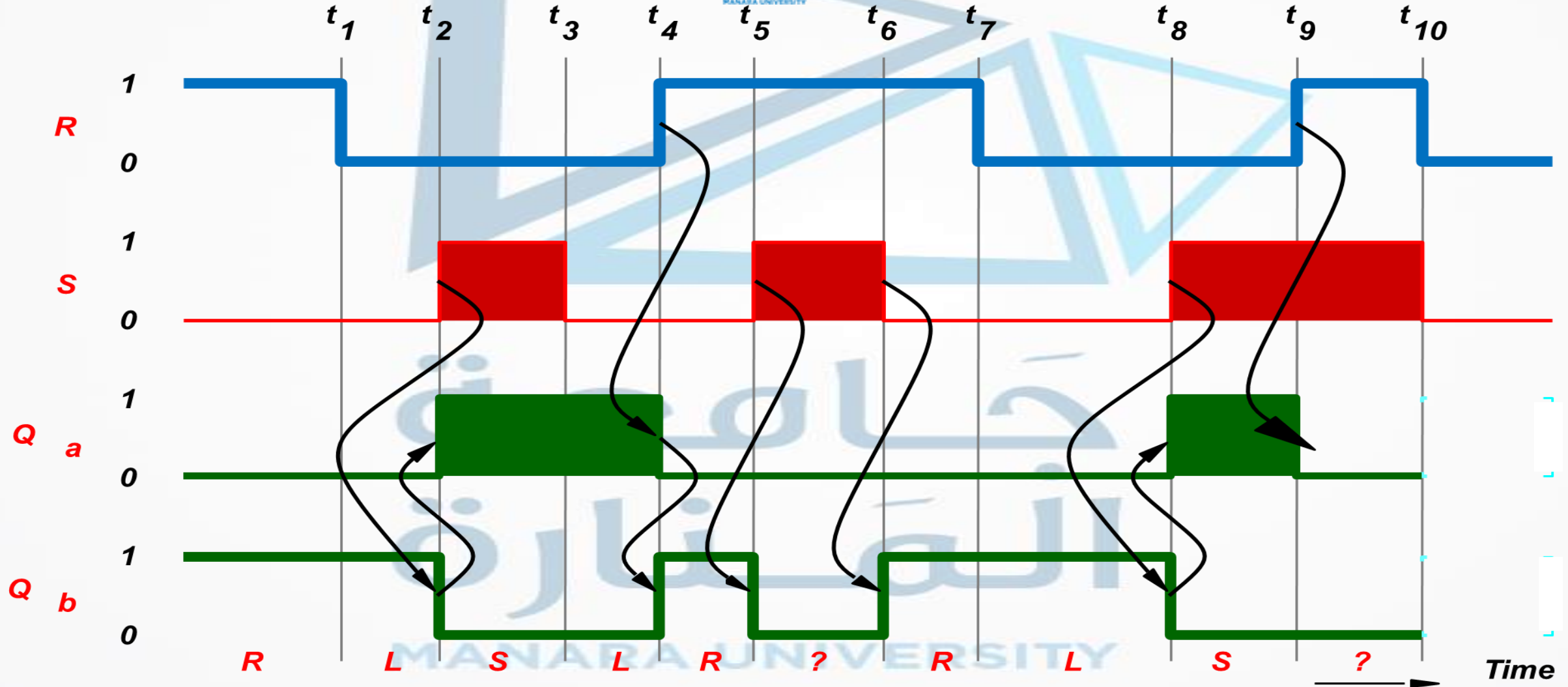Timing Diagram for the Basic Latch with NOR Gates





Latch with NAND Gates

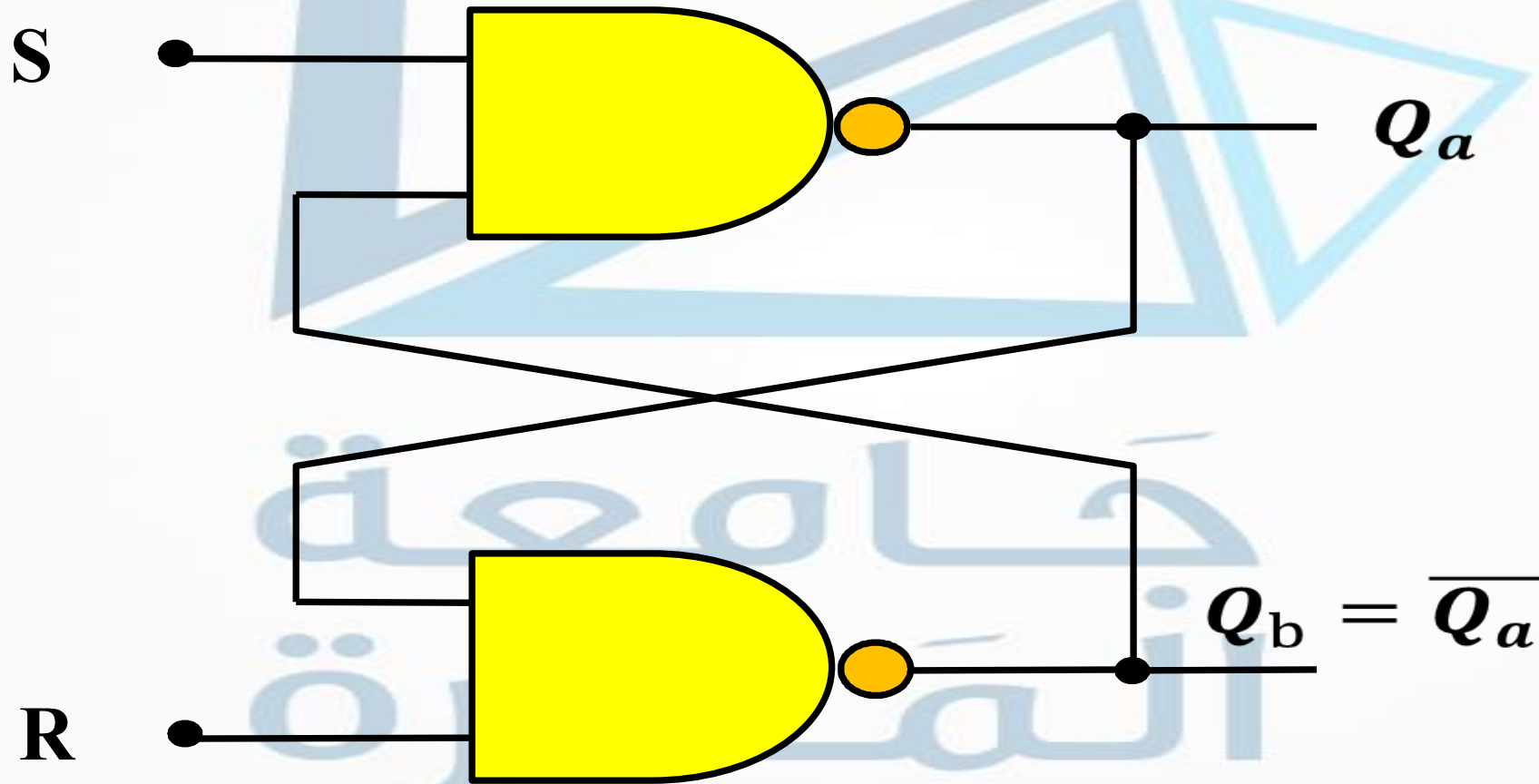


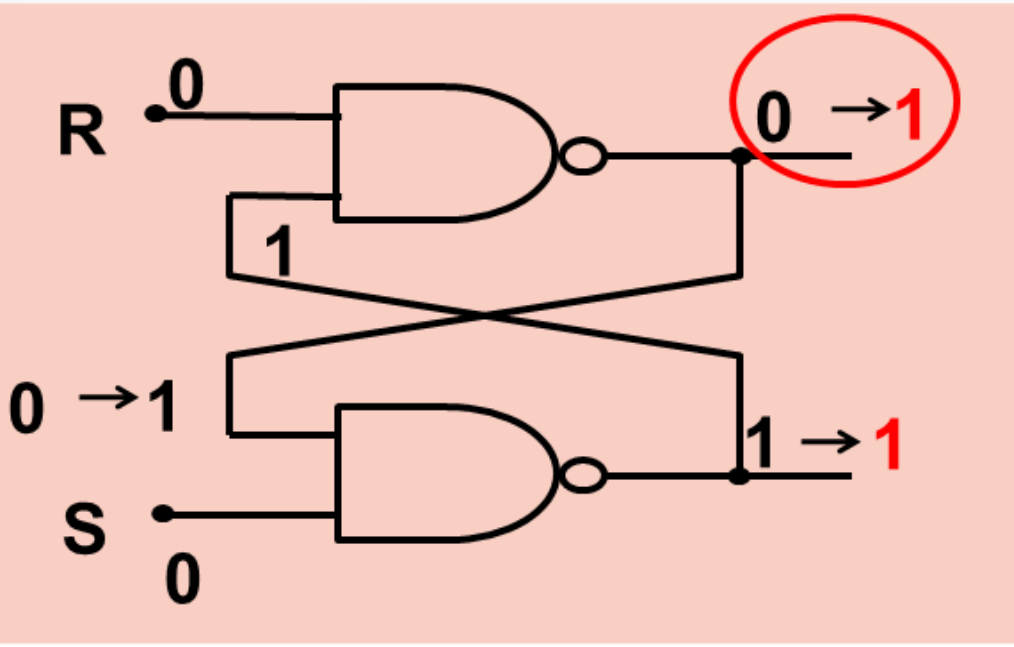


R=0 , S=0
?

 
 


R=1 , S=0
RESET

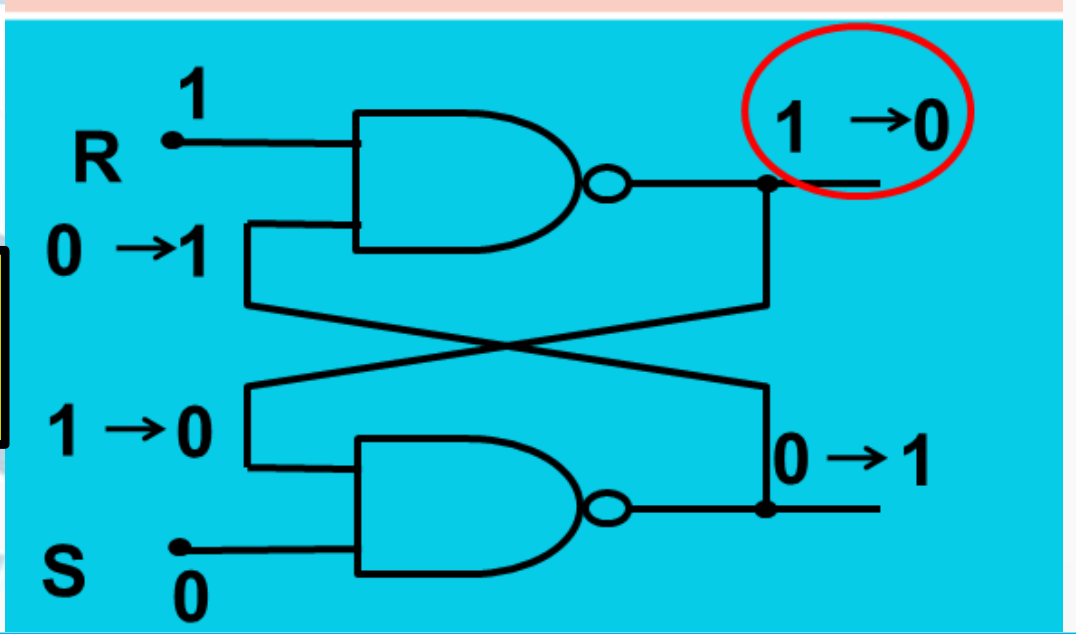


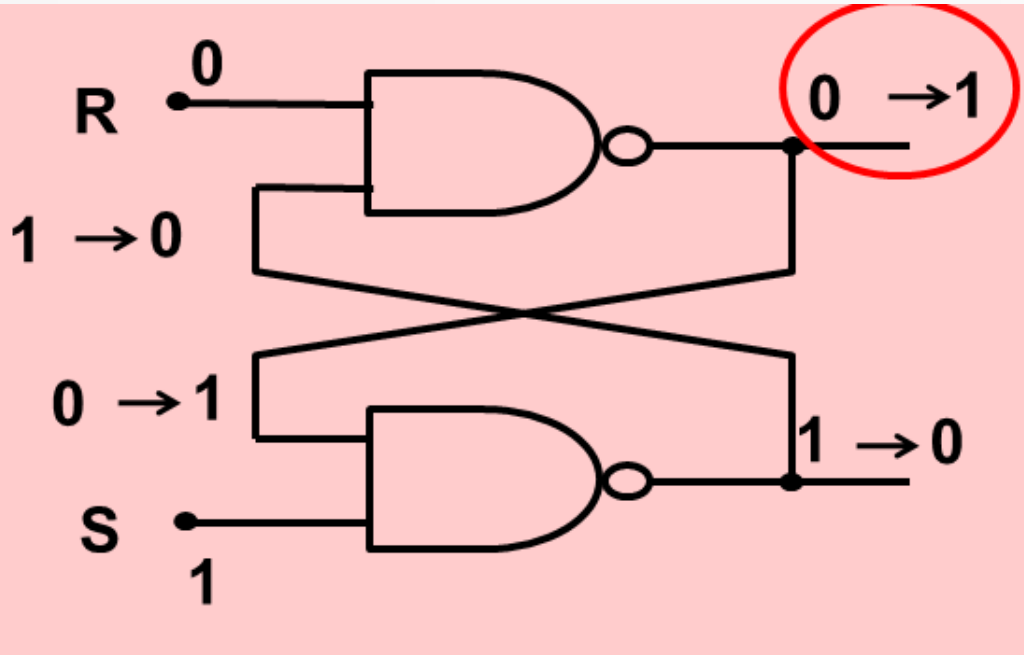

**R=0 , S=1
SET**

  

**R=1 , S=1
LATCH**

 

Characteristic Table Basic Latch with NAND Gates

S	R	Qa-	Qa+	Qb+	state
0	0	0	1	1	R=0 S=0 ?
0	0	1	1	1	
0	1	0	0	1	R=1 S=0 RESET
0	1	1	0	1	
1	0	0	1	0	R=0 S=1 SET
1	0	1	1	0	
1	1	0	0	1	R=1 S=1 LAT
1	1	1	1	0	