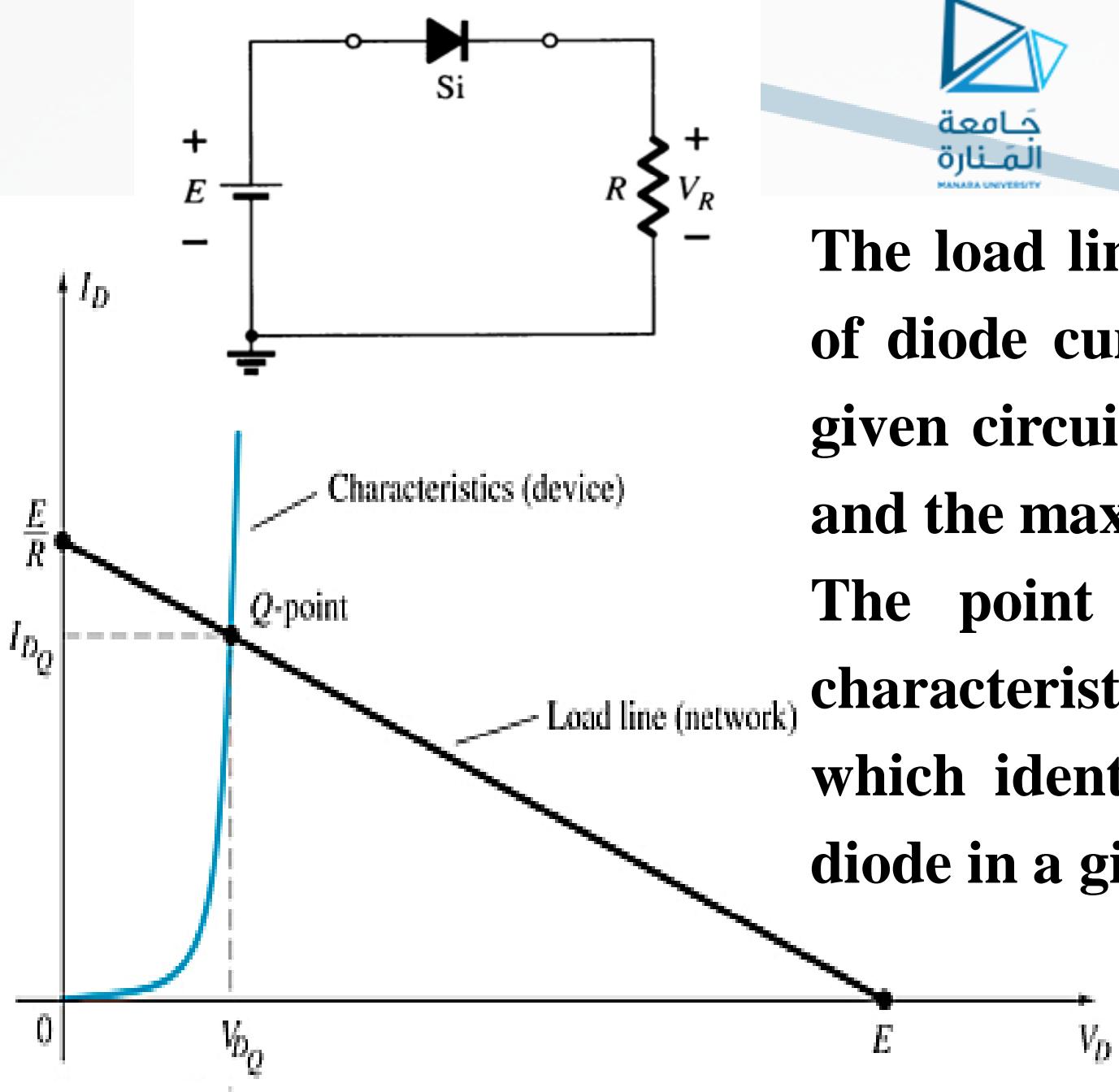


Lecture 4



DIODE PRACTICAL APPLICATIONS

DR. BASSAM ATIEH
MANARA UNIVERSITY



Load-Line Analysis

The load line plots all possible combinations of diode current (I_D) and voltage (V_D) for a given circuit. The maximum I_D equals E/R , and the maximum V_D equals E .

The point where the load line and the characteristic curve intersect is the Q-point, which identifies I_D and V_D for a particular diode in a given circuit.

Series Diode Configurations

Forward Bias

Analysis (for silicon)


- $V_D = 0.7 \text{ V}$ (or $V_D = E$ if $E < 0.7$)
- $V_R = E - V_D$
- $I_D = I_R = I_T = V_R / R$

Reverse Bias

Diodes ideally behave as open circuits

Analysis

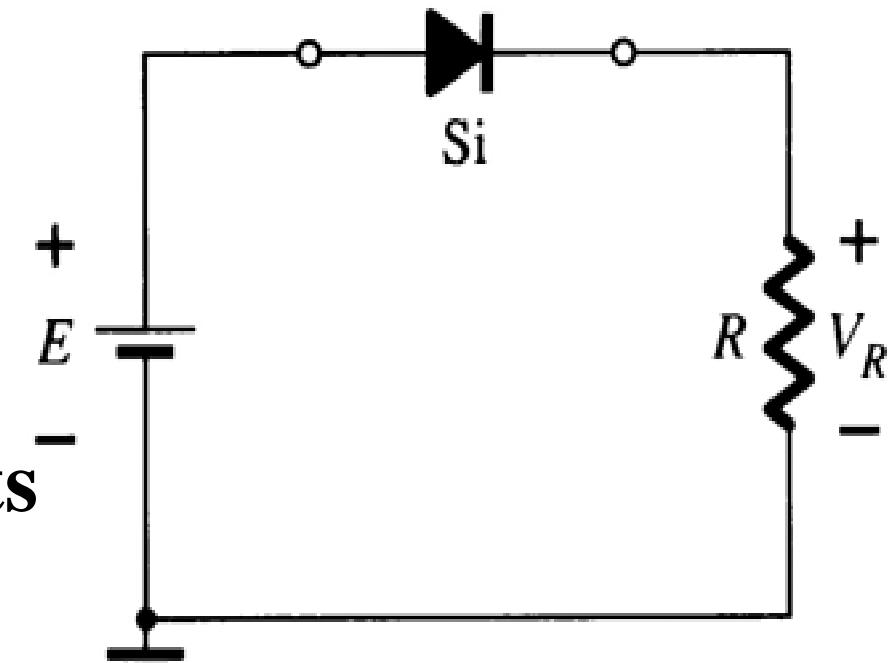- $V_D = E$
- $V_R = 0 \text{ V}$
- $I_D = 0 \text{ A}$



Parallel Configurations


$$V_D = 0.7 \text{ V}$$

$$V_{D1} = V_{D2} = V_O = 0.7 \text{ V}$$

$$V_R = 9.3 \text{ V}$$


$$I_R = \frac{E - V_D}{R} = \frac{10 \text{ V} - .7 \text{ V}}{.33 \text{ k}\Omega} = 28 \text{ mA}$$
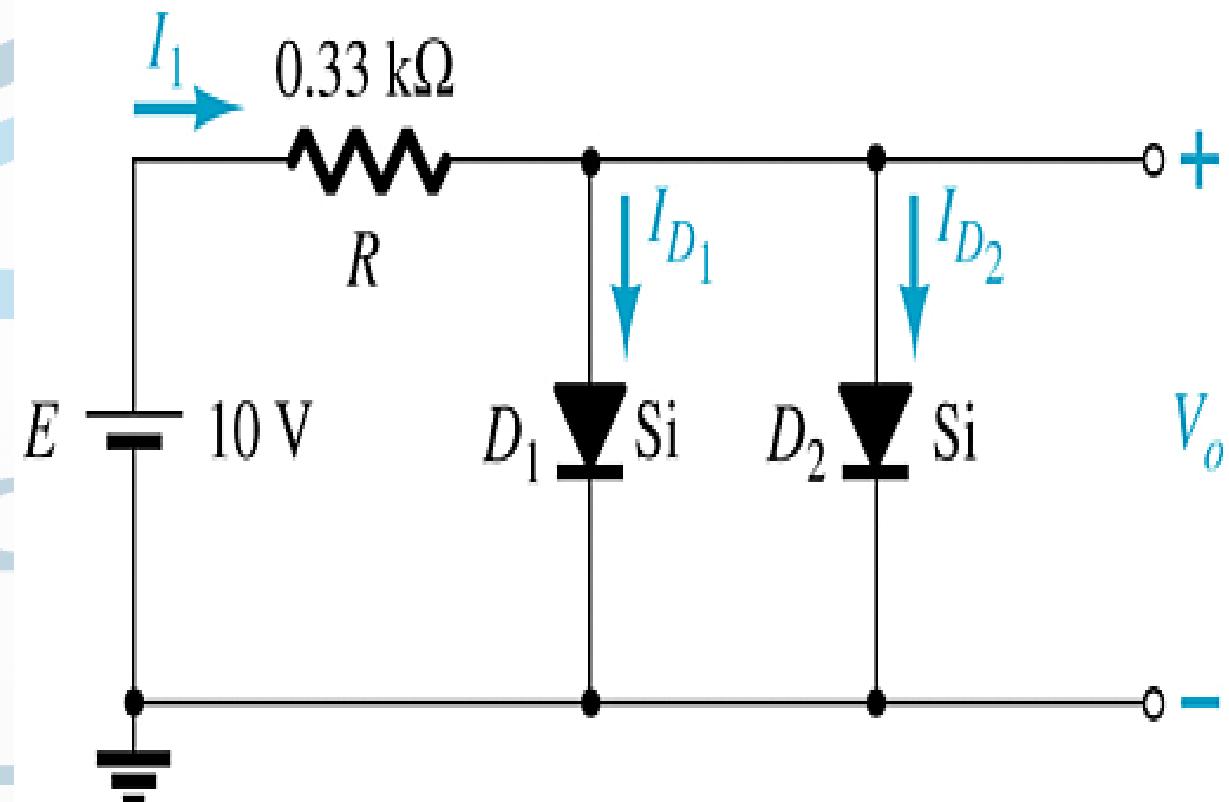
$$I_{D1} = I_{D2} = \frac{28 \text{ mA}}{2} = 14 \text{ mA}$$




يستخدم الديود في مجالات عديدة كالتحديد، التقويم والقص....إلخ . من أجل

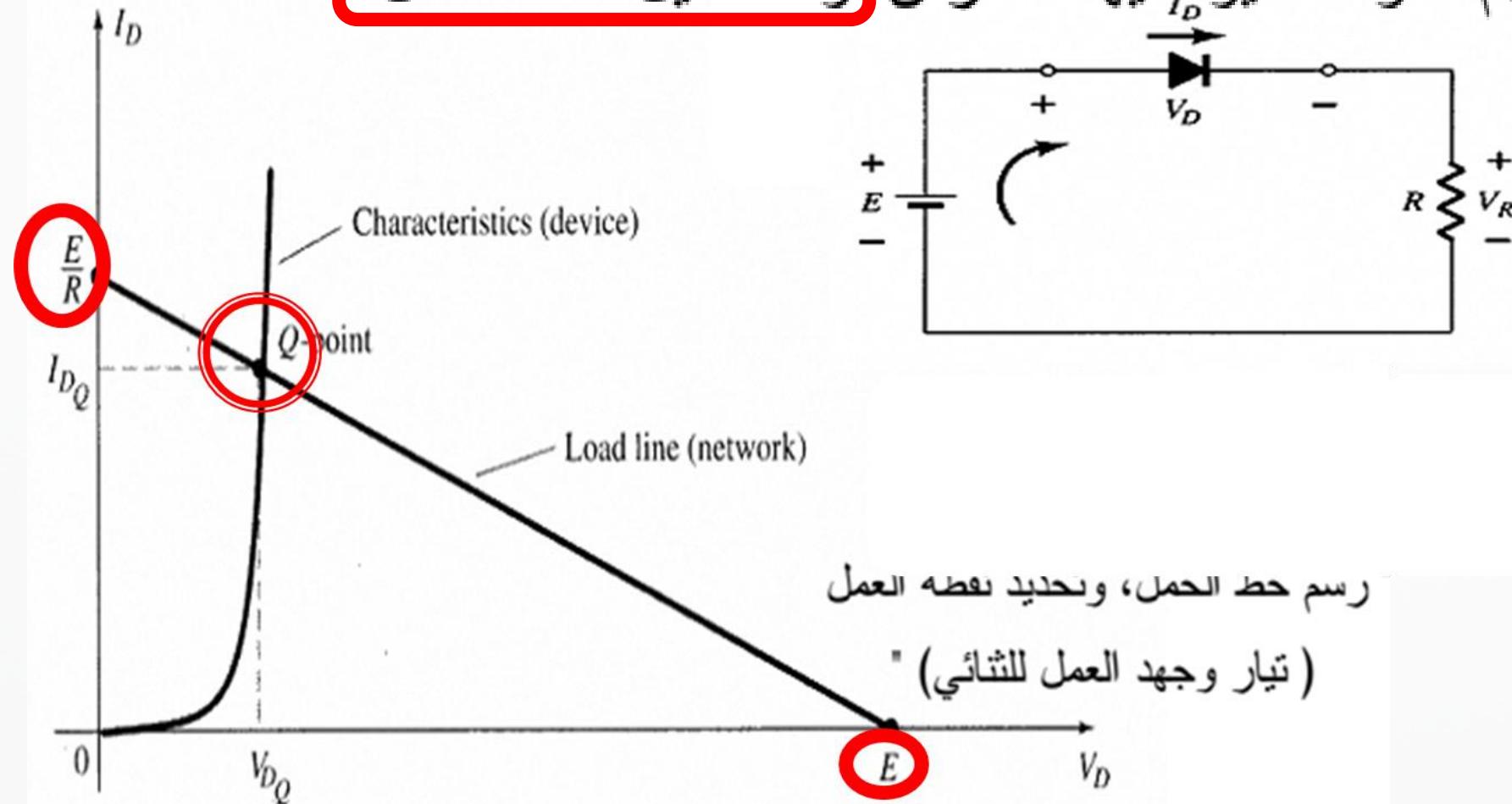حل الدارات وفهم سلوك الديود فيها سندرس أولاً تحليل خط الحمل:



مثال

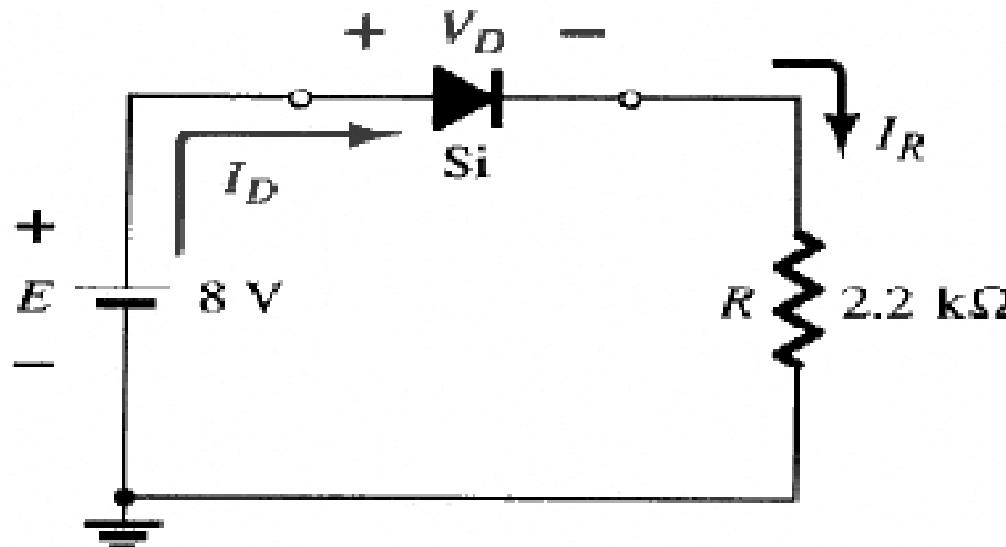أوجد V_D و I_D و V_R في الدارة المبينة في الشكل



$$V_D = 0.7V$$

$$V_R = E - V_D = 8 - 0.7 = 7.3 \text{ volts}$$

$$I_D = I_R = \frac{V_R}{R} = \frac{7.3V}{2.2 * 10^3 \Omega} \Rightarrow$$

$$I_D \cong 3.32 \text{ mA}$$


الديود مستقطب عكسيًا.



$$I_D = 0 \Rightarrow$$

$$E - V_D - V_R = 0 \Rightarrow$$

$$V_D = E - V_R$$

$$V_D = E - 0 = 8 \text{ volts}$$

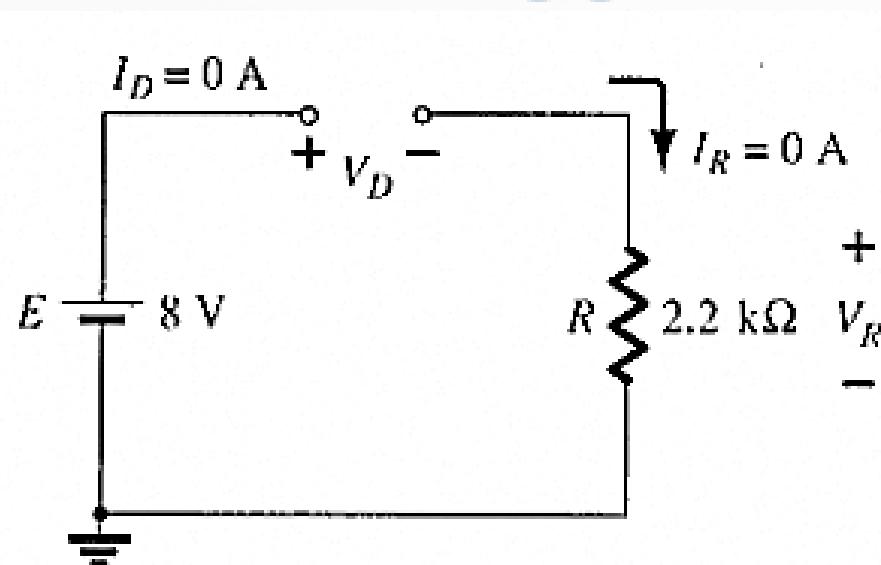

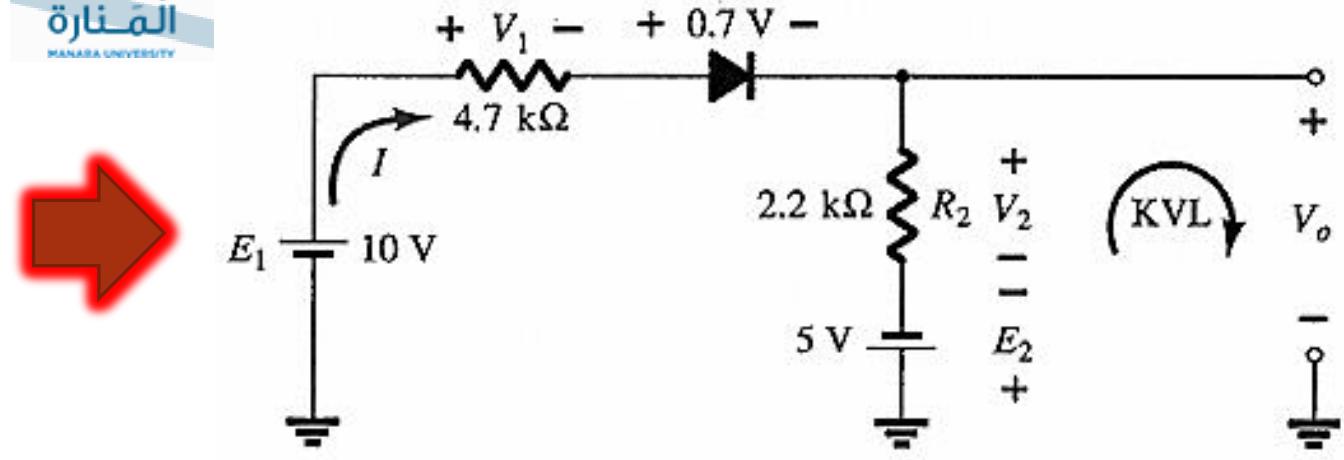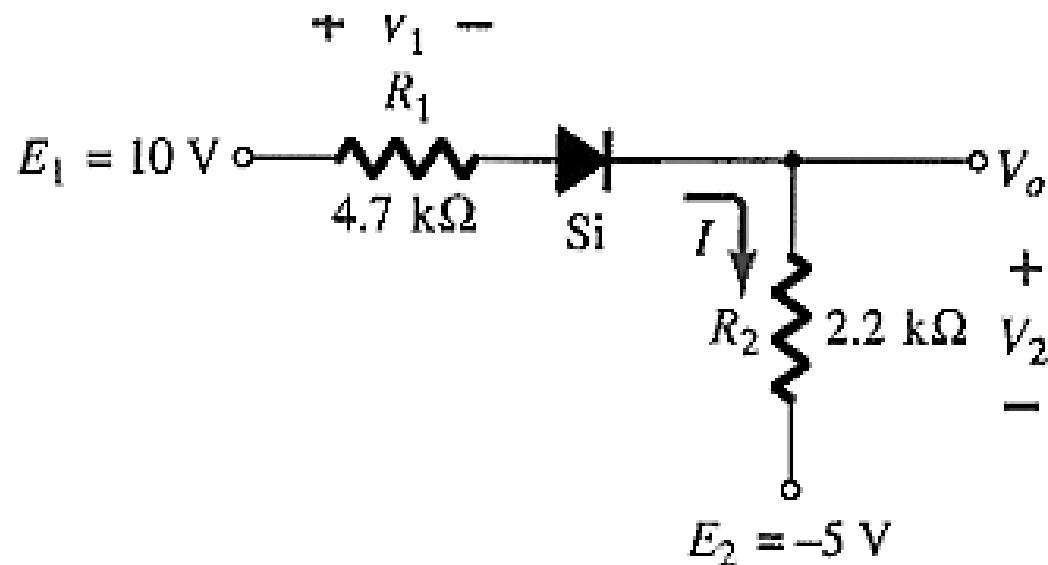

$$I = \frac{E_1 + E_2 - V_D}{R_1 + R_2} = \frac{10 + 5 - 0.7}{(4.7 + 2.2) * 10^3} = \frac{14.3 \text{ volts}}{6.9 * 10^3 \Omega} \Rightarrow$$


$$I = 2.07 \text{ mA}$$

$$V_1 = I * R_1 = 2.07 * 10^{-3} * 4.7 * 10^3 = 9.73 \text{ volts}$$

$$V_2 = I * R_2 = 2.07 * 10^{-3} * 2.2 * 10^3 = 4.55 \text{ volts}$$

$$V_o = V_2 - E_2 = 4.55 - 5 = -0.45 \text{ volts}$$

مثال

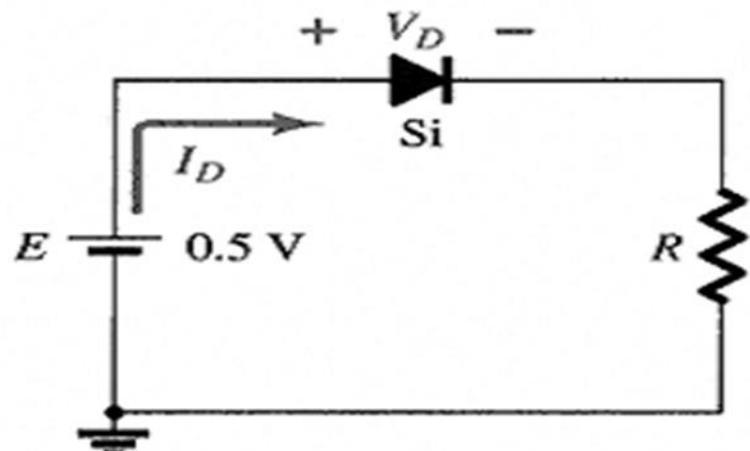


نلاحظ أن جهد التغذية أقل من الجهد اللازم لفتح الديود، لذا فإن التيار المار في الدارة


$$I_D = 0 \text{ Amper}$$

$$V_R = I_R * R = I_D * R = 0 \text{ Volts}$$
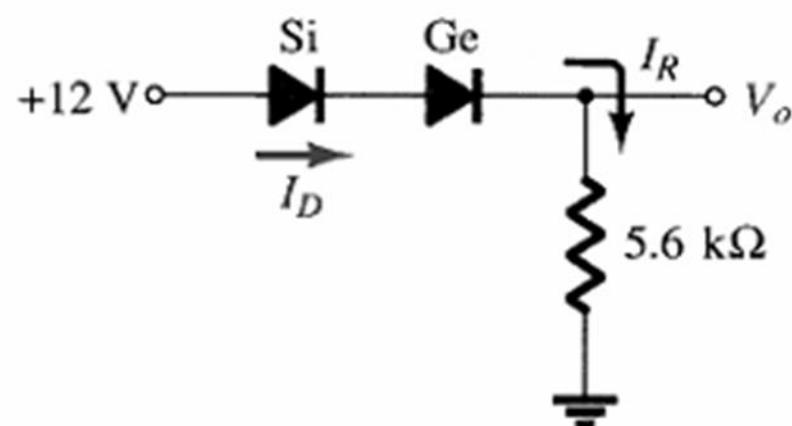
$$V_D = E - V_R = 0.5 - 0 = 0.5 \text{ Volts}$$



الدارة المكافئة


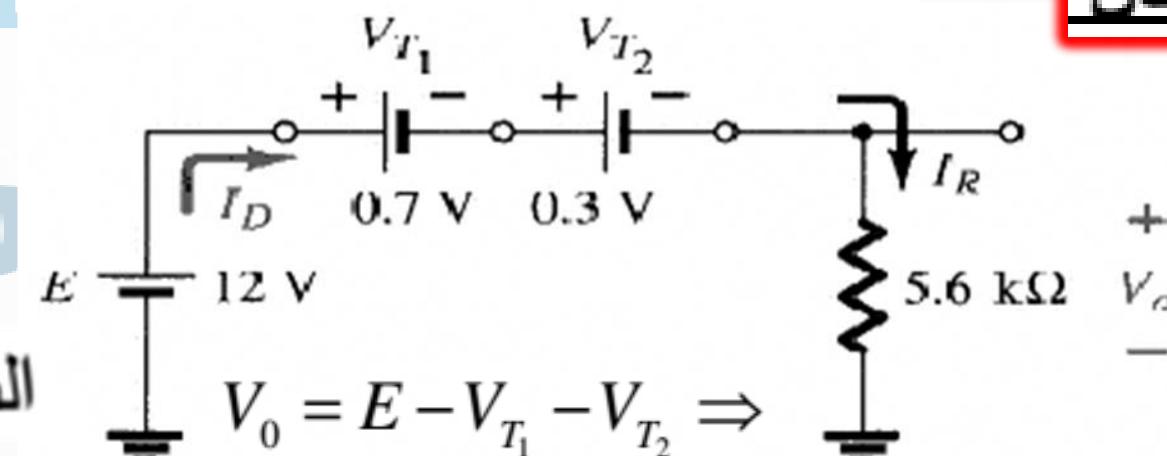


$$V_0 = E - V_{T_1} - V_{T_2} \Rightarrow$$

$$V_0 = 12 - 0.7 - 0.3 = 11 \text{ Volts}$$

$$I_D = I_R = \frac{V_0}{R} = \frac{11}{5.6 * 10^3} \cong 1.96 \text{ mA}$$

مثال

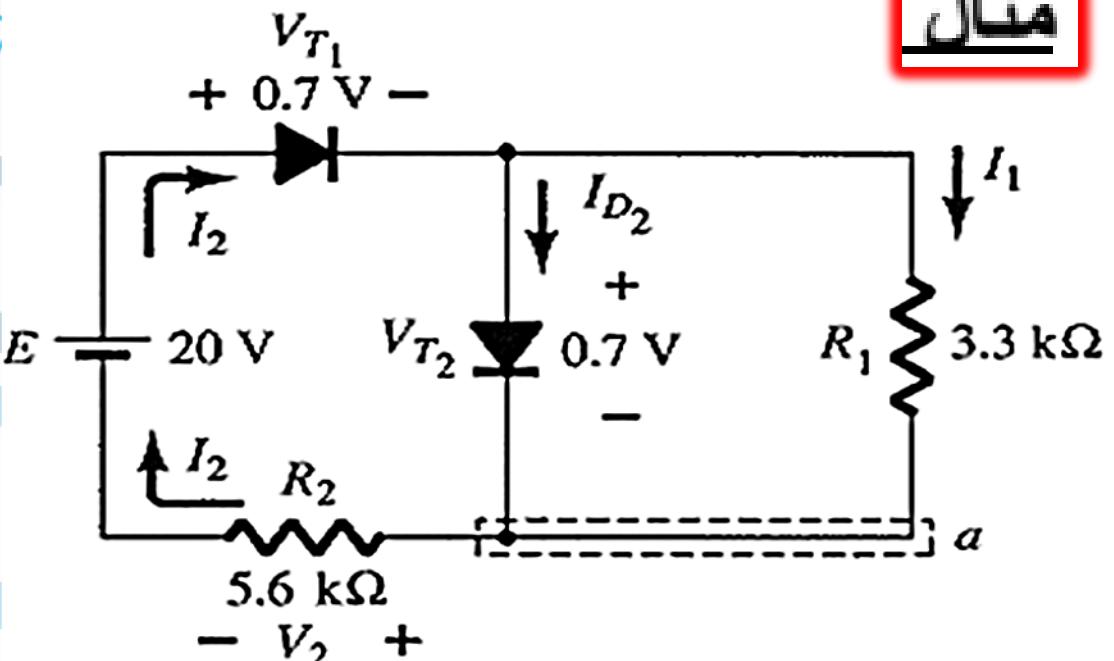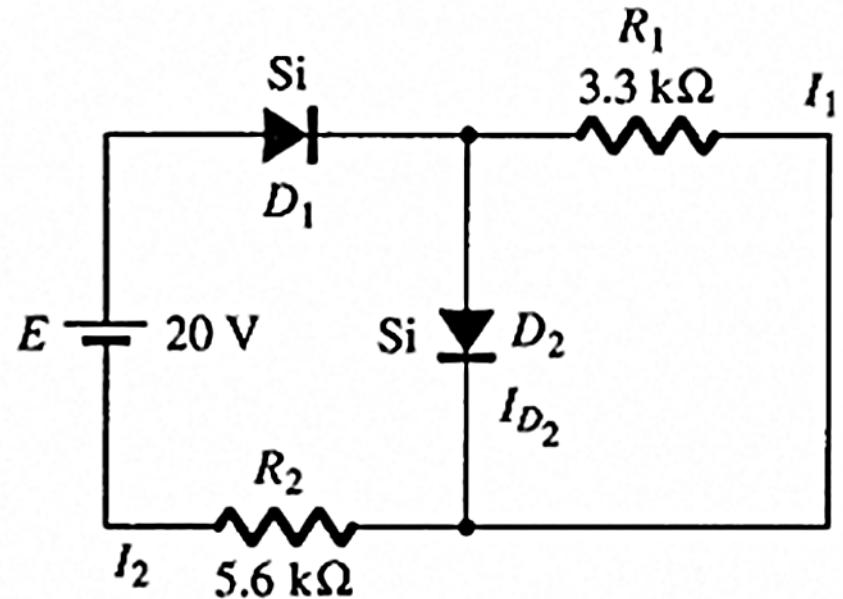

$$I_1 = \frac{V_{T_2}}{R_1} = \frac{0.7v}{3.3 * 10^3 A} = 0.212 \text{ mA}$$

$$-V_2 + E - V_{T_2} - V_{T_1} = 0 \Rightarrow$$

$$V_2 = +E - V_{T_2} - V_{T_1} = 20 - 0.7 - 0.7 \Rightarrow$$

$$V_2 = 18.6 \text{ volts}$$

$$I_2 = \frac{V_2}{R_2} = \frac{18.6v}{5.6 * 10^3 \Omega} = 3.32 \text{ mA}$$

$$\begin{aligned} I_{D_2} + I_1 &= I_2 \Rightarrow \\ I_{D_2} &= I_2 - I_1 = 3.32 \text{ mA} - 0.212 \text{ mA} = 3.108 \text{ mA}. \end{aligned}$$