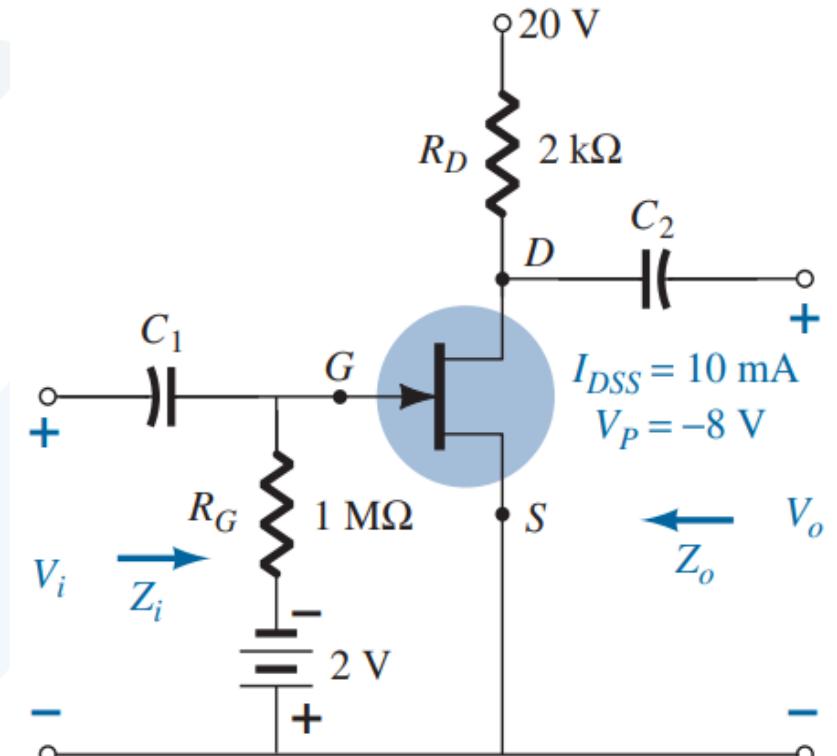


دارات الكترونية المحاضرة ٦ / - عملي



الدكتور السمو عل صالح
المهندس جبران خليل
المهندسة ايه خيربك

AC Equivalent circuit

- The fixed-bias configuration of JFET transistor have an operating point defined by: $V_{GSQ} = -2$ V and $I_{DQ} = 5.625$ mA, with $I_{DSS} = 10$ mA and $V_p = -8$ V. The network is drawn as the following Fig. with an applied signal V_i .
- The value of y_{os} is provided as 40 mS



AC Equivalent circuit

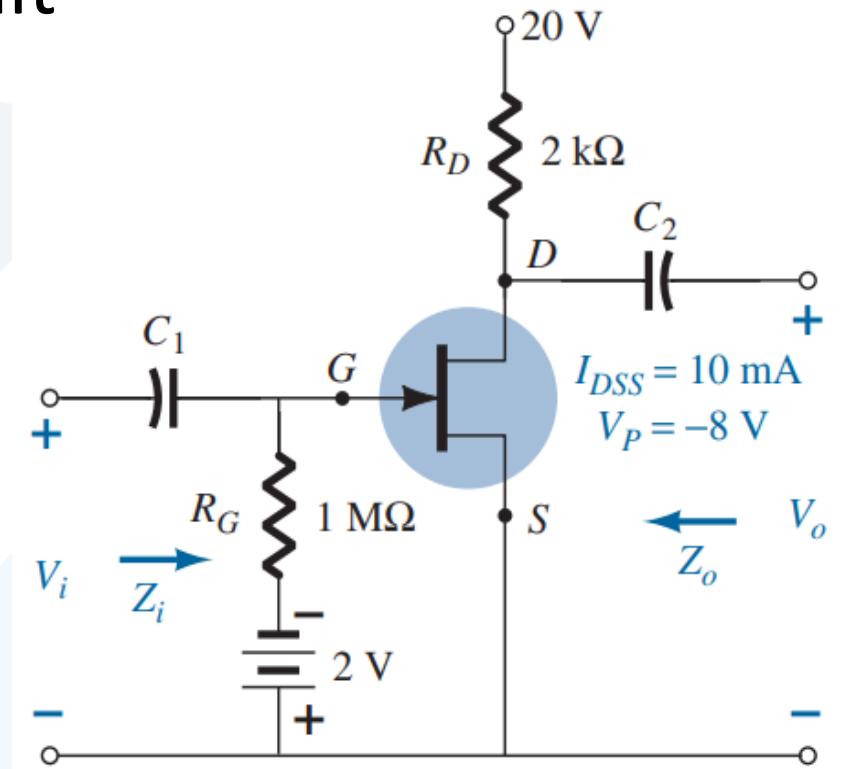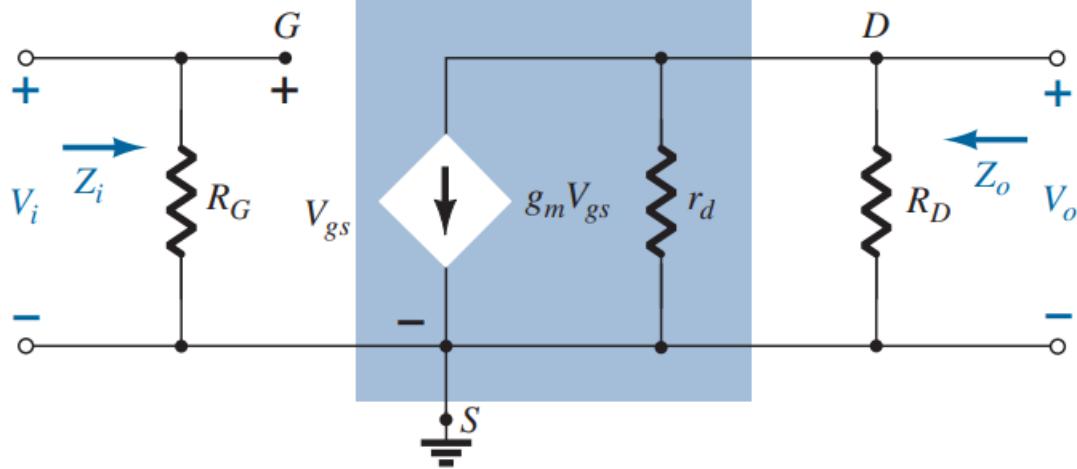

AC Equivalent circuit

a. $g_{m0} = \frac{I_{DSS}}{|V_P|} = \frac{2(10mA)}{8V} = 2.5 \text{ mS}$

$$g_m = g_{m0}\left(1 - \frac{V_{GSQ}}{V_P}\right) = 2.5mS\left(1 - \frac{-2v}{-8v}\right) = 1.88mS$$

b. $r_b = \frac{1}{y_{os}} = \frac{1}{40\mu S} = 25k\Omega$

c. $Z_i = R_G = 1M\Omega$

d. $Z_o = R_D || r_d = 2k\Omega || 25k\Omega$

e. $A_v = -g_m(R_D || r_d) = -(1.88mS)(1.85k\Omega) = -3.48$

f. $A_v = -g_m R_D = -(1.88mS)(2k\Omega) = -3.76$

As demonstrated in part (f), a ratio of $25 k\Omega : 2 k\Omega = 12.5:1$ between r_d and R_D results in a difference of 8% in the solution.