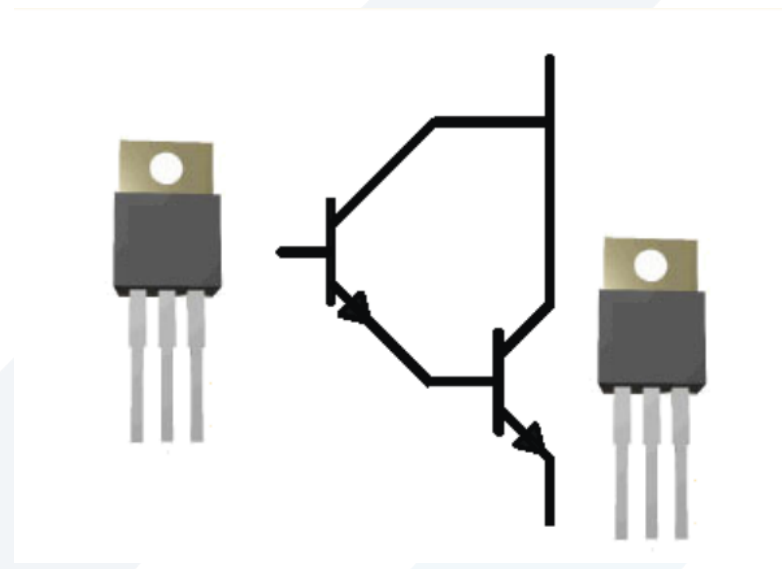


دارات الكترونية 1 المحاضرة /9/ - عملي

الدكتور السموع صالحي
المهندس جبران خليل
المهندسة ايه خيربك

Darlington circuit

A Darlington circuit consists of two transistors connected in series. The base of the second transistor is triggered by the emitter current of the first one




Darlington circuit

Current gain of V1

Measure the base current I_{B1} and the collector current I_{C1} of transistor stage V1.

From these values, calculate the current gain of V1.

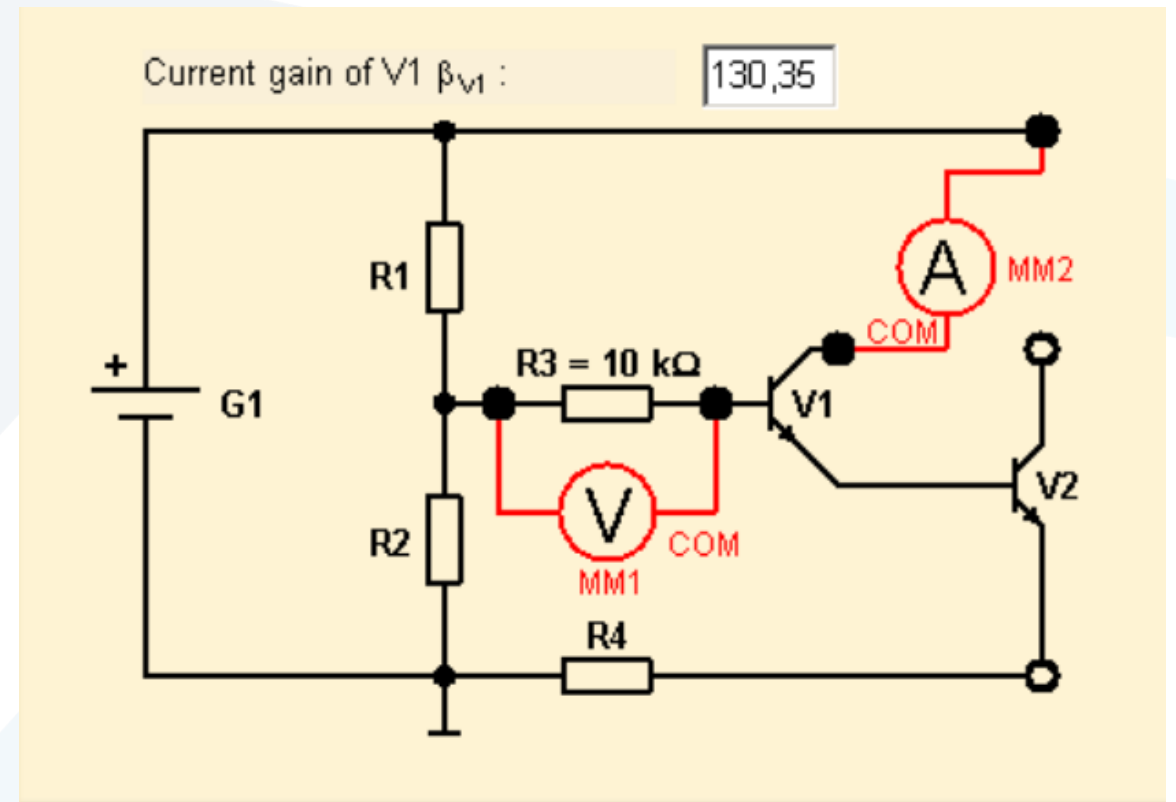- Base current $I_{B1} = U_{R3} / R3$
- Current gain $V = I_C / I_B$



Darlington circuit


Current gain of V2

Measure the base current I_{B2} and the collector current I_{C2} of transistor stage V2.

The base current I_{B2} is measured indirectly by measuring the collector current I_{C1} of V1:

$$I_{C1} \approx I_{E1} = I_{B2}$$

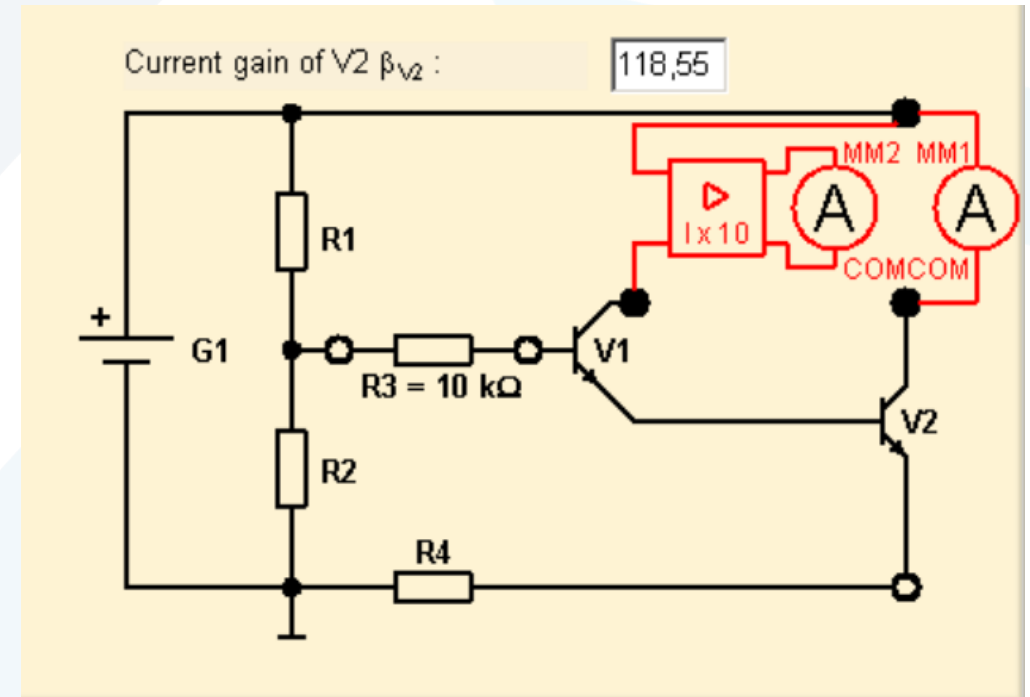- Use I_{C1} and I_{C2} to calculate the approximate value of the current gain of V2



Darlington circuit


Total current gain

Measure the base current I_{B1} of transistor stage V1 and the collector current I_{C2} of transistor stage V2.

Use I_{B1} and I_{C2} to calculate the total current gain2 .

Current gain $V = I_C / I_B$

Base current $I_{B1} = U_{R3} / R3$

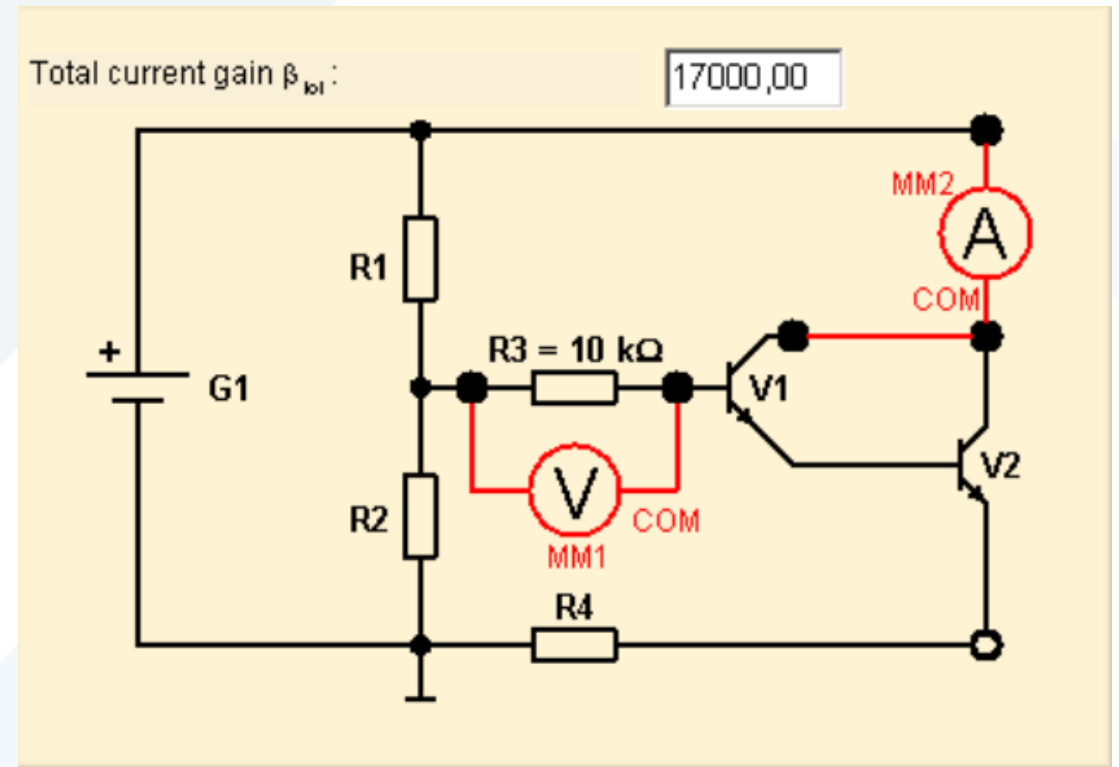

Darlington circuit

Summary of this chapter

- Darlington circuits are available as discrete configurations and as integrated modules.
- An integrated Darlington circuit is termed "Darlington transistor".
- A Darlington circuit consists of two transistors connected in series.
- The base of the second transistor is triggered by the emitter current of the first transistor.
- Consequently, the total gain is the product of the individual transistor gain factors.
- The special property of a Darlington circuit is thus its high current gain