

الالكترونيات الطاقة

Lecture No. 4

دارة تقويم موجة كاملة أحادية الطور جسريه
Bridge Rectifier


ميكاترونيكس - سنة رابعة - فصل ثاني



Dr. Eng. Essa Alghannam
Ph.D. Degree in Mechatronics Engineering


2023

- In half wave rectifier, only **1 half cycle is allowed** and the **remaining half cycle is blocked**. As a result, nearly **half of the applied power is wasted in half wave rectifier**. In addition to this, the output current or voltage produced by half wave rectifier **is not a pure DC but a pulsating DC** which is not much useful.
- The main advantage of center tapped full wave rectifier is that **it allows electric current during both positive and negative half cycles** of the input AC signal. As a result, the DC output of the center tapped full wave rectifier is double of that of a half-wave rectifier. In addition to this, the DC output of center tapped full wave rectifier **contains very fewer ripples**. As a result, the DC output of the center tapped full wave rectifier **is smoother than** the half wave rectifier.
- the center tapped full wave rectifier has one drawback that is the center-tapped transformer used in it is **very expensive and occupies large space**. Also there is an average [mean] component of the source current.
- To cut this extra cost, scientists developed a new type of rectifier known as a bridge rectifier. **In bridge rectifier, center tap is not required**. If **stepping down or stepping up of voltage is not required**, then even the **transformer can be eliminated in** the bridge rectifier.

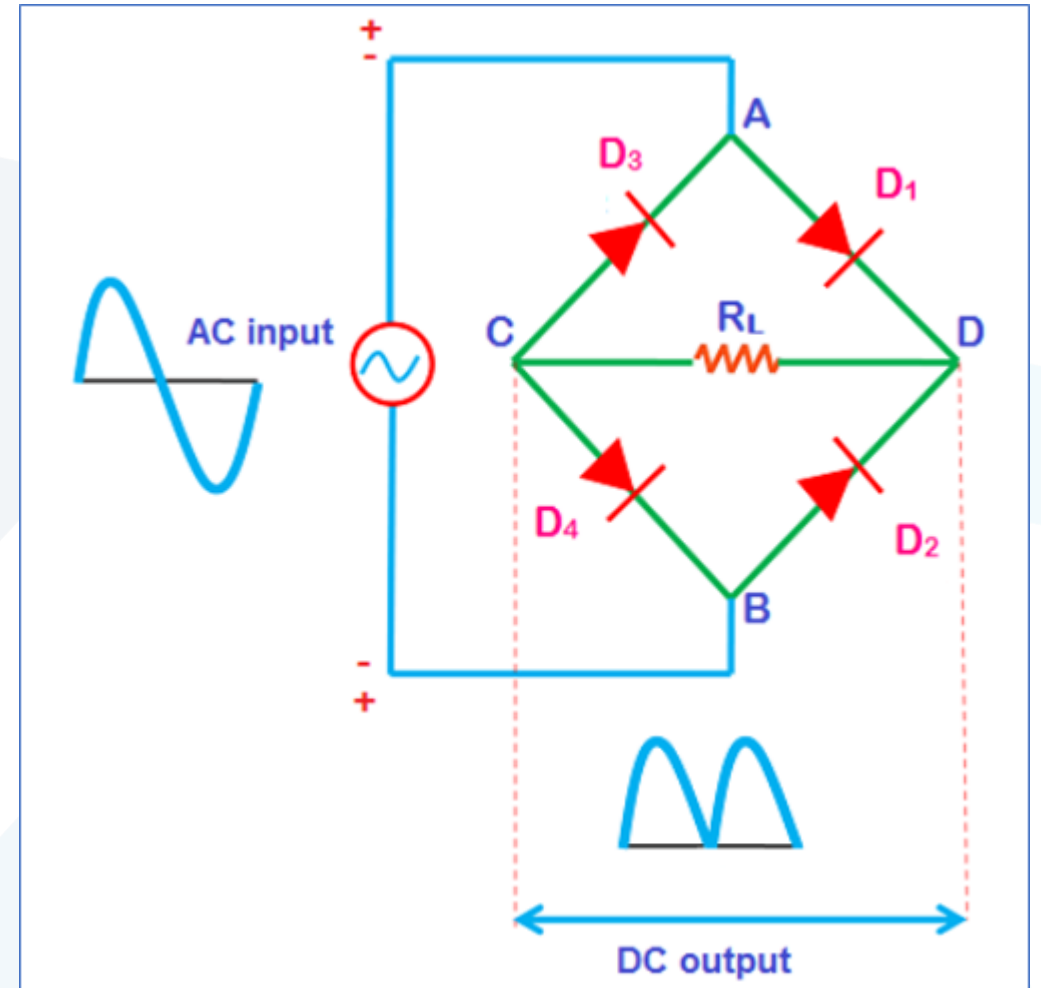- The rectifier efficiency of a bridge rectifier is almost equal to the center tapped full wave rectifier.
- The bridge rectifier is made up of four diodes namely D_1 , D_2 , D_3 , D_4 and load resistor R_L .
- **The four diodes are connected in a closed loop (Bridge) configuration to efficiently convert the Alternating Current (AC) into Direct Current (DC).**



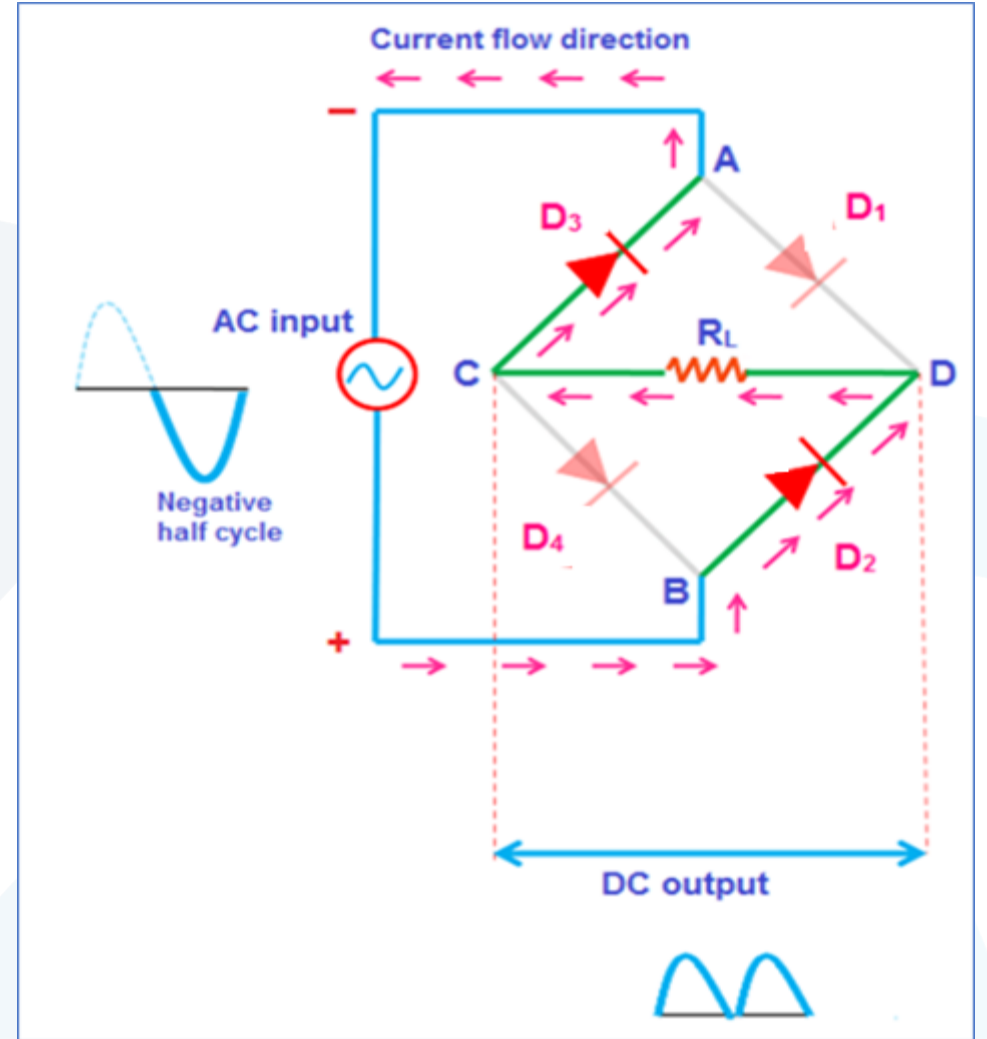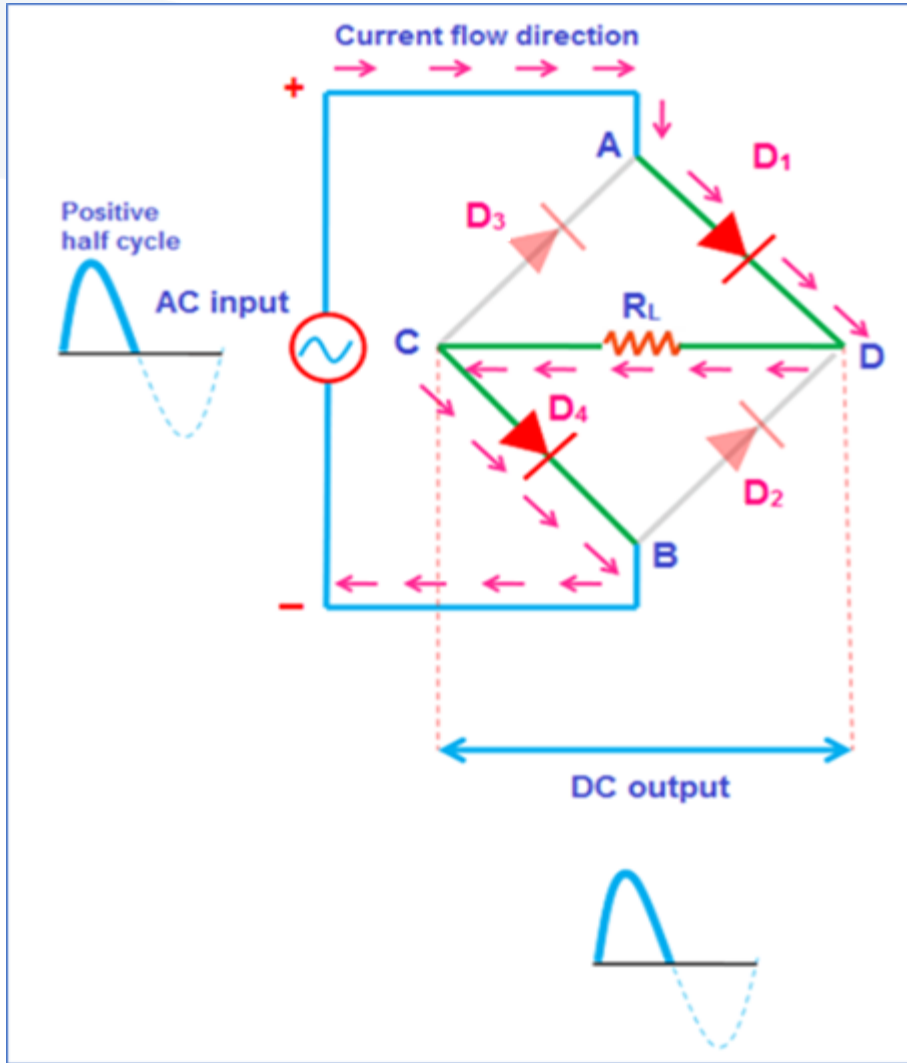

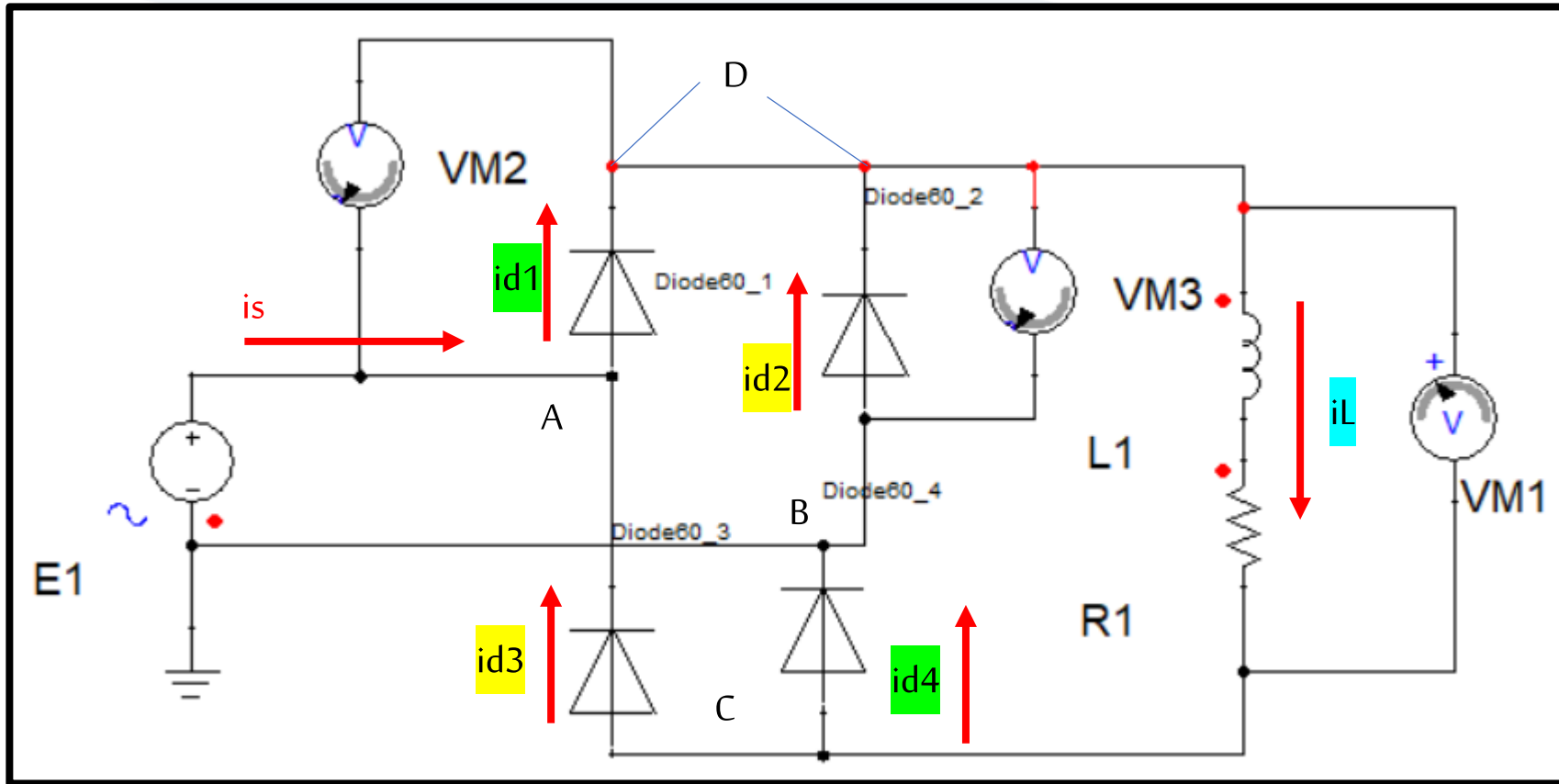

Parameters - E1 - Voltage Source

Parameters | AC - Parameters | Output / Display

Name Show Name

Parameters

EMF Value V Use Pin
Value, Variable, Expression AC use

Time Controlled

Spice compatible

RMS Value

Amplitude V Phase deg

Frequency Hz Offset V

Period s Rise Time s

Periodical

Delay s Fall Time s

Pulse Width s

Outputs

Voltage Current EMF Value

OK Cancel

Parameters - R1 - Resistor

Parameters | Output / Display

Name Show Name

Parameters

Resistance Use Pin
Value, Variable, Expression

Nonlinear $i = f(v)$ Use Pin

Outputs

Voltage Current Resistance

OK Cancel

×

Parameters - L1 - Inductor

Parameters | Output / Display

Name Show Name

Parameters

Inductance Use Pin
Value, Variable, Expression

Nonlinear $i = f(\psi)$ Use Pin

Nonlinear $L = f(i), dL/dt = 0$ Use Pin

Initial Value

Initial Value


Outputs

Voltage Current Inductance

OK Cancel

$$e_1 = u_1 = U_{2m} \sin(\theta) = \sqrt{2}U_{2rms} \sin(\theta)$$


جهد المصدر

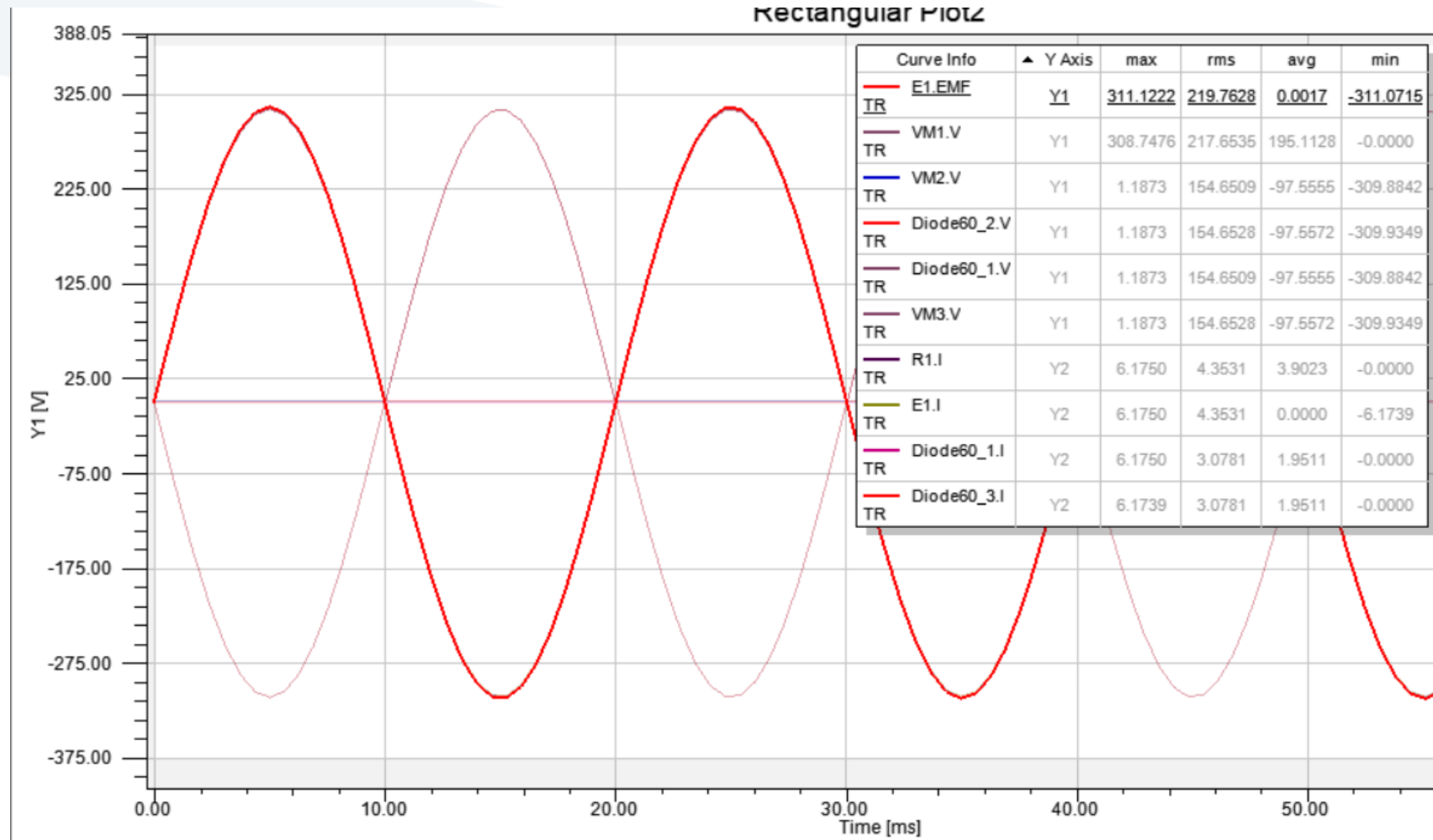

Rectangular Plot2

جهد الحمل

U_{2m}

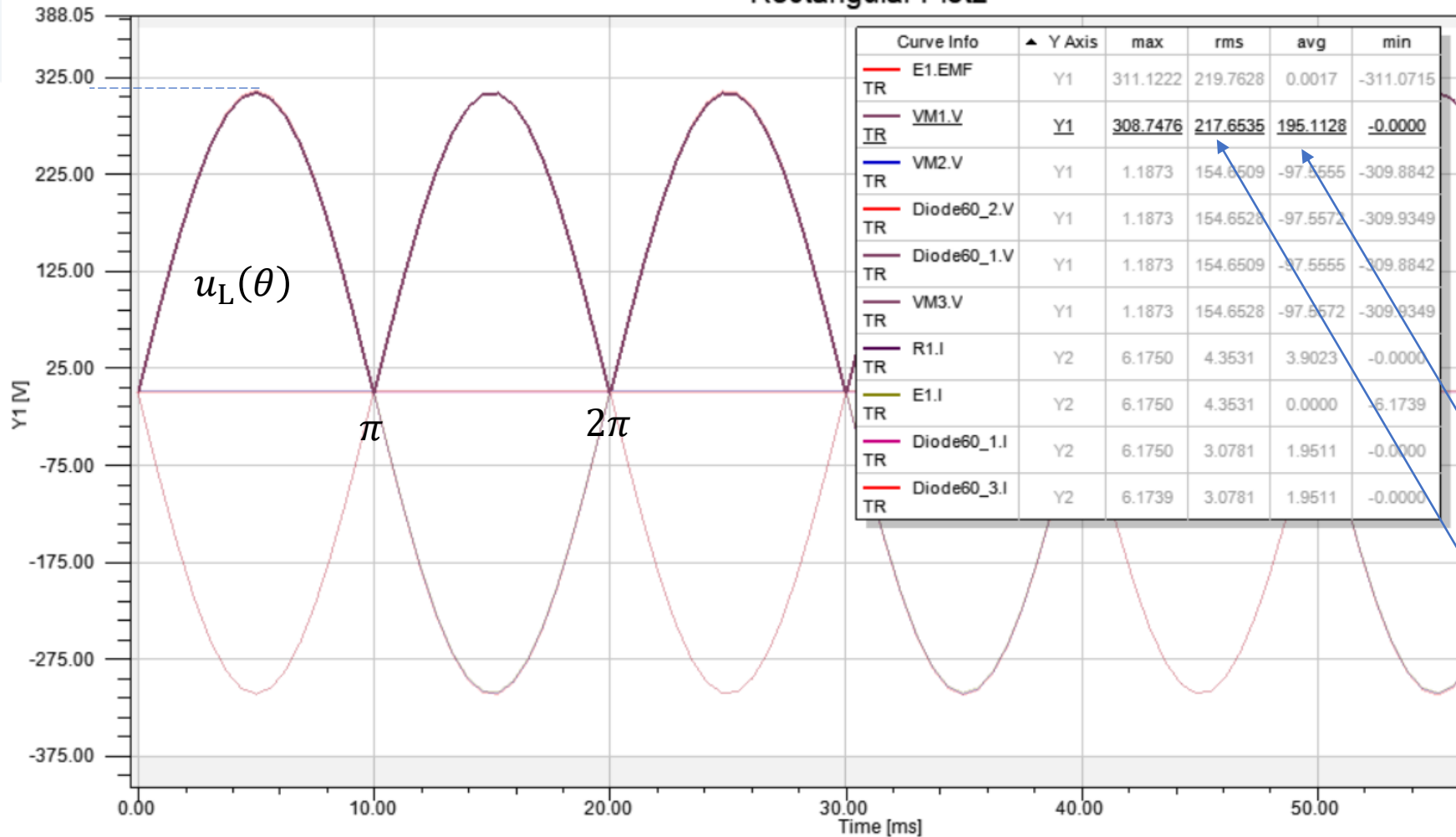

$U_{Lav} = 0.9 \cdot 220 = 198V$
 $U_{Lrms} = 220V$

بارامترات جهد الحمل

يكون الجهد عبر الحمل U_L مكون من مركبة مستمرة DC بالإضافة الى تموج AC.

$$U_{L_{av}} = \frac{2}{2\pi} \left[\int_0^{\pi} U_{2m} \sin(\theta) d\theta \right]$$

$$U_{L_{av}} = \frac{2U_{2m}}{2\pi} [-\cos \theta]_0^{\pi} = \frac{2U_{2m}}{2\pi} [1+1]$$

$$U_{L_{av}} = \frac{2U_{2m}}{\pi} = \frac{2\sqrt{2}}{\pi} U_{2rms} = 0.9U_{2rms} = 198v$$

قيمة جهد الحمل المقوم المتوسطة

قيمة جهد الدخل الفعّالة

العلاقة السابقة تربط قيمة جهد الدخل الفعّالة وقيمة جهد الحمل المتوسطة

قيمة جهد الحمل الفعّالة

$$U_{L_{rms}} = \sqrt{\frac{2}{2\pi} \int_0^{\pi} U_{2m}^2 \sin^2(\theta) d\theta}$$

$$U_{L_{rms}} = \sqrt{\frac{2U_{2m}^2}{4\pi} \int_0^{\pi} [1 - \cos 2\theta] d\theta}$$

$$U_{L_{rms}} = \sqrt{\frac{2U_{2m}^2}{4\pi} \left[\theta - \frac{1}{2} \sin 2\theta \right]_0^{\pi}}$$


$$U_{L_{rms}} = \sqrt{\frac{2U_{2m}^2}{4\pi} \left[\pi - \frac{1}{2} \sin 2\pi - 0 + \frac{1}{2} \sin 0 \right]} = \frac{\sqrt{2}U_{2m}}{2} = U_{2rms} = 220v$$

قيمة جهد الدخل الفعّالة

$$i_L = \left| \frac{U_{2m}}{R} \sin(\theta) \right| = \left| \frac{\sqrt{2}U_{2rms}}{R} \sin(\theta) \right| = |I_{2m} \sin(\theta)|$$

$$I_{2m} = \frac{U_{2m}=311v}{R=50ohm} = 6.22A$$

تيار الحمل

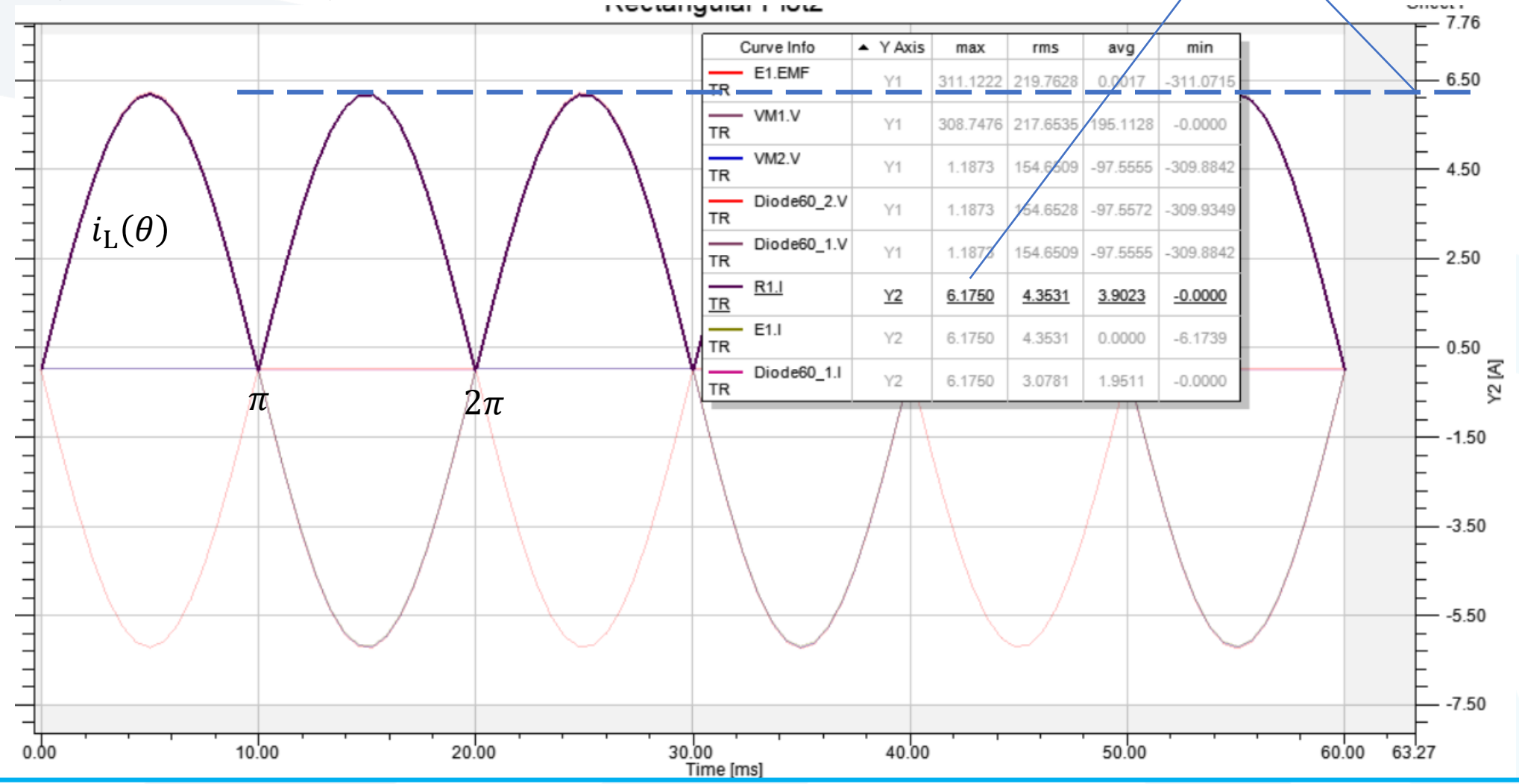

يكون التيار عبر الحمل i_L مكون من مركبة مستمرة DC بالإضافة الى تموج AC.

$$I_{L_{av}} = \frac{2}{2\pi} \left[\int_0^{\pi} \frac{U_{2m}}{R} \sin(\theta) d\theta \right]$$

$$I_{L_{av}} = \frac{2\sqrt{2}}{\pi R} U_{2rms} = 0.9 \frac{U_{2rms}}{R} = 0.9 \frac{220}{50} = 3.96A$$

قيمة تيار الحمل المقوم المتوسطة

قيمة جهد الدخل الفعّالة

قيمة تيار الحمل الفعّالة

$$I_{L_{rms}} = \sqrt{\frac{2}{2\pi} \int_0^{\pi} \frac{U_{2m}^2}{R^2} \sin^2(\theta) d\theta}$$

قيمة جهد الدخل الفعّالة

قيمة جهد الحمل الفعّالة

$$I_{L_{rms}} = \frac{\sqrt{2}U_{2m}}{2R} = \frac{U_{2rms}}{R} = \frac{U_{L_{rms}}}{R} = \frac{220v}{50\Omega} = 4.4A$$

Form factor

Form factor is defined as the ratio of RMS value to the DC value

F.F = RMS value / DC value

$$\frac{I_{L_{rms}}}{I_{L_{av}}} = \frac{\frac{U_{2rms}}{R}}{\frac{2\sqrt{2}}{\pi R} U_{2rms}} = \frac{\pi}{2\sqrt{2}} = 1.11$$


بنسب قيمتي التيار الفعّالة والمتوسطة إلى بعضها تنتج العلاقة التالية:


Ripples factor

- Ripples factor = rms value of AC component of the output voltage / DC component of the output voltage
- The ripple factor is also simply defined as the ratio of ripple voltage to the DC voltage
- Ripple factor = Ratio of ripple voltage / DC voltage.
- The ripple factor should be kept as minimum as possible to construct a good rectifier.
- The ripple factor is given as:

$$\gamma = \sqrt{\left(\frac{U_{L_{rms}}}{U_{L_{av}}}\right)^2 - 1} = \sqrt{\left(\frac{U_{2rms}}{\frac{2\sqrt{2}}{\pi} U_{2rms}}\right)^2 - 1} = \sqrt{\left(\frac{\pi}{2\sqrt{2}}\right)^2 - 1} = 0.48$$

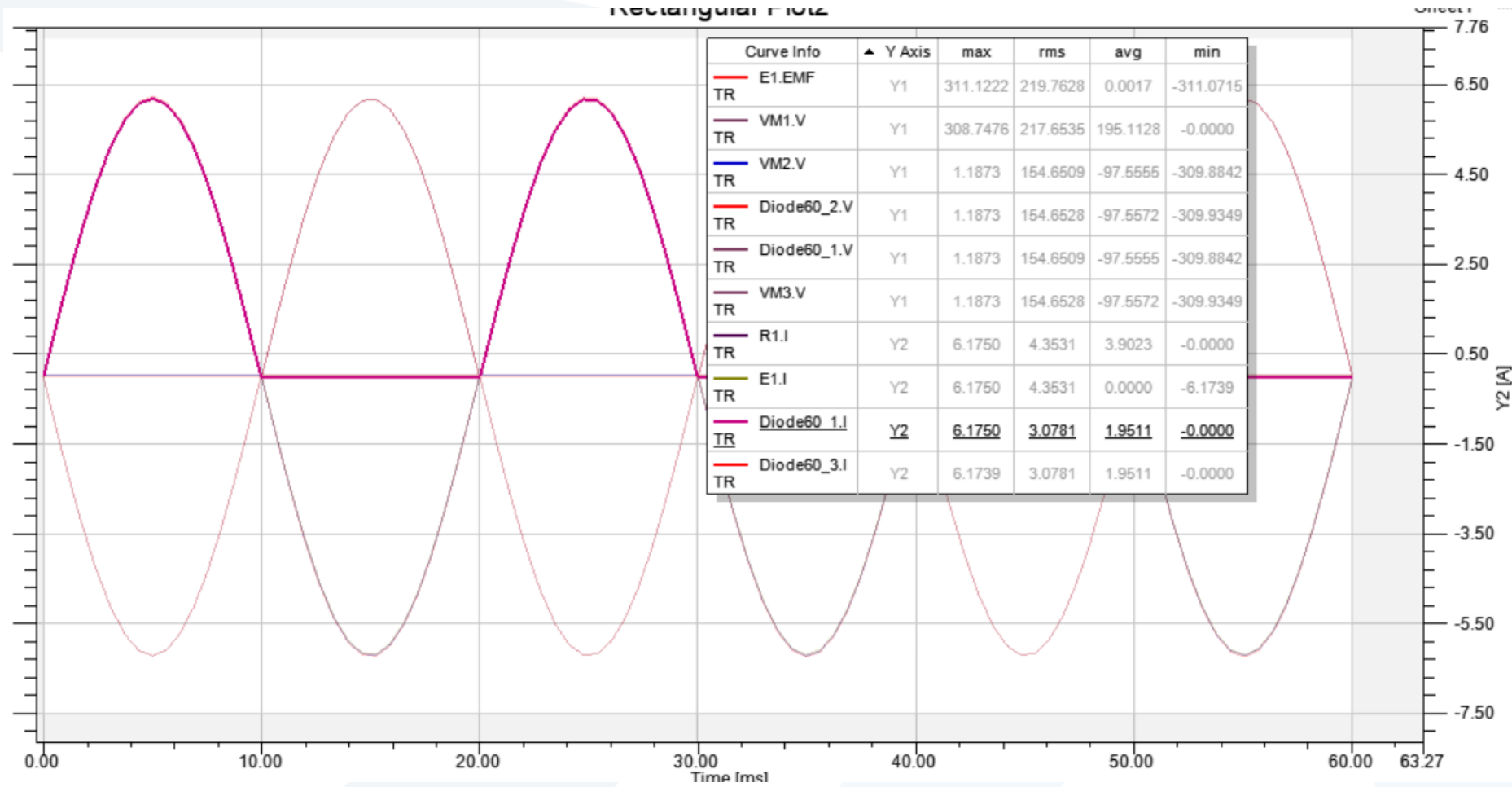- The unwanted ripple present in the output along with the DC voltage is 48% of the DC magnitude.



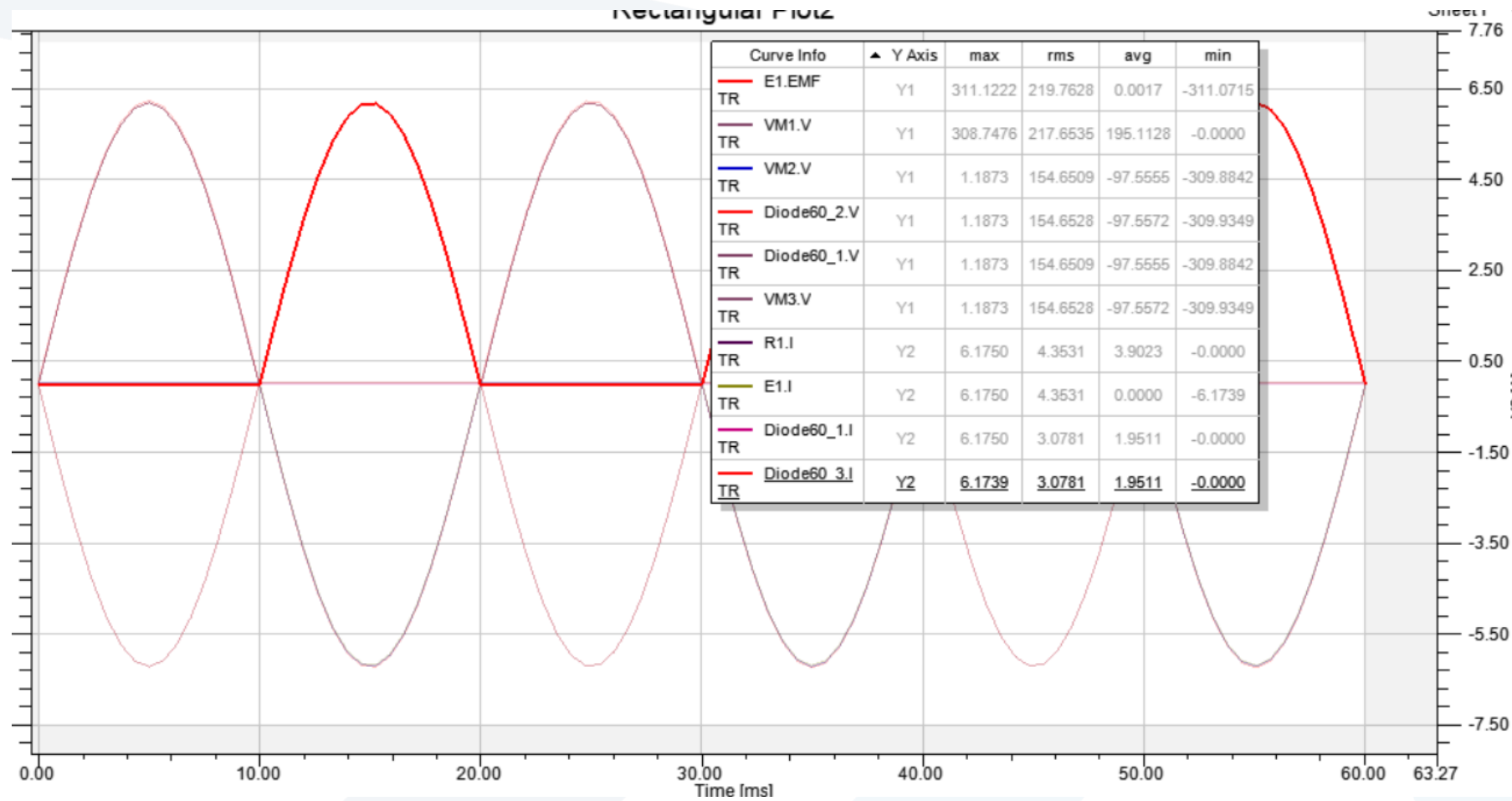

$$I_{D_{av}} = \frac{1}{2\pi} \left[\int_0^{\pi} \frac{U_{2m}}{R} \sin(\theta) d\theta \right]$$

قيمة تيار الحمل
المقوم
المتوسطة

$$I_{D_{av}} = \frac{\sqrt{2}}{\pi R} U_{2rms} = 0.45 \frac{U_{2rms}}{R} = \frac{I_{L_{av}}}{2} = 1.98A$$

قيمة تيار الديود المتوسطة

قيمة جهد الدخل الفعّالة

قيمة تيار الديود الفعّالة

$$I_{D_{rms}} = \sqrt{\frac{1}{2\pi} \int_0^{\pi} \frac{U_{2m}^2}{R^2} \sin^2(\theta) d\theta}$$

قيمة جهد الدخل الفعّالة


قيمة جهد الحمل الفعّالة

$$I_{D_{rms}} = \frac{U_{2m}}{2R} = \frac{U_{2rms}}{\sqrt{2}R} = \frac{U_{L_{rms}}}{\sqrt{2}R} = 3.11A$$



جامعة
المنارة
MANARA UNIVERSITY

تيار المنبع

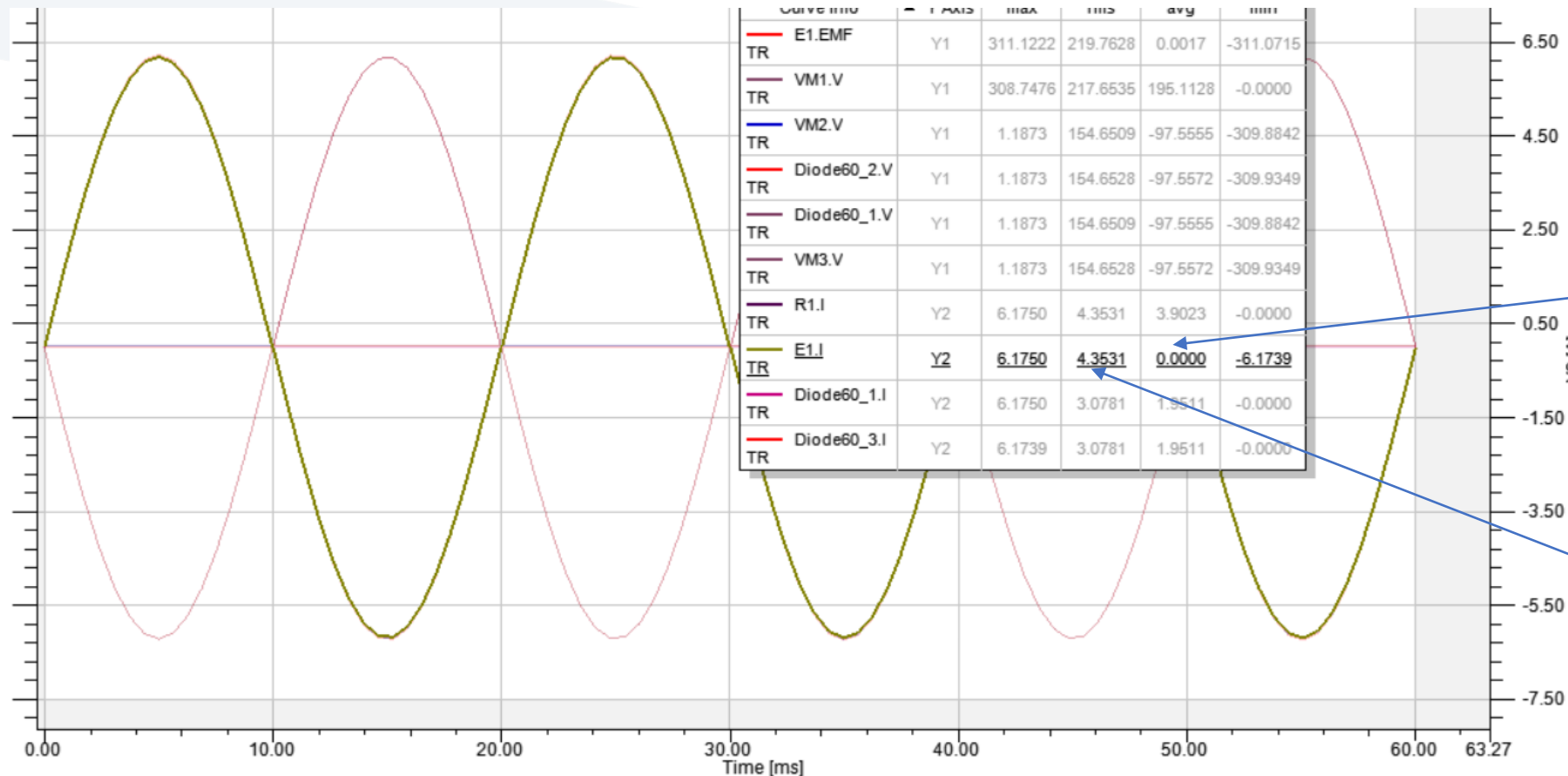

تيار المنبع قيمة
متوسطة

$$I_{S_{av}} = 0V$$

تيار المنبع قيمة فعالة
كونها موجة جيبيه صافية

$$I_{S_{rms}} = \frac{I_{S_m}}{\sqrt{2}} = \frac{\frac{U_{2m}}{R}}{\sqrt{2}} = \frac{U_{2rms}}{R} = \frac{\frac{311}{\sqrt{2}}}{\sqrt{2}} = 4.39A$$

Rectifier efficiency

- Rectifier efficiency is defined as the ratio of output DC power to the input AC power.
- The rectifier efficiency of a full wave rectifier is 81.5%.


$$P_{out} (DC) = I_{L_{av}}^2 R = 3.96^2 * 50 [W] = 784$$

$$P_{in} (AC) = I_{S_{rms}}^2 R = 4.4^2 * 50 [W] = 968 [W]$$

$$P_{in} (AC) = I_{S_{rms}} U_{S_{rms}} = 4.4 * 220 [W] = 968 [W]$$

$$\eta = \frac{P_{out} (DC)}{P_{in} (AC)} \approx 81\%$$

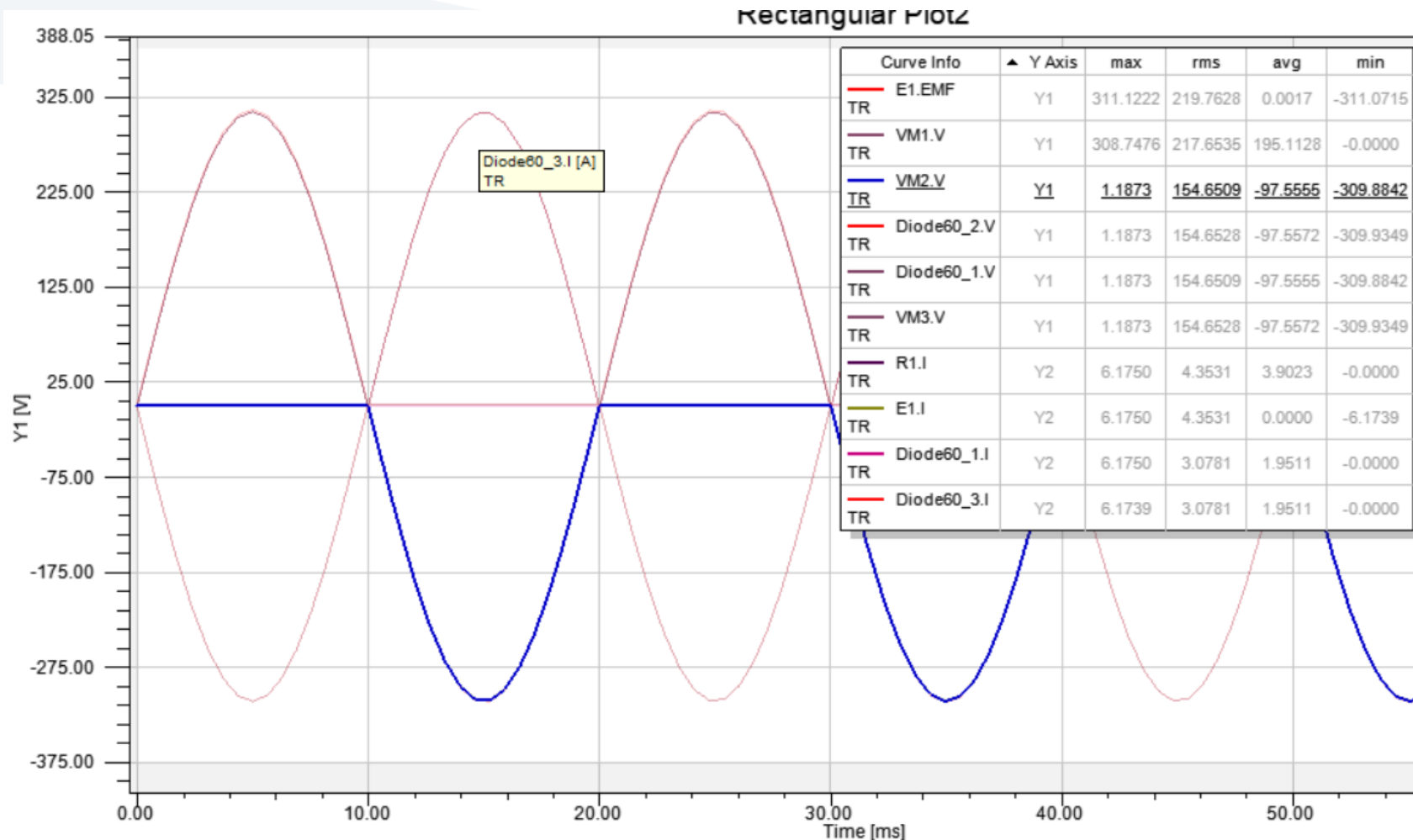
Peak inverse voltage (PIV) جهد الديود الأول



$VD1 = e1$
في نصف الموجة الثاني
الديود الأول انحياز عكسي
بينما الديود الثاني انحياز
أمامي

$VD1 = 0$
في نصف الموجة الأول
الديود الأول انحياز أمامي

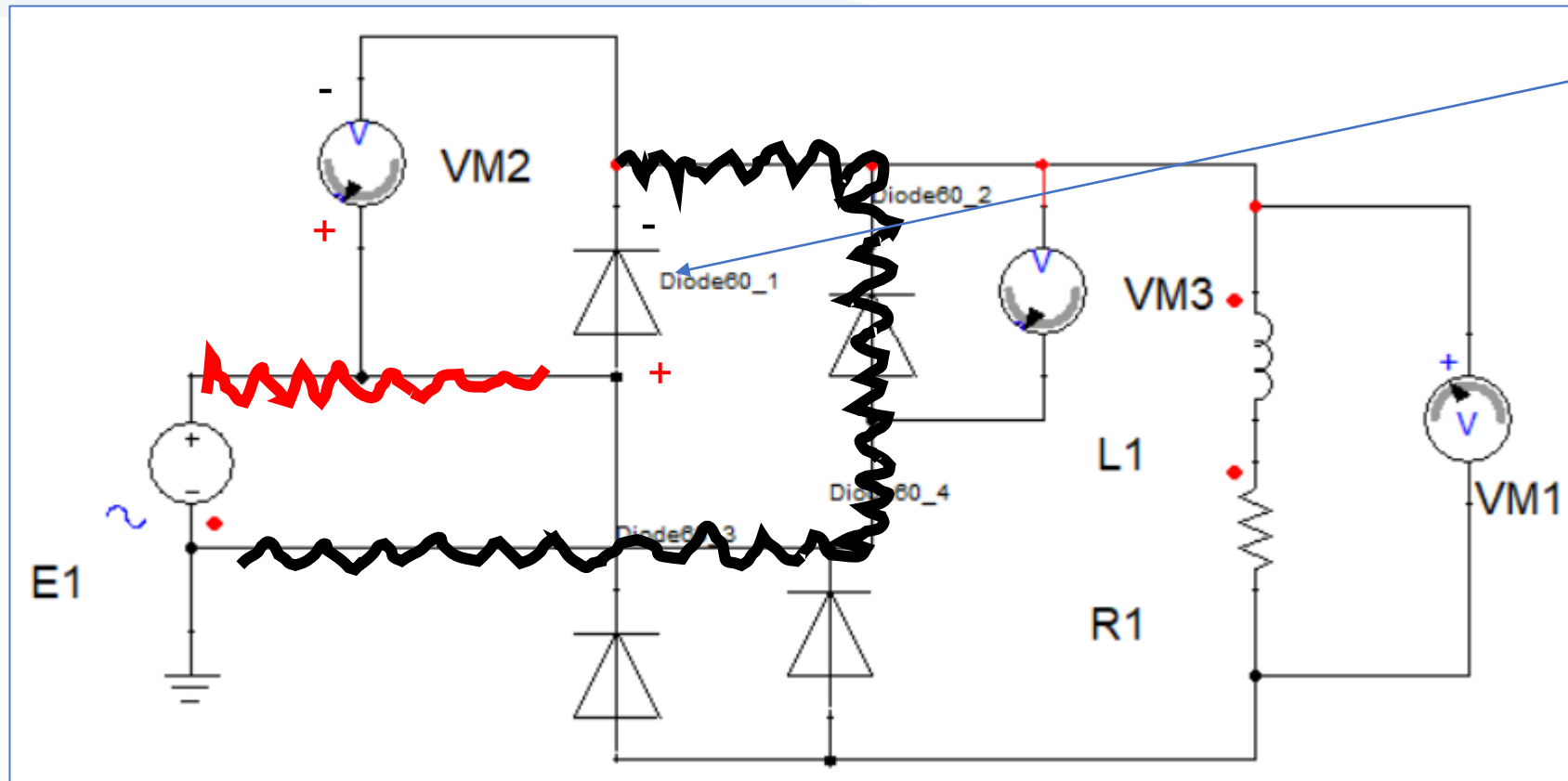Peak inverse voltage (PIV) جهد الديود الأول




$$VD1 = e1$$

في نصف الموجة الثاني
الديود الأول انحياز عكسي
بينما الديود الثاني انحياز
أمامي

$$VD1 = 0$$

في نصف الموجة الأول
الديود الأول انحياز أمامي

$$V_{DRMAX} = -U_{2m}$$

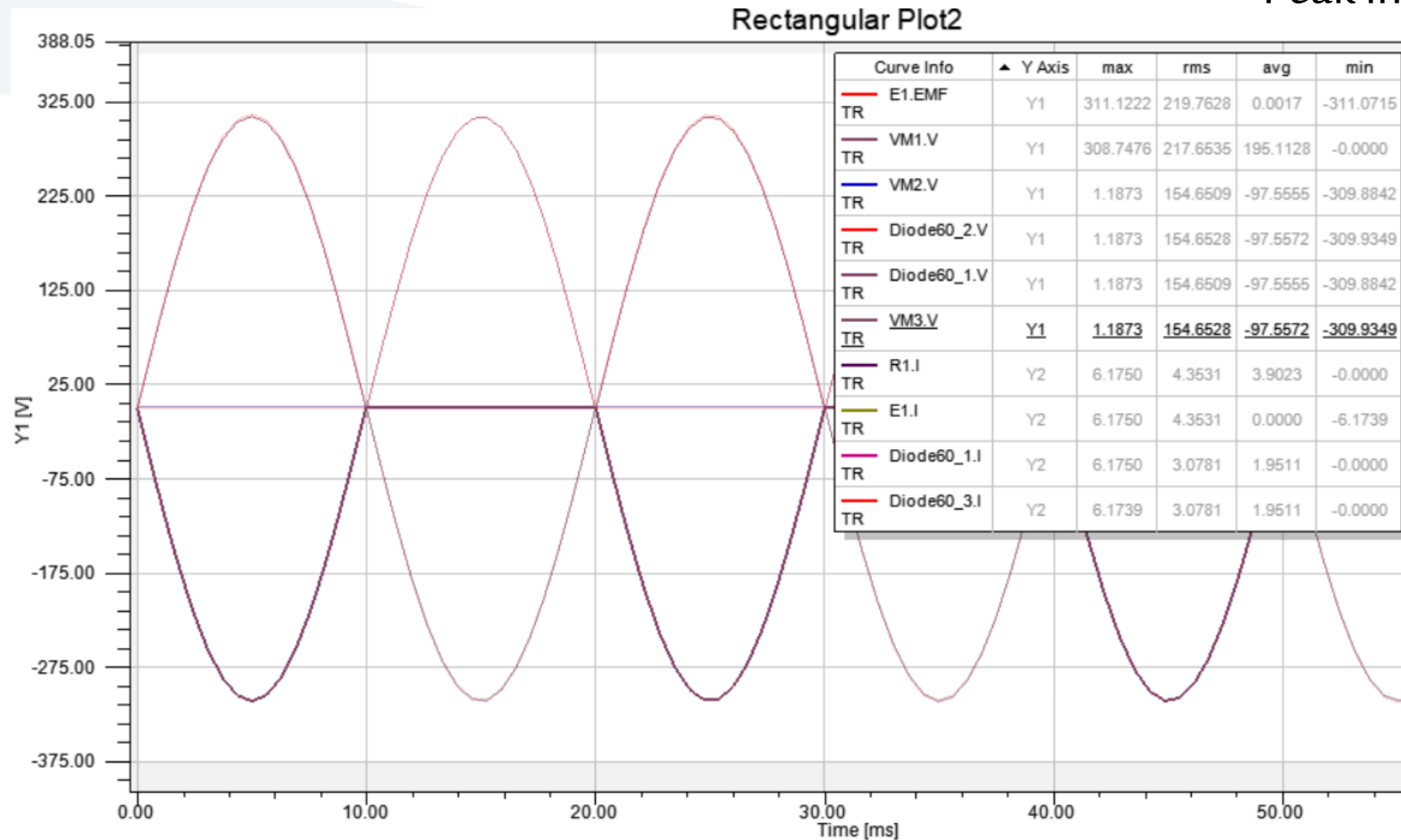

$$VD2 = -e1$$

في نصف الموجة الأول
الديود الثاني انحياز عكسي
والديود الأول انحياز أمامي

$$VD2 = 0$$


في نصف الموجة الثاني
الديود الثاني انحياز أمامي

جهد الديود الثاني

Peak inverse voltage (PIV)

$$VD2 = -e1$$

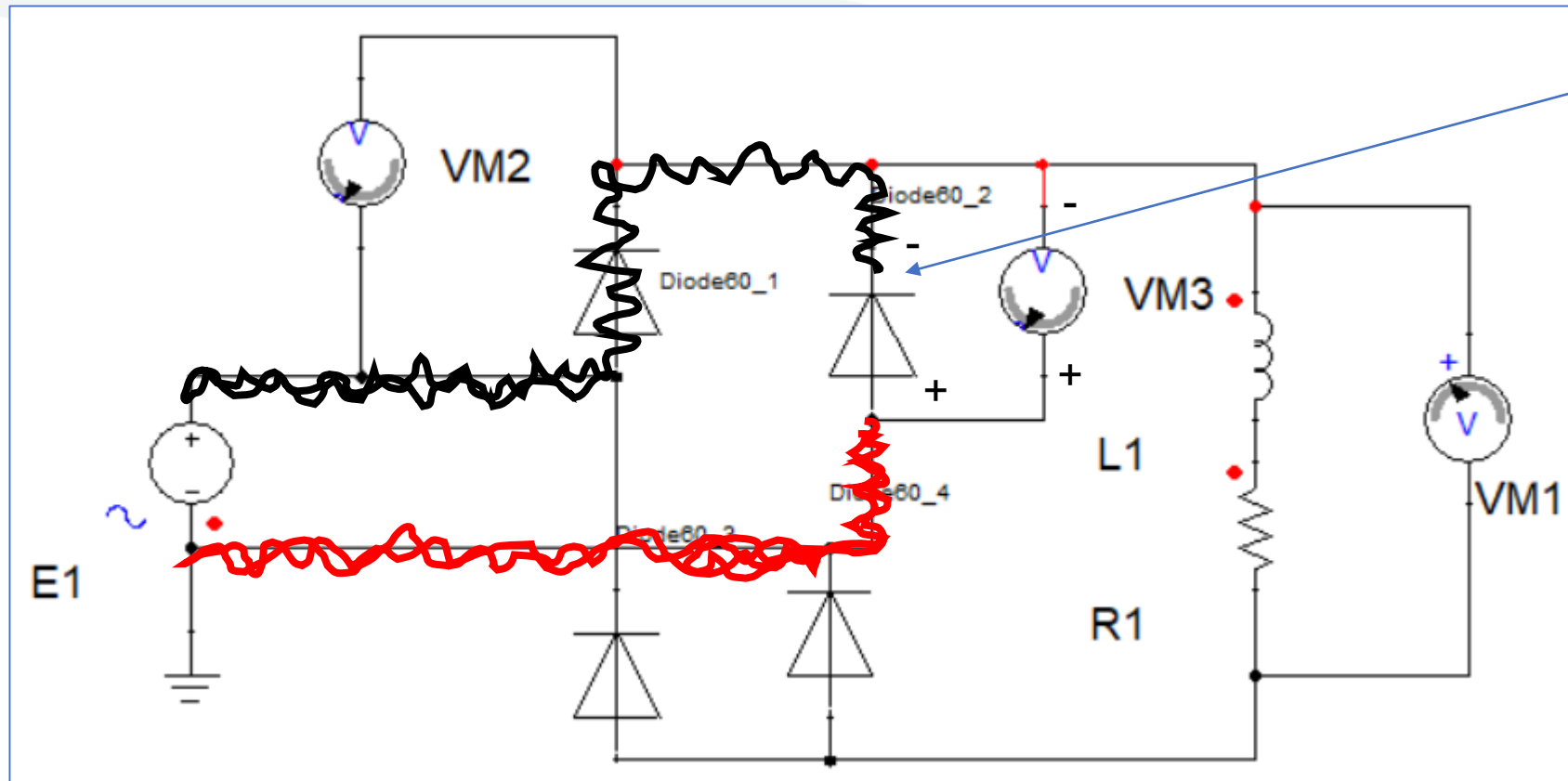في نصف الموجة الأول
الديود الثاني انحياز عكسي
والديود الأول انحياز أمامي



$$VD2 = 0$$

في نصف الموجة الثاني
الديود الثاني انحياز أمامي

$$V_{DRMAX} = -U_{2m}$$



المنبع الأول

جهد الحمل

جهد الديود الأول

جهد الديود الثاني

جهد الديود الأول

جهد الديود الثاني

تيار الحمل


تيار المنبع

تيار الديود الأول

تيار الديود الثالث

Curve Info	▲ Y Axis	max	rms	avg	min
E1.EMF TR	Y1	311.1222	219.7628	0.0017	-311.0715
VM1.V TR	Y1	308.7476	217.6535	195.1128	-0.0000
VM2.V TR	Y1	1.1873	154.6509	-97.5555	-309.8842
Diode60_2.V TR	Y1	1.1873	154.6528	-97.5572	-309.9349
Diode60_1.V TR	Y1	1.1873	154.6509	-97.5555	-309.8842
VM3.V TR	Y1	1.1873	154.6528	-97.5572	-309.9349
R1.I TR	Y2	6.1750	4.3531	3.9023	-0.0000
E1.I TR	Y2	6.1750	4.3531	0.0000	-6.1739
Diode60_1.I TR	Y2	6.1750	3.0781	1.9511	-0.0000
Diode60_3.I TR	Y2	6.1739	3.0781	1.9511	-0.0000

حمولة مختلطة أومية مع تحريضية

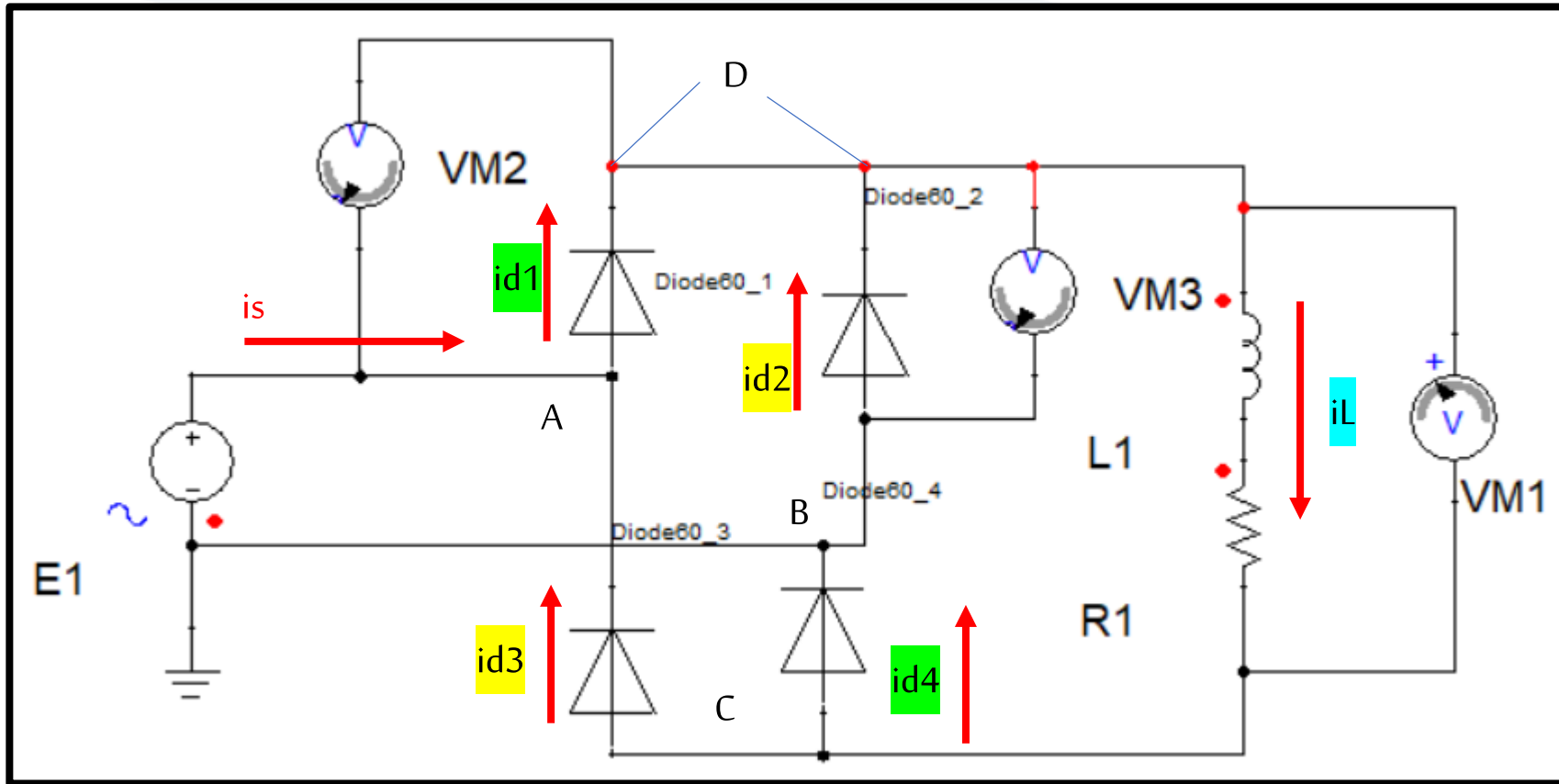

Parameters - L1 - Inductor ×

Parameters | Output / Display

Name Show Name

Parameters

Inductance Use Pin
Value, Variable, Expression

Nonlinear
 $i = f(\psi)$ Use Pin


Nonlinear
 $L = f(i), dL/dt = 0$ Use Pin

Initial Value


Initial Value


Outputs

Voltage Current Inductance

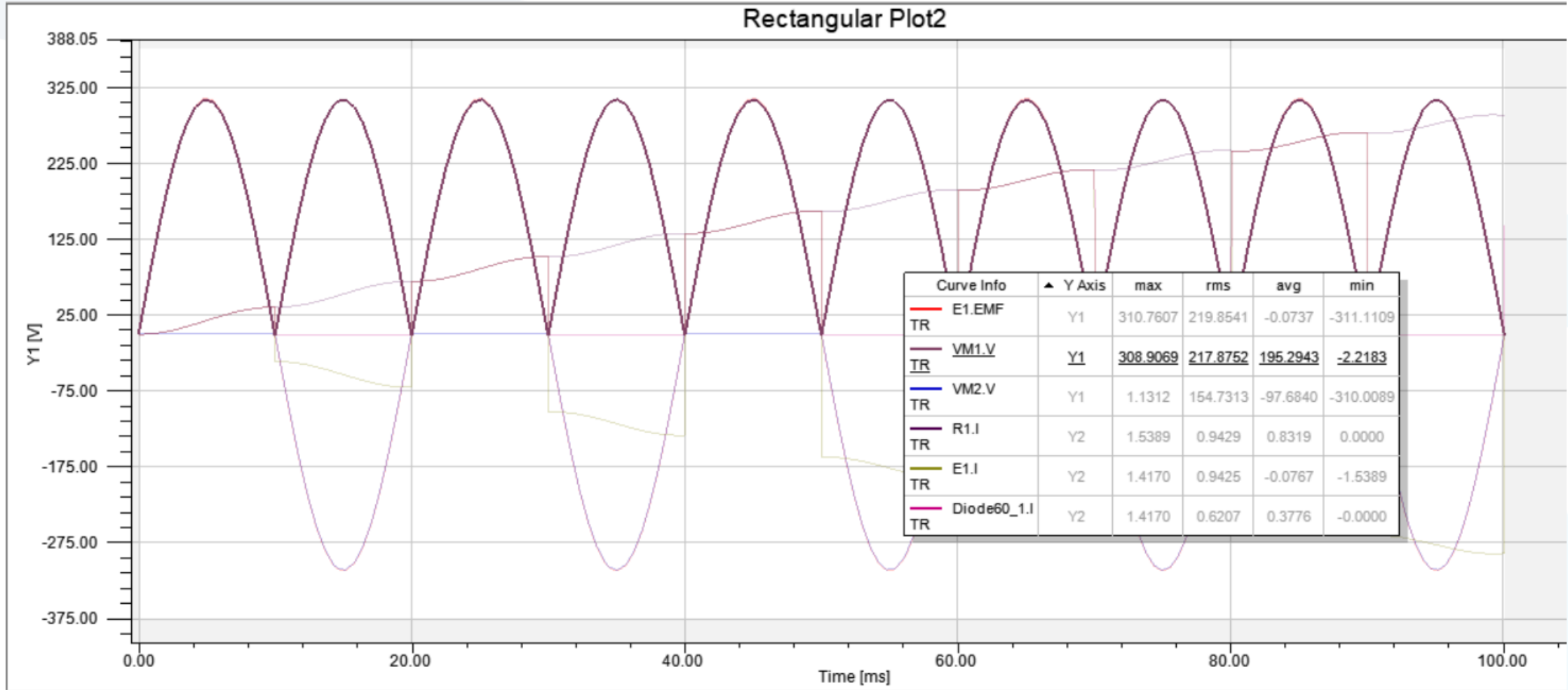

Rectangular Plot2

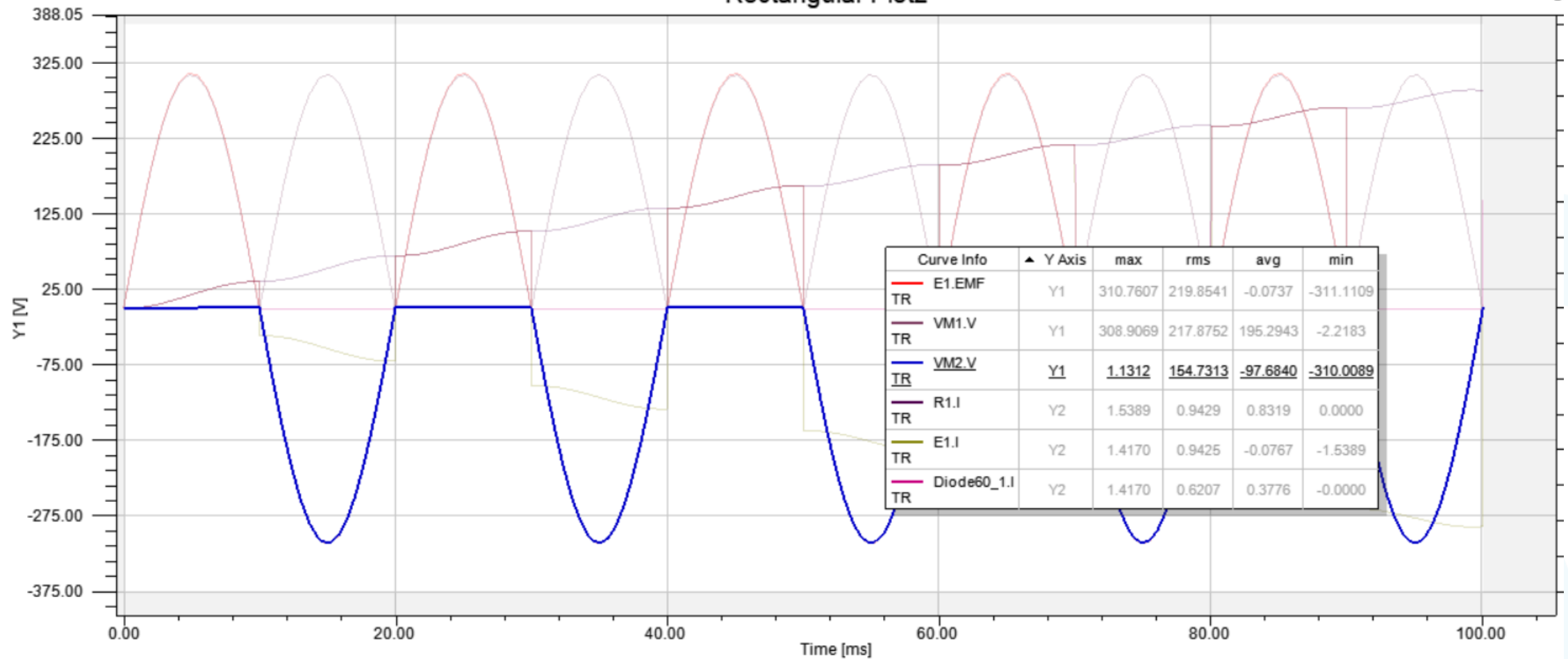

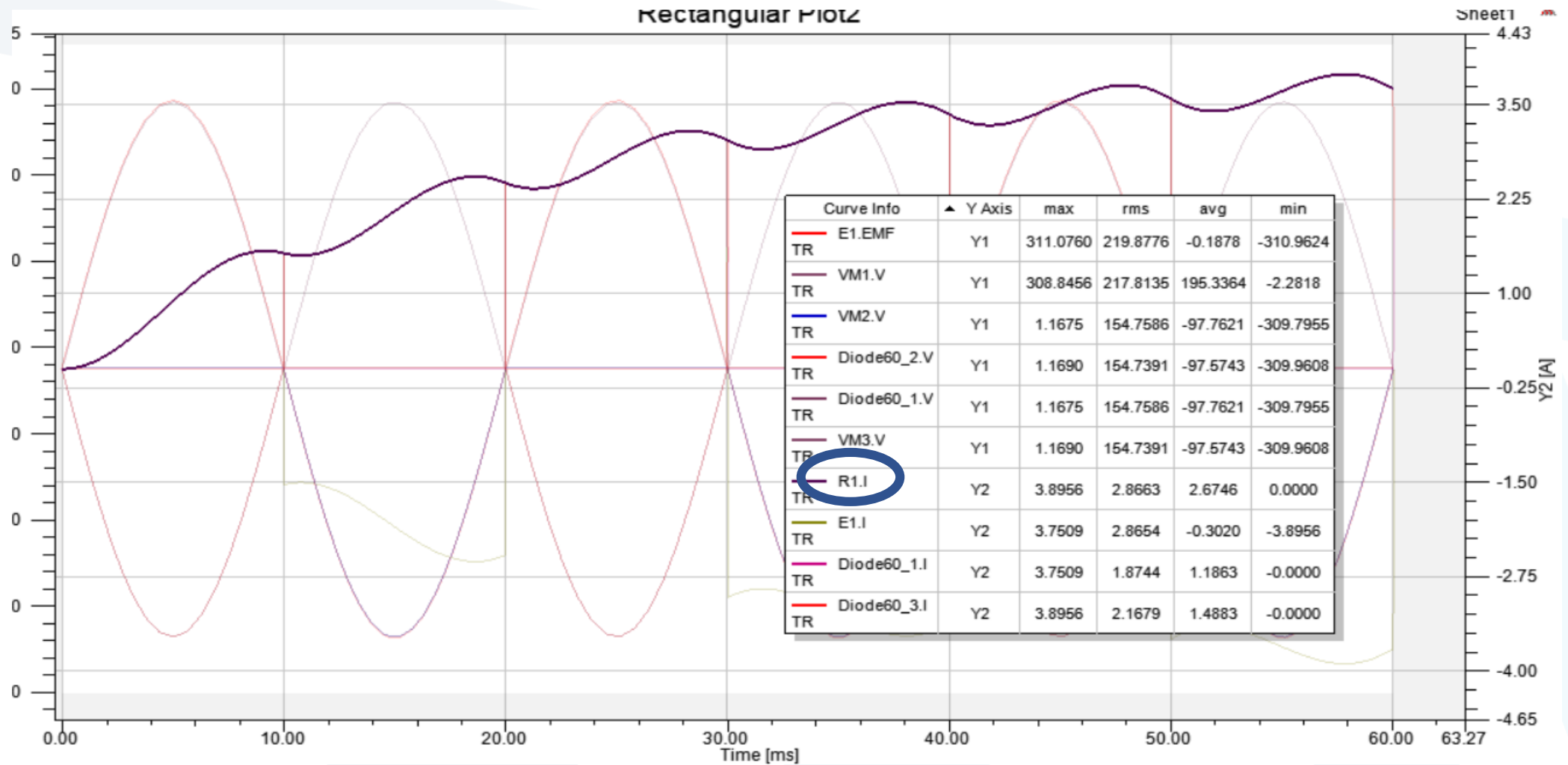





جامعة
المنارة
MANARA UNIVERSITY


Rectangular Plot

Sheet 1

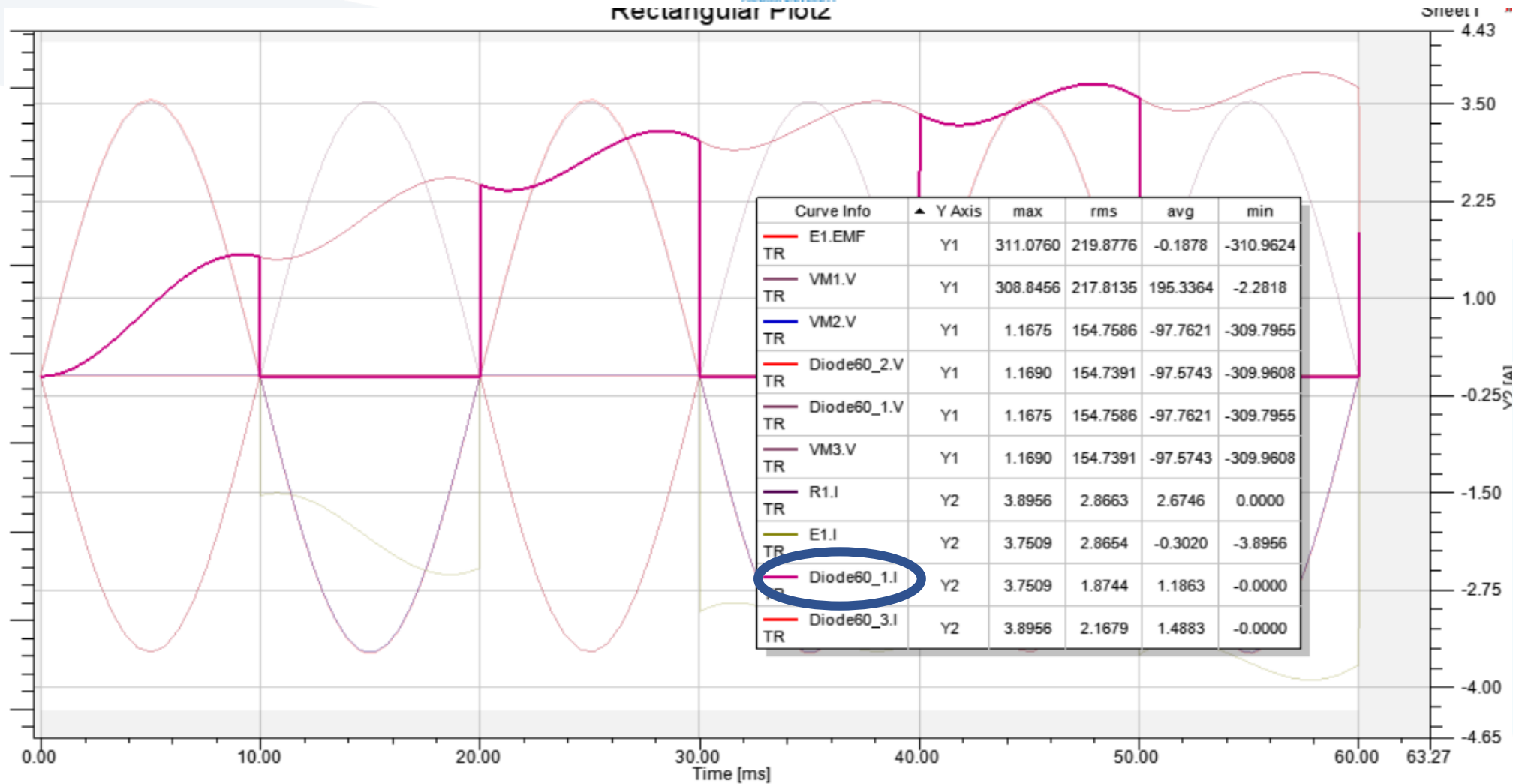



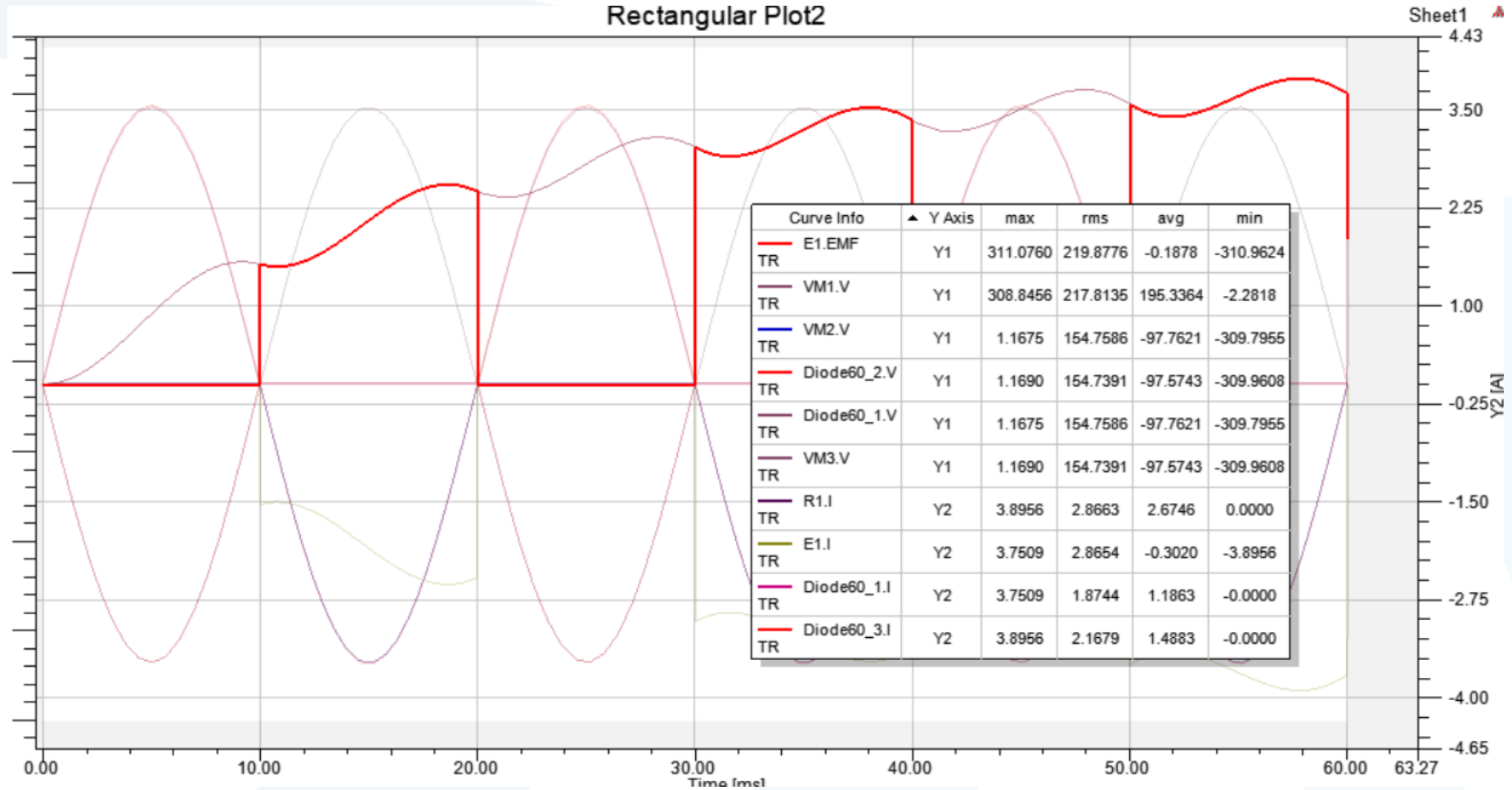

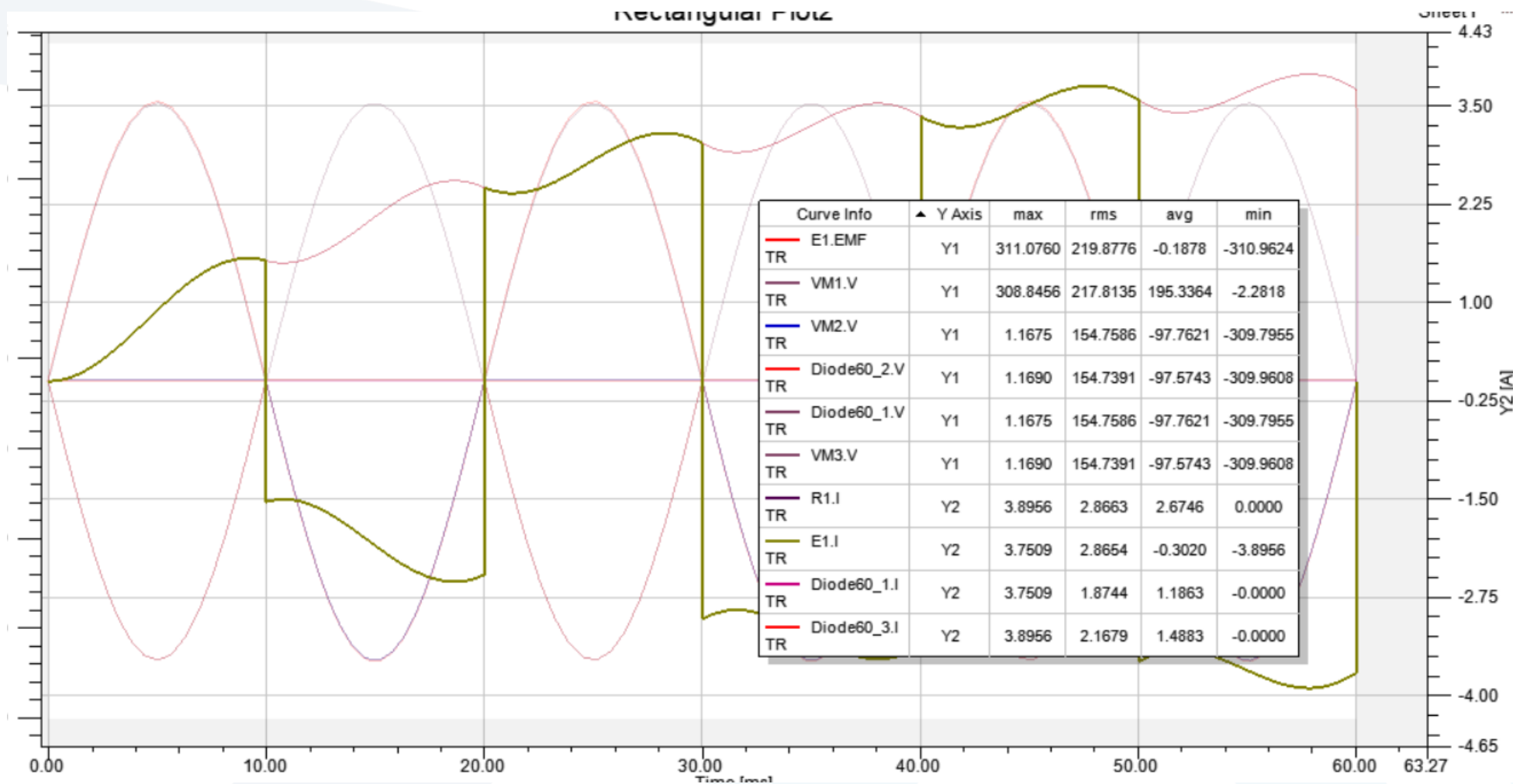






تيار الديود
الأول والرابع







Curve Info	▲ Y Axis	max	rms	avg	min
 E1.EMF TR	Y1	311.0760	219.8776	-0.1878	-310.9624
 VM1.V TR	Y1	308.8456	217.8135	195.3364	-2.2818
 VM2.V TR	Y1	1.1675	154.7586	-97.7621	-309.7955
 Diode60_2.V TR	Y1	1.1690	154.7391	-97.5743	-309.9608
 Diode60_1.V TR	Y1	1.1675	154.7586	-97.7621	-309.7955
 VM3.V TR	Y1	1.1690	154.7391	-97.5743	-309.9608
 R1.I TR	Y2	3.8956	2.8663	2.6746	0.0000
 E1.I TR	Y2	3.7509	2.8654	-0.3020	-3.8956
 Diode60_1.I TR	Y2	3.7509	1.8744	1.1863	-0.0000
 Diode60_3.I TR	Y2	3.8956	2.1679	1.4883	-0.0000

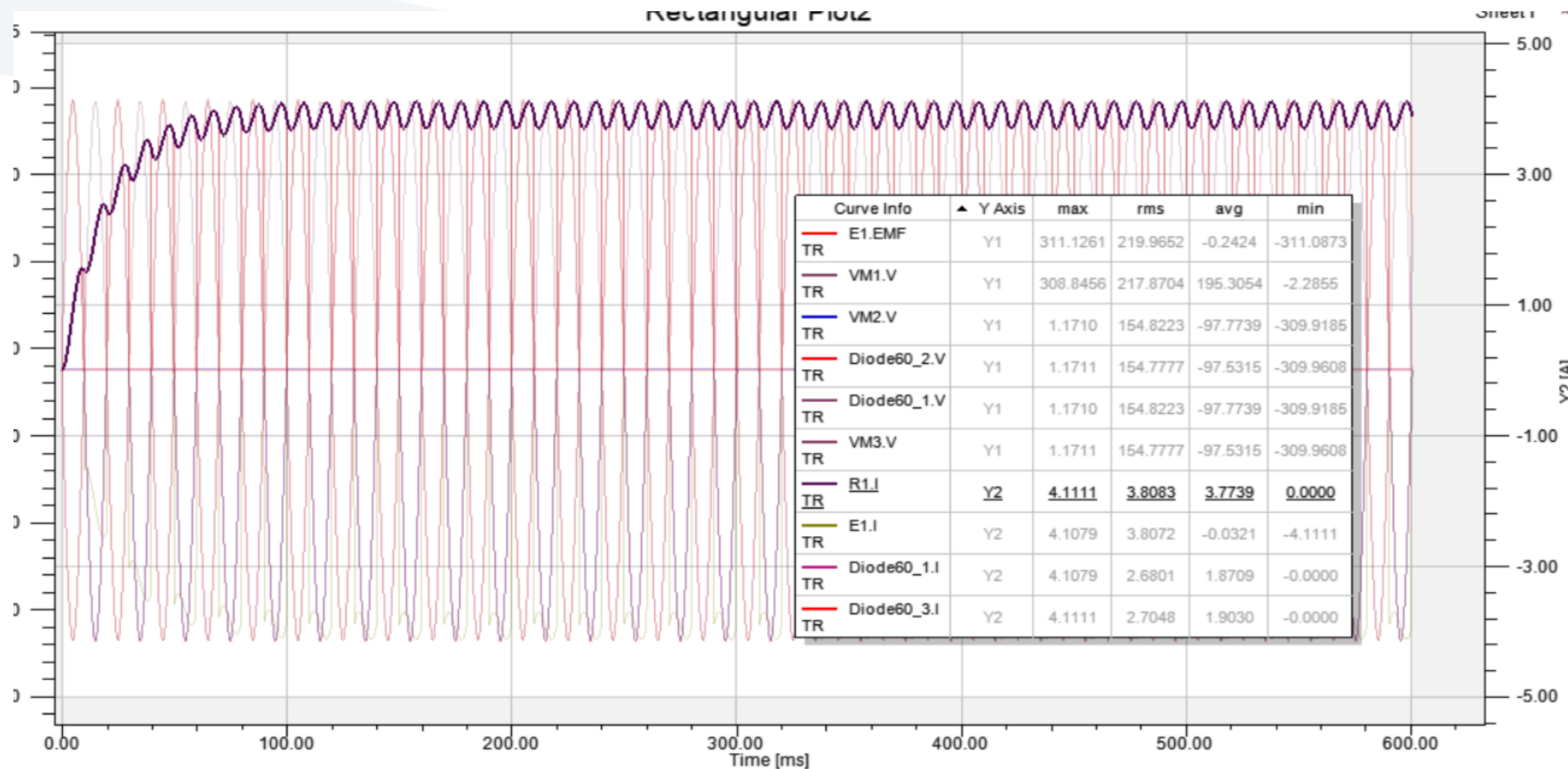

انتهت المحاضرة