

Lecture 5



BJT TRANSISTORS

DR. BASSAM ATIEH



جامعة
المنارة
MANARA UNIVERSITY

Transistor Construction



جامعة
المنصورة
MANARA UNIVERSITY

There are two types of transistors:

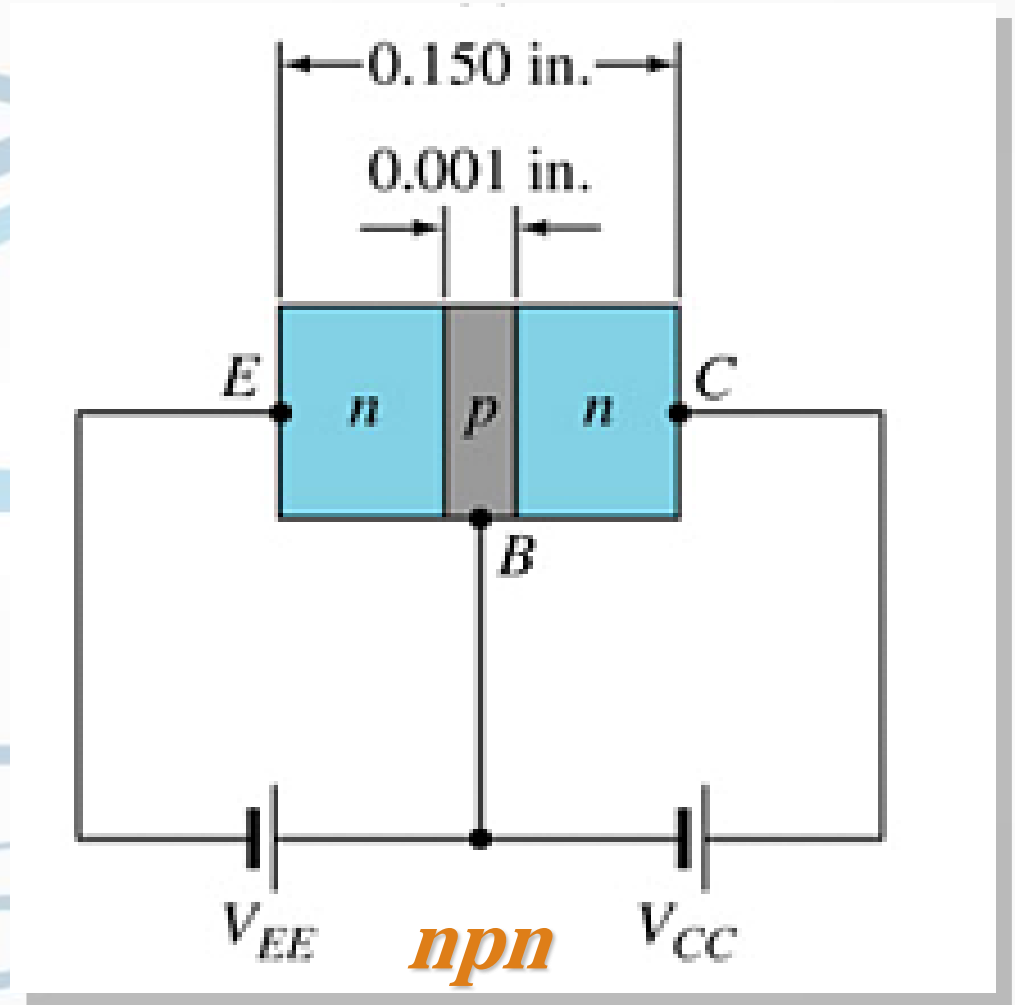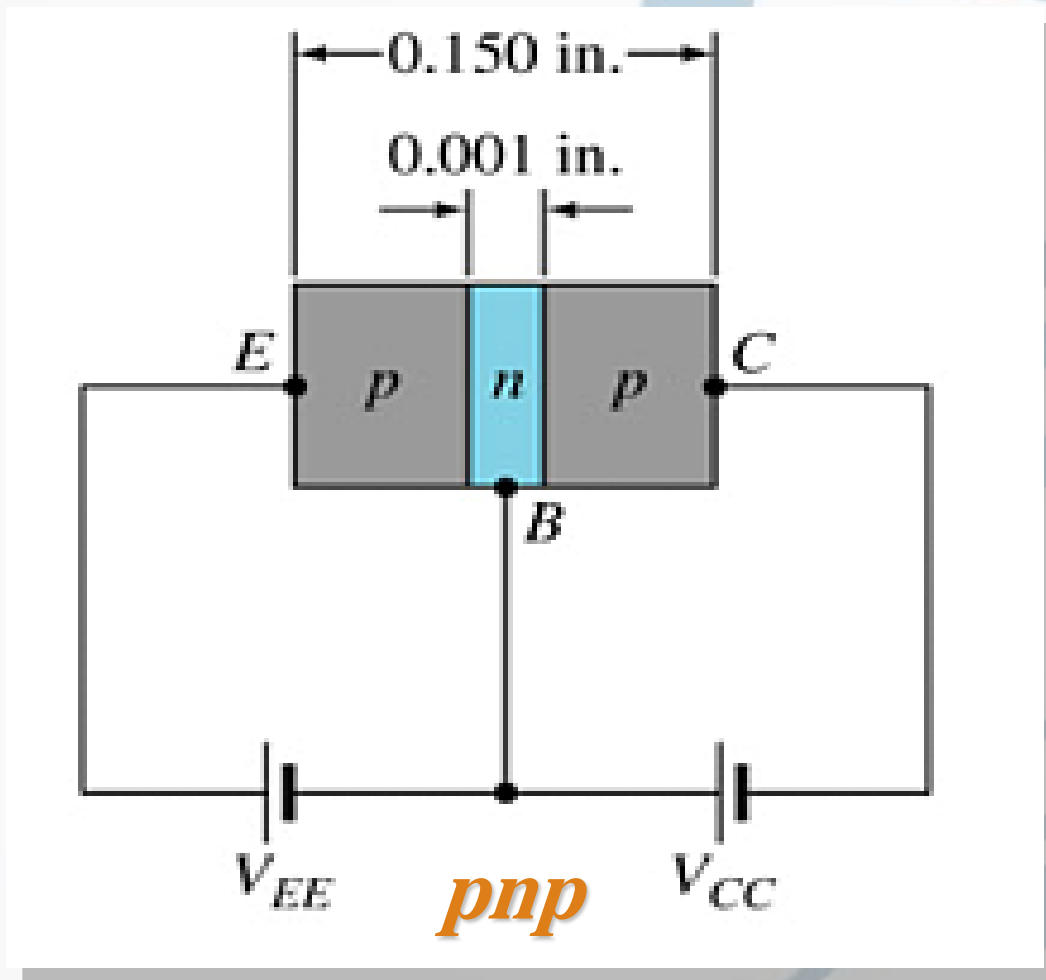


The terminals are labeled:

E – Emitter B – Base - Collector

Transistor Operation

With the external sources, V_{EE} and V_{CC} , connected as shown:

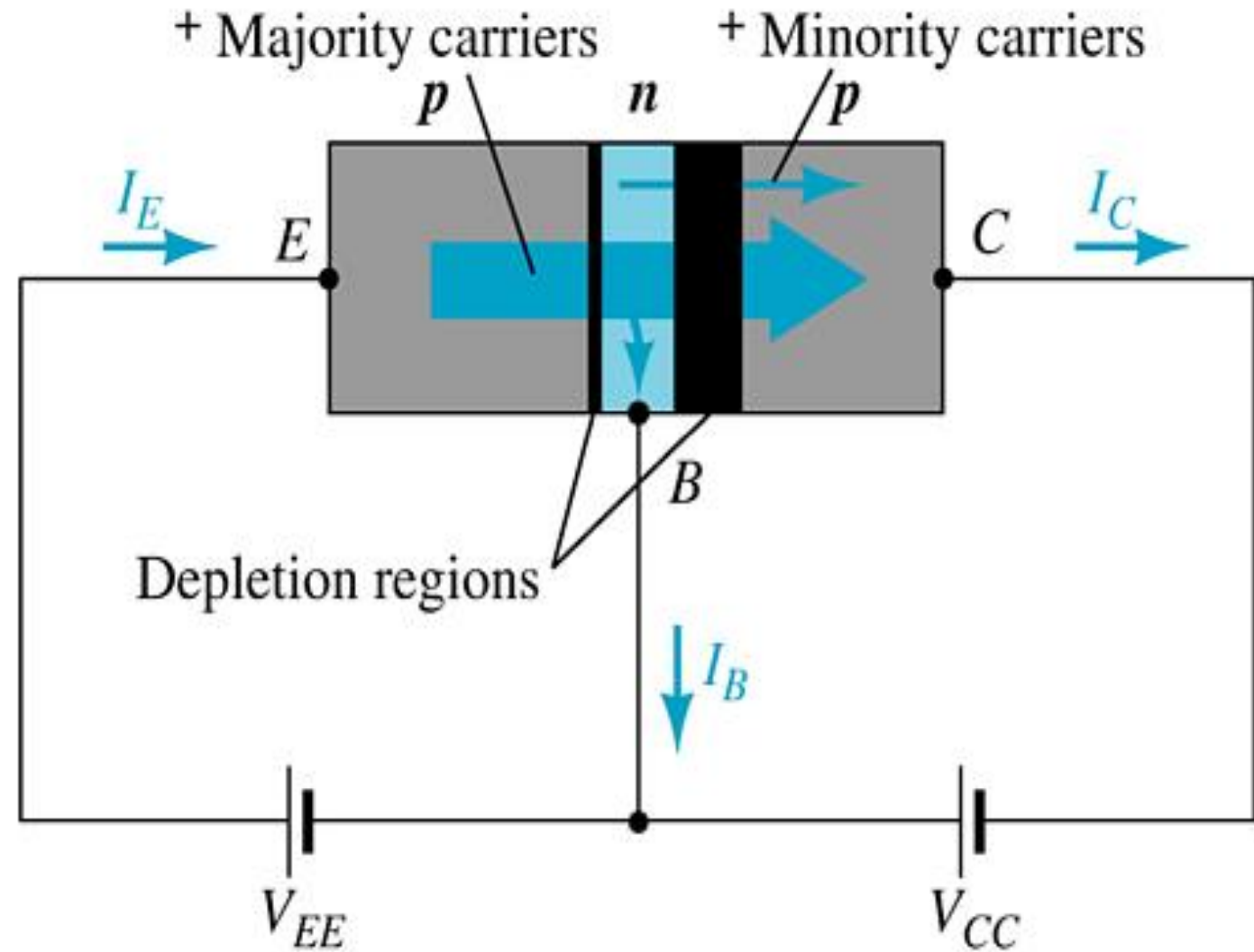- The emitter-base junction is forward biased
- The base-collector junction is reverse biased




Currents in a Transistor

Emitter current is the sum of the collector and base currents:





$$I_E = I_C + I_B$$

The collector current is comprised of two currents:
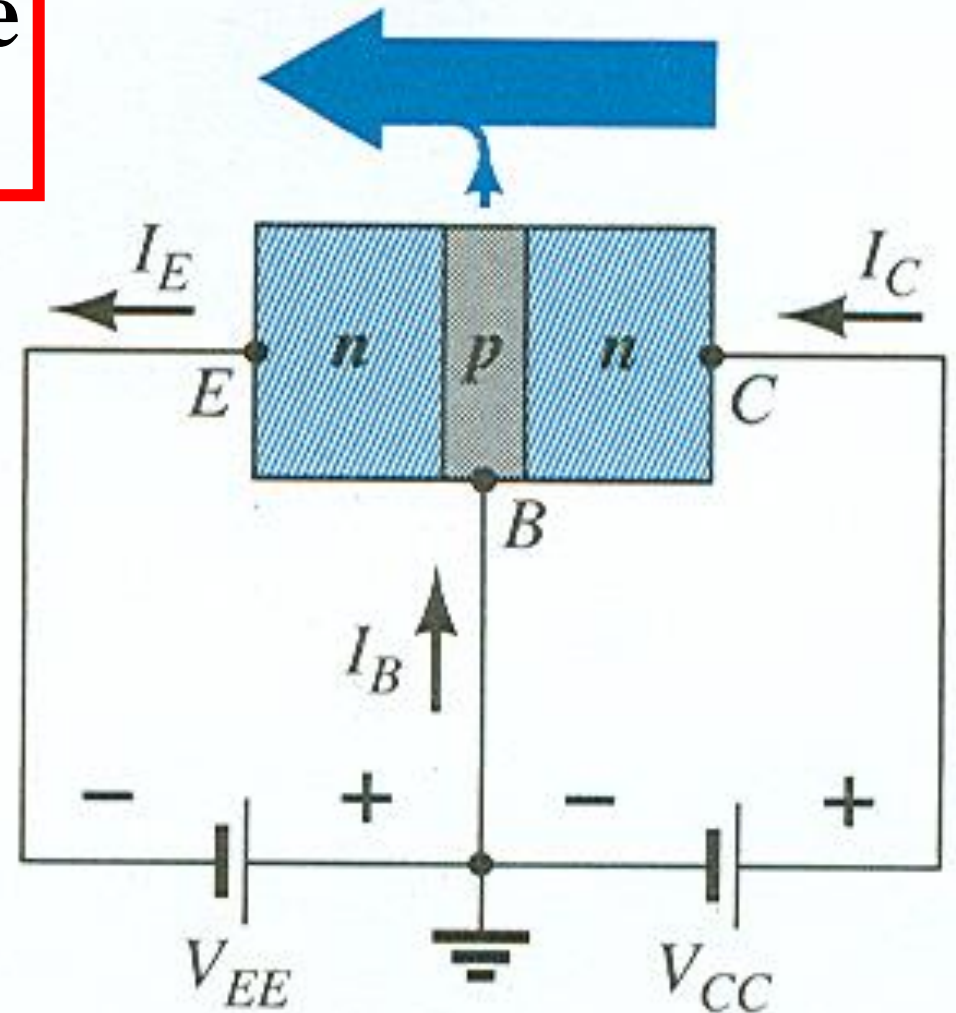
$$I_C = I_{C_{\text{majority}}} + I_{C_{\text{minority}}}$$



Common-Base Configuration

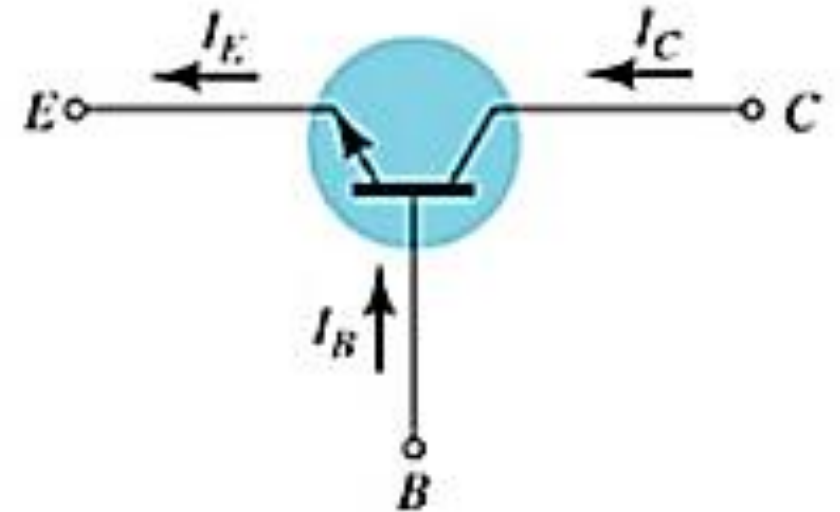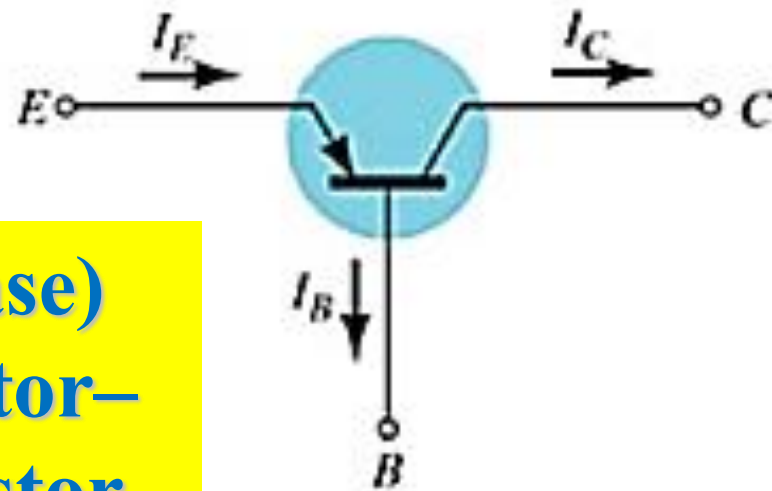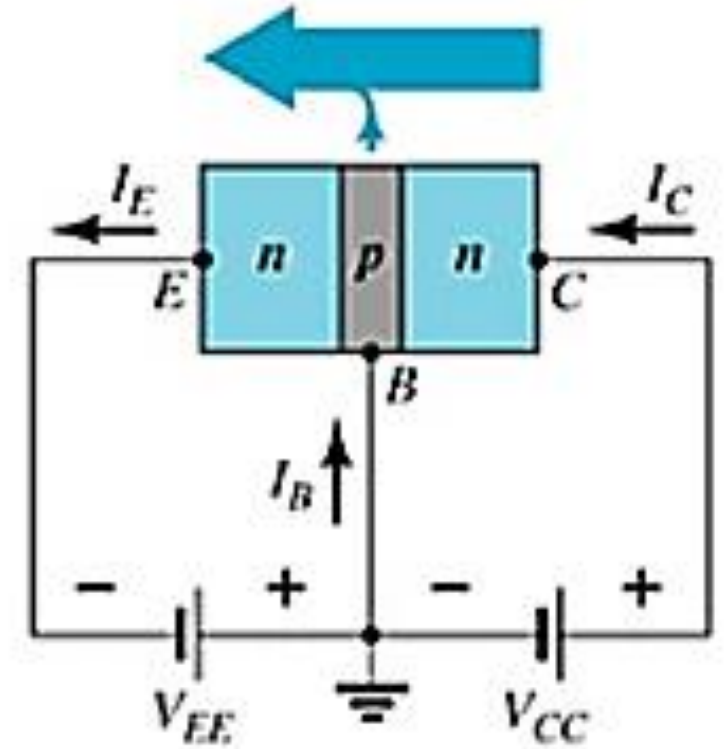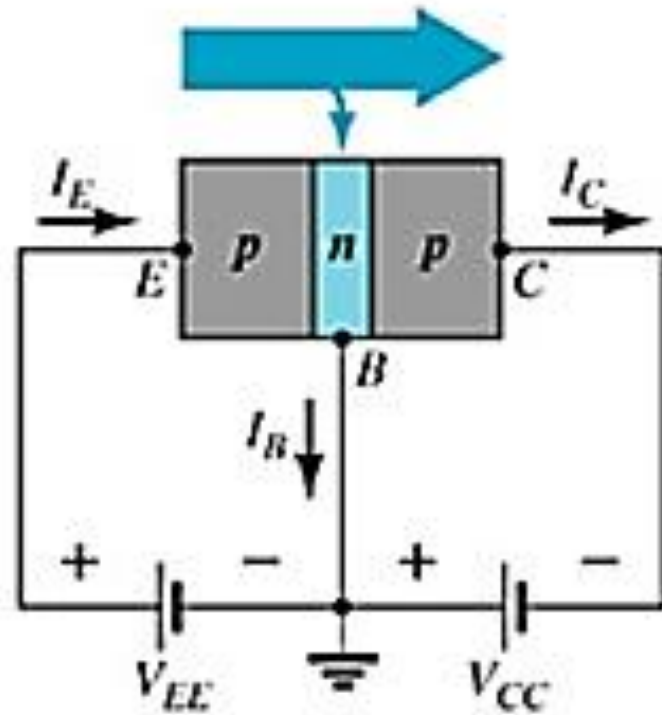


input (emitter–base)
and output (collector–
base) of the transistor.

Common-Base Amplifier



Output Characteristics

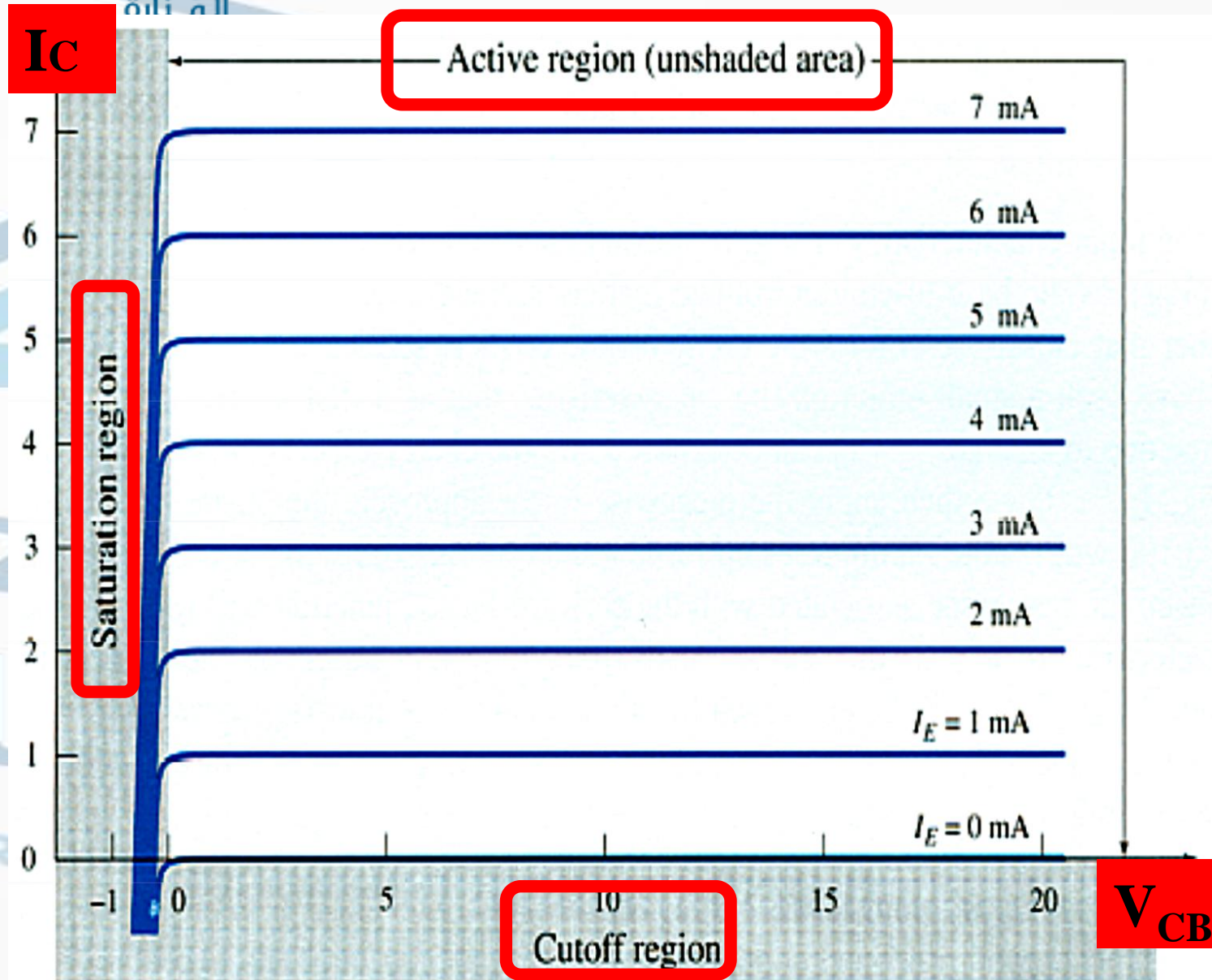This graph demonstrates the output current (I_C) to an output voltage (V_{CB}) for various levels of input current (I_E).




Common-Base Amplifier



Input Characteristics

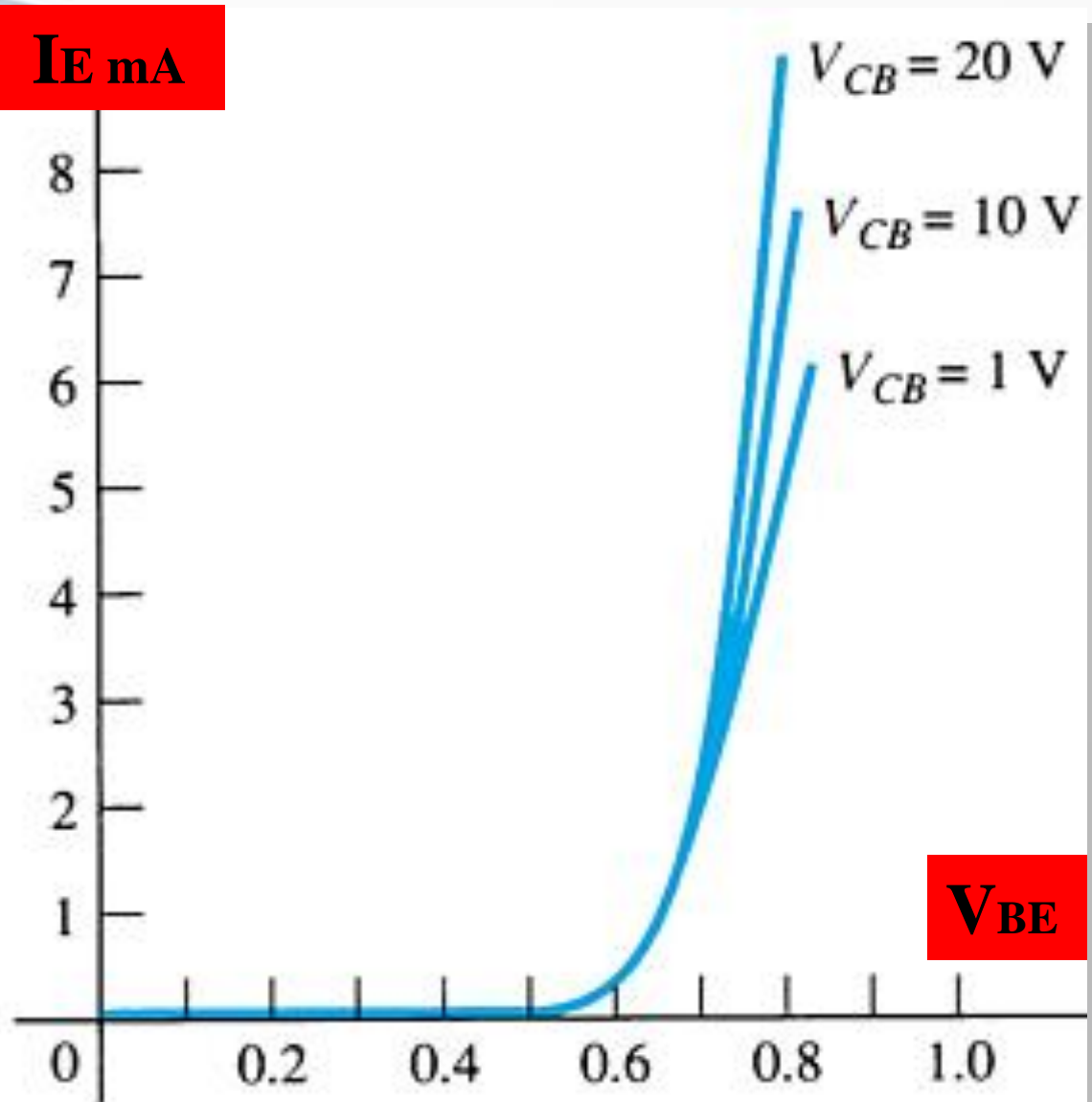This curve shows the relationship between of input current (I_E) to input voltage (V_{BE}) for three output voltage (V_{CB}) levels.



Operating Regions



- **Active** – Operating range of the amplifier.
- **Cutoff** – The amplifier is basically off. There is voltage, but little current.
- **Saturation** – The amplifier is full on. There is current, but little voltage.

Approximations

• Emitter and collector currents:

$$I_C \cong I_E$$

• Base-emitter voltage:

$$V_{BE} = 0.7 \text{ V (for Silicon)}$$

Alpha (α)

Alpha (α) is the ratio of I_C to I_E :

$$\alpha_{\text{dc}} = \frac{I_C}{I_E}$$

- Ideally: $\alpha = 1$
- In reality: α is between 0.9 and 0.998

Alpha (α) in the AC mode:

$$\alpha_{\text{ac}} = \frac{\Delta I_C}{\Delta I_E}$$

Transistor Amplification



جامعة
المنارة
MANARA UNIVERSITY


Currents and Voltages:

$$I_E = I_i = \frac{V_i}{R_i} = \frac{200\text{mV}}{20\Omega} = 10\text{mA}$$

$$I_C \approx I_E$$

$$I_L \approx I_i = 10\text{mA}$$
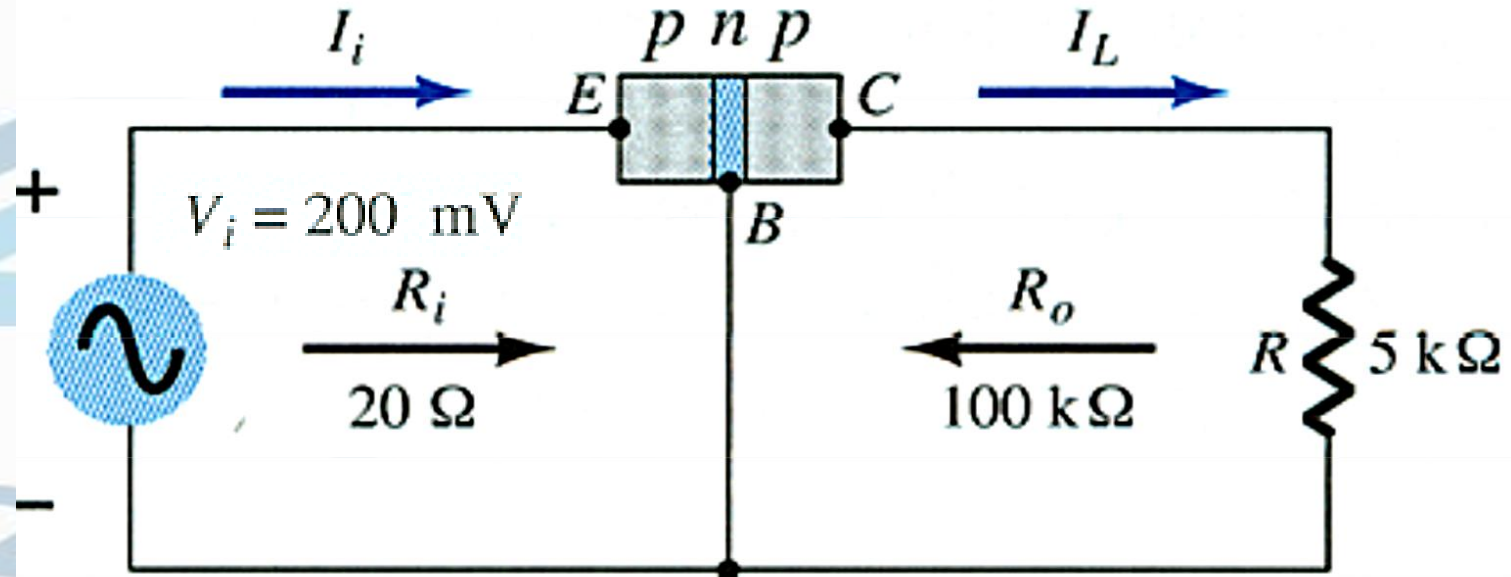
$$V_L = I_L R = (10\text{mA})(5\text{k}\Omega) = 50\text{V}$$





Voltage Gain:

$$A_v = \frac{V_L}{V_i} = \frac{50\text{V}}{200\text{mV}} = 250$$

Common-Emitter Configuration

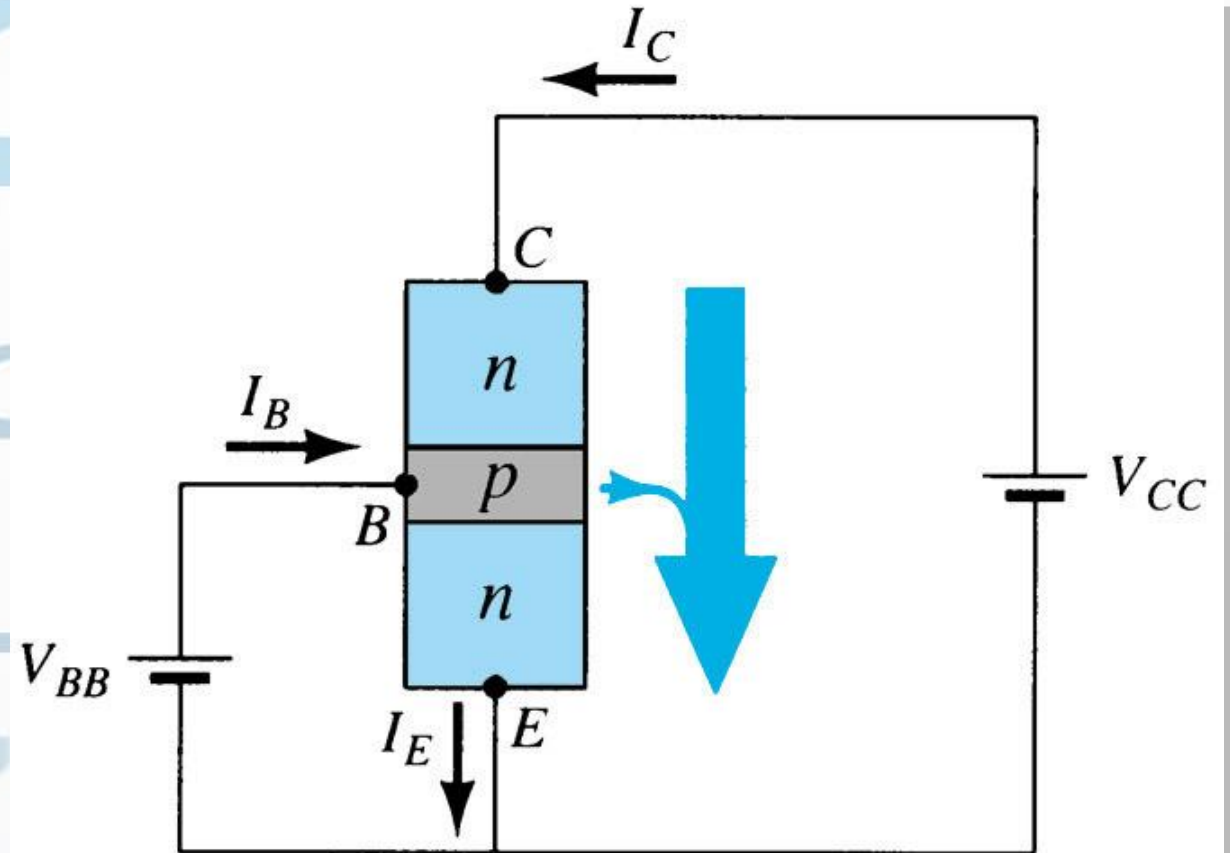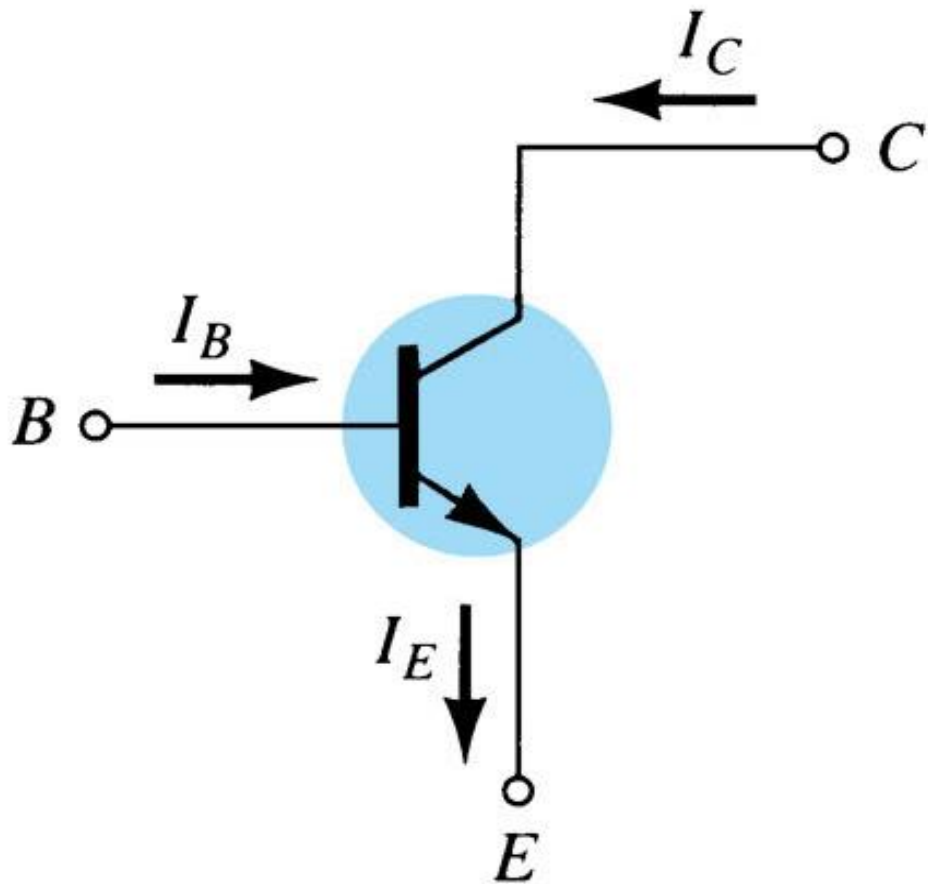- input (base-emitter) and output (collector-emitter).



I_C (mA)

Common-Emitter Characteristics


Output Characteristics

Collector Characteristics

(Saturation region)

(Active region)

(Cutoff region)

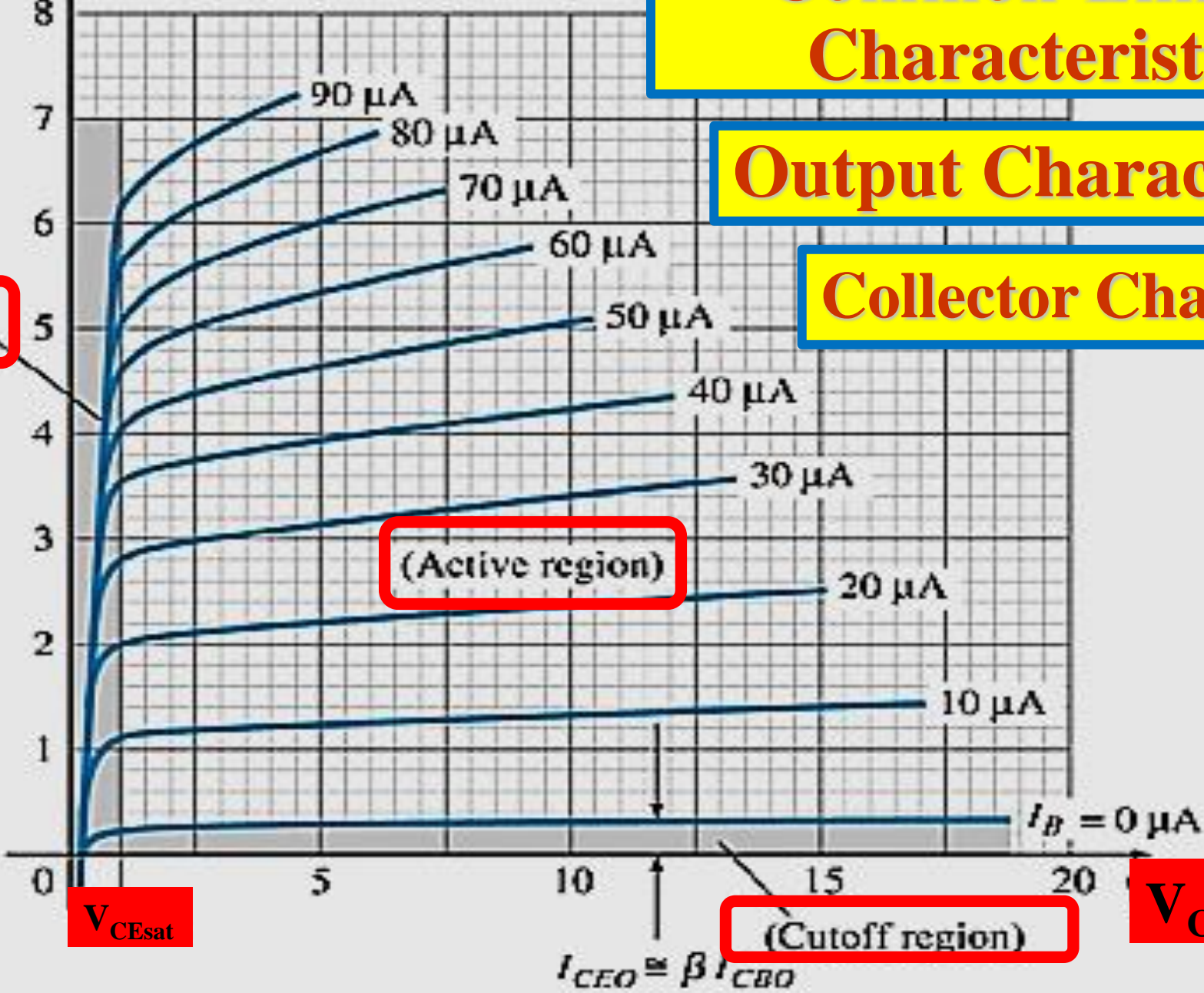

V_{CEsat}

V_{CE}


$$I_{CEO} \approx \beta I_{CBO}$$

Common-Emitter Characteristics



Input Characteristics

Base Characteristics

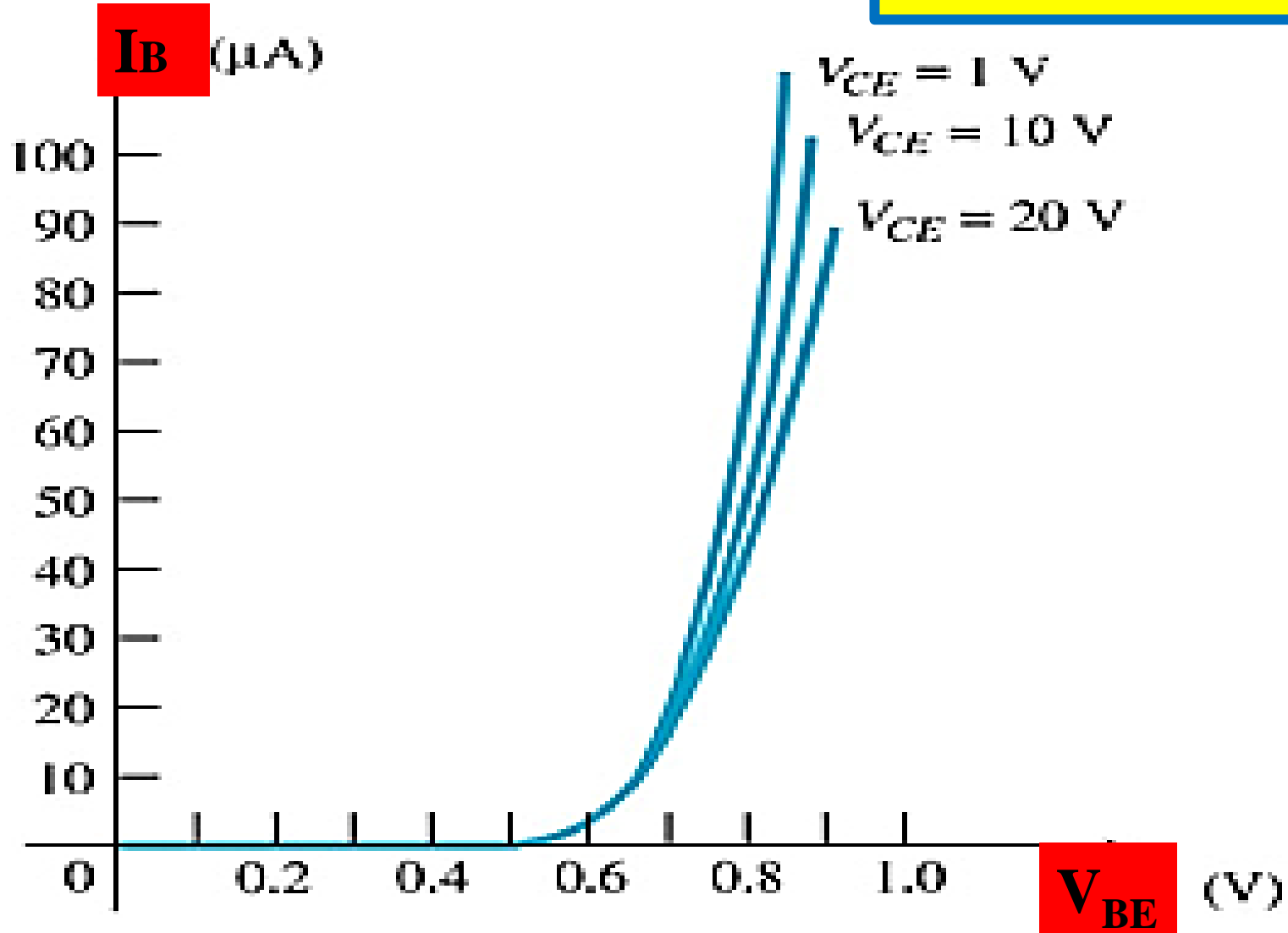

Common-Emitter Amplifier Currents



- Ideal Currents

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E$$

- Actual Currents

$$I_C = \alpha I_E + I_{CBO}$$

where I_{CBO} = minority collector current

I_{CBO} is usually so small that it can be ignored, except in high power transistors and in high temperature environments.

When $I_B = 0 \mu\text{A}$ the transistor is in cutoff, but there is some minority current flowing called I_{CEO} .

$$I_{CEO} = \frac{I_{CBO}}{1 - \alpha} \Big|_{I_B = 0 \mu\text{A}}$$

Beta (β)

β : represents the amplification factor of a transistor.
(β is sometimes referred to as h_{fe} ; a term used in transistor modeling calculations)

- In DC mode:

$$\beta_{dc} = \frac{I_C}{I_B}$$

- In AC mode:

$$\beta_{ac} = \left. \frac{\Delta I_C}{\Delta I_B} \right|_{V_{CE} = \text{constant}}$$

I_C mA

Beta (β)


Determining β from a Graph

$$\beta_{AC} = \frac{(3.2\text{mA} - 2.2\text{mA})}{(30\mu\text{A} - 20\mu\text{A})}$$

$$= \frac{1\text{mA}}{10\mu\text{A}} \Big|_{V_{CE}=7.5} = 100$$

$$\beta_{DC} = \frac{2.7\text{mA}}{25\mu\text{A}} \Big|_{V_{CE}=7.5}$$

$$= 108$$

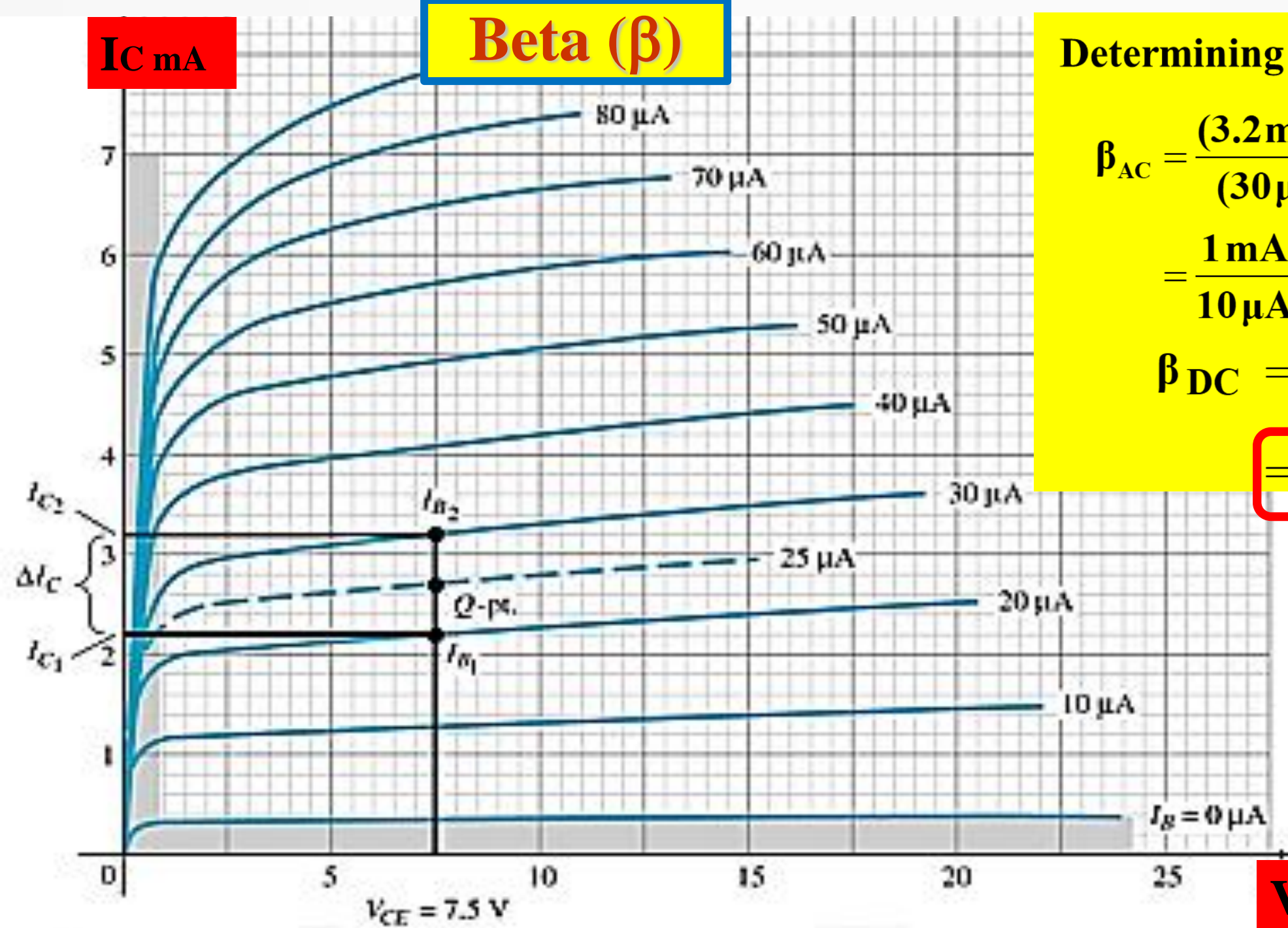

V_{CE}

Relationship between amplification factors β and α :



$$\alpha = \frac{\beta}{\beta + 1} \quad \beta = \frac{\alpha}{\alpha - 1}$$

Relationship Between Currents


$$I_C = \beta I_B \quad I_E = (\beta + 1) I_B$$

Common-Collector Configuration

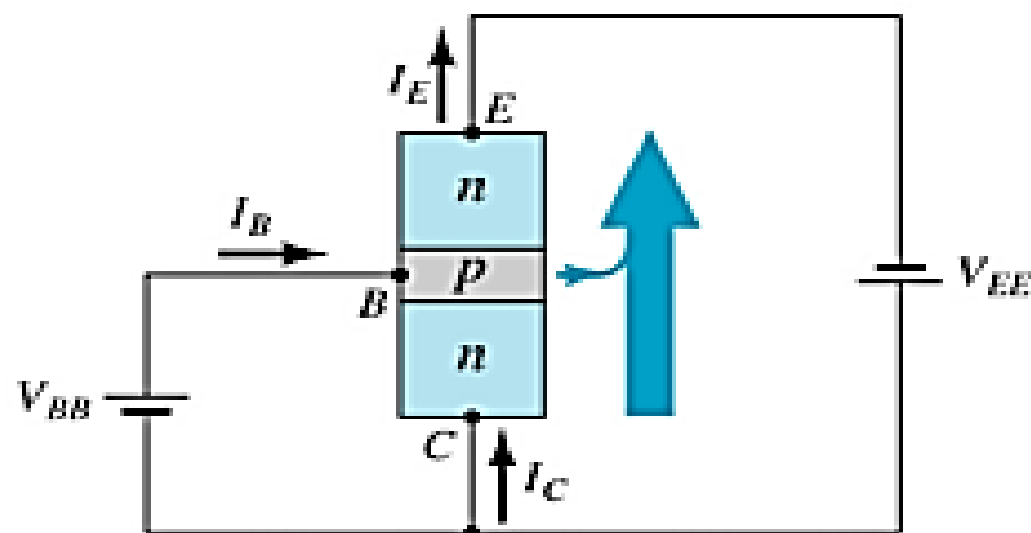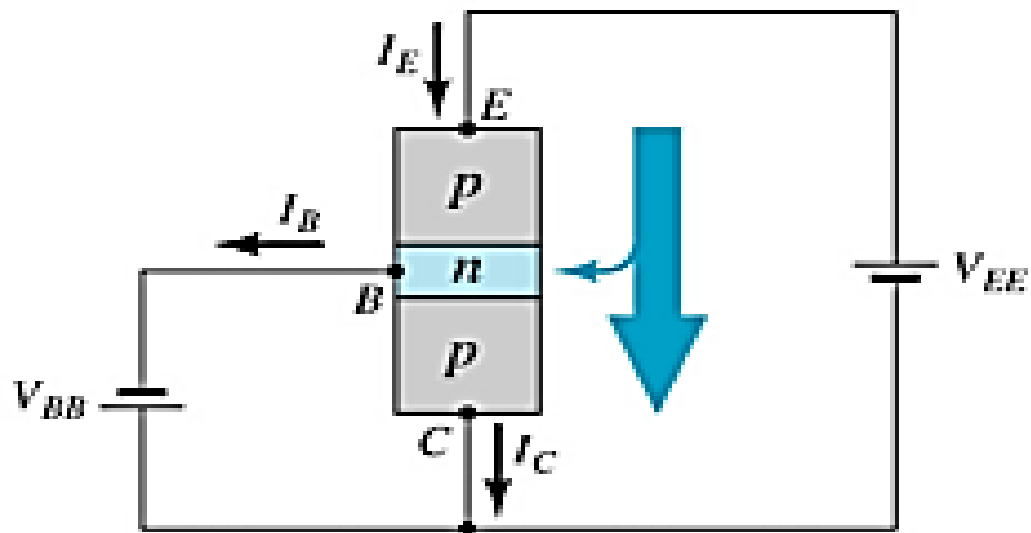
The input is on the base and the output is on the emitter.



PNP

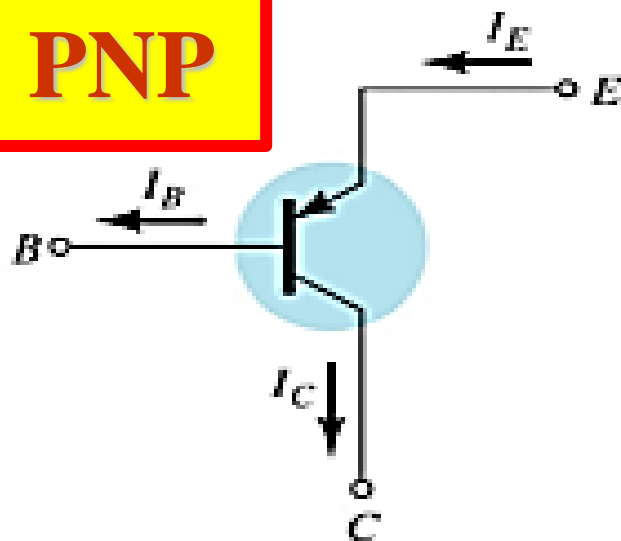


NPN

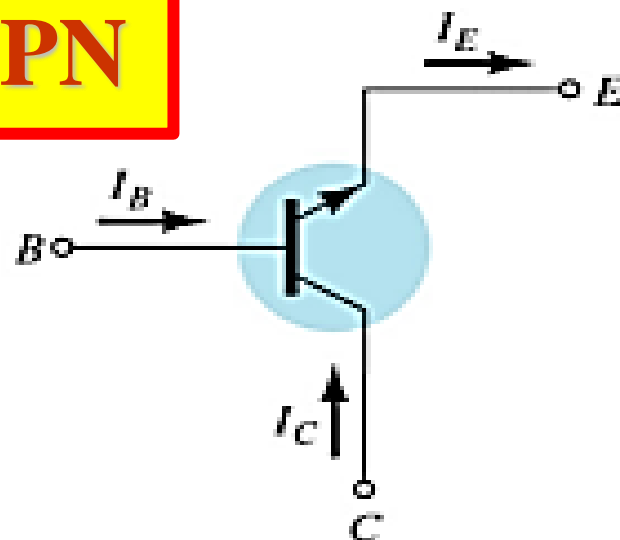

Output Characteristics

The characteristics are similar to those of the common-emitter configuration, except the vertical axis is I_E .

(Saturation region)

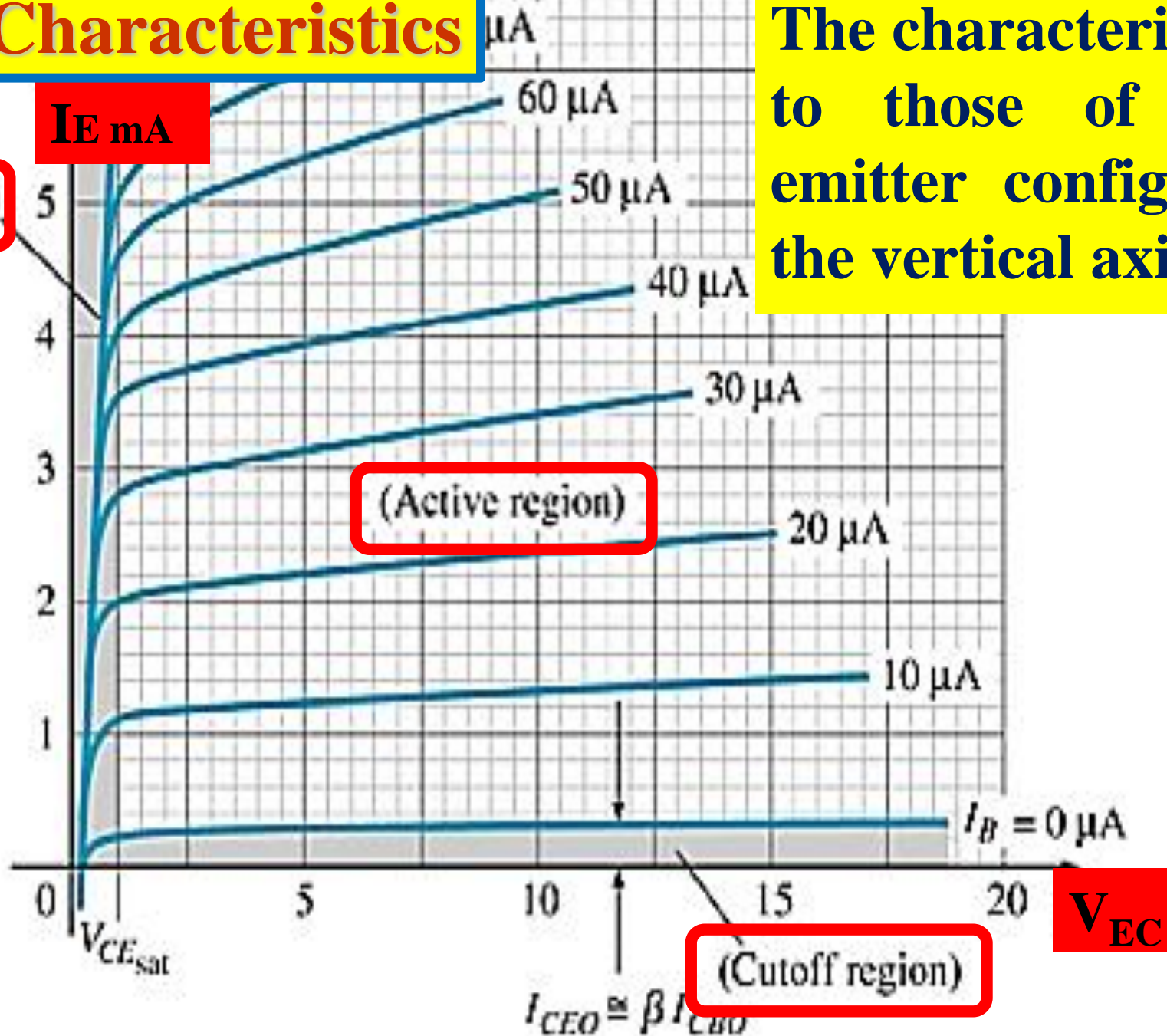


(Active region)

(Cutoff region)

V_{EC}

I_E mA

Operating Limits for Each Configuration

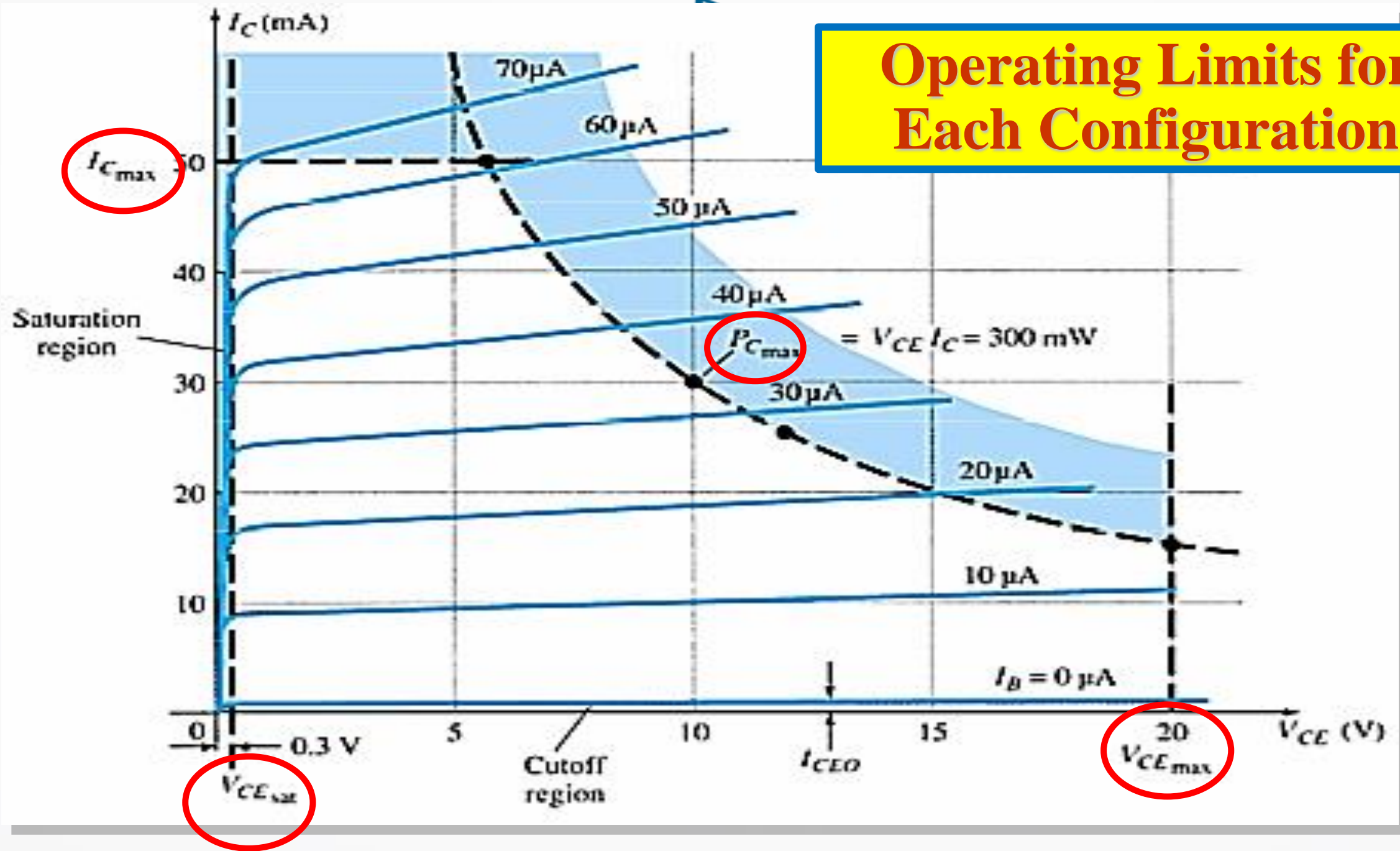

Power Dissipation

Common-base:

$$P_{Cmax} = V_{CB} I_C$$

Common-emitter:

$$P_{Cmax} = V_{CE} I_C$$

Common-collector:

$$P_{Cmax} = V_{CE} I_E$$



V_{CE} (volt)	I_C (mA)	المتصل J_C	المتصل J_E	نظام العمل
$V_{CE} = V_{CE sat} \approx 0$	$I_{C sat} \approx \frac{V_{CC}}{R_C}$	أمامي	أمامي	الإشباع
$V_{CE} = V_{CE cut-off} \approx V_{CC}$	$I_C = I_{C cut-off} \approx 0$	عكسي	عكسي	القطع
$V_{CE sat} < V_{CEQ} < V_{CC}$	$I_{C cut-off} < I_{CQ} < I_{C sat}$	عكسي	أمامي	الفعال

Transistor Specification Sheet


MAXIMUM RATINGS

Rating	Symbol	2N4123	Unit
Collector-Emitter Voltage	V_{CE0}	30	Vdc
Collector-Base Voltage	V_{CB0}	40	Vdc
Emitter-Base Voltage	V_{EB0}	5.0	Vdc
Collector Current - Continuous	I_C	200	mA dc
Total Device Dissipation @ $T_A = 25^\circ\text{C}$ Derate above 25°C	P_D	625 5.0	mW mW/°C
Operating and Storage Junction Temperature Range	T_j, T_{stg}	-55 to +150	°C

THERMAL CHARACTERISTICS

Characteristic	Symbol	Max	Unit
Thermal Resistance, Junction to Case	$R_{\theta JC}$	83.3	°C/W
Thermal Resistance, Junction to Ambient	$R_{\theta JA}$	200	°C/W

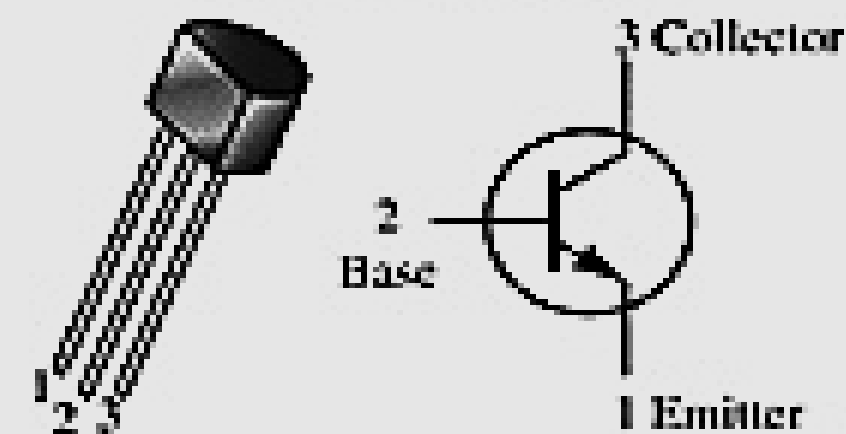2N4123
CASE 29-04, STYLE 1
TO-92 (TO-226AA)



**GENERAL PURPOSE
TRANSISTOR
NPN SILICON**

ELECTRICAL CHARACTERISTICS (T_A = 25°C unless otherwise noted)

Characteristic	Symbol	Min	Max	Unit
----------------	--------	-----	-----	------

OFF CHARACTERISTICS

Collector-Emitter Breakdown Voltage (1) (I _C = 1.0 mA dc, I _E = 0)	V _{(BR)CEO}	30		Vdc
Collector-Base Breakdown Voltage (I _C = 10 μA dc, I _E = 0)	V _{(BR)CBO}	40		Vdc
Emitter-Base Breakdown Voltage (I _E = 10 μA dc, I _C = 0)	V _{(BR)EBO}	5.0	–	Vdc
Collector Cutoff Current (V _{CE} = 20 Vdc, I _E = 0)	I _{CBO}	–	50	nA dc
Emitter Cutoff Current (V _{BE} = 3.0 Vdc, I _C = 0)	I _{EBO}	–	50	nA dc

ON CHARACTERISTICS

DC Current Gain(1) (I _C = 2.0 mA dc, V _{CE} = 1.0 Vdc) (I _C = 50 mA dc, V _{CE} = 1.0 Vdc)	h _{FE}	50 25	150 –	–
Collector-Emitter Saturation Voltage(1) (I _C = 50 mA dc, I _B = 5.0 mA dc)	V _{CE(sat)}	–	0.3	Vdc
Base-Emitter Saturation Voltage(1) (I _C = 50 mA dc, I _B = 5.0 mA dc)	V _{BE(sat)}	–	0.95	Vdc



SMALL-SIGNAL CHARACTERISTICS

Current-Gain – Bandwidth Product ($I_C = 10 \text{ mAdc}$, $V_{CE} = 20 \text{ Vdc}$, $f = 100 \text{ MHz}$)	f_T	250		MHz
Output Capacitance ($V_{CE} = 5.0 \text{ Vdc}$, $I_C = 0$, $f = 100 \text{ MHz}$)	C_{obo}	-	4.0	pF
Input Capacitance ($V_{BE} = 0.5 \text{ Vdc}$, $I_C = 0$, $f = 100 \text{ kHz}$)	C_{ibo}	-	8.0	pF
Collector-Base Capacitance ($I_C = 0$, $V_{CB} = 5.0 \text{ V}$, $f = 100 \text{ kHz}$)	C_{cb}	-	4.0	pF
Small-Signal Current Gain ($I_C = 2.0 \text{ mAdc}$, $V_{CE} = 10 \text{ Vdc}$, $f = 1.0 \text{ kHz}$)	h_{fe}	50	200	-
Current Gain – High Frequency ($I_C = 10 \text{ mAdc}$, $V_{CE} = 20 \text{ Vdc}$, $f = 100 \text{ MHz}$) ($I_C = 2.0 \text{ mAdc}$, $V_{CE} = 10 \text{ V}$, $f = 1.0 \text{ kHz}$)	h_{fe}	2.5 50	- 200	-
Noise Figure ($I_C = 100 \mu\text{Ade}$, $V_{CE} = 5.0 \text{ Vdc}$, $R_S = 1.0 \text{ k ohm}$, $f = 1.0 \text{ kHz}$)	NF	-	6.0	dB

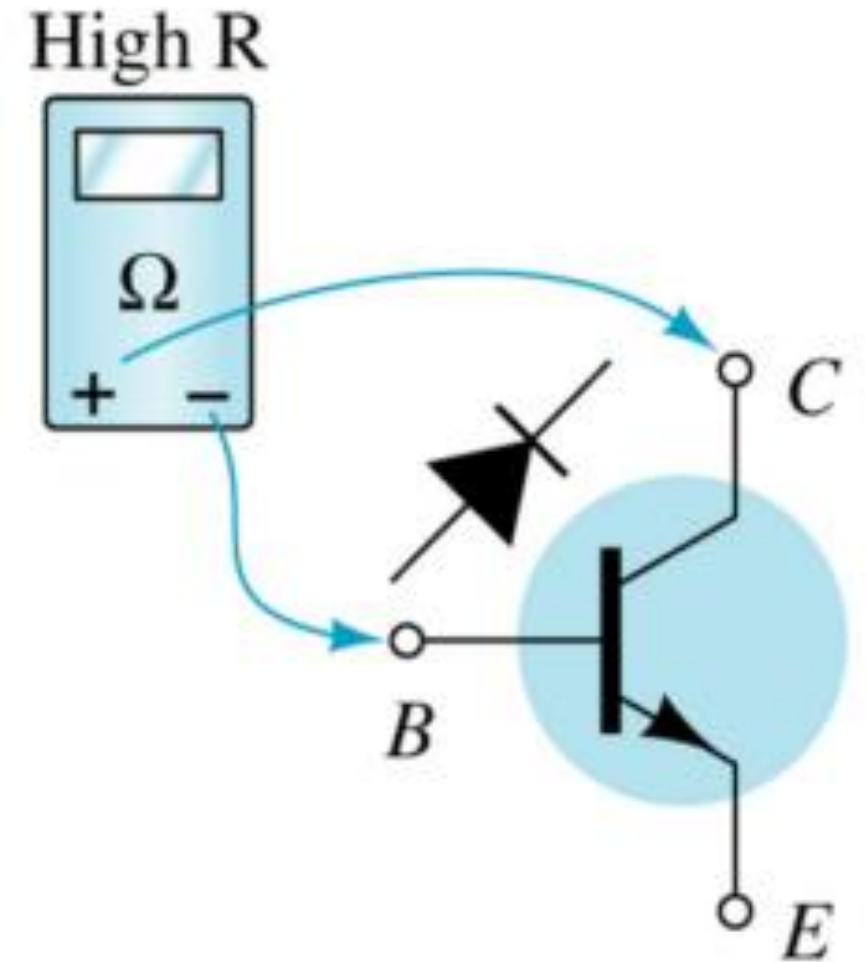
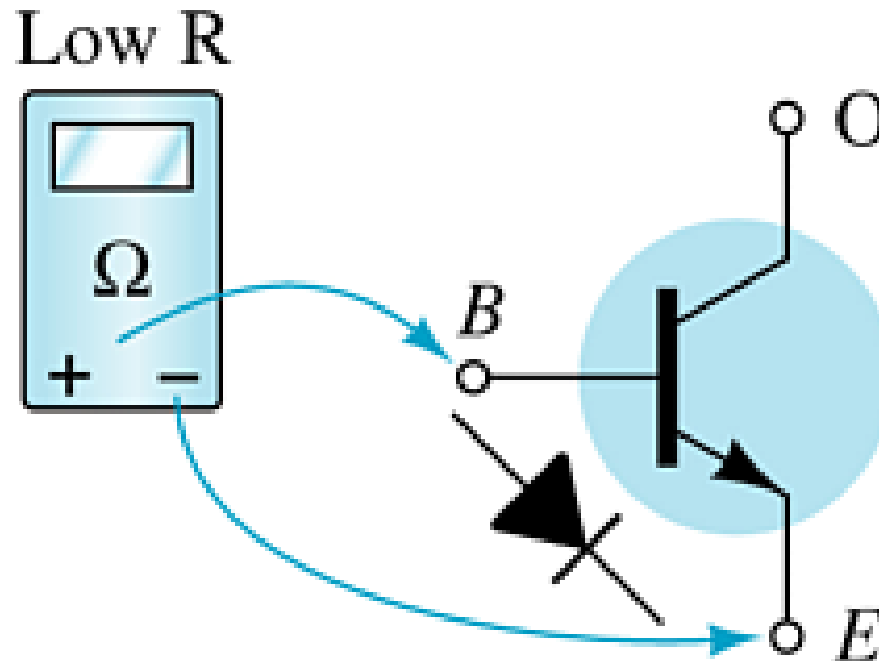
(1) Pulse Test: Pulse Width = 300 μs , Duty Cycle = 2.0%

Transistor Testing



- **Curve Tracer:**
Provides a graph of the characteristic curves.
- **DMM:**
Some DMMs measure β_{DC} or h_{FE} .
- **Ohmmeter:**





Checking a Transistor with an Ohmmeter

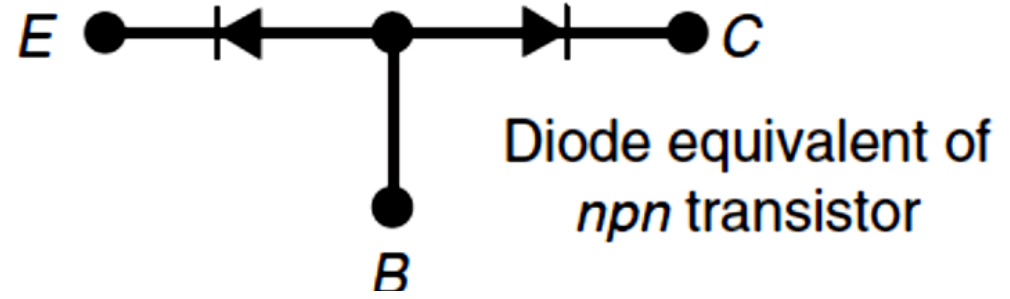
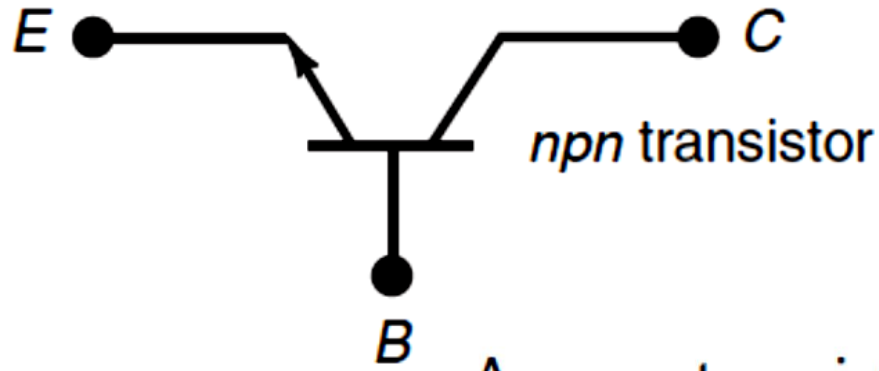


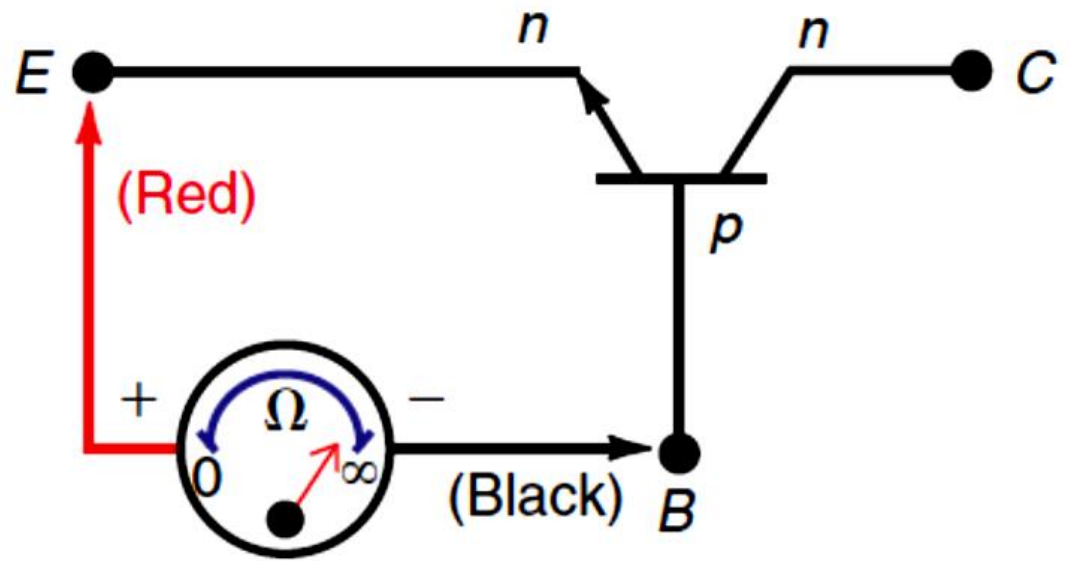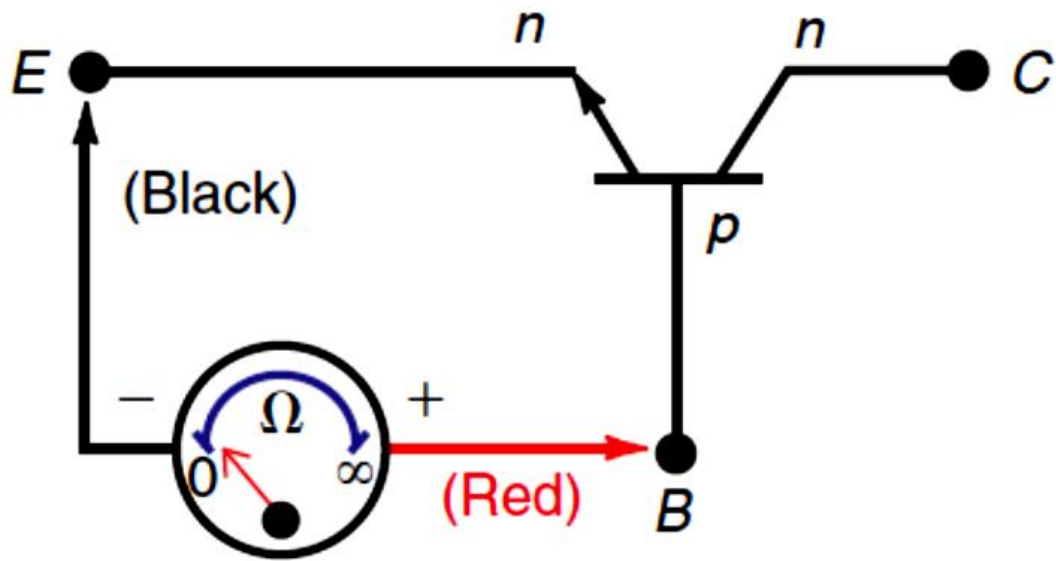An *npn* transistor and its diode equivalent.



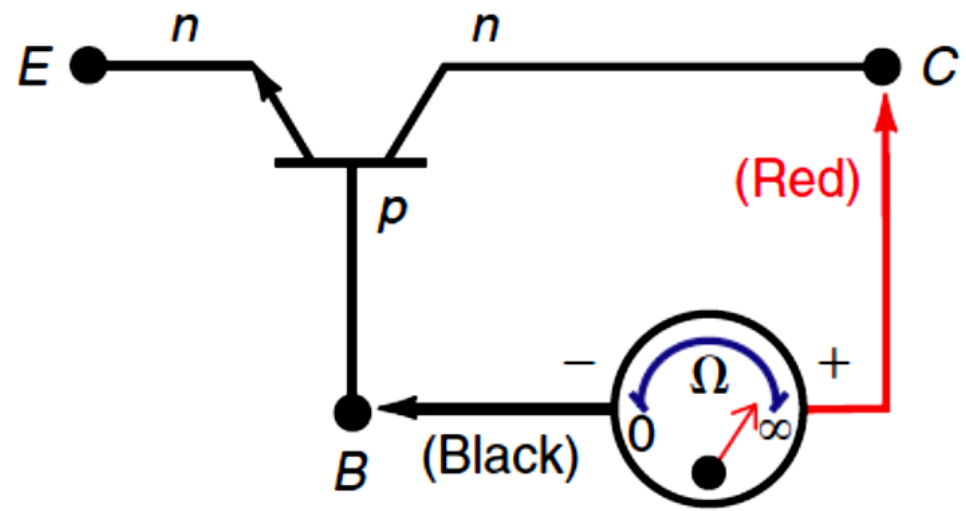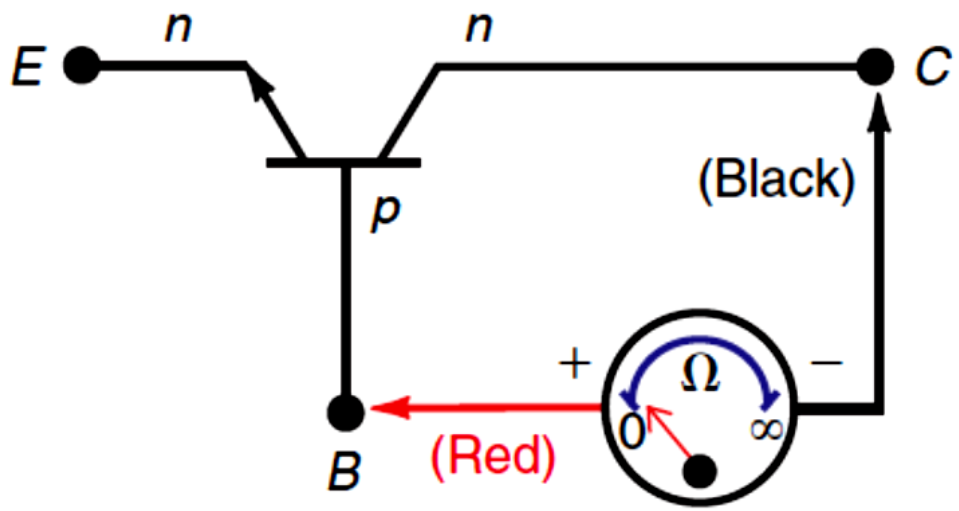

Checking for Proper Transistor Action

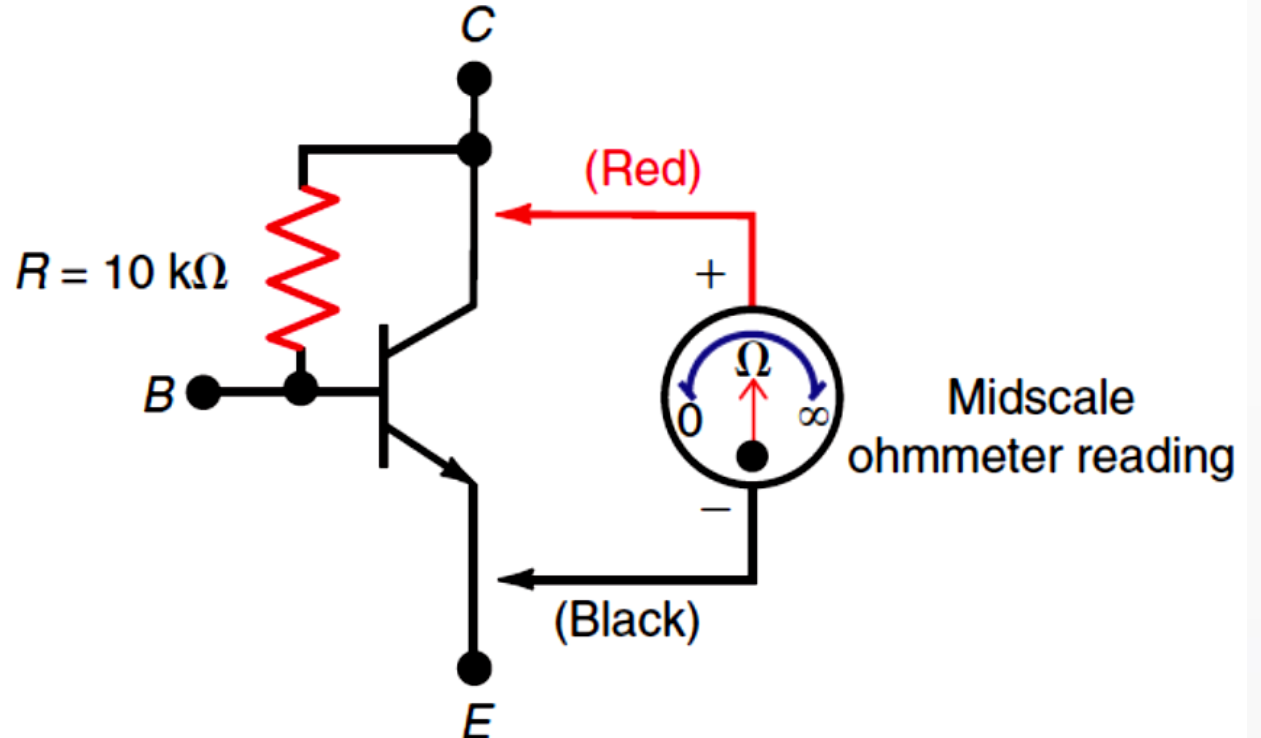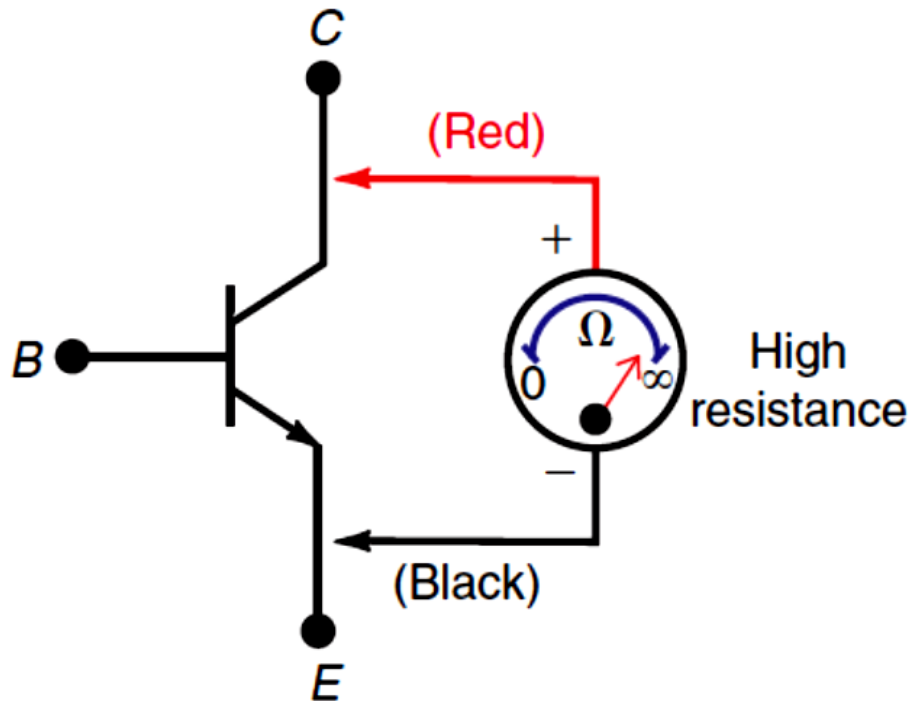

Transistor Terminal Identification

