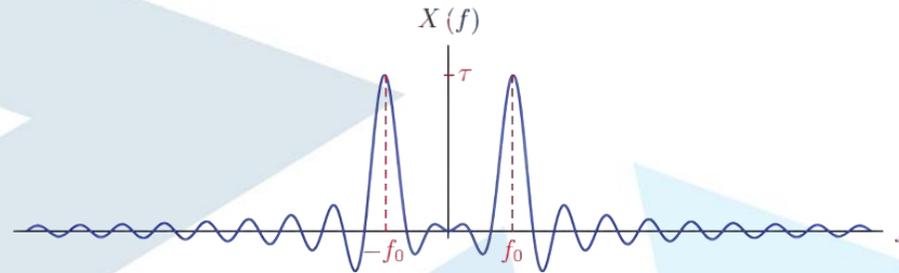


# CECC507: Signals and Systems


## Lecture 5: Analyzing Continuous Time Systems in the Time Domain



**Eng. Aya Kherbek**  
**Eng. Baher Kherbek**  
**Faculty of Engineering**  
**Department of Mechatronics**  
**Manara University**



- Differential equation for RLC circuit

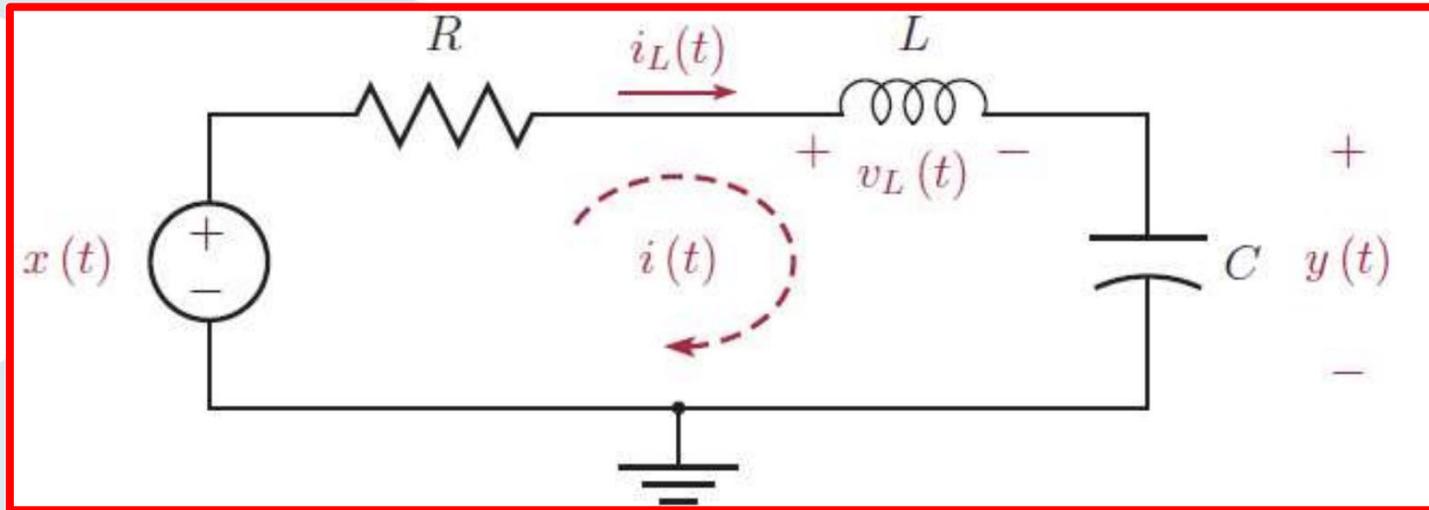


بداية لدينا معادلات كل من جهود العناصر الأساسية من مقاومة و مكثف و تيار كالتالي:

$$v_R(t) = R \cdot i(t)$$

$$v_L(t) = L \cdot \frac{di(t)}{dt}$$

$$i_C(t) = C \cdot \frac{dv_C(t)}{dt}, V_C(t) = y(t)$$

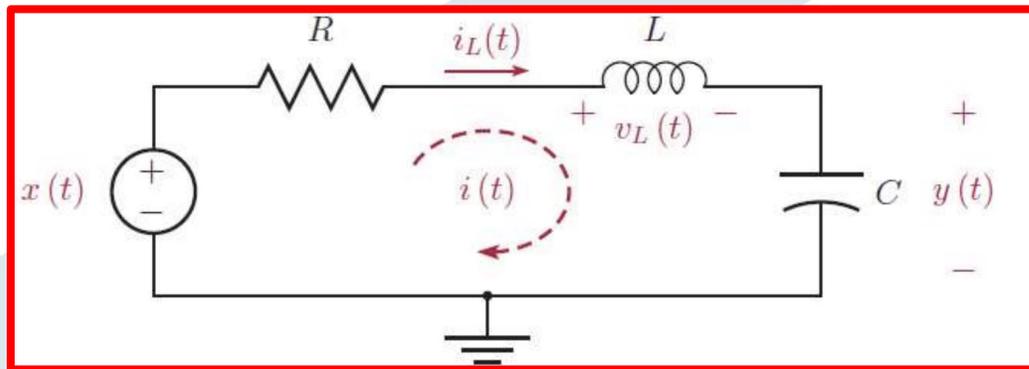نطبق كيرشوف حيث مجموع الجهد ضمن الدائرة يساوي الصفر



$$\sum V_{Drop} = 0$$



$$x(t) - V_R(t) - V_L(t) - V_C(t) = 0$$

$$x(t) - Ri(t) - L \frac{di(t)}{dt} - y(t) = 0$$

ولدينا أيضا:

$$i(t) = i_c(t) = c \frac{dV_c(t)}{dt} = C \frac{dy(t)}{dt}$$

$$x(t) - RC \frac{dy(t)}{dt} - LC \frac{d^2y(t)}{dt^2} - y(t) = 0$$

$$x(t) = RC \frac{dy(t)}{dt} + LC \frac{d^2y(t)}{dt^2} + y(t)$$

$$\frac{1}{LC} x(t) = \frac{R}{L} \frac{dy(t)}{dt} + \frac{d^2y(t)}{dt^2} + \frac{1}{LC} y(t)$$




- Ex1: Use Simulink to draw the output of the following RC circuit :

$$\frac{dy(t)}{dt} + 4y(t) = 4x(t)$$

Let the input signal be a unit step, that is,  
 $x(t) = u(t)$ .


Draw the solution  $y(t)$  for  $t \geq 0$  subject to each initial condition specified below:


- $y(0) = 0$
- $y(0) = 5$

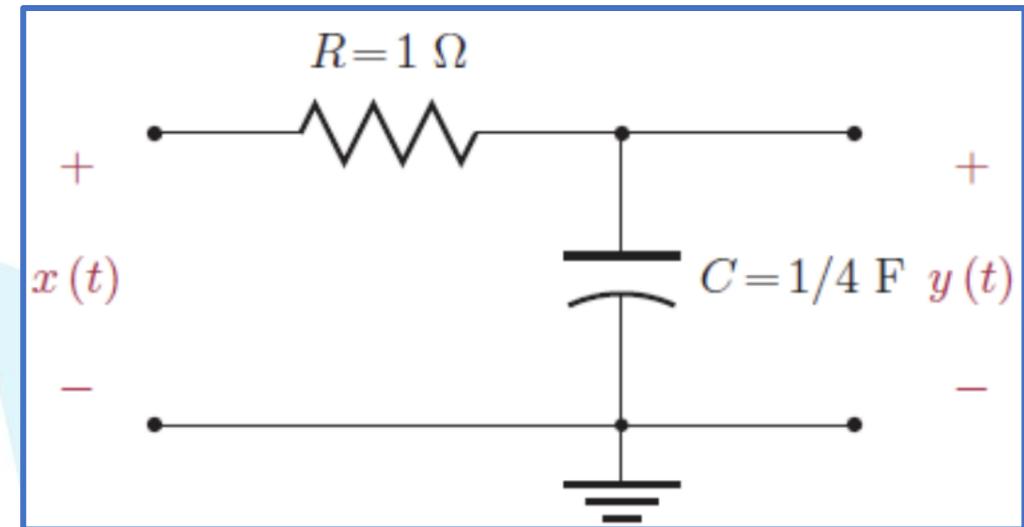

a.

$$y(0) = 0$$

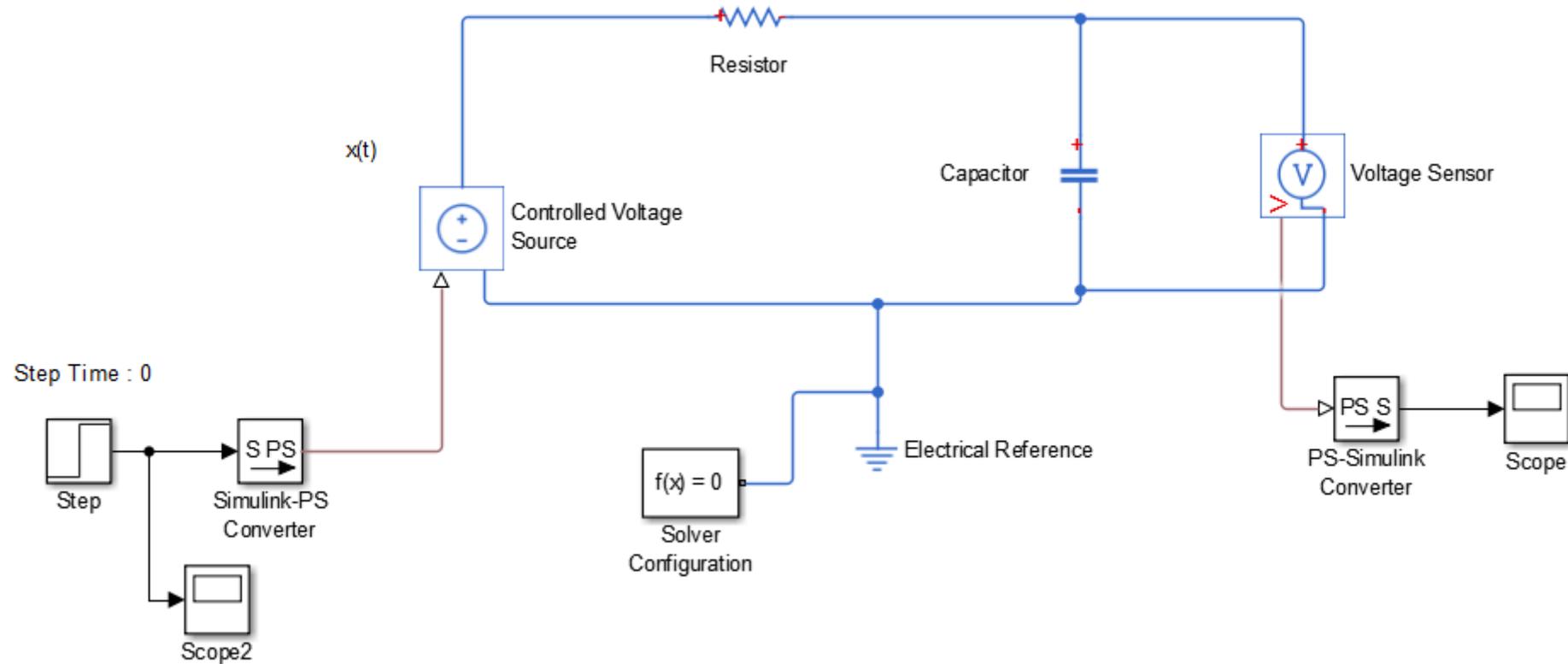

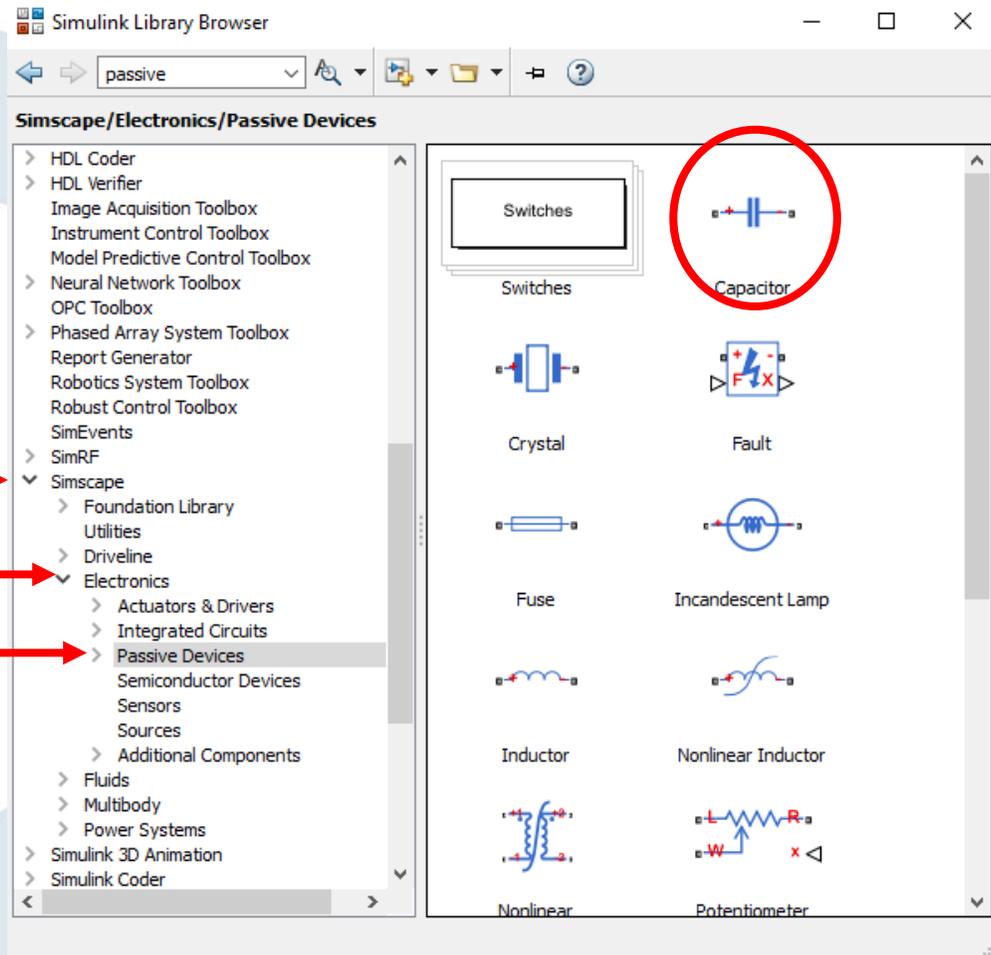

من خلال شجرة البحث الموضحة في الشكل  
 نختار المكثف الموجود في الشجرة:  
 Simscape -> Electronics -> Passive  
 Devices -> Capacitor

حيث يتيح لنا الخيار الحالي وضع قيمة بدائية  
 للمكثف بناء على متطلبات الدارة وفي حالتنا هنا  
 نعطيه قيم بدائية

$y(0) = 0$



Block Parameters: Capacitor

Capacitor  
This block models a capacitor with optional tolerance, operational limits and fault modeling.

Settings

Main Operating Limits Faults

Enable table-based capacitance: No - use constant capacitance

Capacitance: 0.25 F

Capacitance tolerance (%): 5

Tolerance application: None - use nominal value


Series resistance: 1e-6 Ohm


Parallel conductance: 0 1/Ohm

Initial capacitor voltage: 0 V


$y(0) = 0$

OK Cancel Help Apply

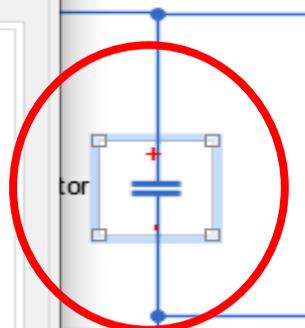

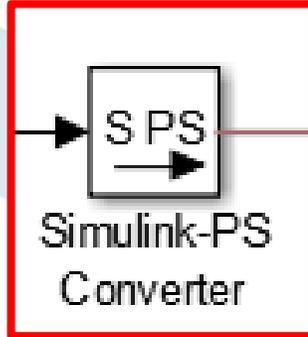


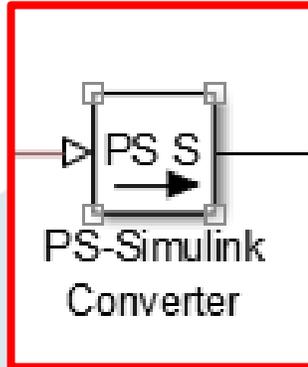
- كتلة **Simulink-PS Converter** تحول الإشارة من Simulink إلى إشارة فيزيائية.
- تُستخدم لربط مصادر Simulink مع عناصر الشبكة الفيزيائية في Simscape.
- تعمل كجسر بين الإشارات الرياضية والمحاكاة الفيزيائية.
- ضرورة لإدخال إشارات التحكم أو المدخلات الزمنية إلى النماذج الفيزيائية.



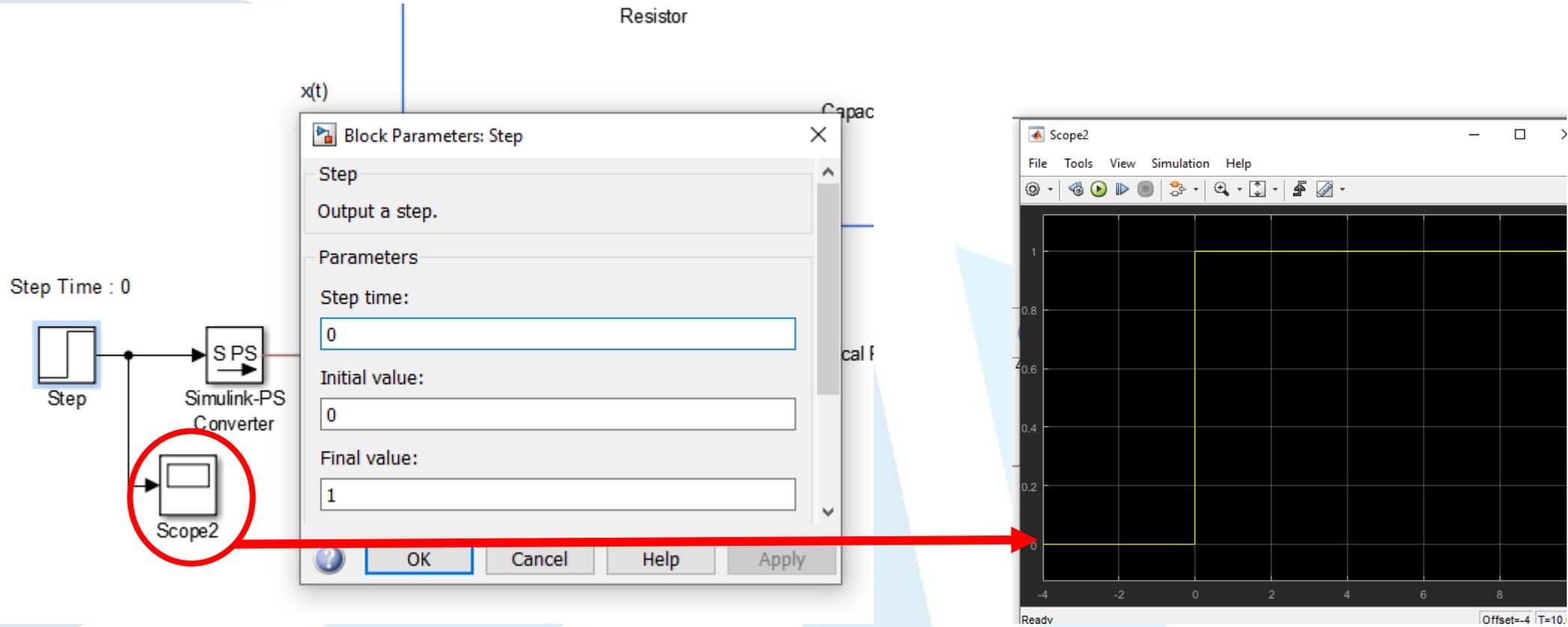- تقوم بتحويل الإشارة الفيزيائية (Physical Signal) القادمة من شبكة Simscape إلى إشارة Simulink عادية.
- تُستخدم عندما تريد مراقبة أو معالجة نتائج النماذج الفيزيائية داخل بيئة Simulink (مثل عرضها على Scope أو استخدامها في حسابات إضافية).
- تعمل كجسر من النمذجة الفيزيائية إلى الإشارات الرياضية في Simulink.
- ضرورة لإخراج قيم من الشبكة الفيزيائية إلى أدوات التحليل أو العرض في Simulink.







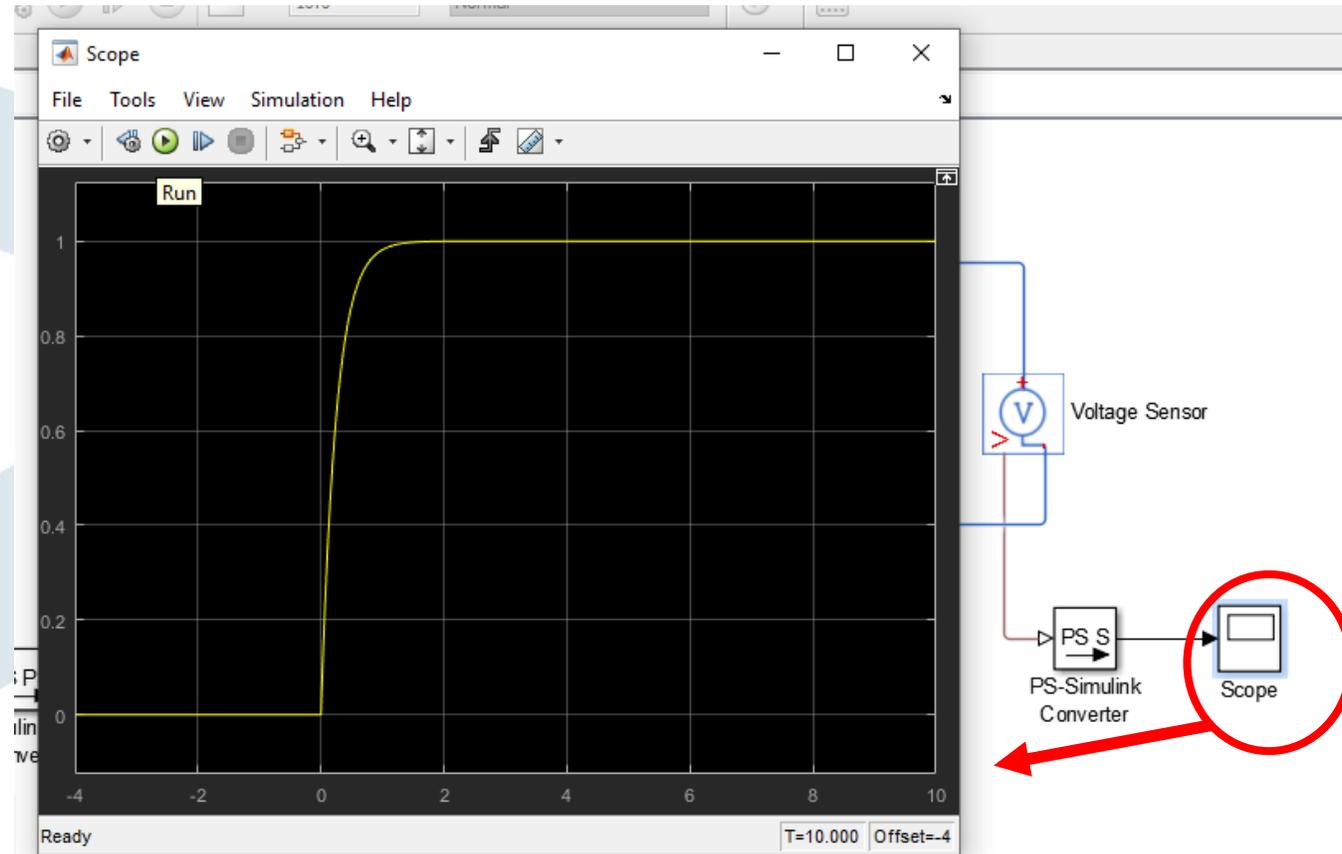

b

$$y(0) = 5$$

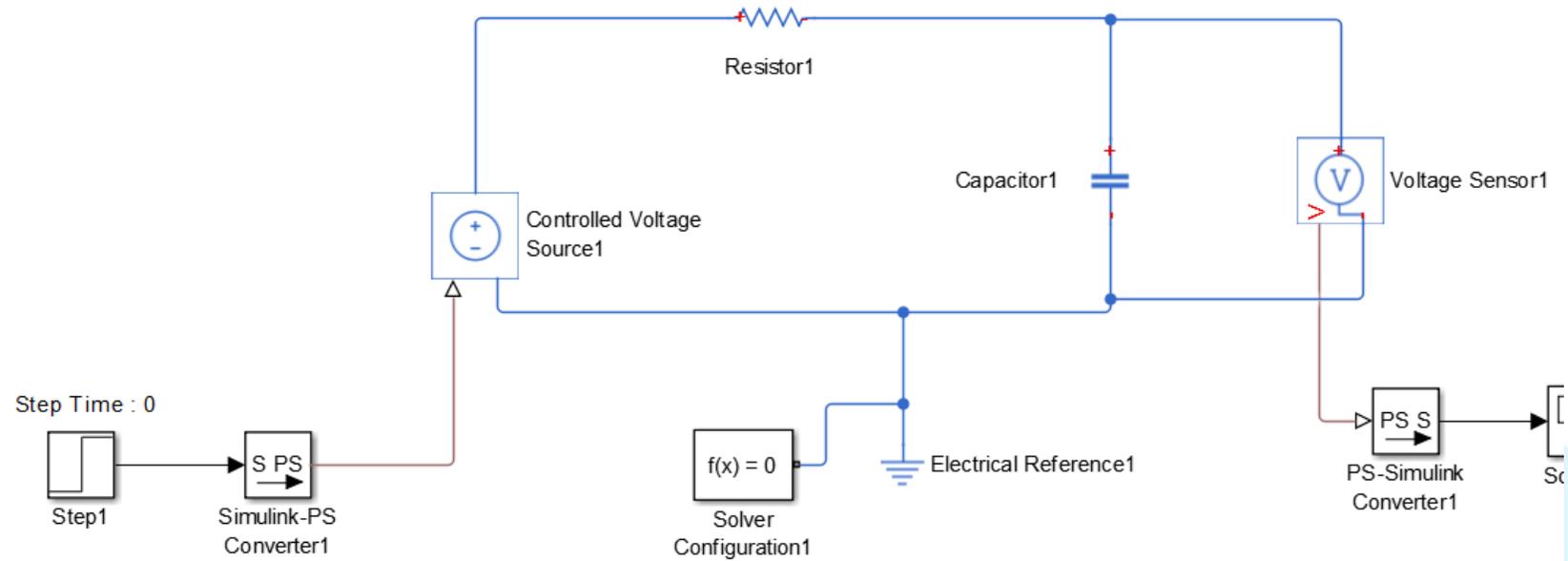

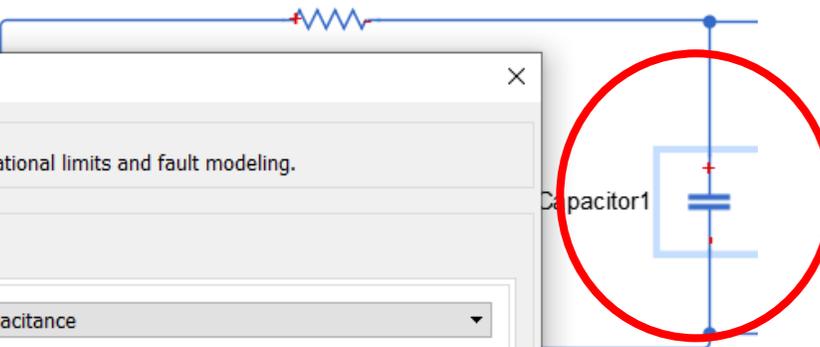

Block Parameters: Capacitor1

Capacitor  
This block models a capacitor with optional tolerance, operational limits and fault modeling.

Settings

Main Operating Limits Faults

Enable table-based capacitance: No - use constant capacitance

Capacitance: 0.25 F

Capacitance tolerance (%): 5

Tolerance application: None - use nominal value

Series resistance: 1e-6 Ohm

Parallel conductance: 0 1/Ohm

Initial capacitor voltage: 5 V


**$y(0) = 5$**

OK Cancel Help Apply

Capacitor1

Electrical Reference1



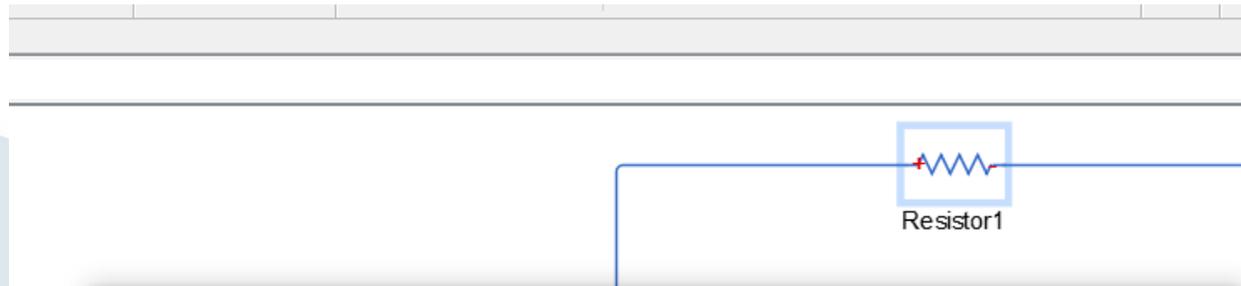

Block Parameters: Resistor1

Resistor

This block models a resistor with optional tolerance, operational limits, fault and thermal noise modeling. To model temperature effects, select the thermal variant of this block by right-clicking on the block and selecting Simscape block choices and Show thermal port.

Settings

Main Operating Limits Faults Noise


Resistance: 1 Ohm

Tolerance (%): 5

Tolerance application: None - use nominal value

OK Cancel Help Apply



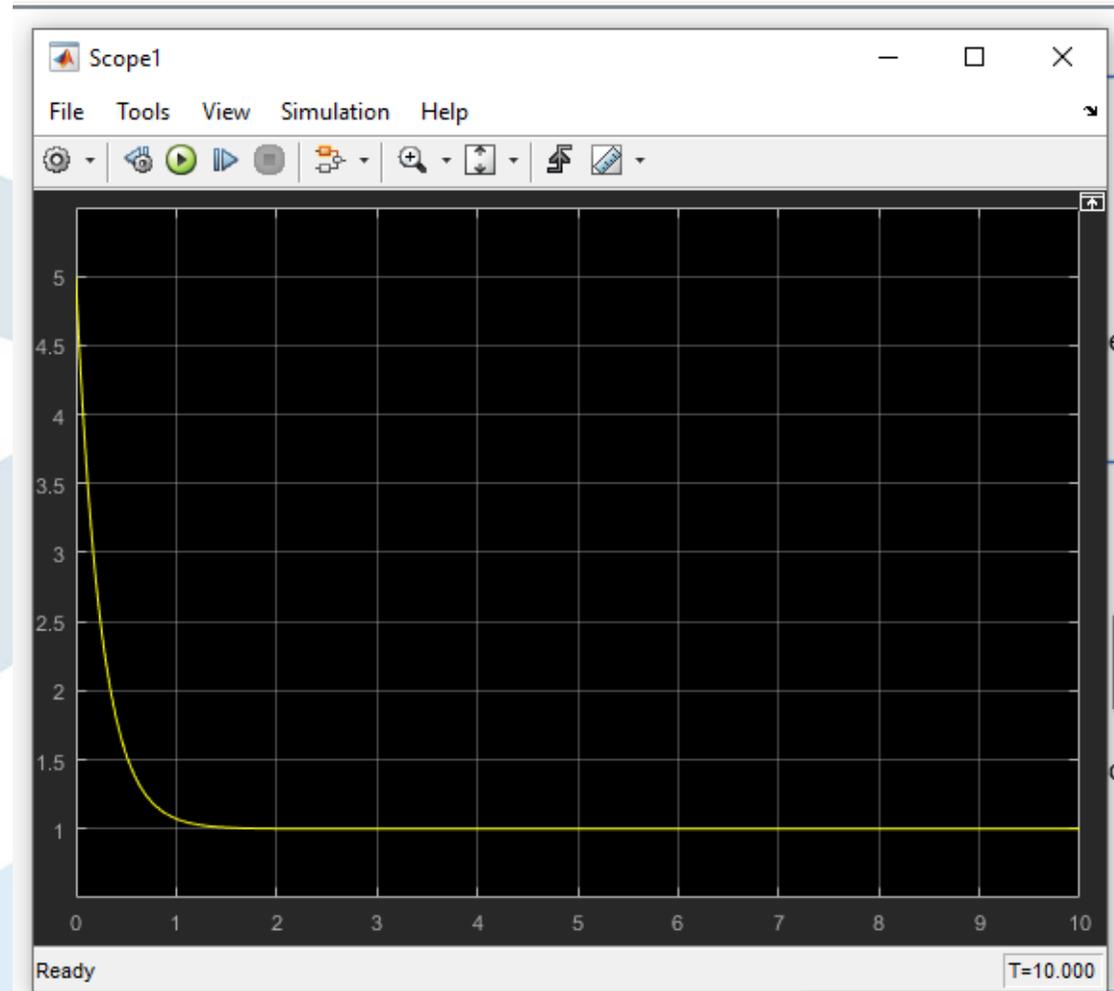

## **Example 2: Natural response of a second-order system (RLC circuit)**


At time  $t=0$  the initial inductor current is  $i(0)=0.5\text{A}$  and the initial capacitor voltage is  $y(0) = 2\text{v}$ .  $\mathbf{x(t)=0}$ .

**Draw the output voltage  $y(t)$  using Simulink if:**

- The element values are  $R=2\Omega$ ,  $L=1\text{H}$  and  $C=1/26\text{ F}$**
- The element values are  $R=6\Omega$ ,  $L=1\text{H}$  and  $C=1/9\text{ F}$**



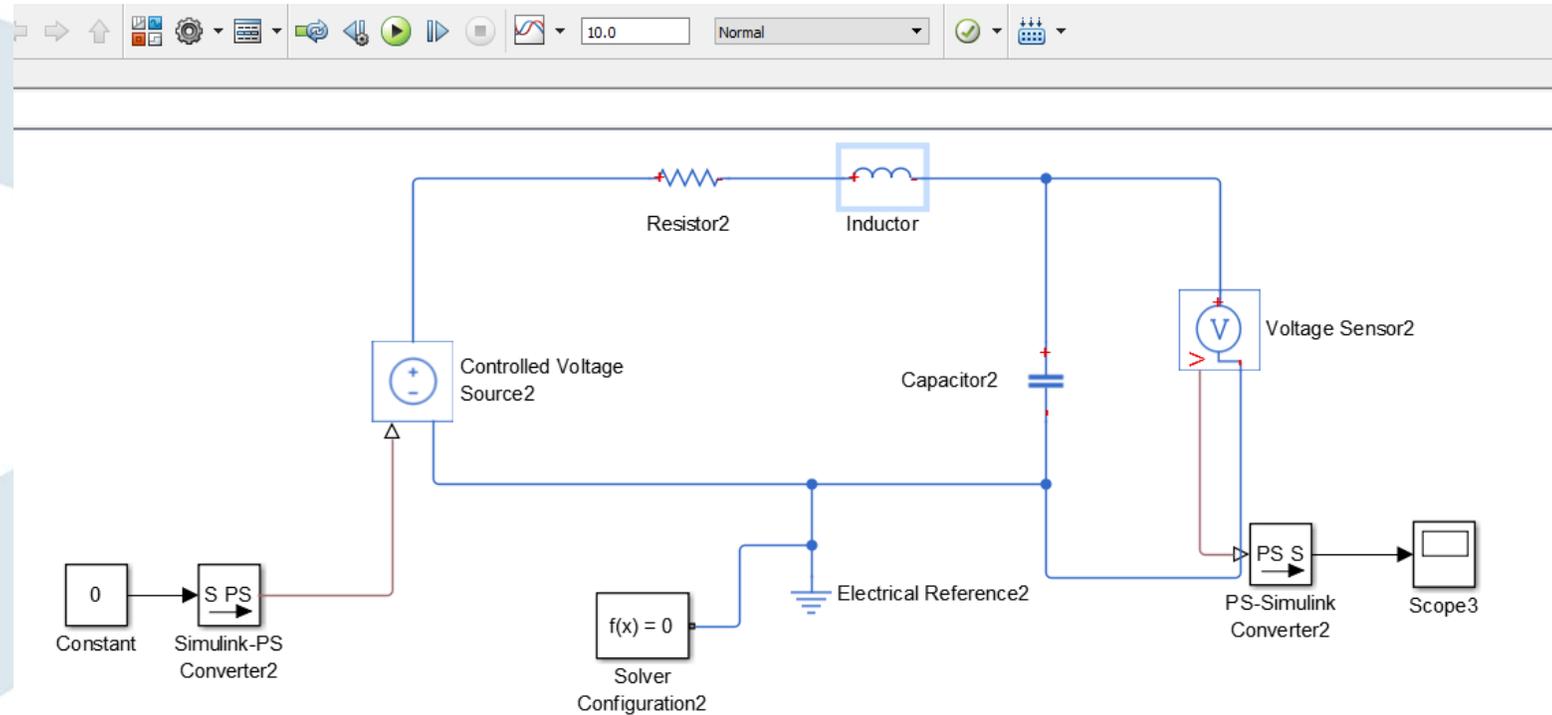a. The element values are  $R=2\Omega$ ,  $L=1H$  and  $C=1/26 F$



Block Parameters: Capacitor2

Capacitor

This block models a capacitor with optional tolerance, operational limits and fault modeling.

Settings

Main Operating Limits Faults

Enable table-based capacitance: No - use constant capacitance

Capacitance: 1/26 F

Capacitance tolerance (%): 5

Tolerance application: None - use nominal value


Series resistance: 1e-6 Ohm

Parallel conductance: 0 1/Ohm

Initial capacitor voltage: 2 V

$y(0) = 2$

OK Cancel Help Apply

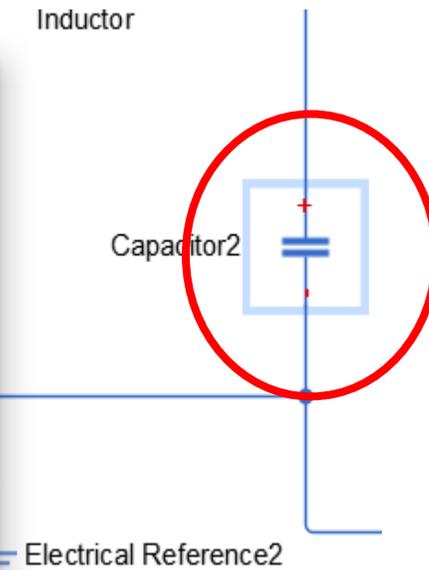



Block Parameters: Resistor2

Resistor

This block models a resistor with optional tolerance, operational limits, fault and thermal noise modeling. To model temperature effects, select the thermal variant of this block by right-clicking on the block and selecting Simscape block choices and Show thermal port.

Settings

Main Operating Limits Faults Noise


Resistance: 2 Ohm

Tolerance (%): 5

Tolerance application: None - use nominal value

OK Cancel Help Apply



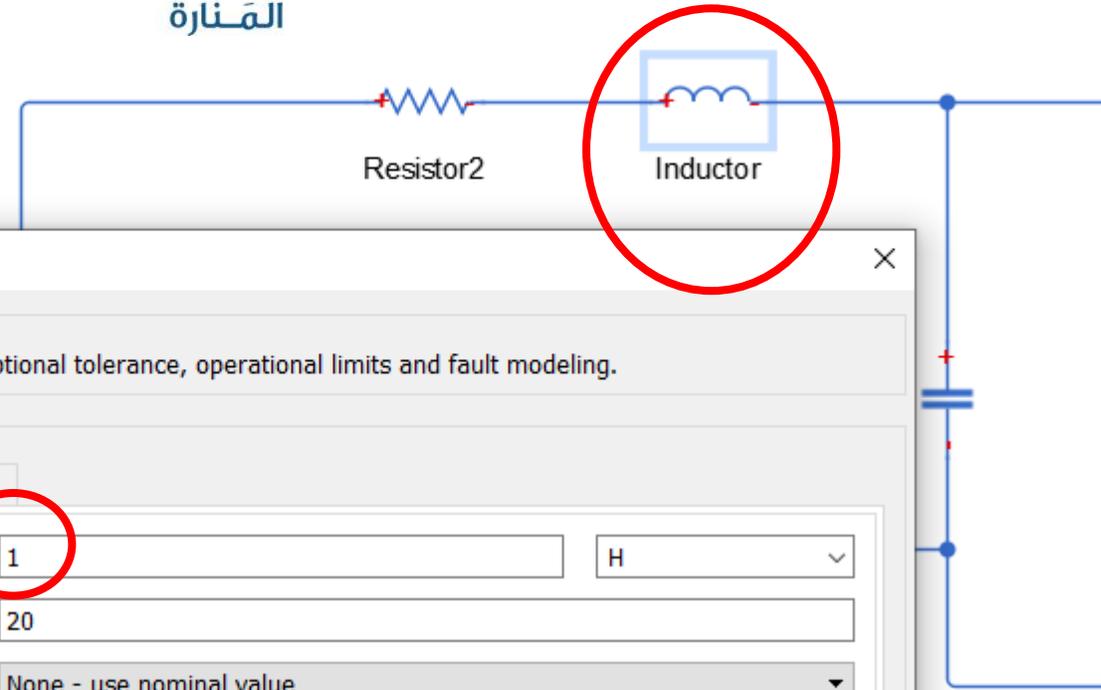

Block Parameters: Inductor

Inductor

This block models an inductor with optional tolerance, operational limits and fault modeling.

Settings

Main Operating Limits Faults

Inductance: 1 H

Tolerance (%): 20

Tolerance application: None - use nominal value



Series resistance: 0 Ohm

Parallel conductance: 1e-9 1/Ohm


Initial inductor current: 0.5 A


OK Cancel Help Apply



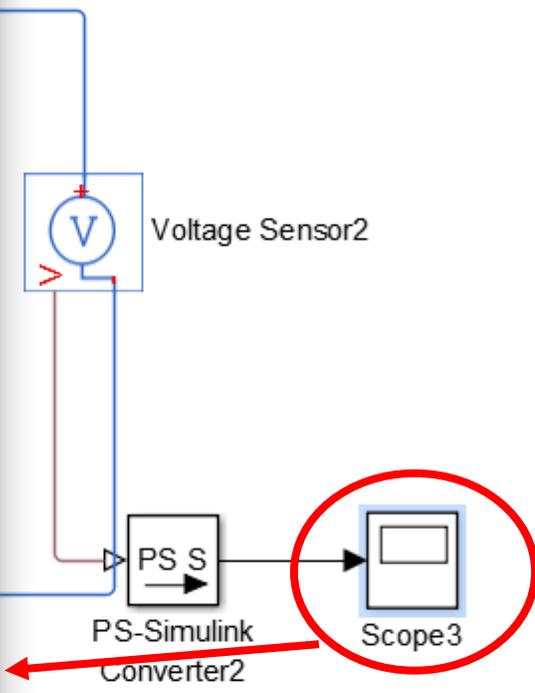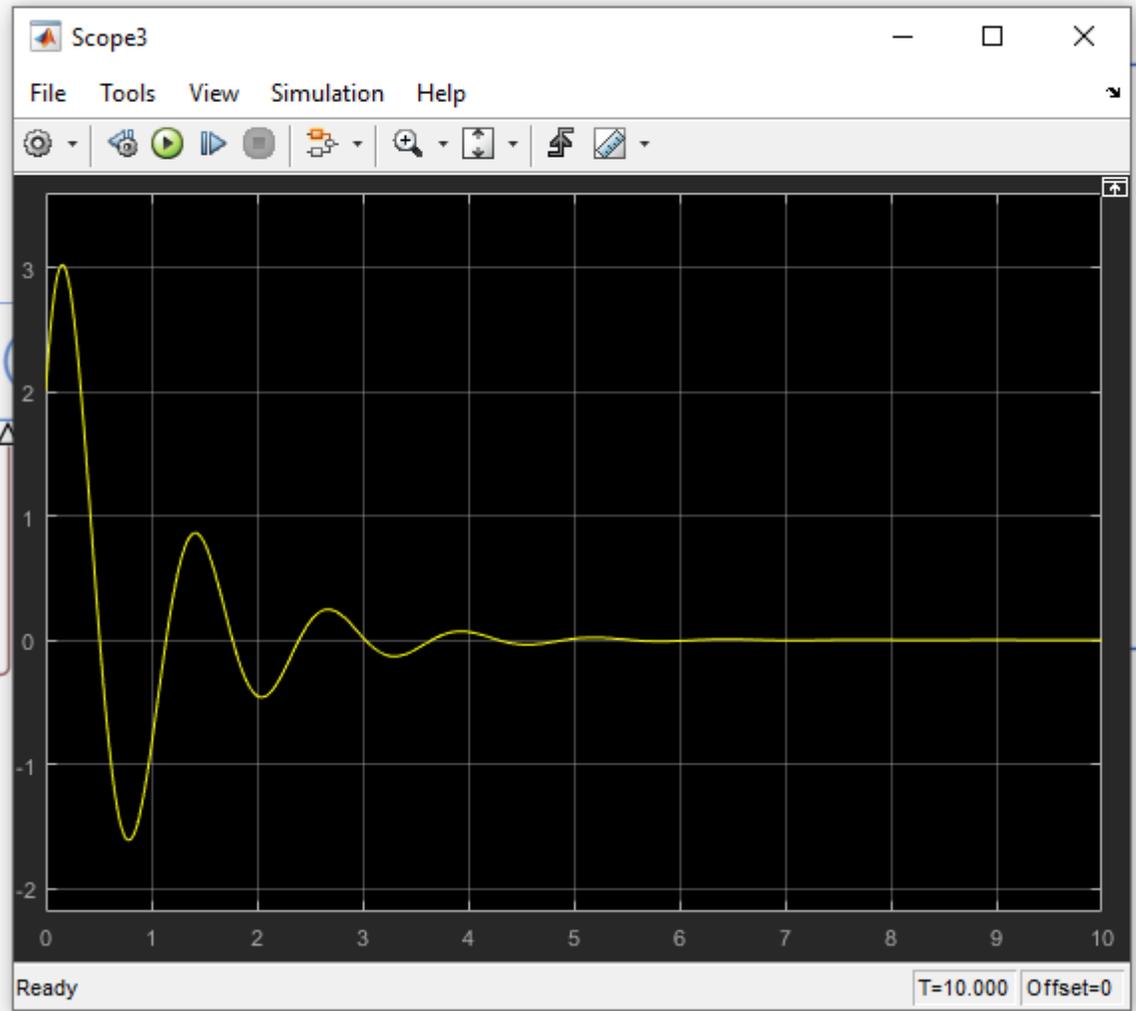

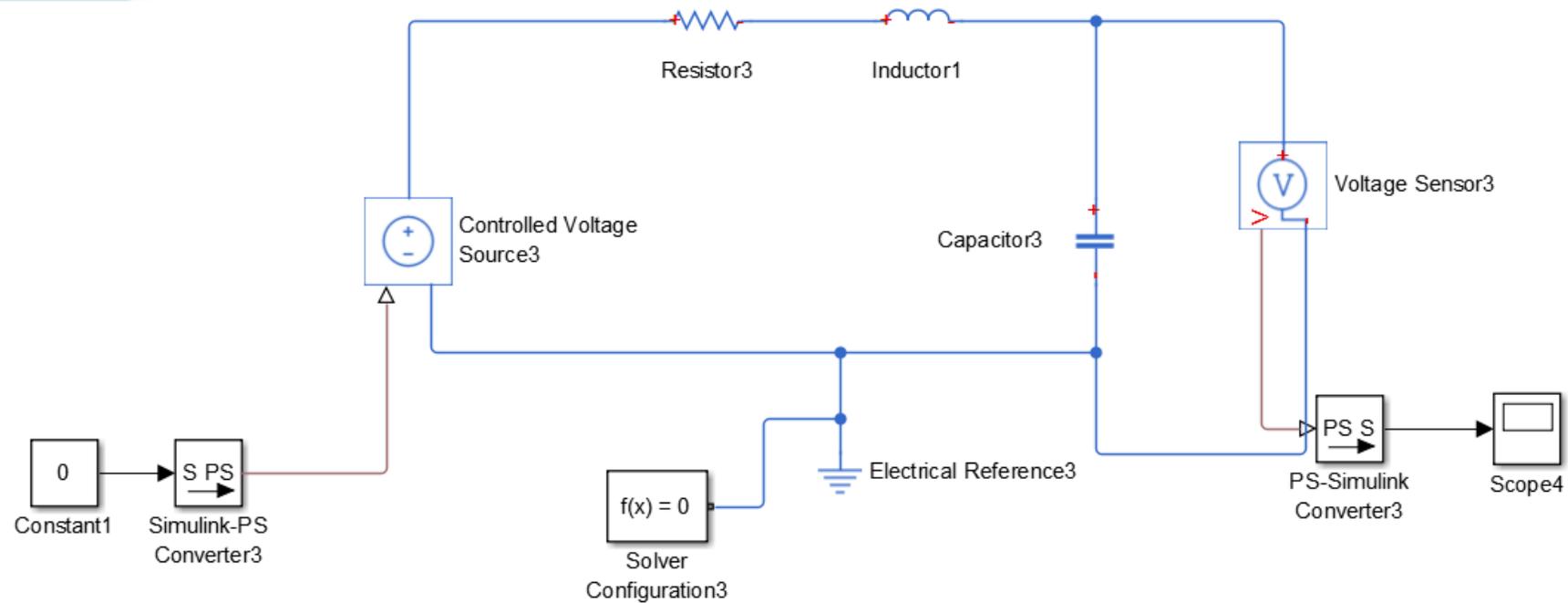b. The element values are  $R=6\Omega$ ,  $L=1H$  and  $C=1/9 F$



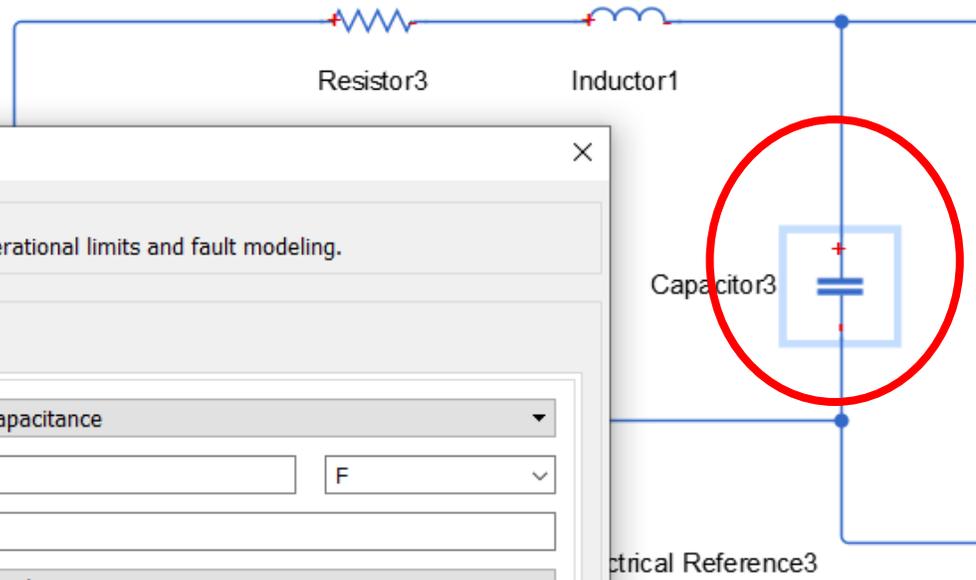

Block Parameters: Capacitor3

Capacitor  
This block models a capacitor with optional tolerance, operational limits and fault modeling.

Settings

Main Operating Limits Faults

Enable table-based capacitance: No - use constant capacitance

Capacitance: 1/9 F

Capacitance tolerance (%): 5

Tolerance application: None - use nominal value

Series resistance: 1e-6 Ohm


Parallel conductance: 0 1/Ohm

Initial capacitor voltage: 2 V

$y(0) = 2$

OK Cancel Help Apply



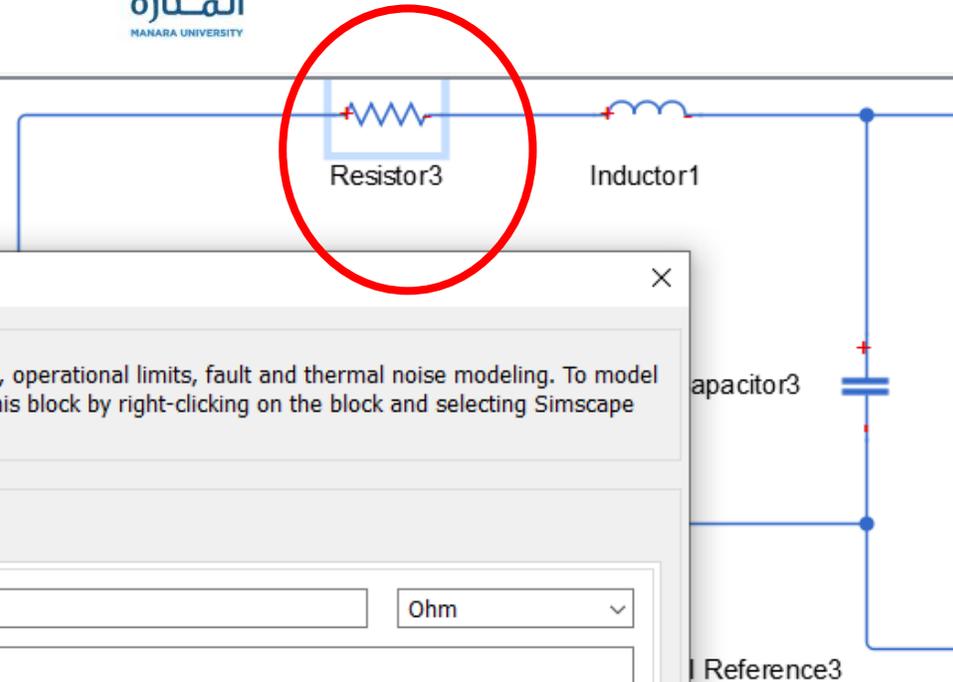

Block Parameters: Resistor3

Resistor

This block models a resistor with optional tolerance, operational limits, fault and thermal noise modeling. To model temperature effects, select the thermal variant of this block by right-clicking on the block and selecting Simscape block choices and Show thermal port.

Settings

Main Operating Limits Faults Noise

Resistance:  Ohm

Tolerance (%):

Tolerance application:

OK Cancel Help Apply





Resistor3

Inductor1

Capacitor3

Electrical Referen

Block Parameters: Inductor1

Inductor

This block models an inductor with optional tolerance, operational limits and fault modeling.

Settings

Main Operating Limits Faults

Inductance: 1 H

Tolerance (%): 20

Tolerance application: None - use nominal value


Series resistance: 0 Ohm

Parallel conductance: 1e-9 1/Ohm

Initial inductor current: 0.5 A


OK Cancel Help Apply




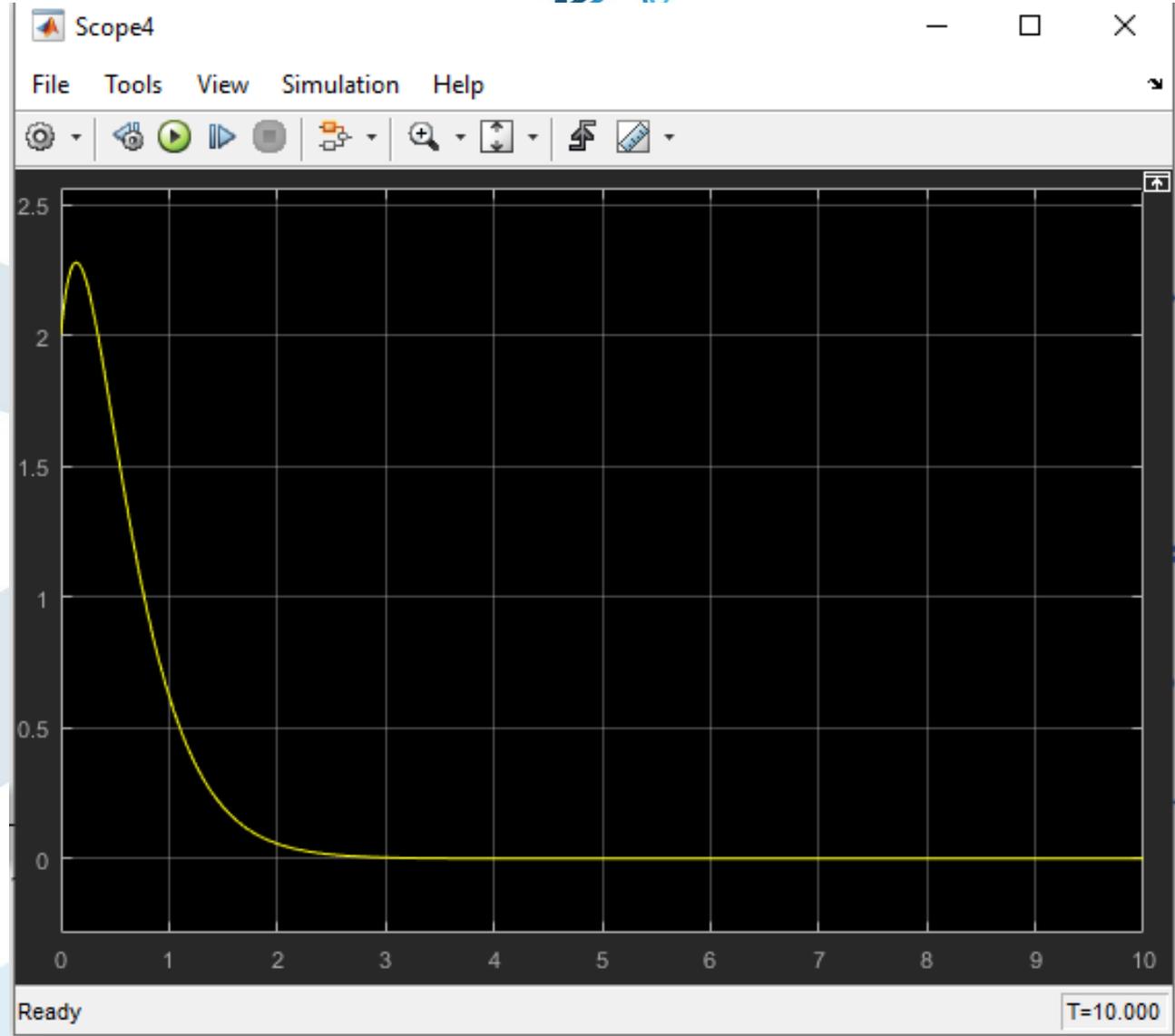

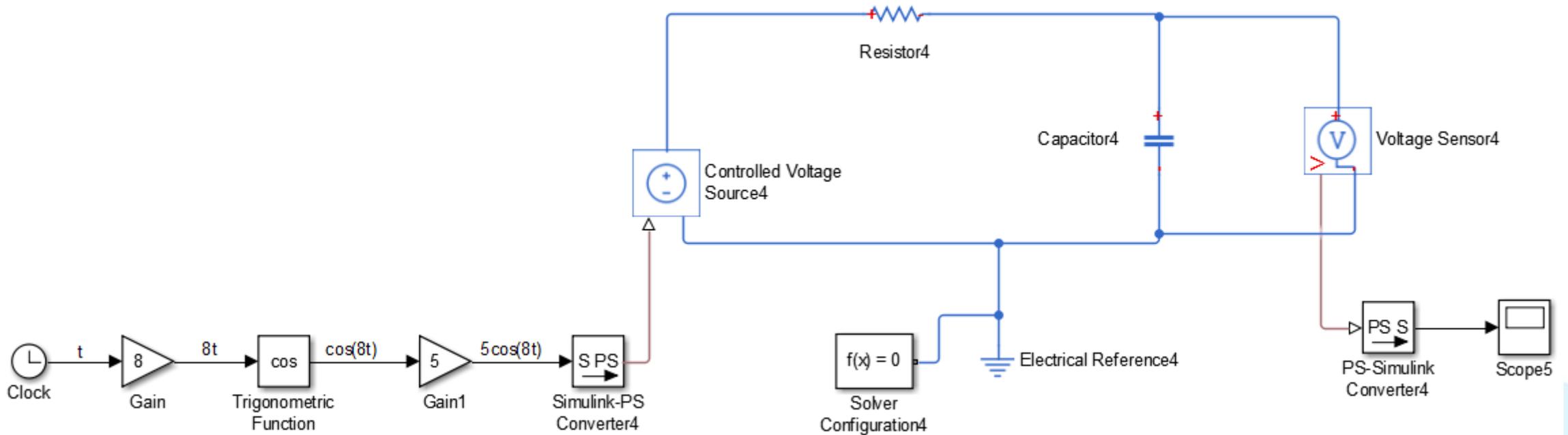**Example 3:** Forced response of the first-order system for sinusoidal input The initial value of the output signal is  $y(0) = 5v$ .  
**Draw the output voltage  $y(t)$  using Simulink in response to a sinusoidal input signal in the form  $x(t) = 5 \cos(8t)$ .**





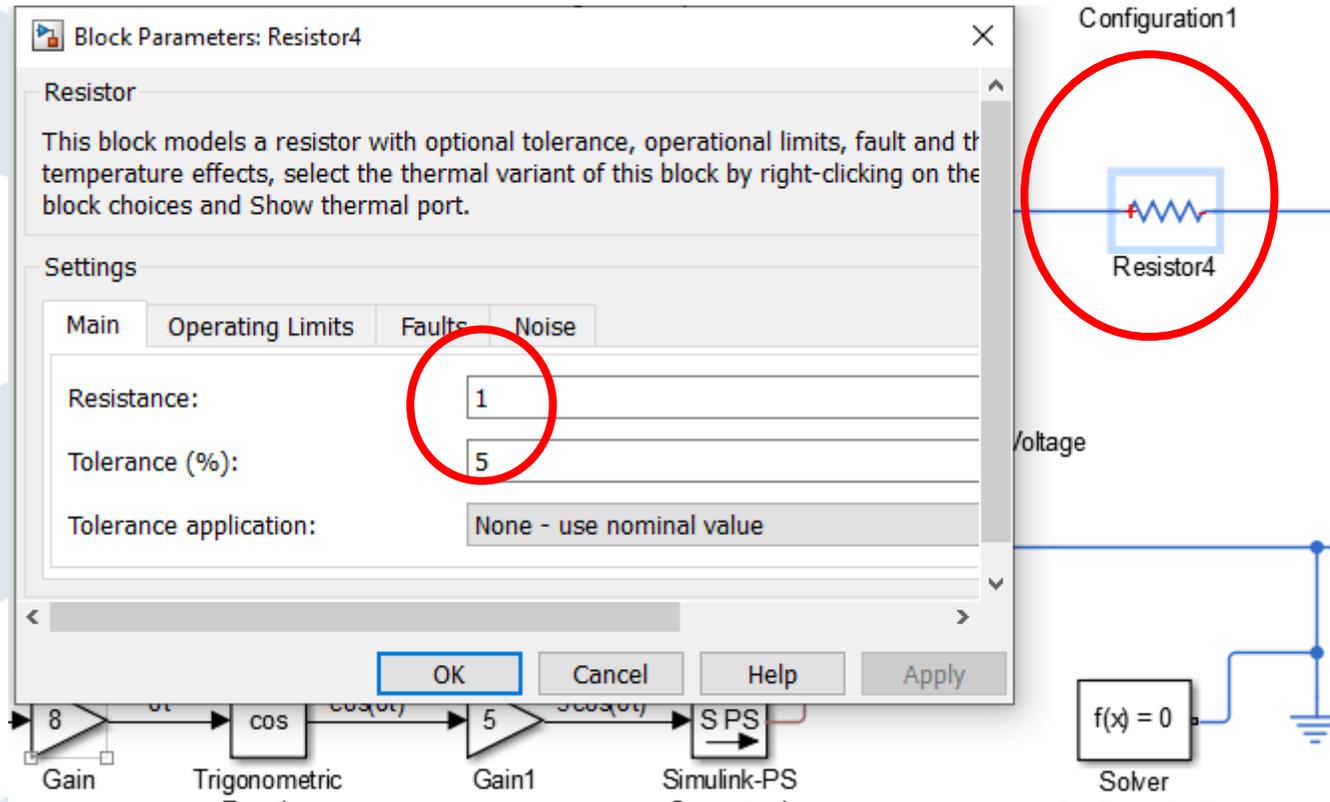

Block Parameters: Resistor4

Resistor

This block models a resistor with optional tolerance, operational limits, fault and temperature effects, select the thermal variant of this block by right-clicking on the block choices and Show thermal port.

Settings

Main Operating Limits Faults Noise

Resistance: 1

Tolerance (%): 5

Tolerance application: None - use nominal value

Configuration1

Resistor4

Voltage

Gain 8

Trigonometric cos

Gain1 5

Simulink-PS SPS

Solver f(x) = 0



Settings

Main Operating Limits Faults

Enable table-based capacitance: No - use constant capacitance

Capacitance: 0.25 F

Capacitance tolerance (%): 5


Tolerance application: None - use nominal value

Series resistance: 1e-6 Ohm

Parallel conductance: 0 1/Ohm


Initial capacitor voltage: 5 V

OK Cancel Help Apply

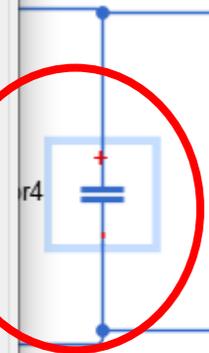

reference4



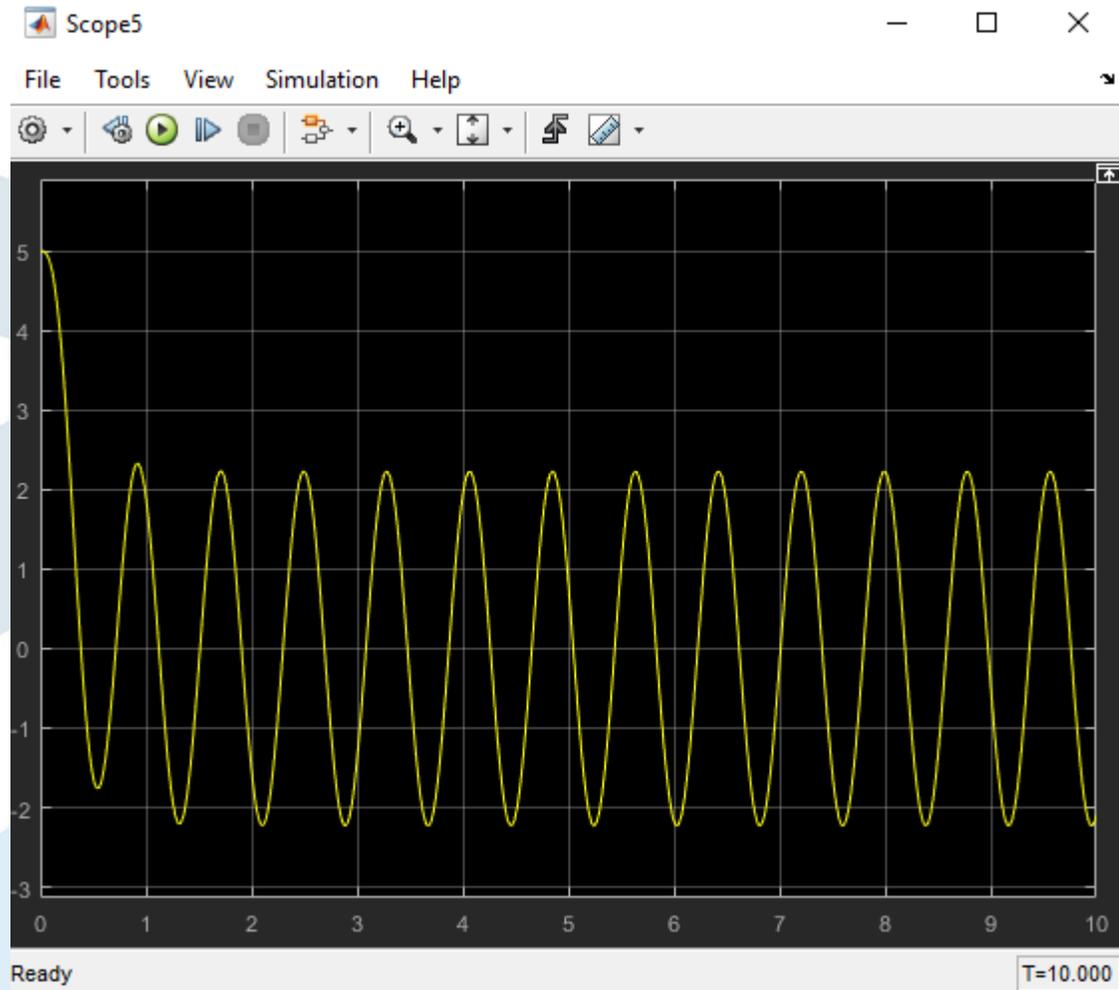

# Thanks for Listening

